

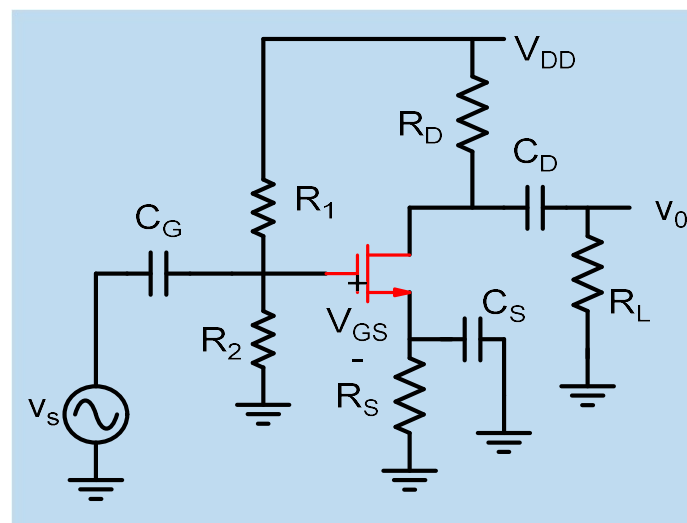
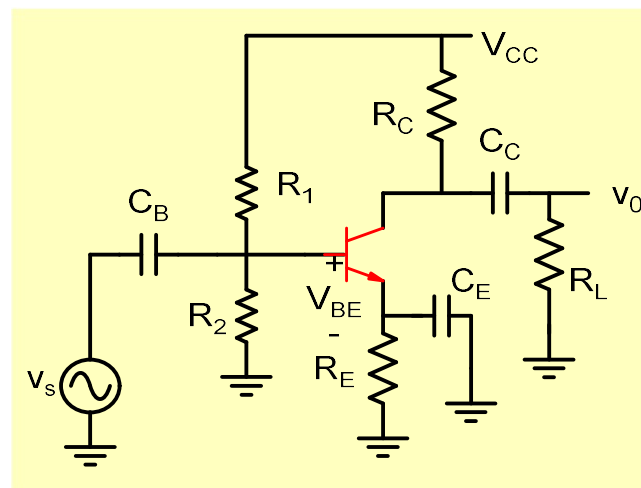
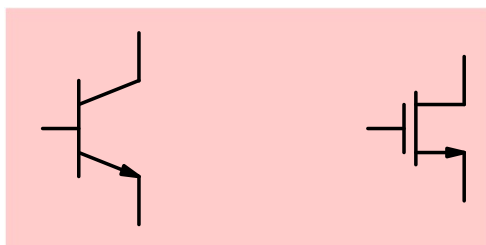
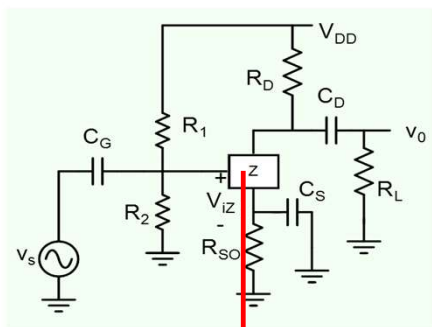



ESC201T: Introduction to Electronics

Lecture 28: Transistor Circuits


B. Mazhari
Dept. of EE, IIT Kanpur

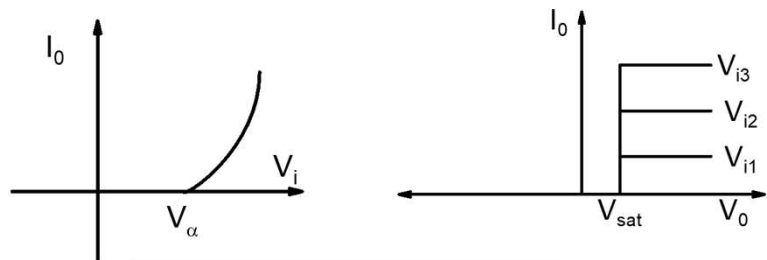

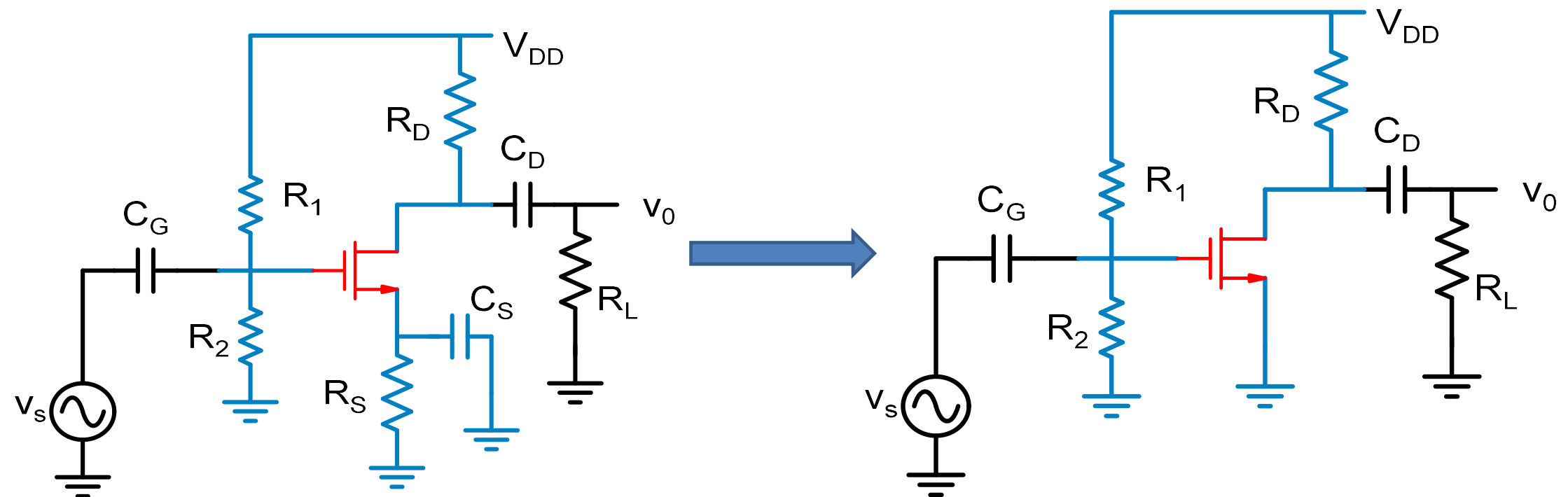


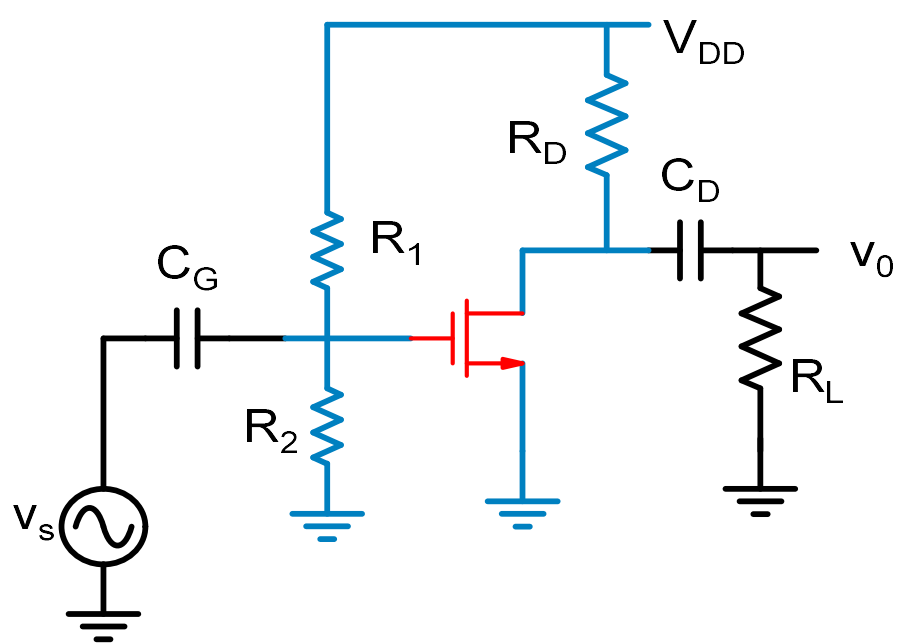

dc analysis




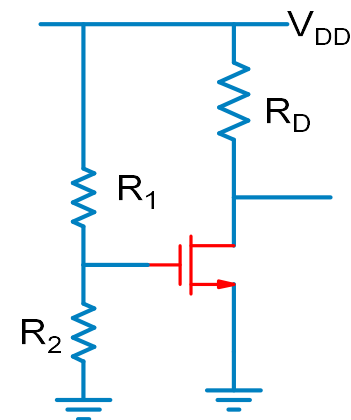


ac or small signal analysis


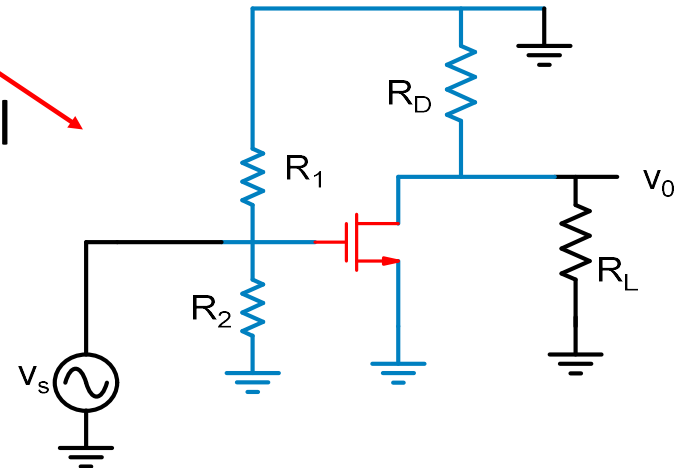


$$A_V = \frac{v_o}{v_s}$$

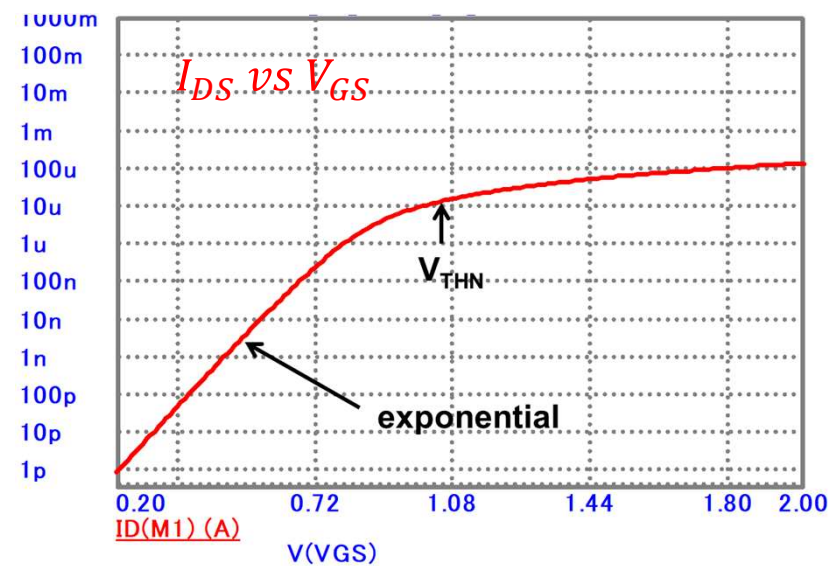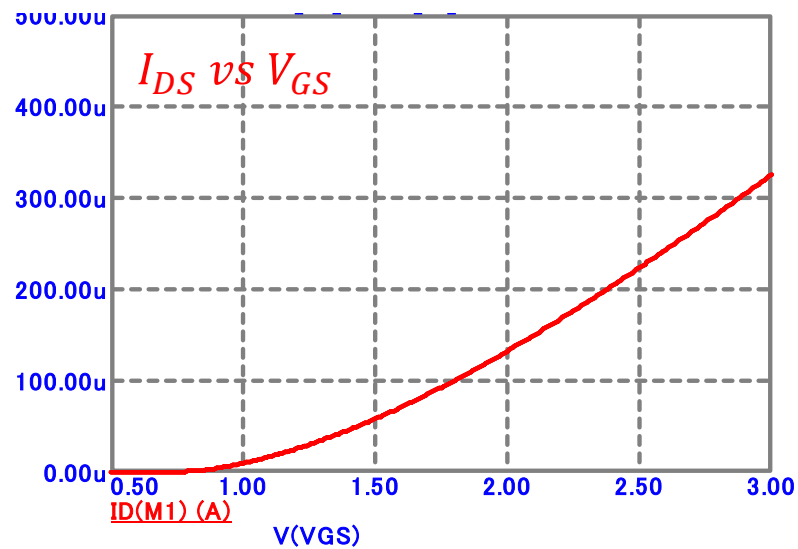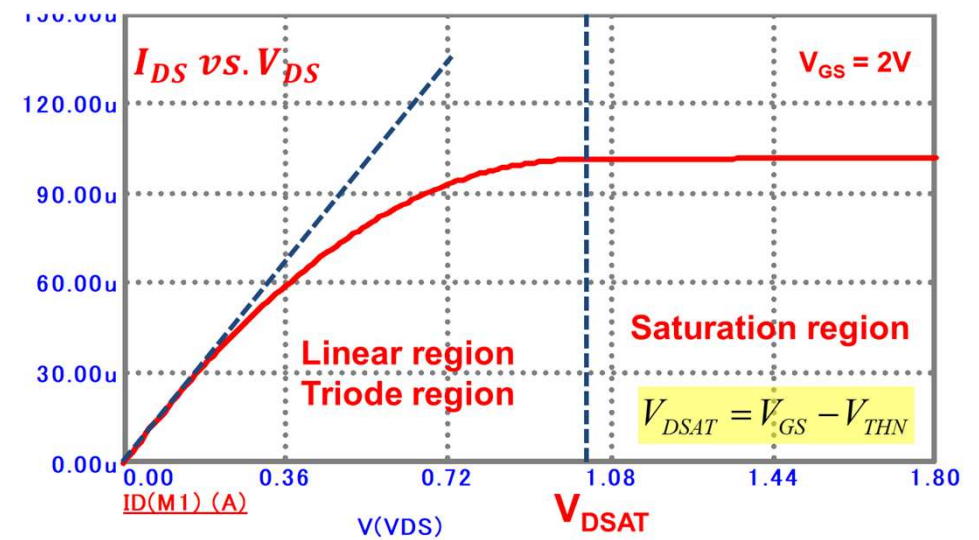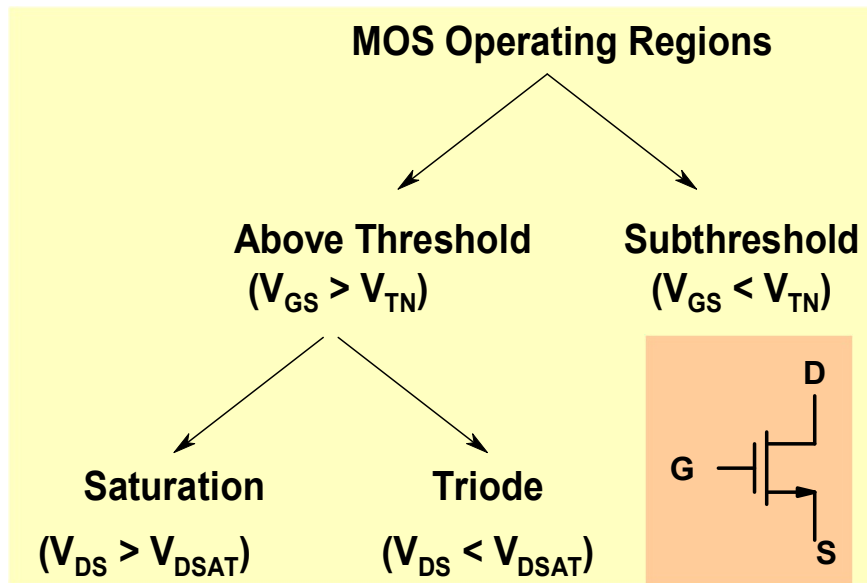Need dc and ac (or small signal incremental) model of the transistors




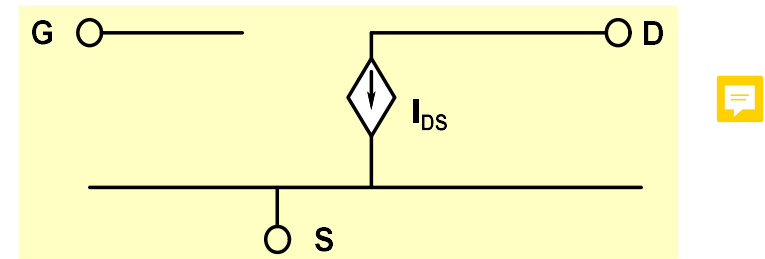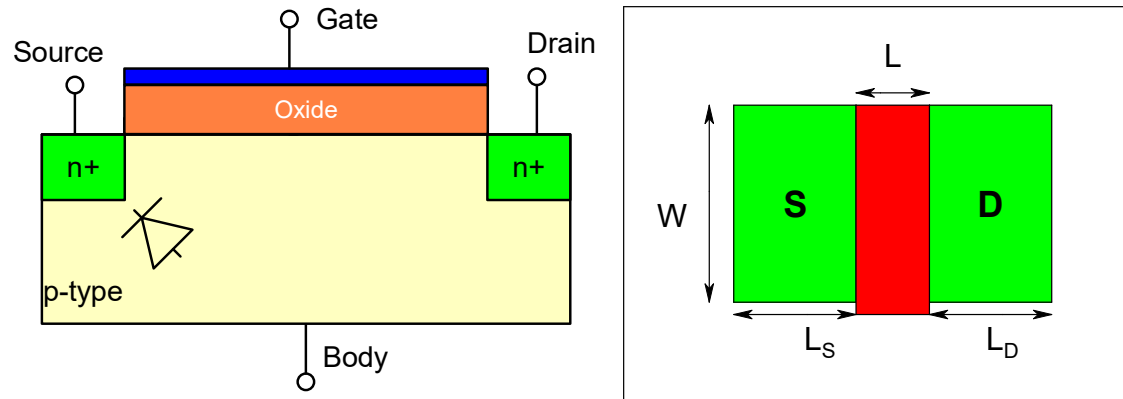The dc and ac models of the transistor in saturation region can be represented in the form of an equivalent circuit:



$$I_{DS} = \frac{\beta_N}{2} (V_{GS} - V_{THN})^2 ; \beta_N = KP_N \times \frac{W}{L}$$

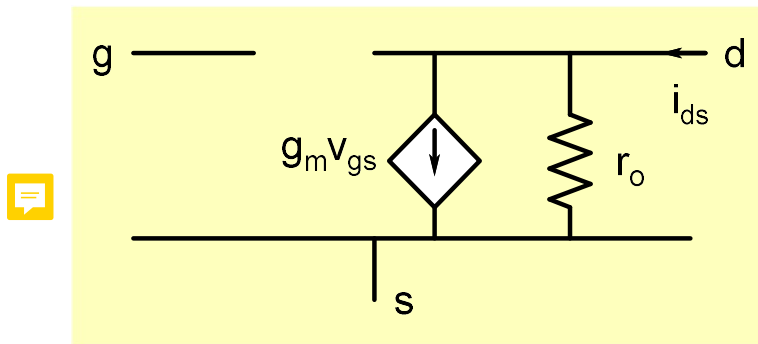KP_N : Transconductance parameter $\frac{\mu A}{V^2}$




$$g_m = \frac{2I_{DSQ}}{V_{GSQ} - V_{THN}} = \sqrt{2I_{DSQ}\beta}$$

$$r_o = \frac{1}{\lambda_n I_{DSQ}}$$

λ_N is the channel length modulation parameter

$$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01V^{-1}$$



dc Model: Triode (or Linear)

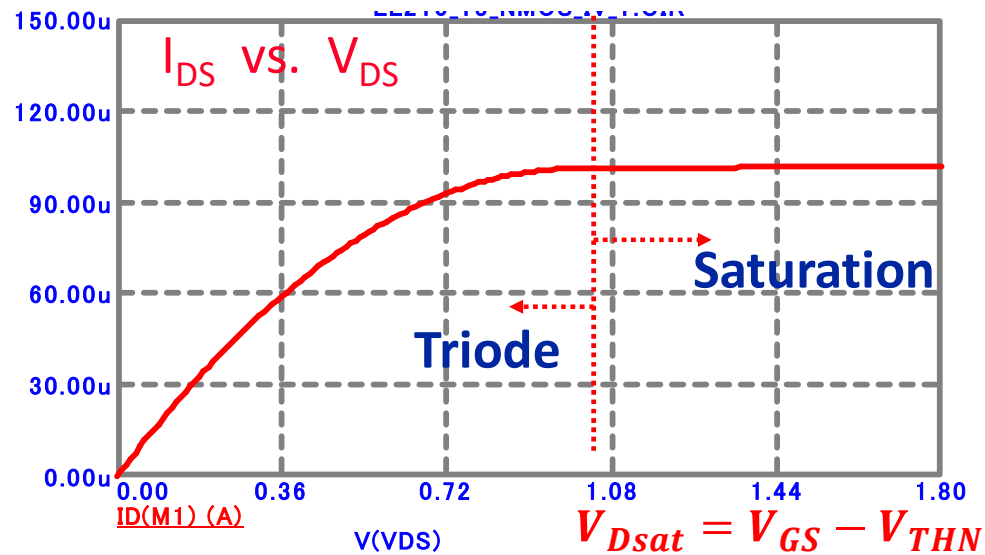

$$I_{DS} = \beta_N \left\{ (V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right\}$$

For simplicity we will only consider cases where $I_{DS} \approx KP_N \times \frac{W}{L} \times (V_{GS} - V_{THN}) \times V_{DS}$

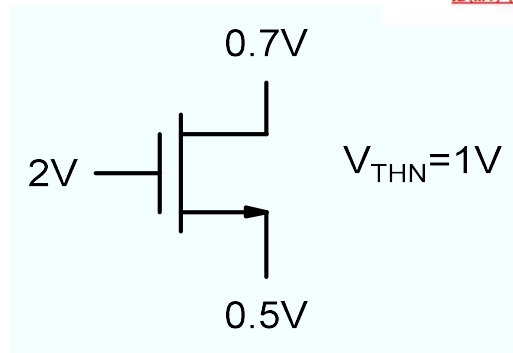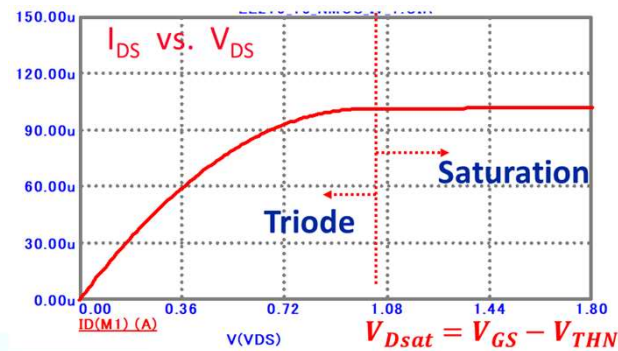
Which mode is the transistor operating in ?



$$V_{GS} = 1.5 ; V_{DS} = 0.2$$


$$V_{DSAT} = V_{GS} - V_{THN} = 0.5$$
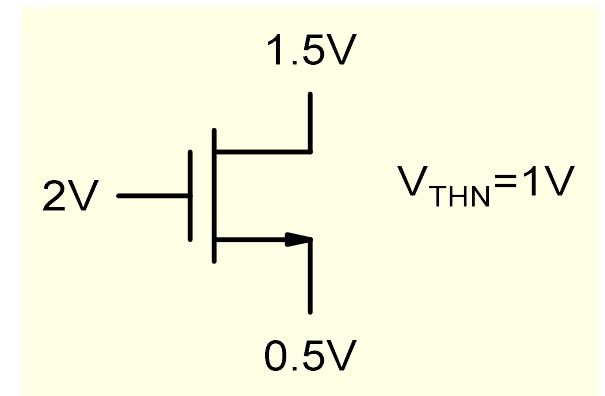
$$V_{DS} < V_{DSAT} \Rightarrow \text{Linear}$$




$$V_{DSAT} = 0.5 ; V_{DS} = 1V$$

Saturation


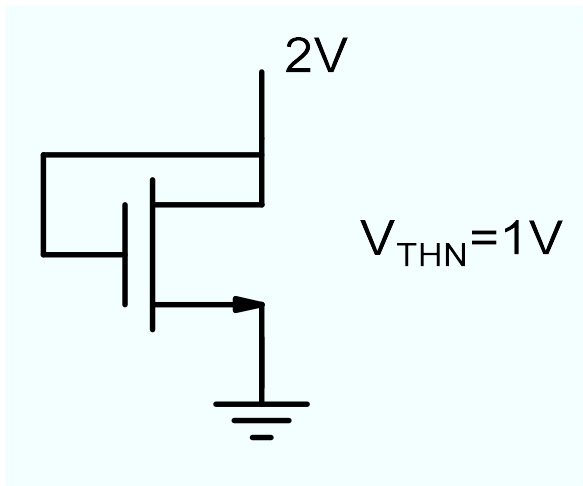


$$V_{GS} = 2 ; V_{DS} = 2$$

Saturation

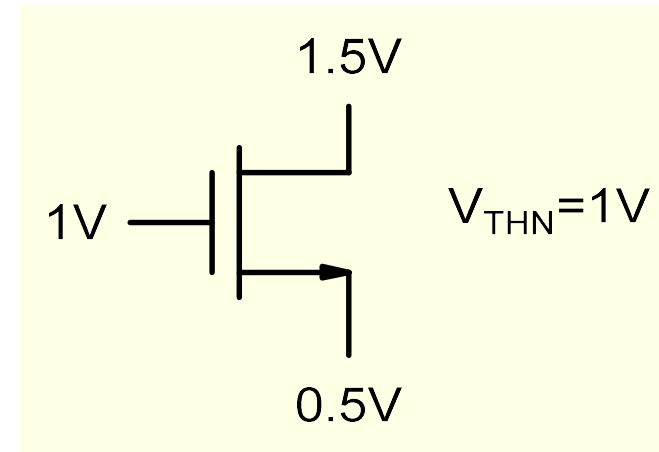


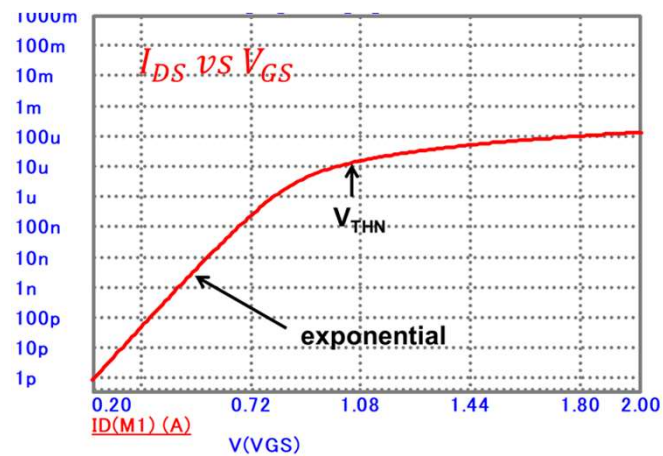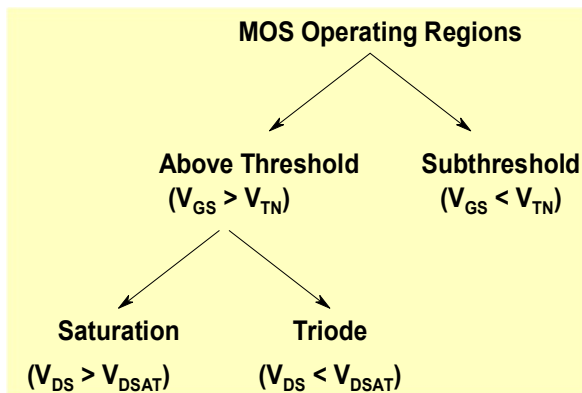$V_{GS} = 0.5V < V_{THN}$ Transistor is in sub-threshold mode of operation



MOSFET Circuits

Example-1

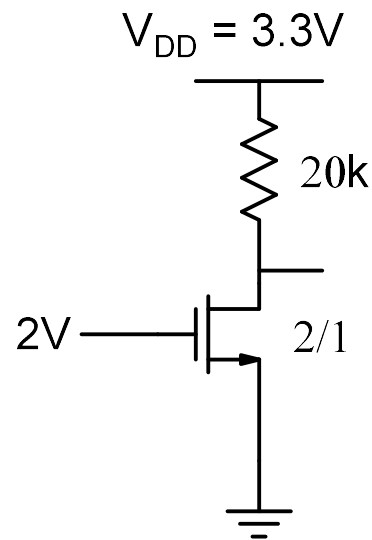

$$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01V^{-1}$$

Determine I_{DS} and V_{DS}


Assume saturation mode of operation

$$I_{DS} = KP_N \times \frac{W}{L} \times \frac{(V_{GS} - V_{THN})^2}{2} = 10^{-4} A$$

$$V_{DS} = V_{DD} - I_{DS} \times R_D = 1.2V$$


$$V_{Dsat} = V_{GS} - V_{THN} = 1V$$

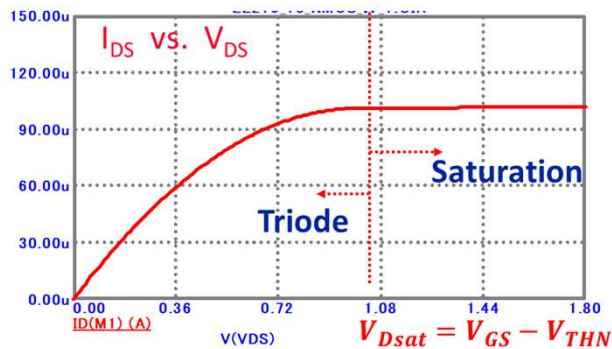Since $V_{DS} > V_{Dsat}$ our assumption is correct



MOSFET Circuits

Example-2

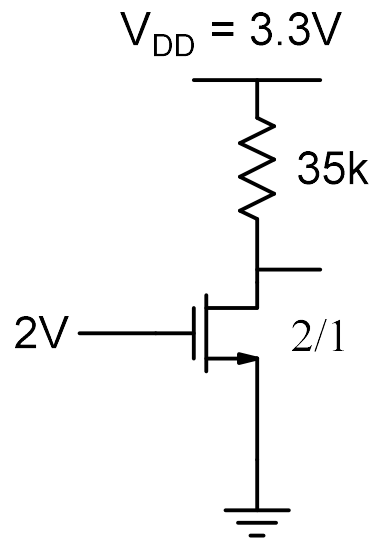

$$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01V^{-1}$$

Determine I_{DS} and V_{DS}

Assume saturation mode of operation


$$I_{DS} = KP_N \times \frac{W}{L} \times \frac{(V_{GS} - V_{THN})^2}{2} = 10^{-4} A$$

$V_{DS} = V_{DD} - I_{DS} \times R_D = -0.2V$ so assumption incorrect


$$I_{DS} \approx KP_N \times \frac{W}{L} \times (V_{GS} - V_{THN}) \times V_{DS}; V_{DS} = V_{DD} - I_{DS} \times R_D$$

$$\Rightarrow I_{DS} = 8.25 \times 10^{-5} A; V_{DS} = 0.412V$$

$$V_{Dsat} = V_{GS} - V_{THN} = 1V$$

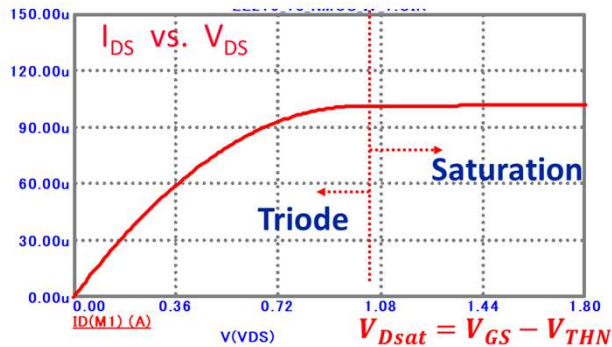

Example-3

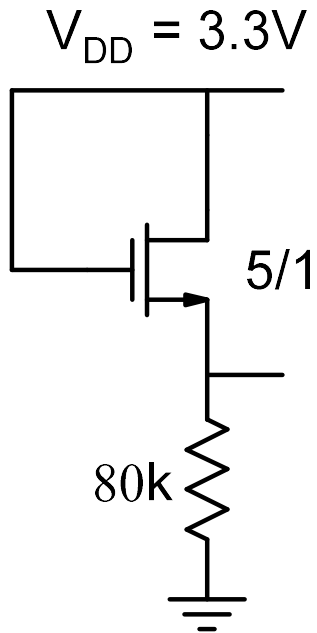

$$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01V^{-1}$$

Determine I_{DS} and V_{DS}


$$V_{DS} = V_{GS}$$
$$\Rightarrow V_{DS} > V_{GS} - V_{THN} = V_{DSAT} \Rightarrow \text{Saturation}$$

$$I_{DS} = KP_N \times \frac{W}{L} \times \frac{(V_{GS} - V_{THN})^2}{2}; V_{GS} = 3.3 - I_{DS} \times 80 \times 10^3$$
$$\Rightarrow I_{DS} = 2.48 \times 10^{-5} A; V_{GS} = 1.315V$$


For the other solution $V_{GS} = 0.653V$ which is not possible since it is less than V_{THN}

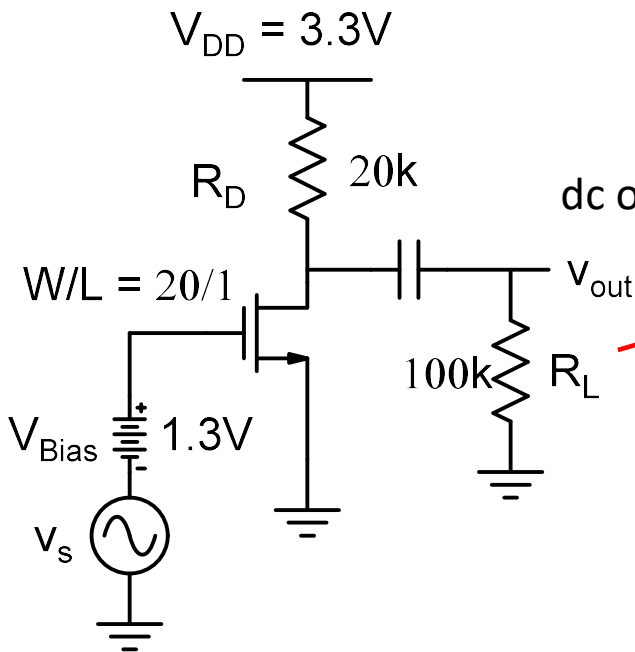Example-4

Determine the voltage gain of the amplifier $\frac{v_{out}}{v_s}$



dc or Bias point analysis

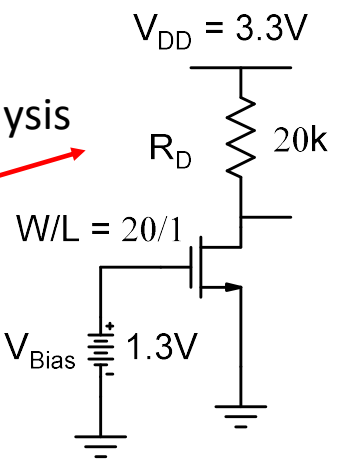


$$I_{DS} = KP_N \times \frac{W}{L} \times \frac{(V_{GS}-V_{THN})^2}{2} = 90\mu A$$

$$V_{DSQ} = V_{DD} - I_{DSQ} \times R_D = 1.5V$$


$$V_{Dsat} = V_{GS} - V_{THN} = 0.3V$$

So Transistor is biased in saturation

ac or small signal analysis

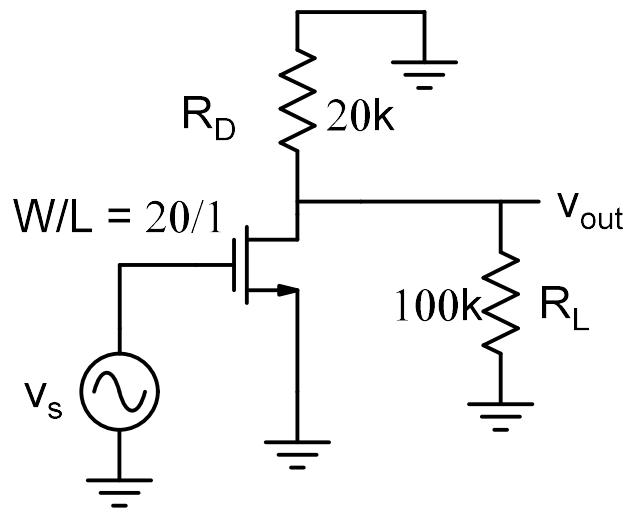


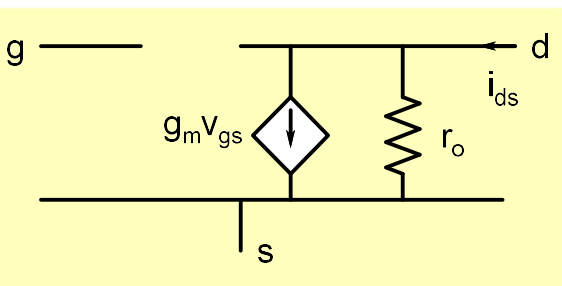
$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0V^{-1}$



$$g_m = \frac{2I_{DSQ}}{V_{GSQ} - V_{THN}} = \sqrt{2I_{DSQ}\beta}$$

$$= 6 \times 10^{-4} \Omega^{-1}$$

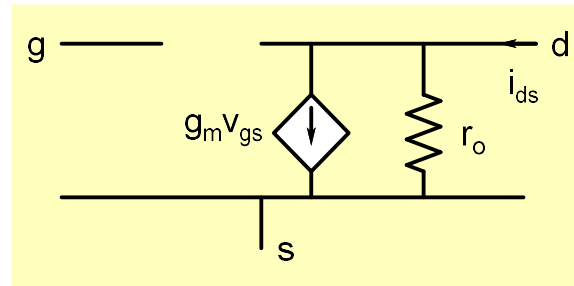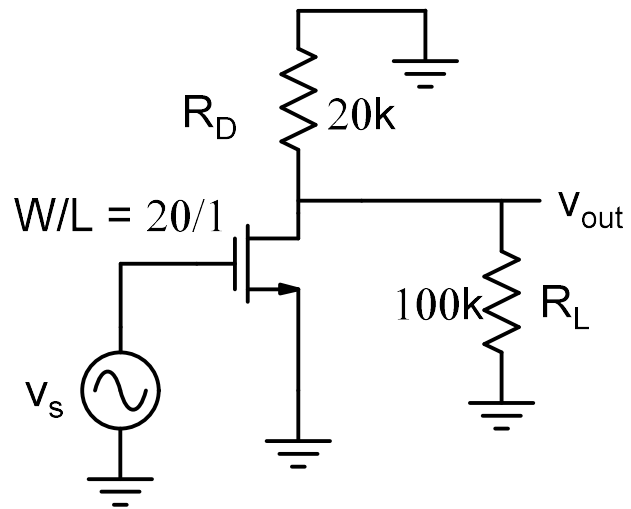
$$r_o = \frac{1}{\lambda_n I_{DSQ}} = \infty$$



$$g_m = \frac{2I_{DSQ}}{V_{GSQ} - V_{THN}} = \sqrt{2I_{DSQ}\beta}$$

$$= 6 \times 10^{-4} \Omega^{-1}$$



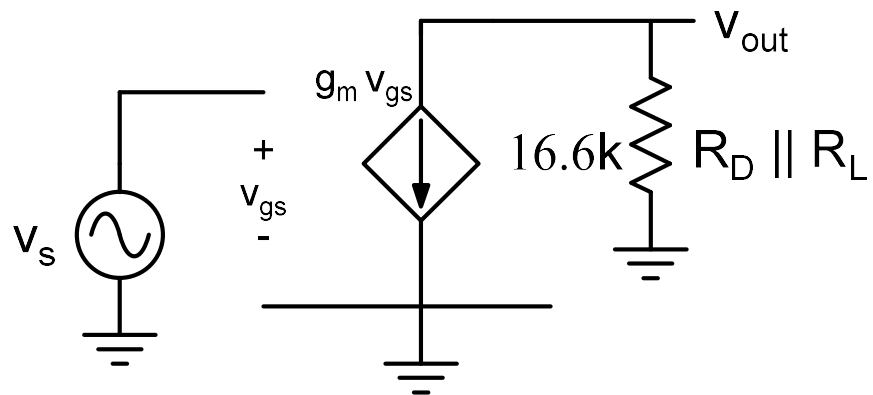
$$r_o = \frac{1}{\lambda_n I_{DSQ}} = \infty$$



$$\frac{v_{out}}{v_s} = -g_m \times R_D \parallel R_L = -10$$

Example-5 Plot V_{OUT} vs. V_{IN} curve.

MOS Digital NOT gate

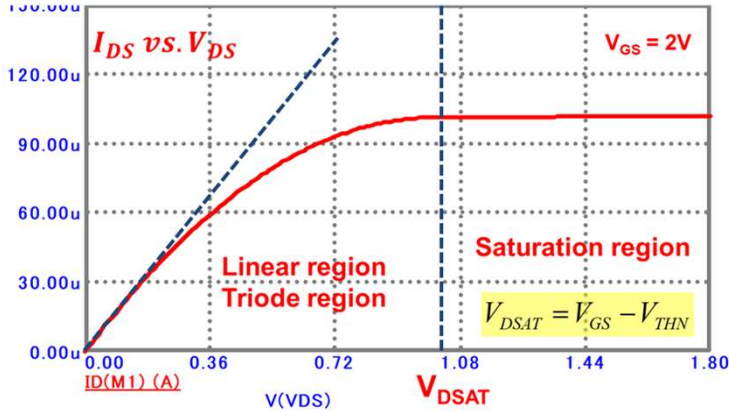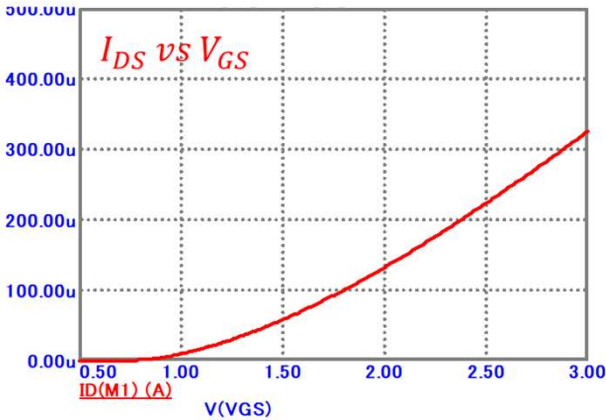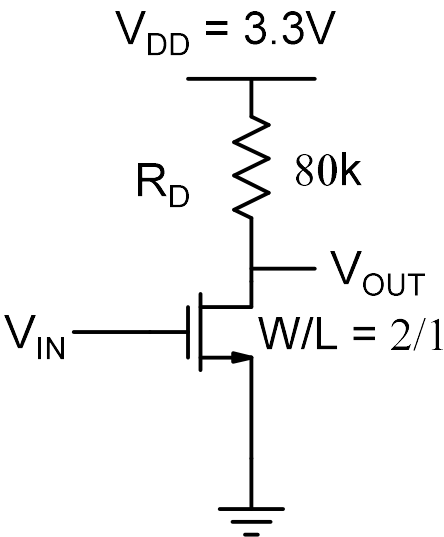

$$K P_N = 100 \mu A / V^2; V_{THN} = 1V; \lambda_n = 0.01 V^{-1}$$

$$V_{out} = V_{DD} - I_{DS} \times R_D$$

$$I_{DS} = K P_N \times \frac{W}{L} \times (V_{IN} - V_{THN}) \times V_{out}$$

