
 


ESC201T : Introduction to Electronics

Lecture 39: Sequential circuit design-3

B. Mazhari
Dept. of EE, IIT Kanpur



Sequential Circuits: Summary

 



- we need to know how the system goes from one state to another in response to the inputs and how the outputs respond to these changes

Synthesis involves the following tasks:

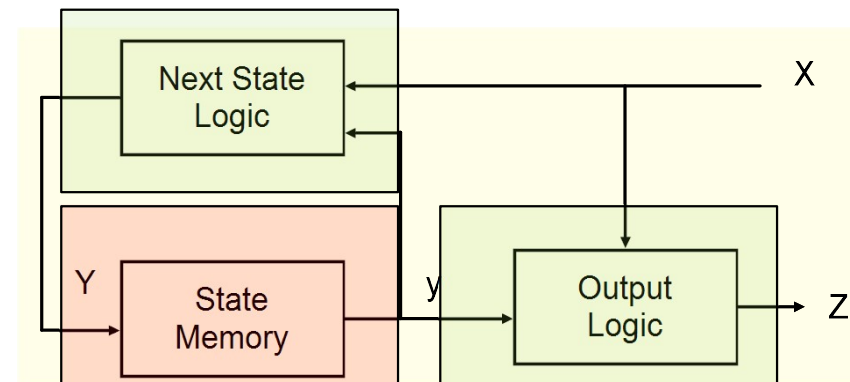 - Number of storage elements
- State Encoding
- Choosing a flipflop type to implement states
- Synthesize next state logic
- Synthesize output logic




Counters

  


A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

In state S_0 , the output ABC is 000, in S_1 001 and so on

 There are 8 states so 3 FFs are at least required. Let us choose T FF.




PS			NS					
A	B	C	A	B	C	T_A	T_B	T_C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

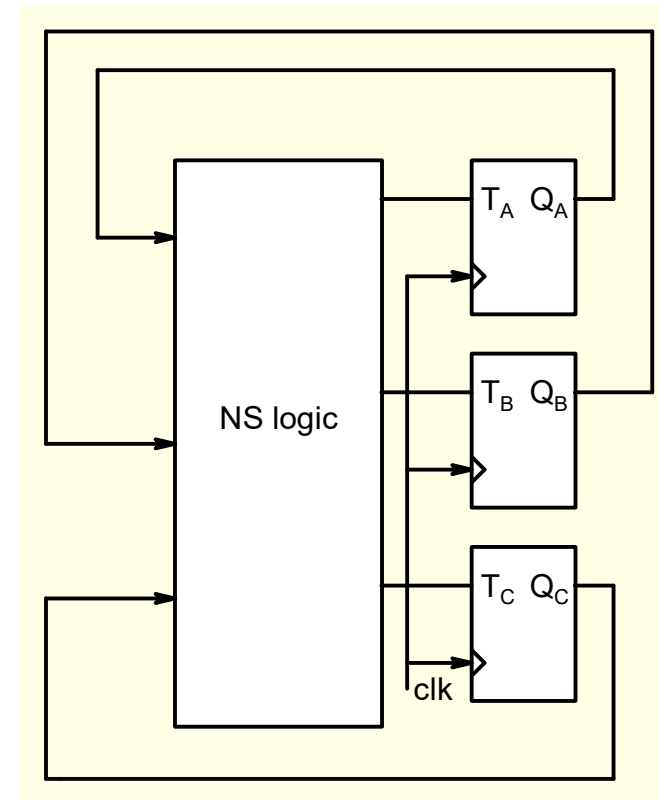


$$T_A = B.C ; T_B = C ; T_C = 1$$

Binary UP counter

 


A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

 


$$T_A = B.C ; T_B = C ; T_C = 1$$

Counter with Enable


 


Counter is in Hold state.

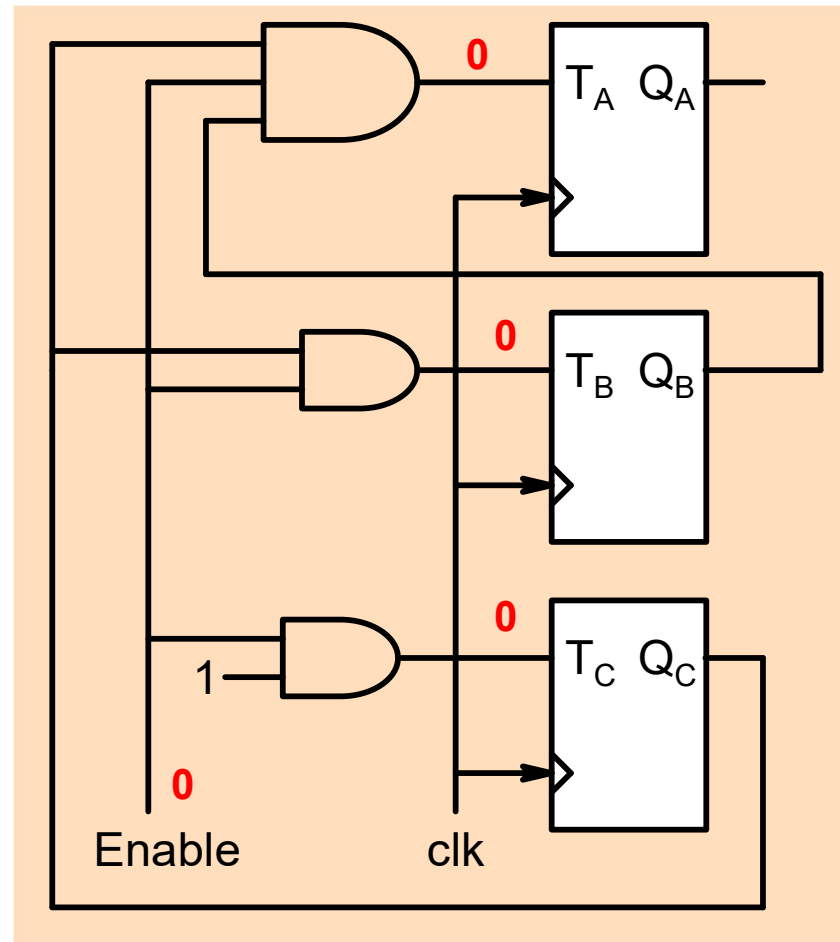

When Enable = 1, the counter begins the count.

Counter with Asynchronous Reset

  


When Enable = 1, the counter begins the count.

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1
0	0	0	0

- D toggles every clock cycle
- B toggles only when D is 1
- C toggles only when both C and D are 1
- A toggles only when B C D are 1

T FF toggles when T=1

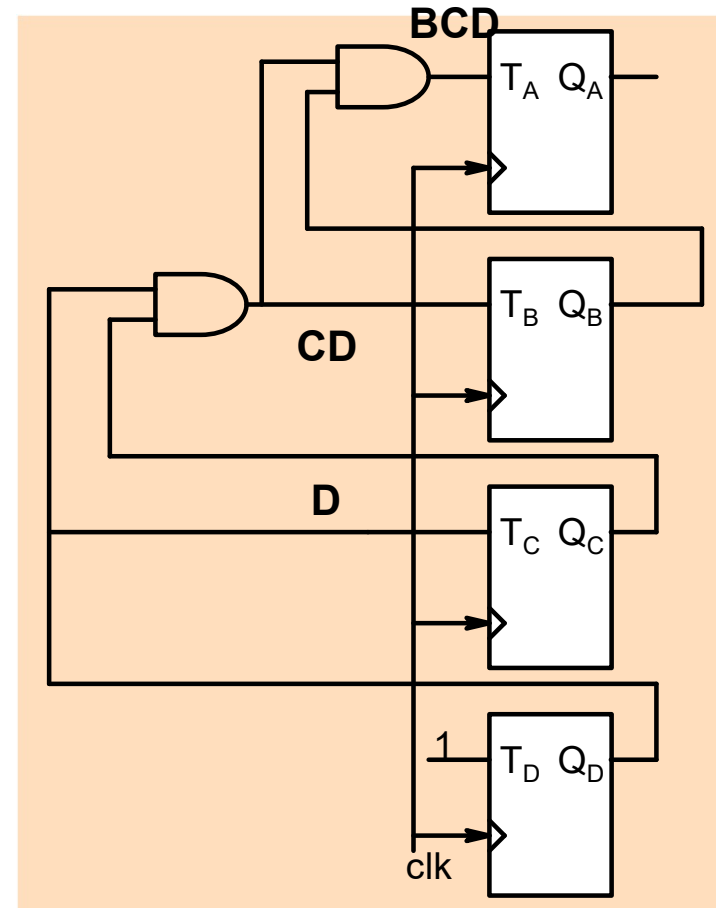


4-bit Down Counter

A B C D


1 1 1 1
1 1 1 0
1 1 0 1
1 1 0 0
1 0 1 1
1 0 1 0
1 0 0 1
1 0 0 0
0 1 1 1
0 1 1 0
0 1 0 1
0 1 0 0
0 0 1 1
0 0 1 0
0 0 0 1
0 0 0 0
1 1 1 1

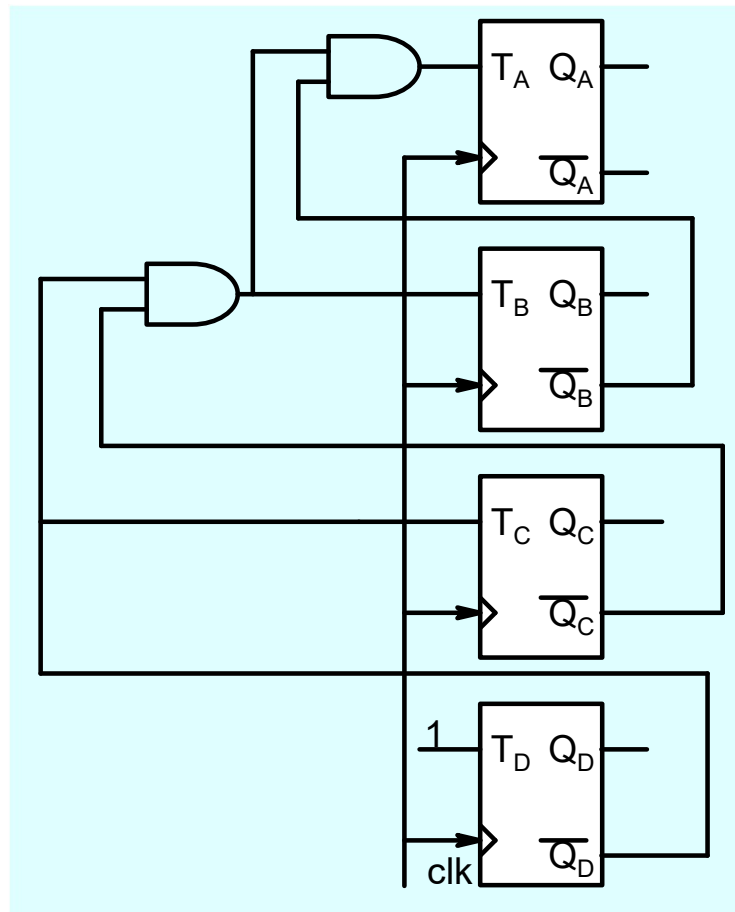- D toggles every clock cycle
- C toggles only when D is 0
- B toggles only when both C and D are 0
- A toggles only when D C B are 0




Counters

A	B	C
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

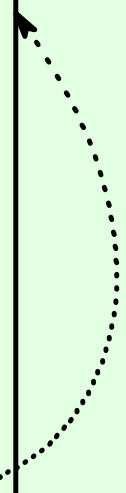


Binary down counter

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

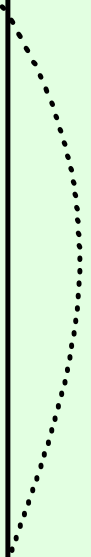



Decade counter
Modulo-10 Counter

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

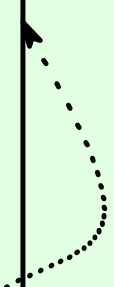

Modulo-5 Counter

4-bit Up-Down Counter

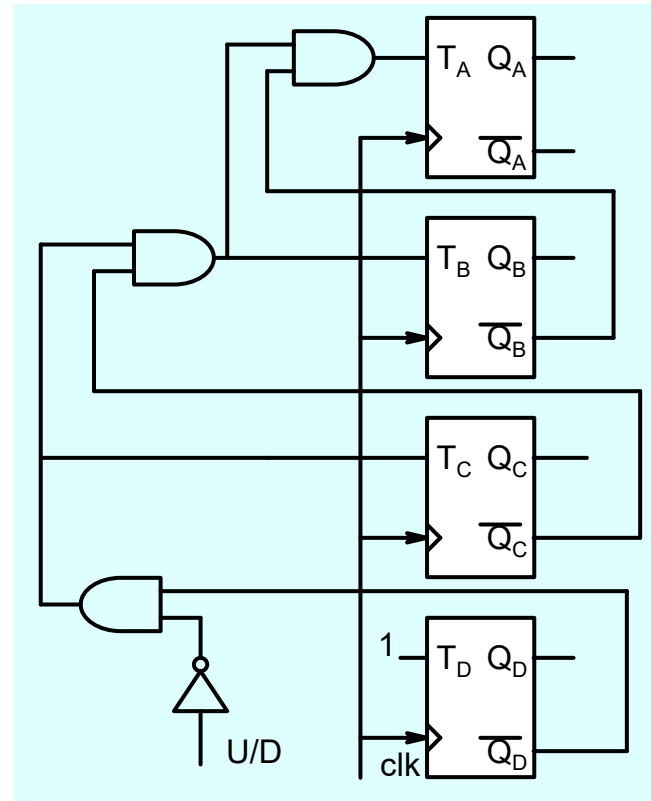 


Merging of the two structures gives an Up/down counter

BCD Counter


Binary Coded Decimal (BCD): each decimal digit is coded as a 4-bit binary number

$$25 = 0010 \ 0101$$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1

 

BCD counter from 0 to 99

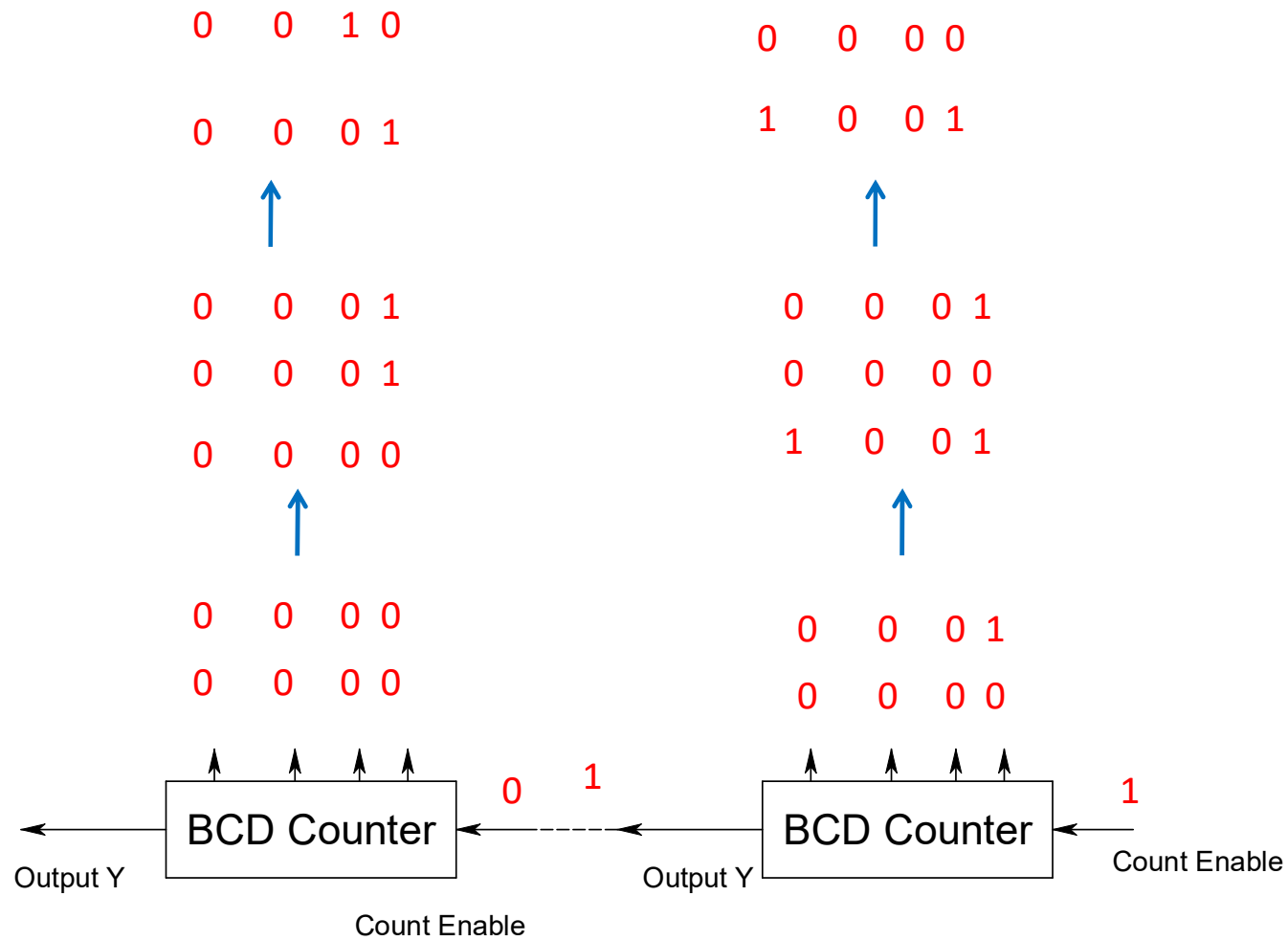

Counter with Unused States

PS			NS								
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

There are two unused states 011 and 111. one approach to handle this situation is that, while evaluating expressions for J K , we use don't care conditions corresponding to these unused states

Counter with Unused States

PS			NS								
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

A	BC			
	00	01	11	10
0	0	0	X	1
1	X	X	X	X

$$J_A = B$$

Counter with Unused States



PS			NS								
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

$$J_A = B \quad K_A = B$$

$$J_B = C \quad K_B = 1$$


$$J_C = \overline{B} \quad K_C = 1$$

  After synthesizing the circuit, one needs to check that if by chance the counter goes into one of the unused states, after one or more clock cycles, it enters a used state and then remains among the used states




We can see that if by chance the counter goes into unused states 111 or 011, then after a clock cycle it enters one of the used states.


Counter as frequency divider

 

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

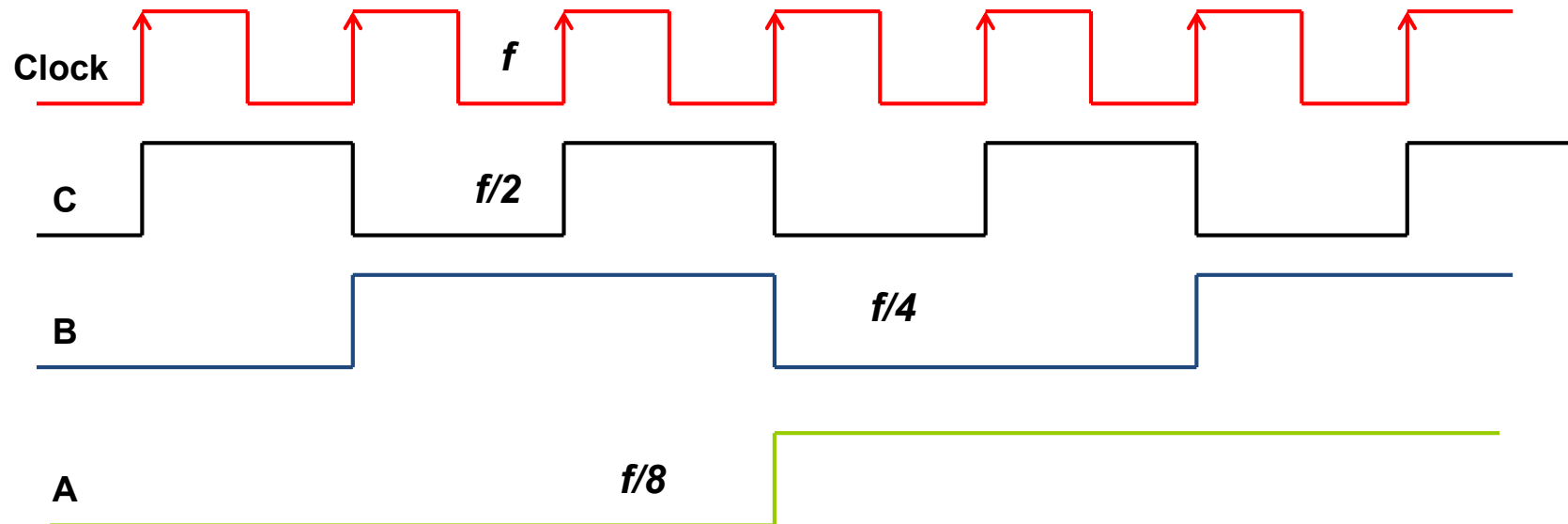

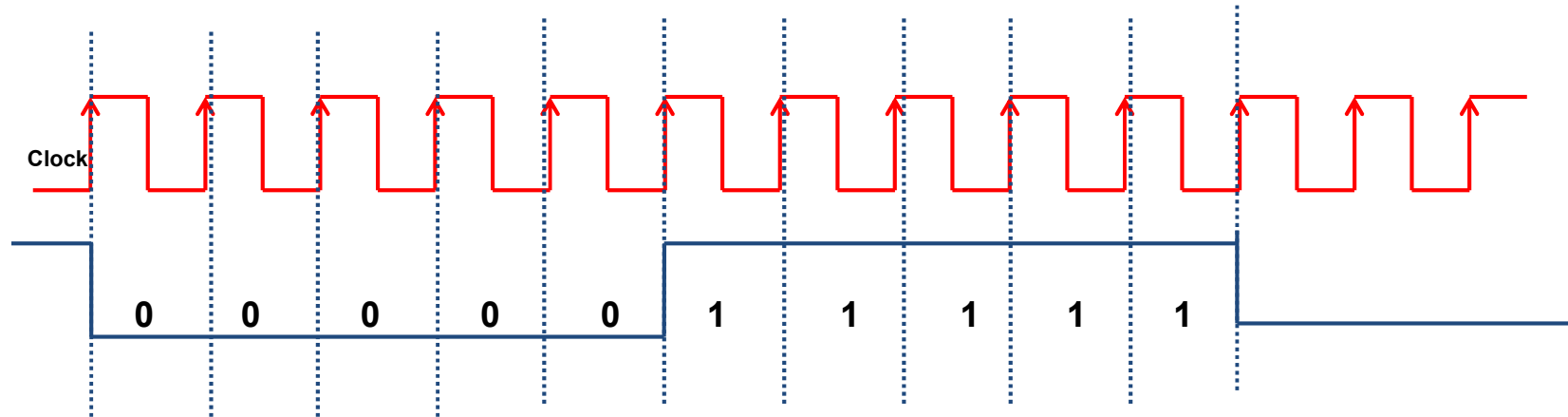Example From a frequency of 10KHz, generate the following signal of frequency 1KHz




A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1



This will have a frequency of 1KHz but it will not have the same waveform

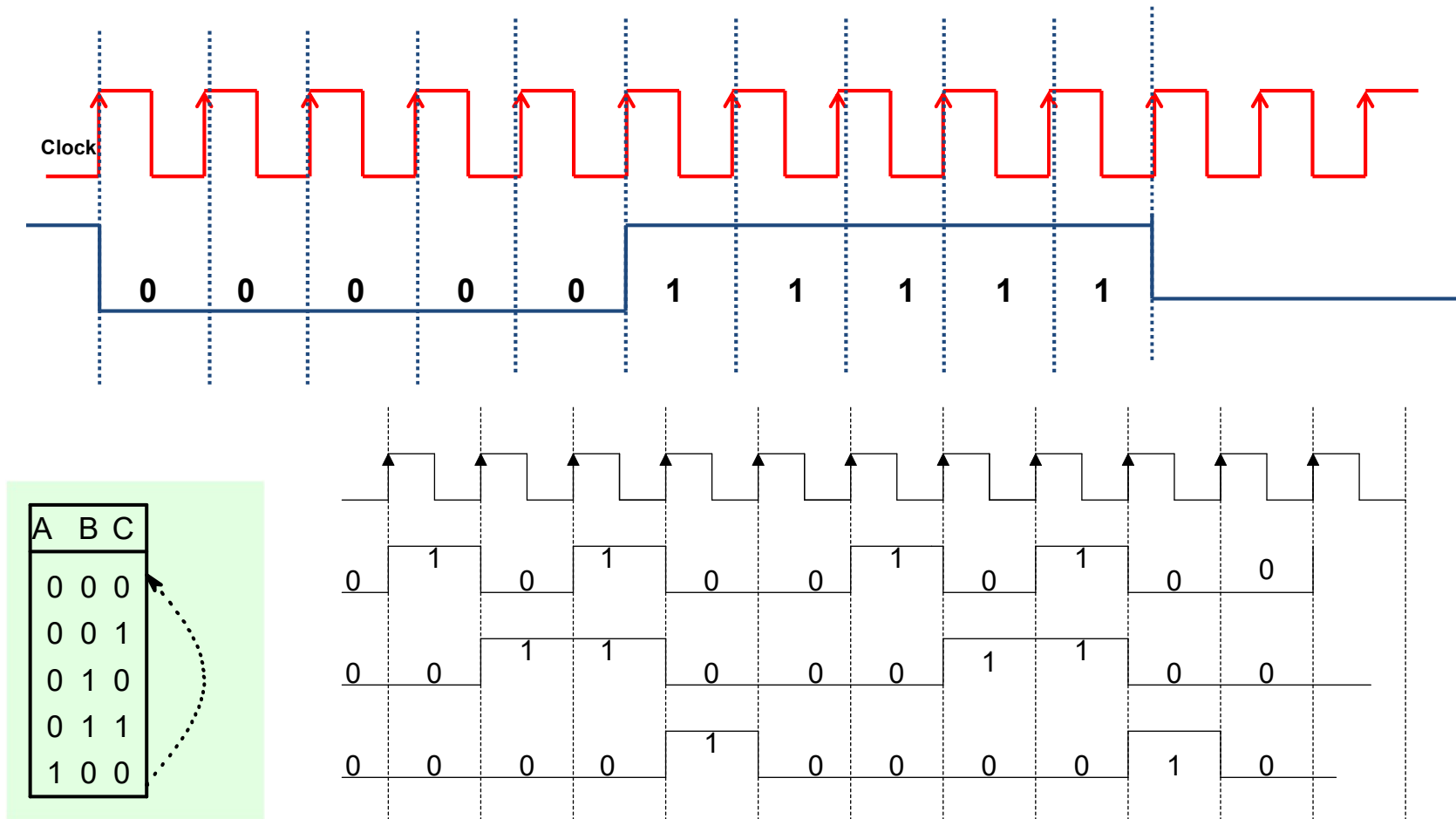
Example

From a frequency of 10KHz, generate a signal of frequency 1KHz



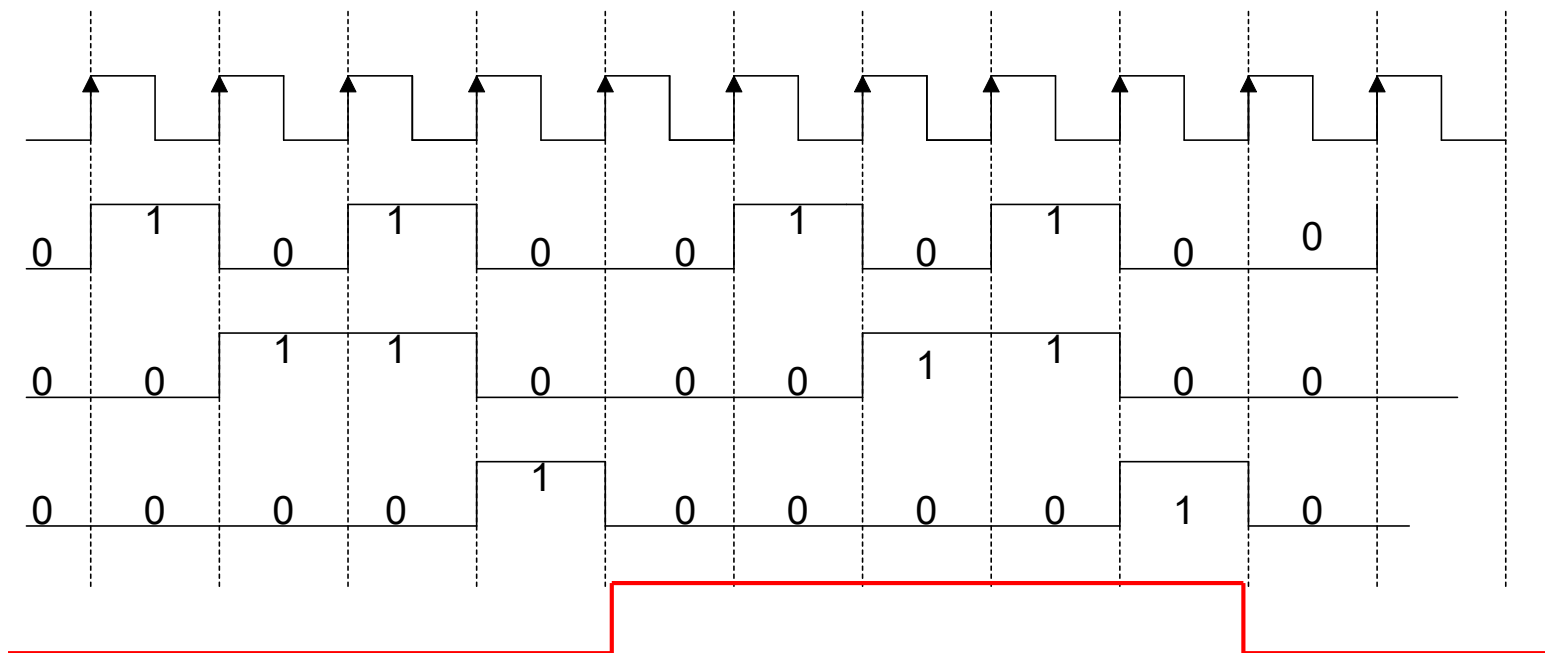 The idea is to generate a divide by 5 counter first and then divide it again by 2 to get the required waveform




 


Alternatively design a divide by 10 counter with the following states

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0

 Example From a frequency of 10KHz, generate the following signal of frequency 2KHz



 
A divide by 5 counter is required that has 5 states.




A will give the required waveform.

Ring Counter


T_3	T_2	T_1	T_0
0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0

 

Alternative Implementation

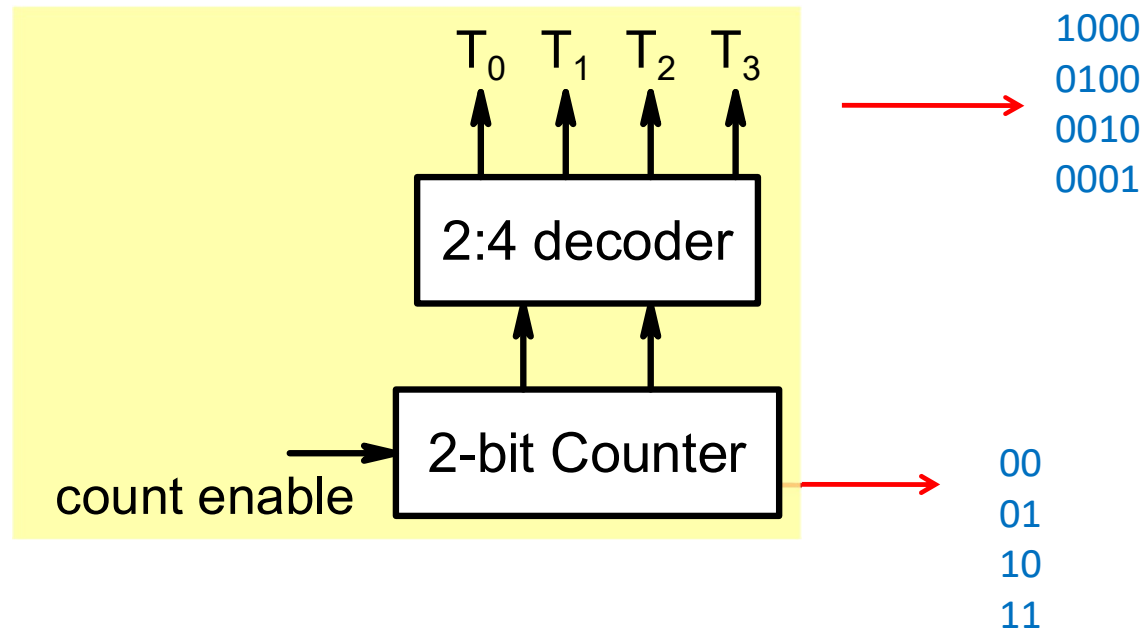


Ripple Counter

 

T FF toggles when $T = 1$; otherwise Hold state


Clock is negative edge Triggered

Ripple Counter

 

0	1	2	3	4	5	-----15	
0	1	0	1	0	1	-----1	0
0	0	1	1	0	0	-----1	0
0	0	0	0	1	1	-----1	0
0	0	0	0	0	0	-----1	0

Ripple Down Counter

 

0 1 0


0 1 1

0 1 1

0 1 1


BCD Ripple Counter

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

 

BCD Ripple Counter

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

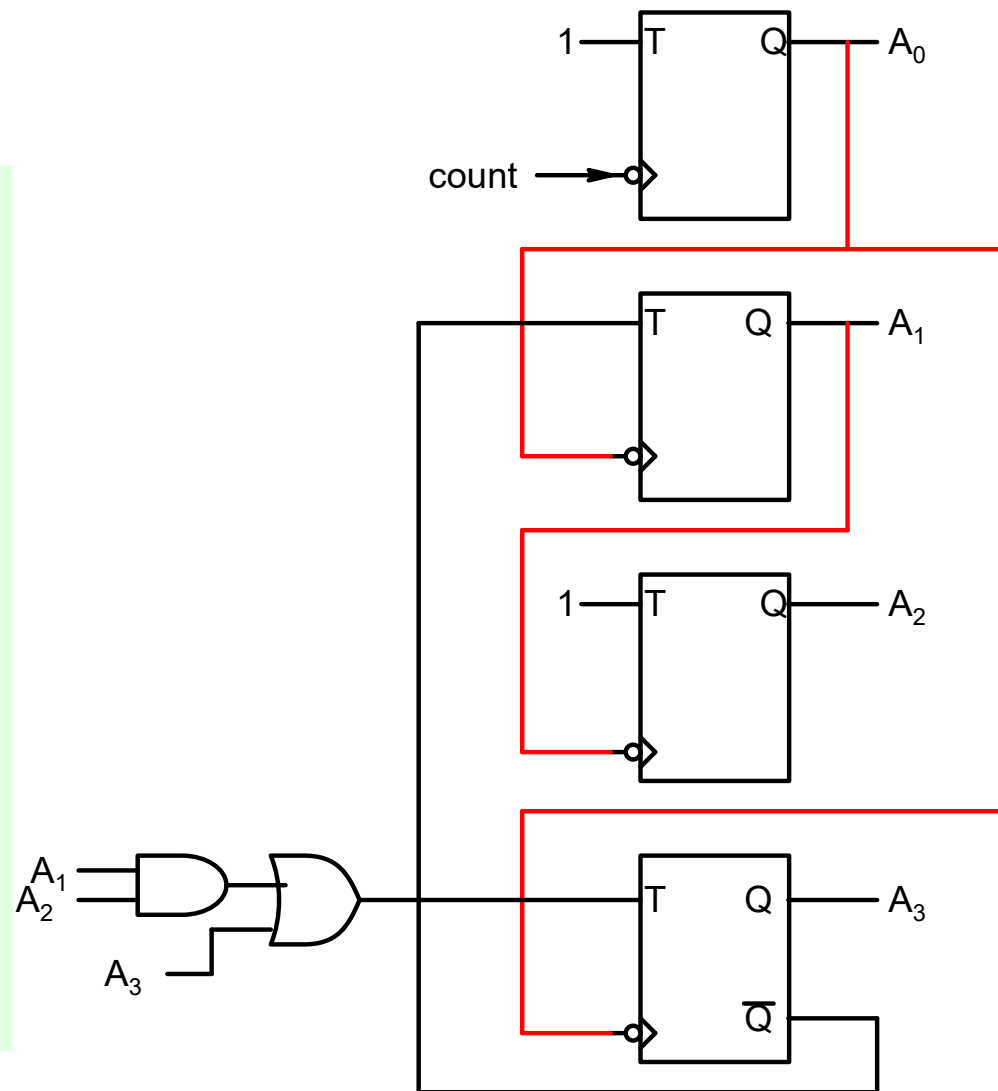

Cascading of BCD counters

