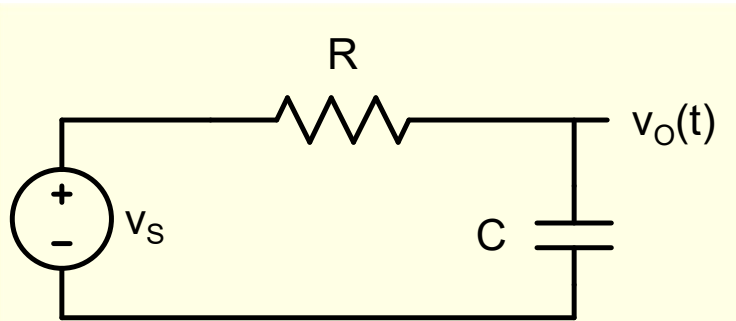


ESC201T : Introduction to Electronics

Lecture 16: Bode Plots and Filters


B. Mazhari
Dept. of EE, IIT Kanpur

Frequency Response



$$v_S(t) = v_{S0} \cos(\omega t)$$

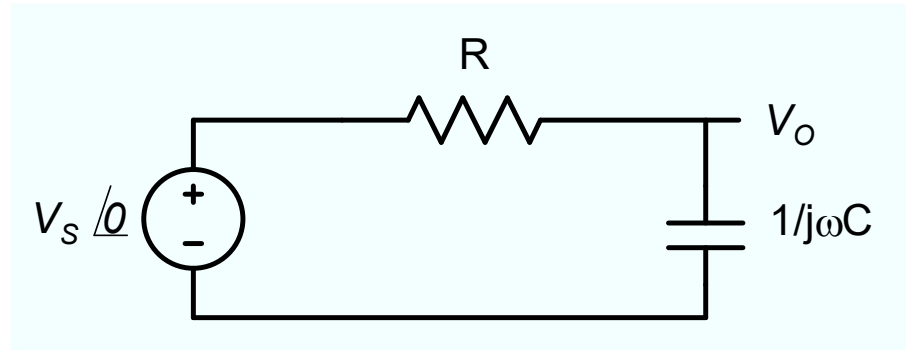
$$H(\omega) = \frac{V_O(\omega)}{V_S(\omega)}$$



$$H(\omega) = \frac{1}{1 + j\omega CR}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$$


$$\phi(\omega) = -\tan^{-1}(\omega CR)$$

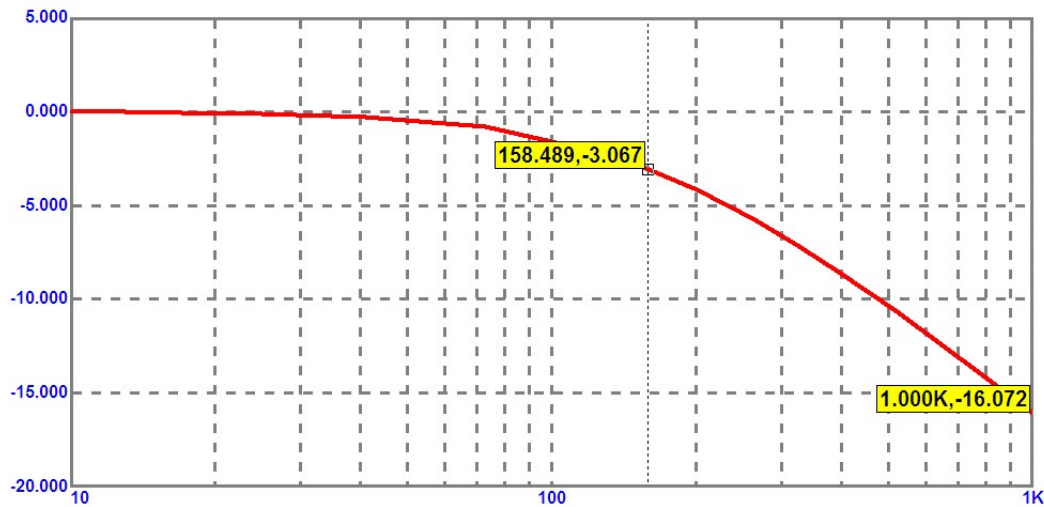


Sketching of Transfer function

$$H(\omega) = \frac{10}{1 + j\frac{\omega}{10^3}} \times \frac{1}{1 + j\frac{\omega}{10^4}}$$

$$20\text{Log}_{10}(|H(\omega)|) = 20 - 10\text{Log}_{10}(1 + (\frac{\omega}{10^3})^2) - 10\text{Log}_{10}(1 + (\frac{\omega}{10^4})^2)$$

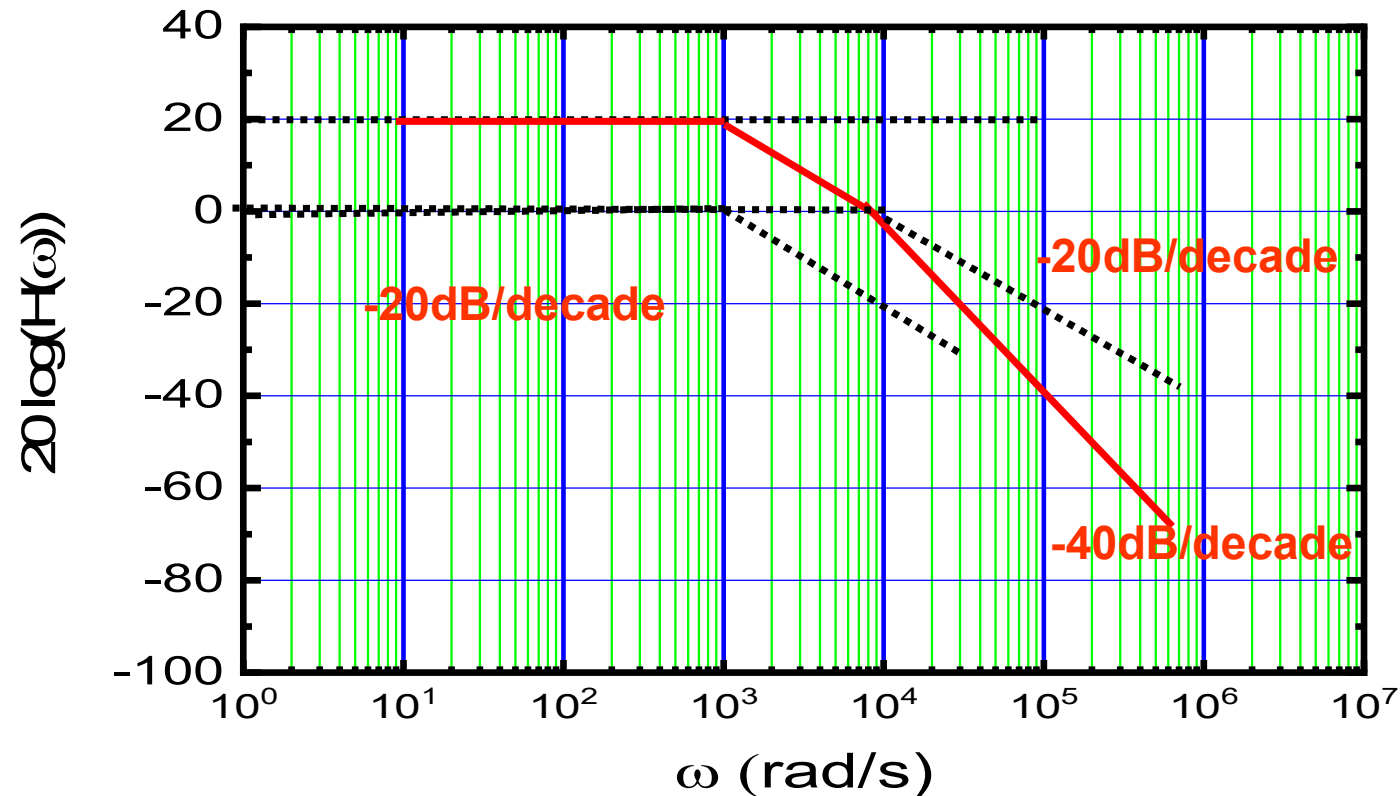

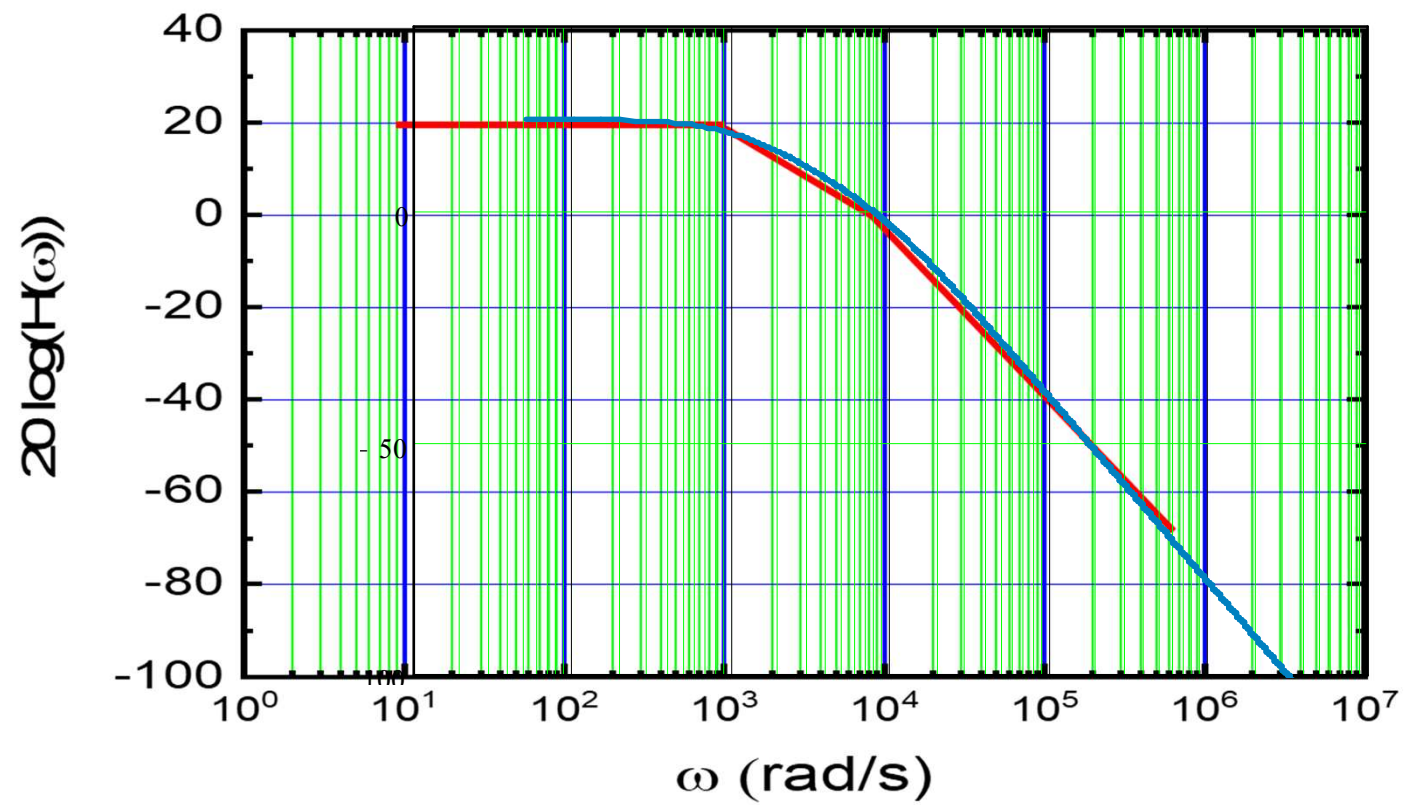


Phase Plot

$$\varphi(\omega) = -\tan^{-1}(\omega/\omega_o)$$

$$\omega \rightarrow 0, \phi \rightarrow 0 \quad \omega \rightarrow \infty, \phi \rightarrow -90^\circ$$

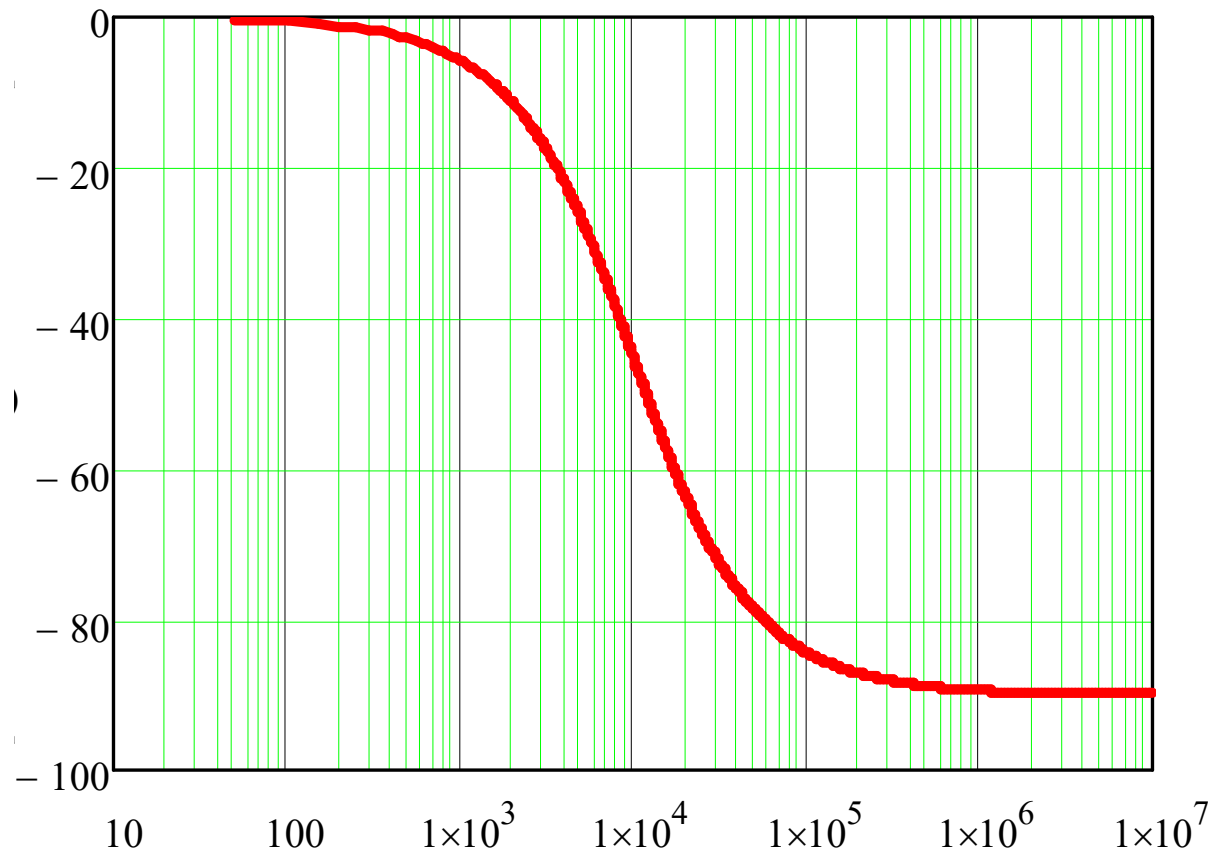
$$\omega = \omega_o, \phi \rightarrow -45^\circ$$



Sketching of Transfer function

$$H(\omega) = \frac{10}{1 + j\frac{\omega}{10^3}} \times \frac{1}{1 + j\frac{\omega}{10^4}} \times \frac{1}{1 + j\frac{\omega}{10^5}}$$

$$20\text{Log}_{10}(|H(\omega)|) = 20 - 10\text{Log}_{10}(1 + (\frac{\omega}{10^3})^2) - 10\text{Log}_{10}(1 + (\frac{\omega}{10^4})^2) - 10\text{Log}_{10}(1 + (\frac{\omega}{10^5})^2)$$

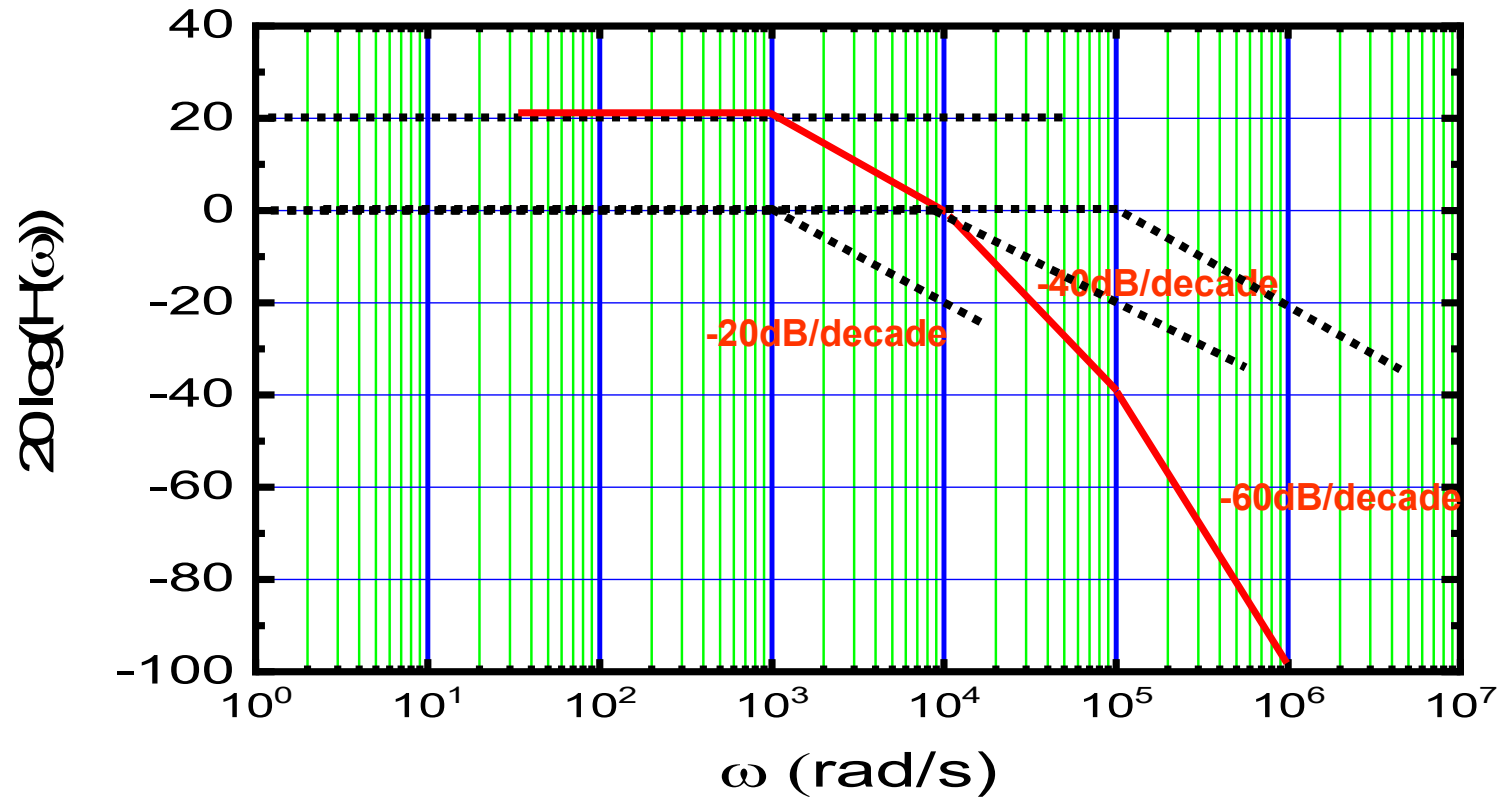


Phase Plot

$$H(\omega) = \frac{10}{1 + j \frac{\omega}{10^3}} \times \frac{1}{1 + j \frac{\omega}{10^4}}$$


$$\begin{aligned} \omega \rightarrow 0, \phi \rightarrow 0 & \quad \omega \rightarrow \infty, \phi \rightarrow -90^\circ \\ \omega = \omega_0, \phi \rightarrow -45^\circ \end{aligned}$$
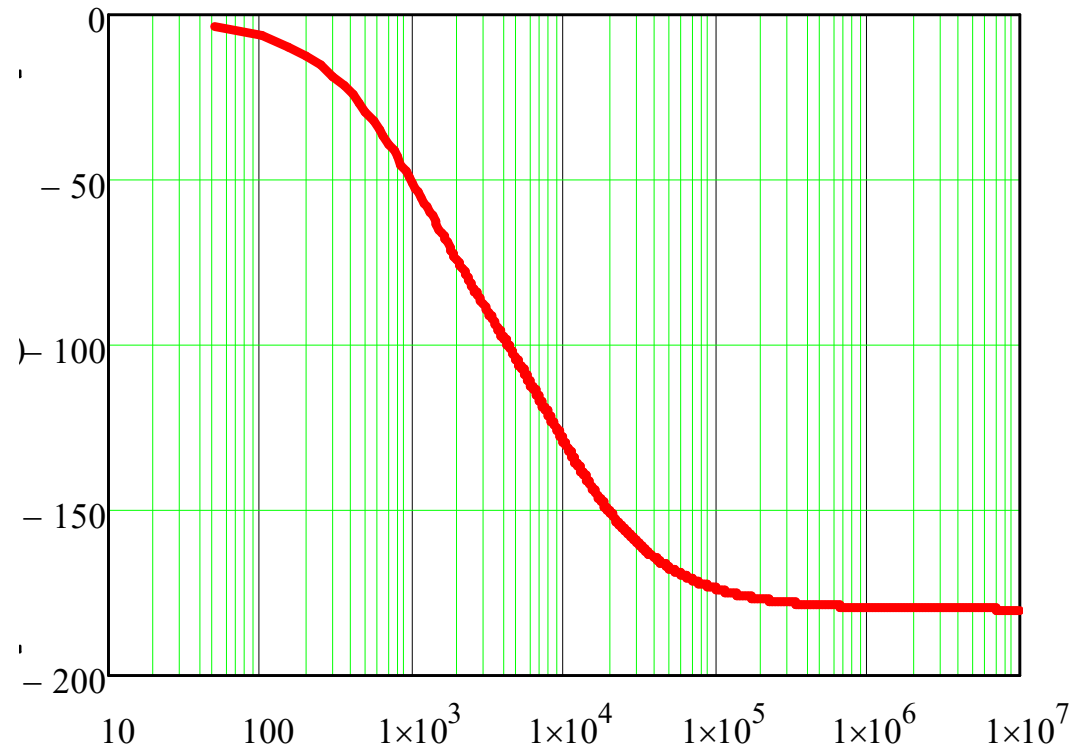
$$\varphi(\omega) = -\tan^{-1}(\omega/10^3) - \tan^{-1}(\omega/10^4)$$




$$H(\omega) = (j\omega)^N$$

$$20\text{Log}_{10}(|H(\omega)|) = 20N \times \text{Log}_{10}(\omega)$$

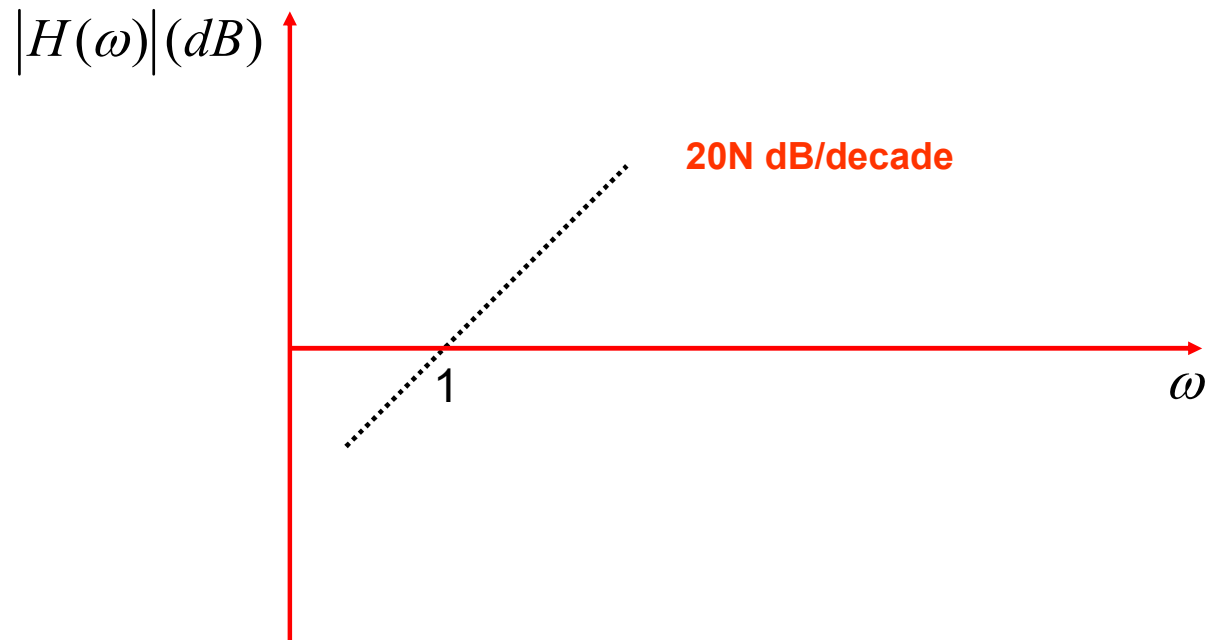

Example

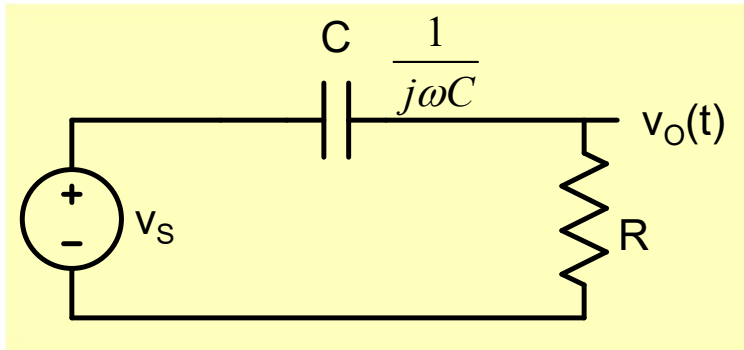

$$H(\omega) = \frac{V_o(\omega)}{V_s(\omega)}$$

$$H(\omega) = \frac{j\omega CR}{1 + j\omega CR}$$


$$H(\omega) = \frac{j(\omega / \omega_{3dB})}{1 + j(\omega / \omega_{3dB})}$$

$$\omega_{3dB} = \frac{1}{RC} \quad ; \quad f_{3dB} = \frac{1}{2\pi RC}$$


$$20\text{Log}_{10}(|H(\omega)|) = 20\log_{10}\left(\frac{\omega}{\omega_{3dB}}\right) - 10\log_{10}\left(1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2\right)$$

$$\phi(\omega) = 90 - \tan^{-1}(\omega CR)$$



$$20\text{Log}_{10}(|H(\omega)|) = 20\log_{10}\left(\frac{\omega}{\omega_{3dB}}\right) - 10\log_{10}\left(1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2\right)$$

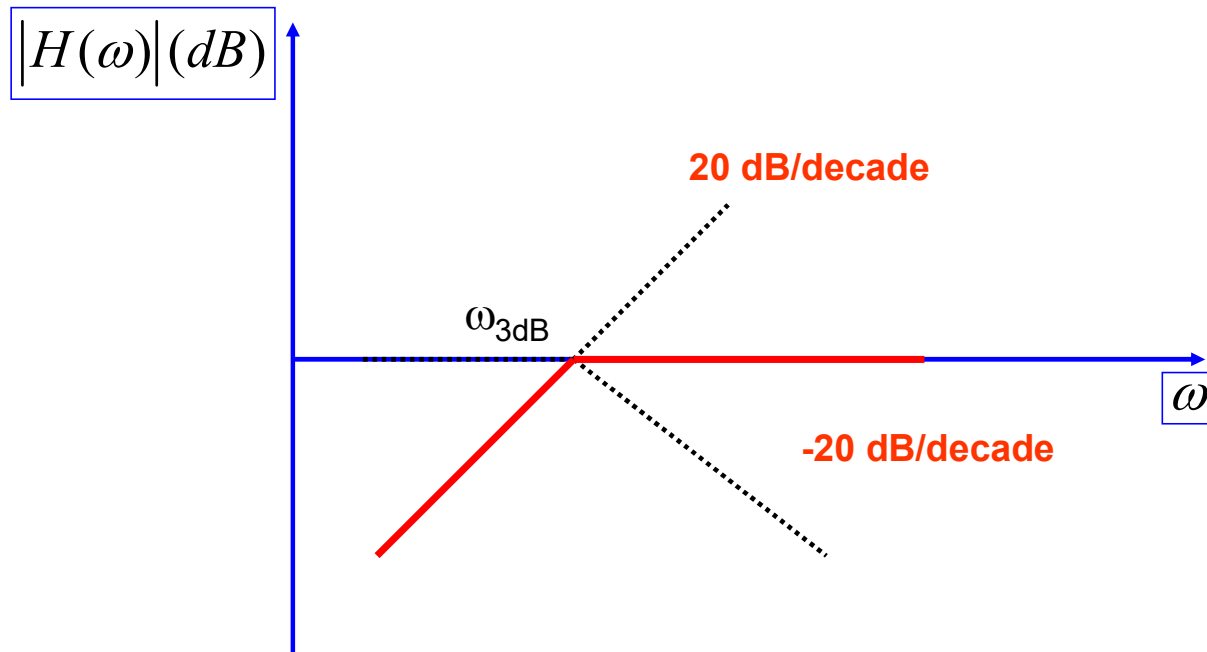

High Pass Filter

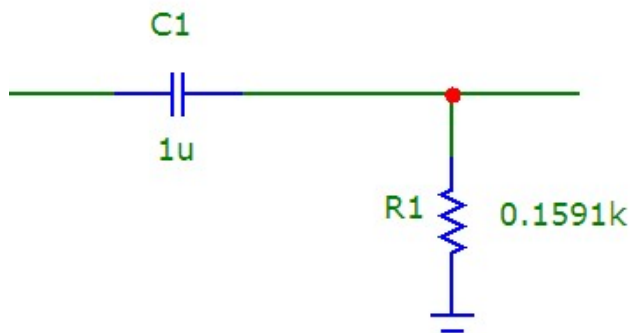

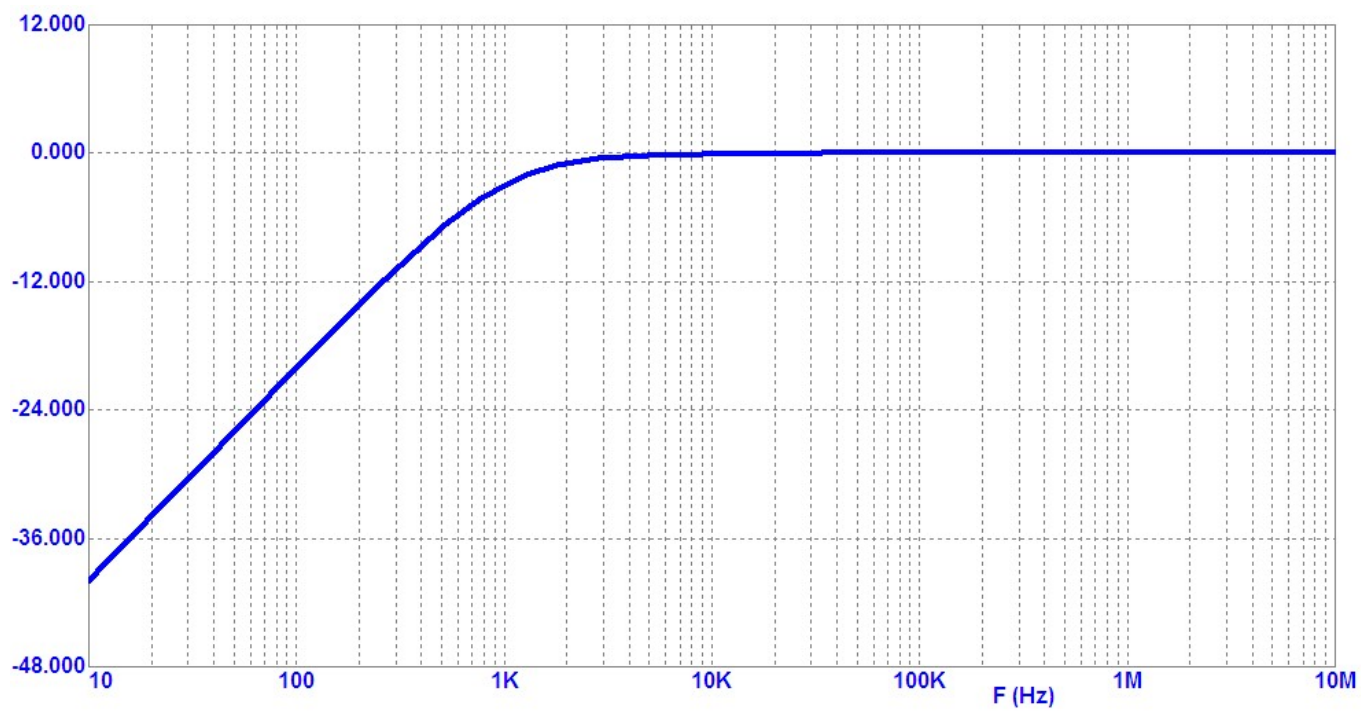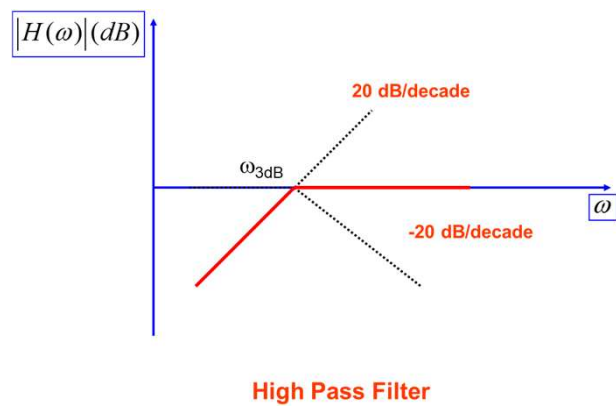
$$f_{3dB} = \frac{1}{2\pi RC} = 10^3 \text{ Hz}$$



Bode Plot segments

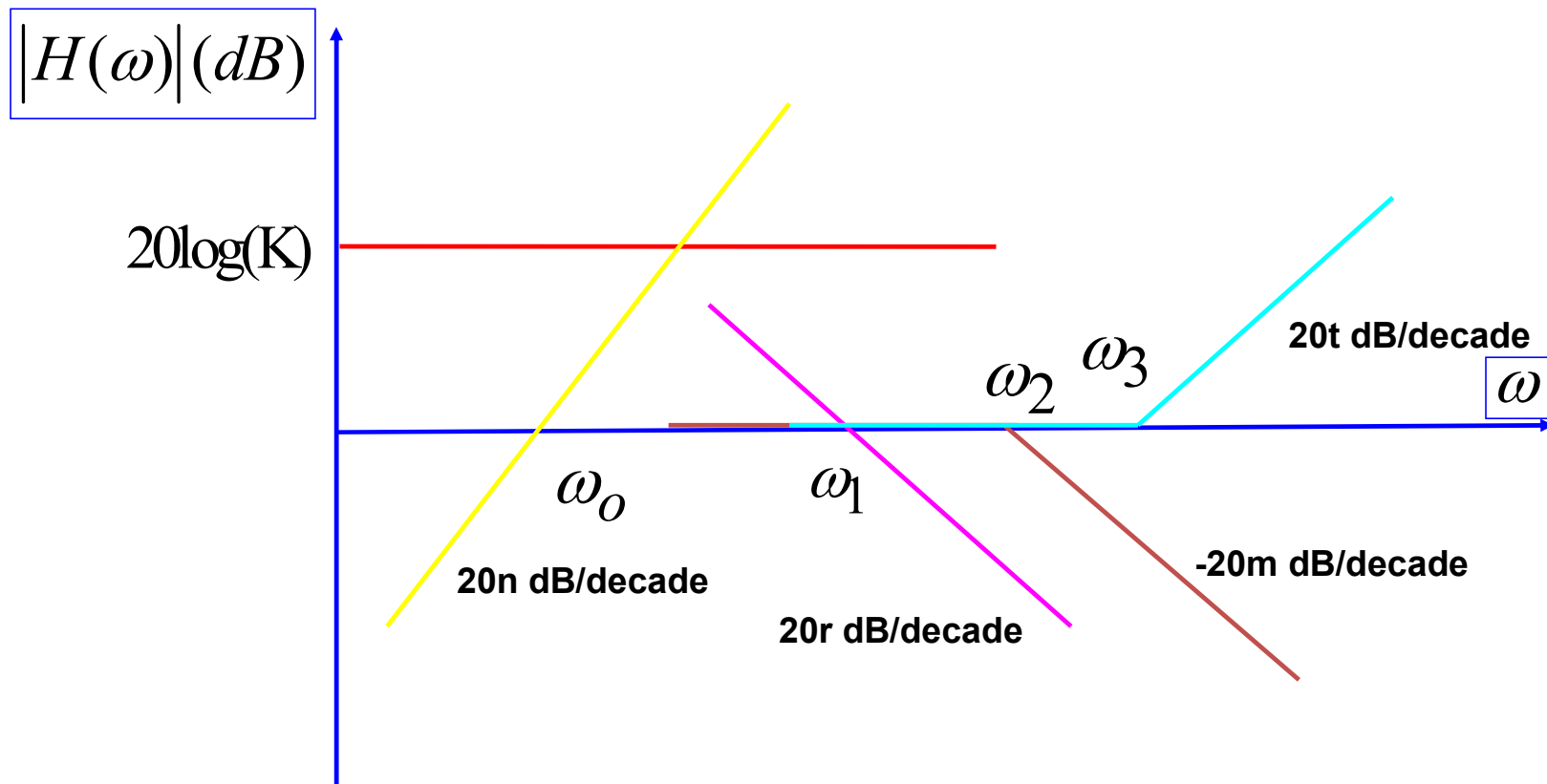
$$H(\omega) = K \times j(\omega / \omega_o)^n \times \frac{1}{j(\omega / \omega_1)^r} \times \frac{1}{\{1 + j(\omega / \omega_2)\}^m} \times \{1 + j(\omega / \omega_3)\}^t$$




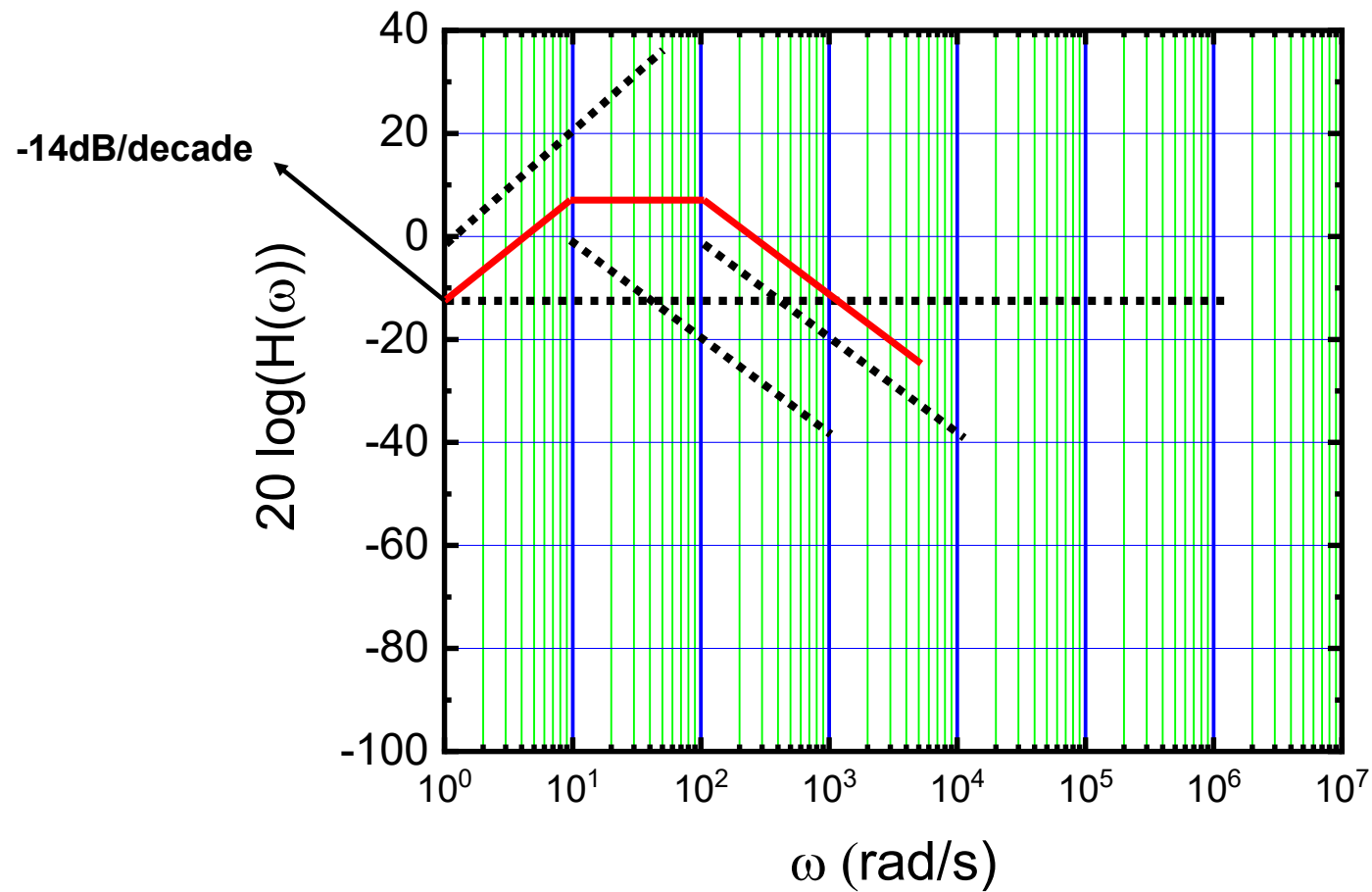Example:


$$H(\omega) = 200 \times j\omega \times \frac{1}{10 + j\omega} \times \frac{1}{100 + j\omega}$$





$$H(\omega) = 0.2 \times j\omega \times \frac{1}{1 + j\frac{\omega}{10}} \times \frac{1}{1 + j\frac{\omega}{100}}$$



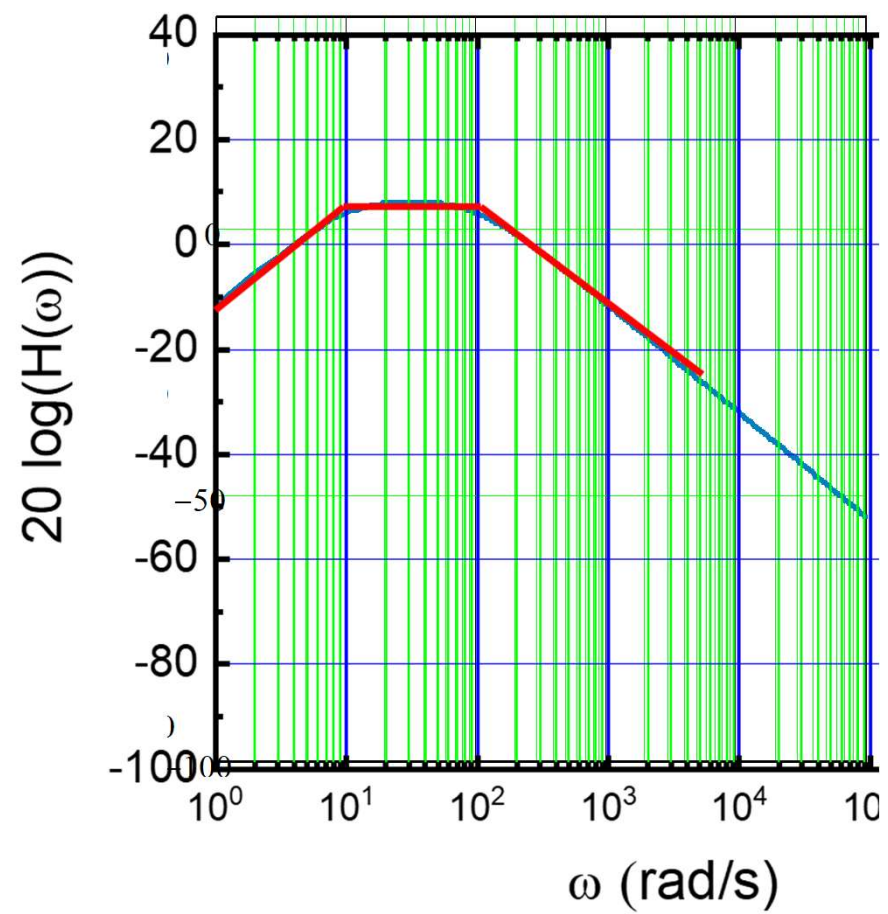


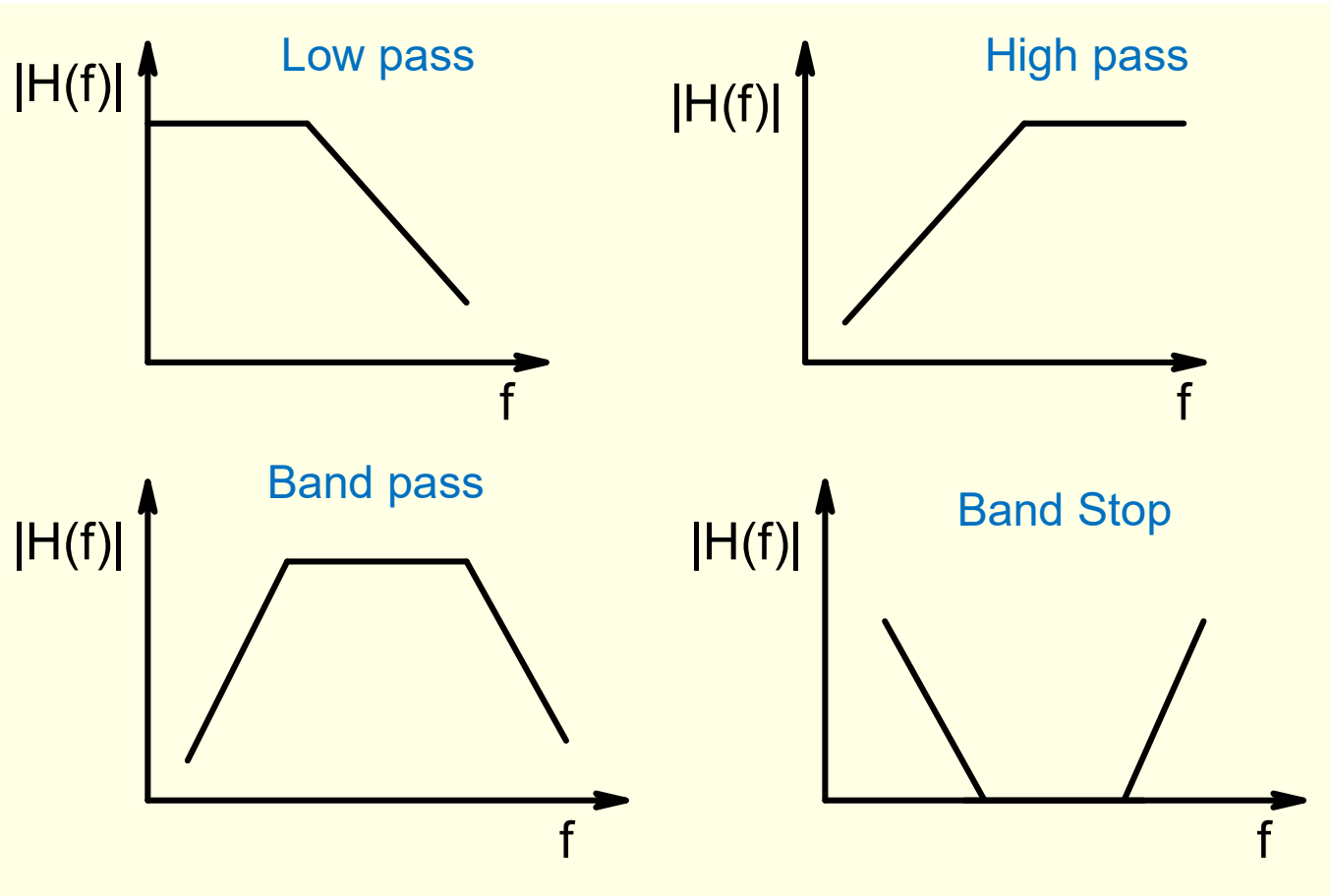Filter -pass a band of frequency and reject the remaining




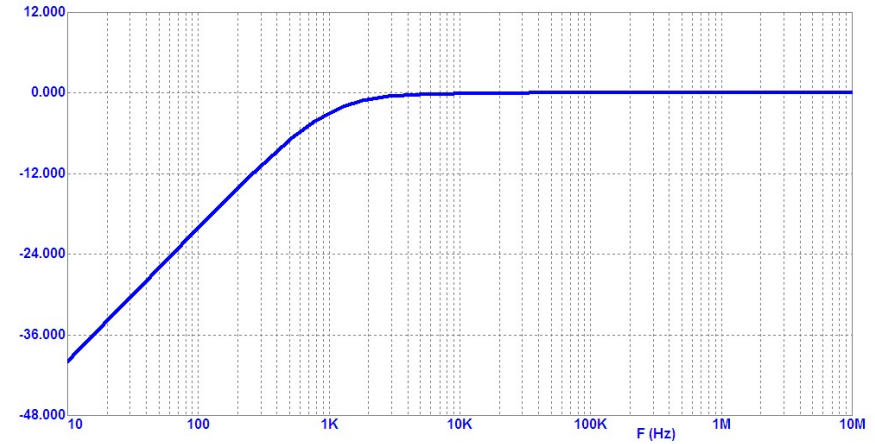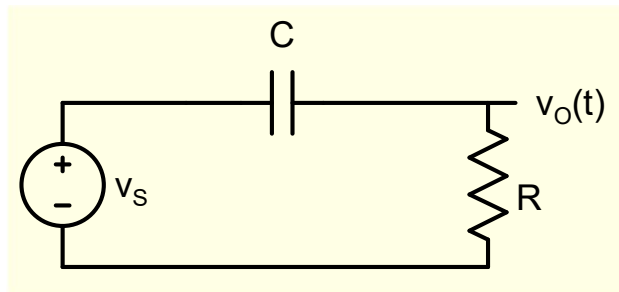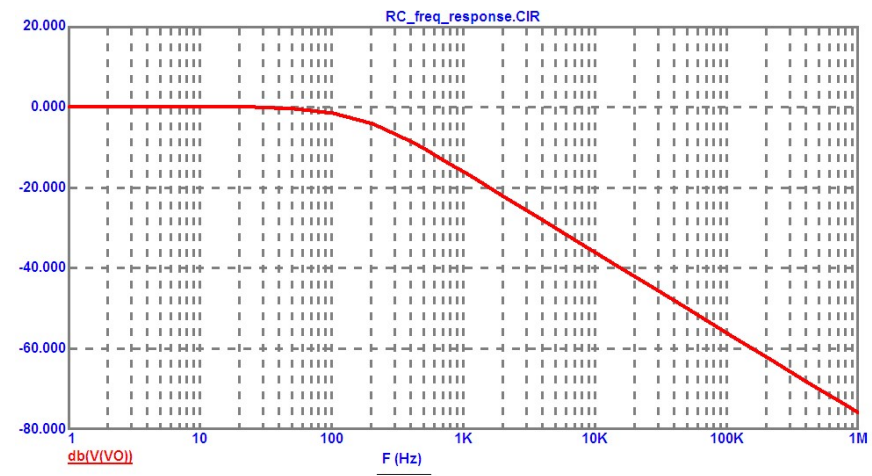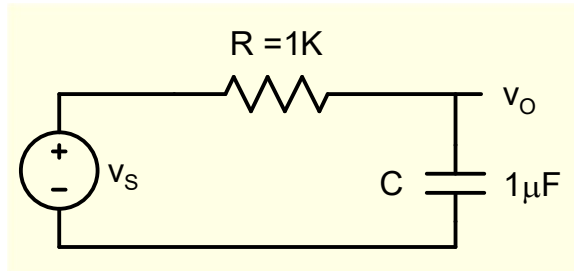

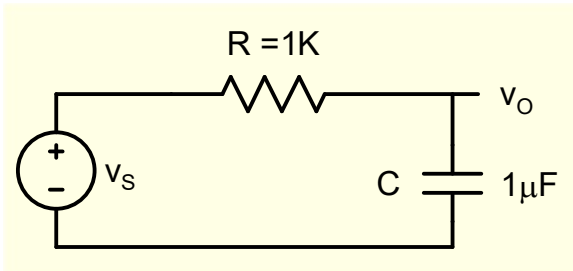
3dB Frequency of single capacitor filters


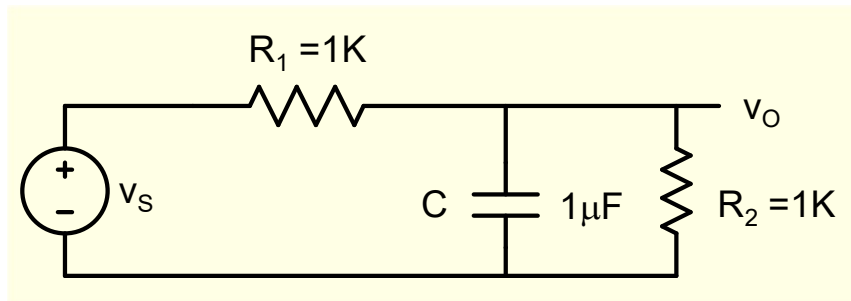
$$\omega_{3dB} = \frac{1}{RC} = 10^3 \text{ rad/s}$$





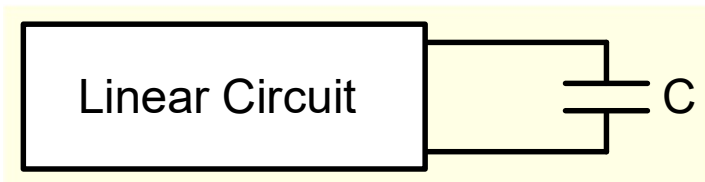
$$\omega_{3dB} = \frac{1}{R_1 \parallel R_2 C}$$




$$\omega_{3dB} = \frac{1}{\tau} = \frac{1}{R_{eq} C}$$

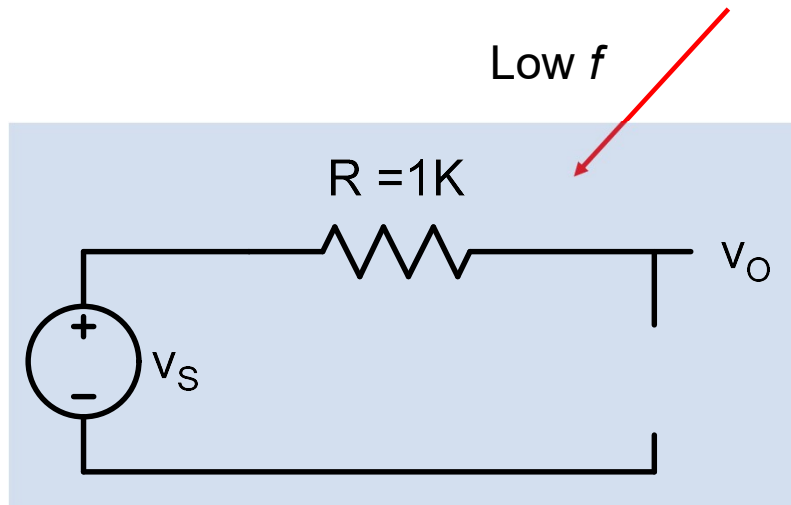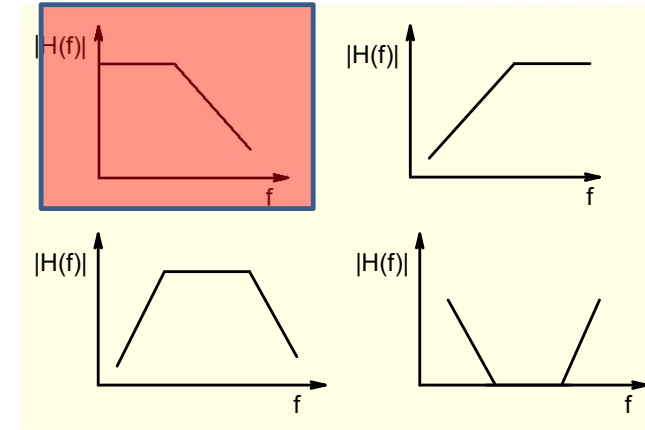
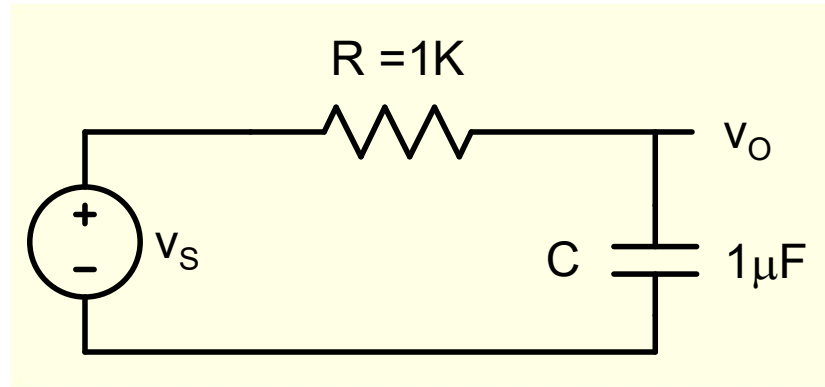
One can often tell the type of filter by looking at behavior at very low and very high frequencies and keeping in mind that capacitor offers very high impedance at low frequencies and very low impedance at high frequencies



$$V_O \sim V_S$$

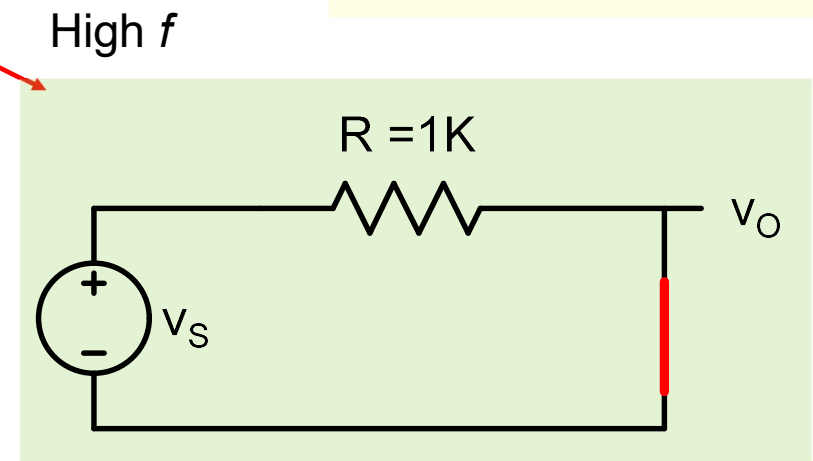


$$V_O \sim 0$$

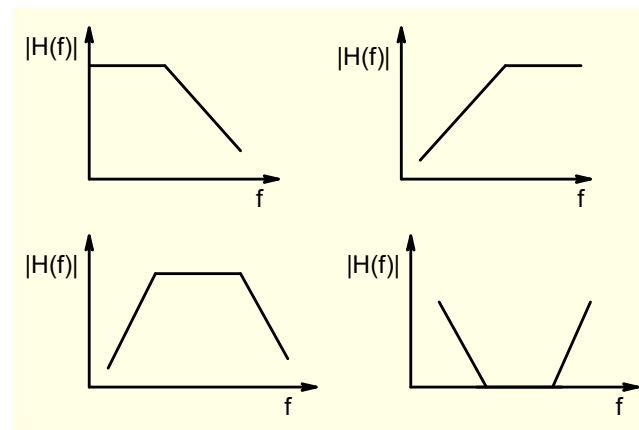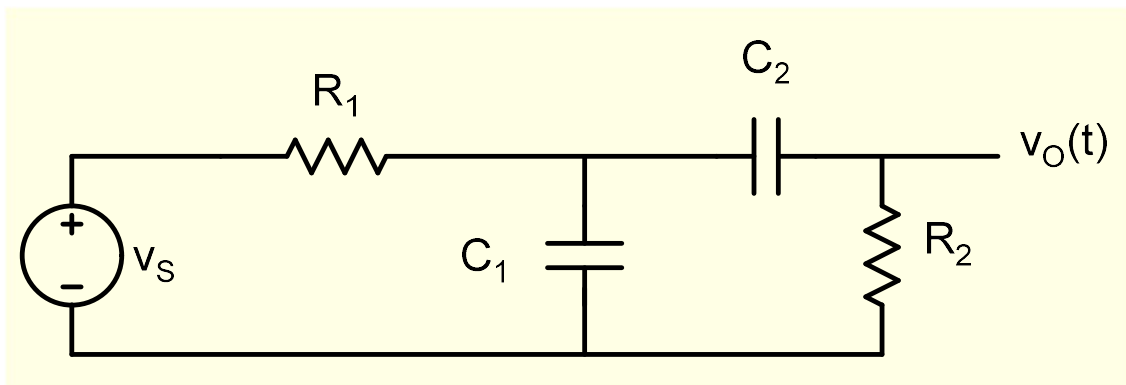


Low f

High f



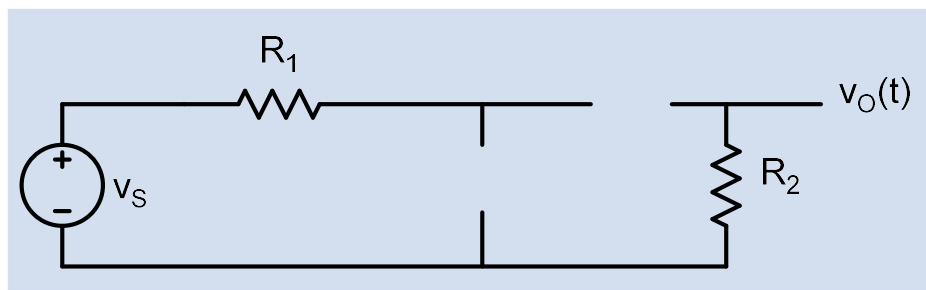


$V_O \sim 0$

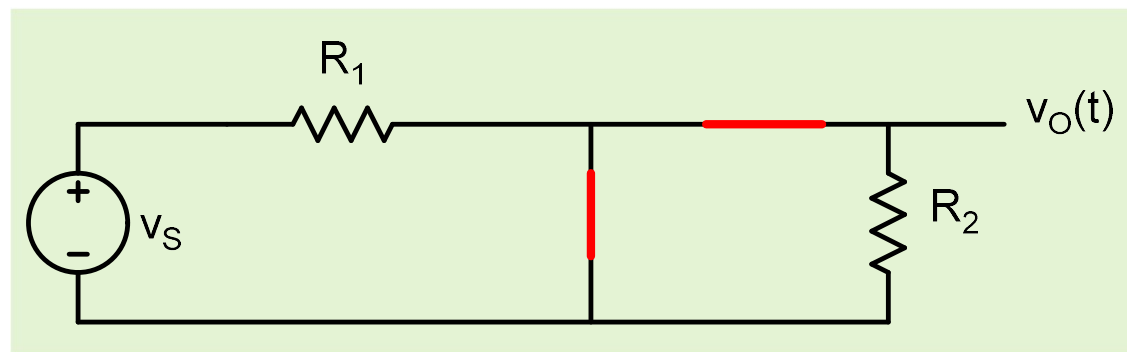

$V_O \sim 0$



Bandpass Filter

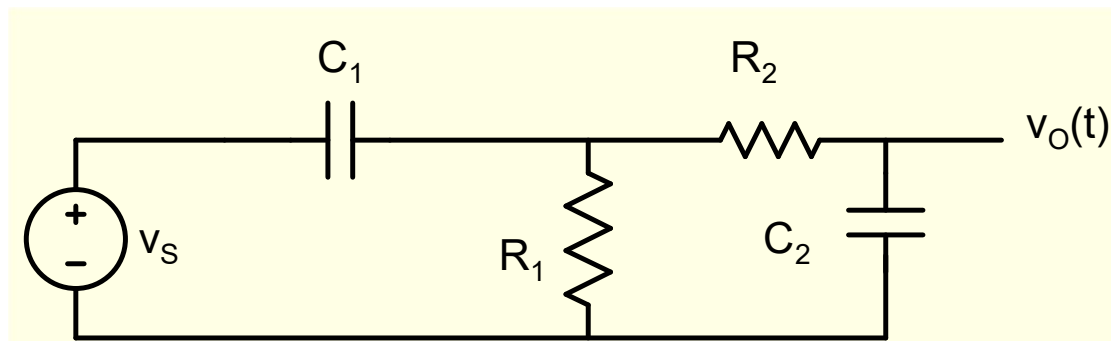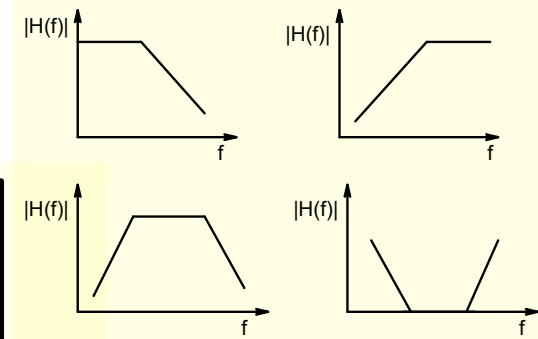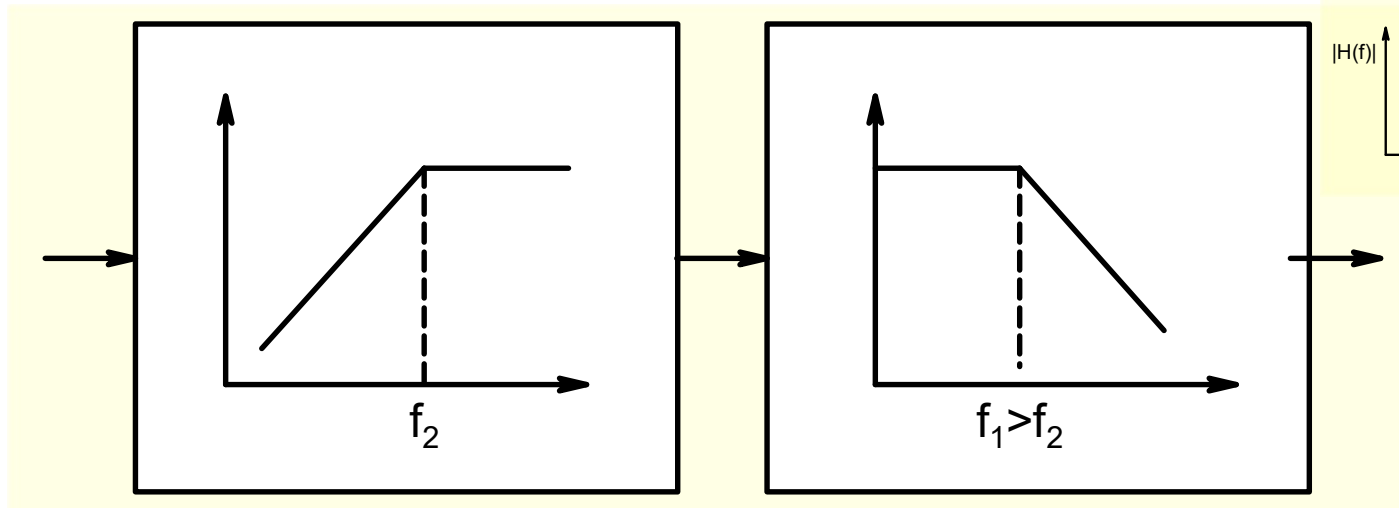



$$f_2 \cong \frac{1}{2\pi R_1 C_1} ; f_1 \cong \frac{1}{2\pi R_2 C_2}$$

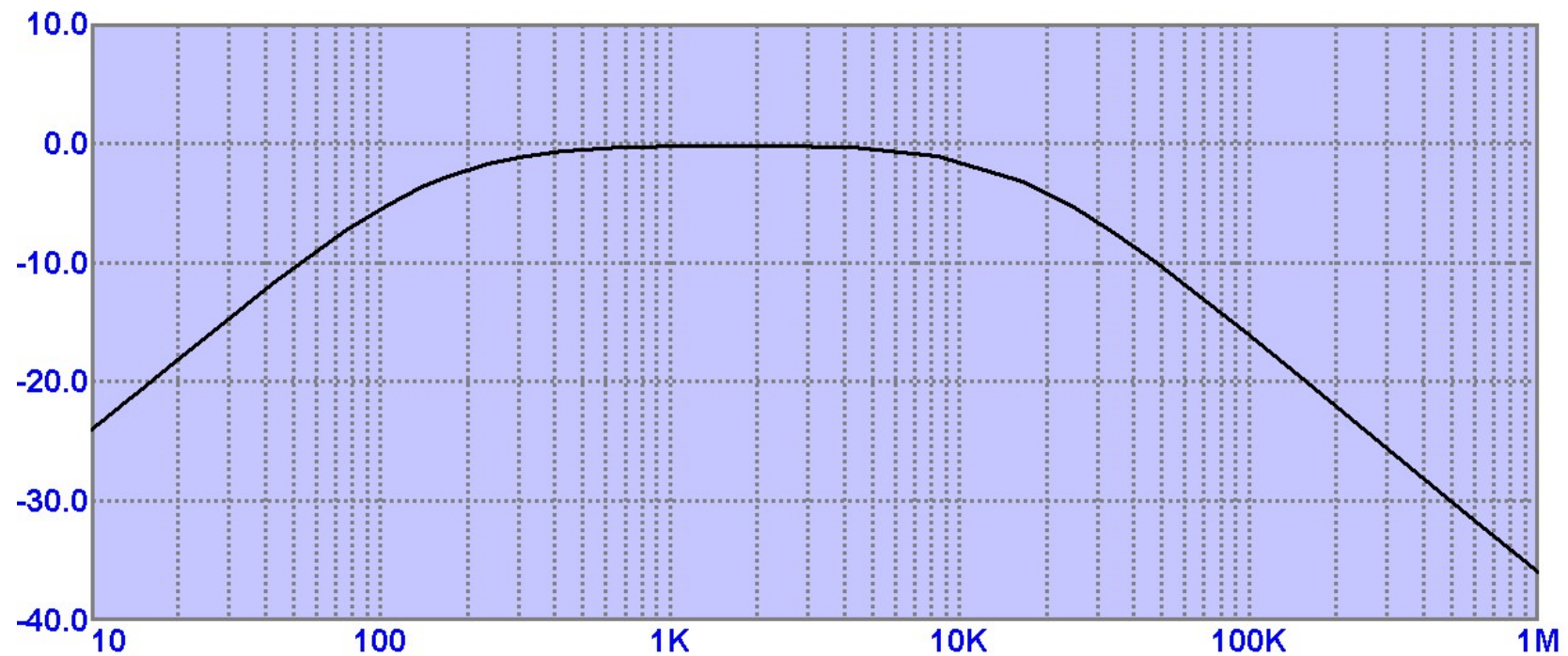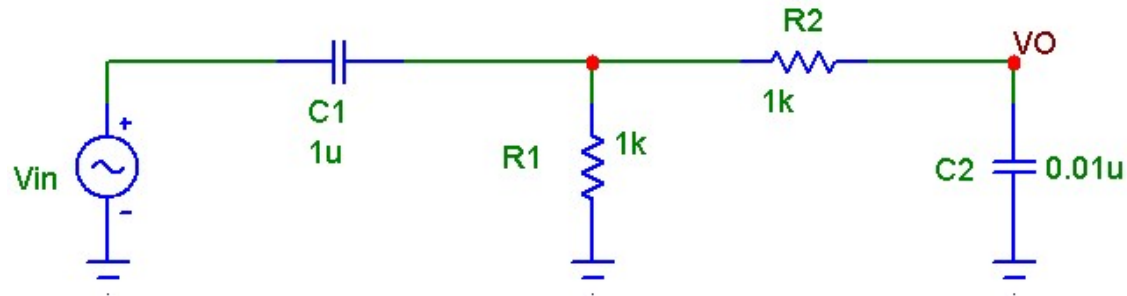Example: Band Pass filter

$$f_2 \cong \frac{1}{2\pi R_1 C_1} ; f_1 \cong \frac{1}{2\pi R_2 C_2}$$




Band-Stop Filter

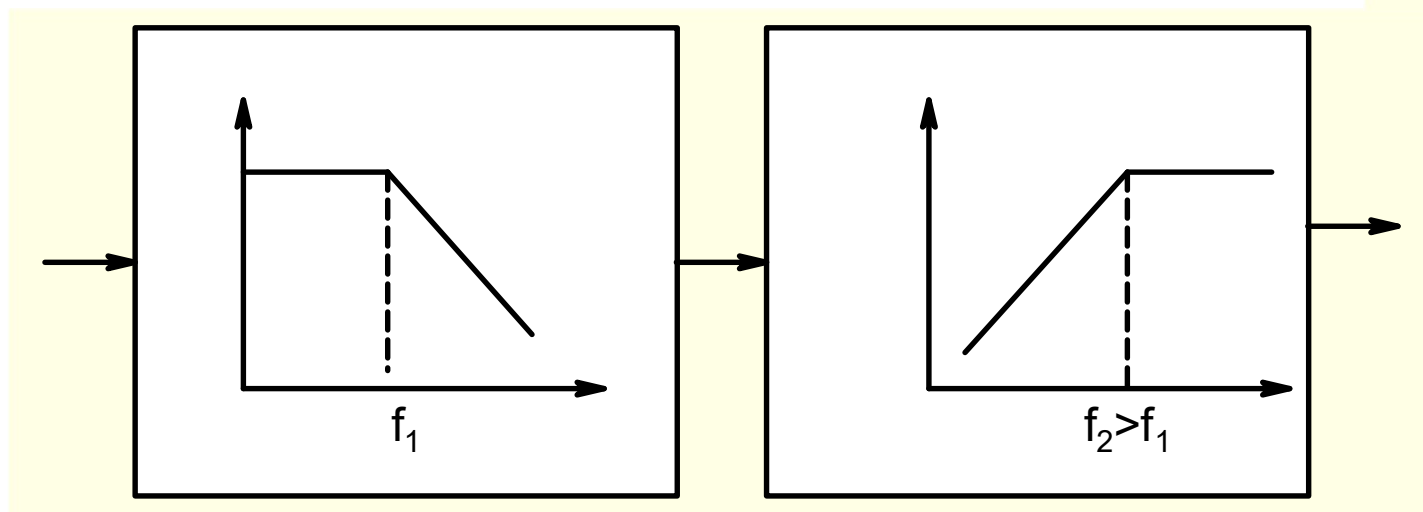
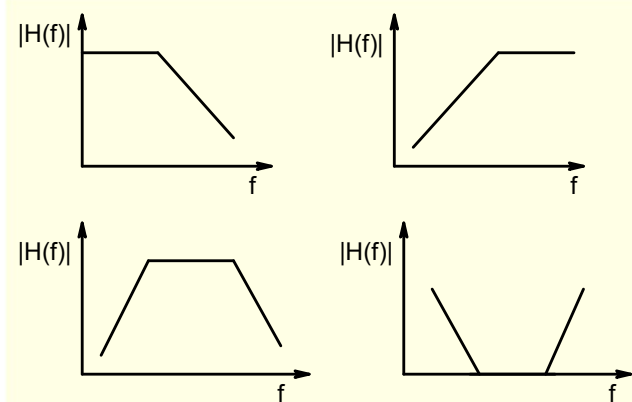


Will this work?


What kind of filter is this?

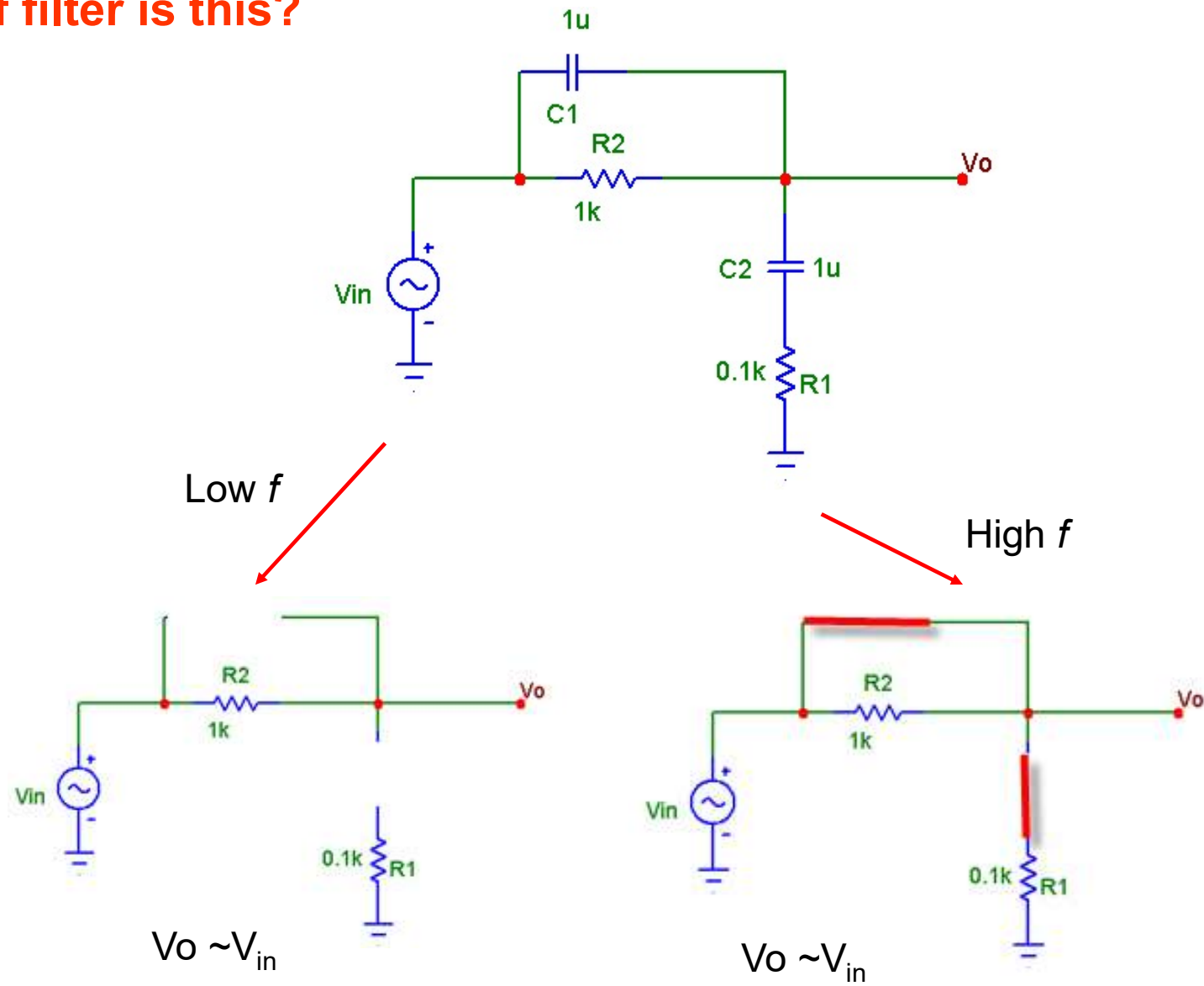

What does this circuit do?

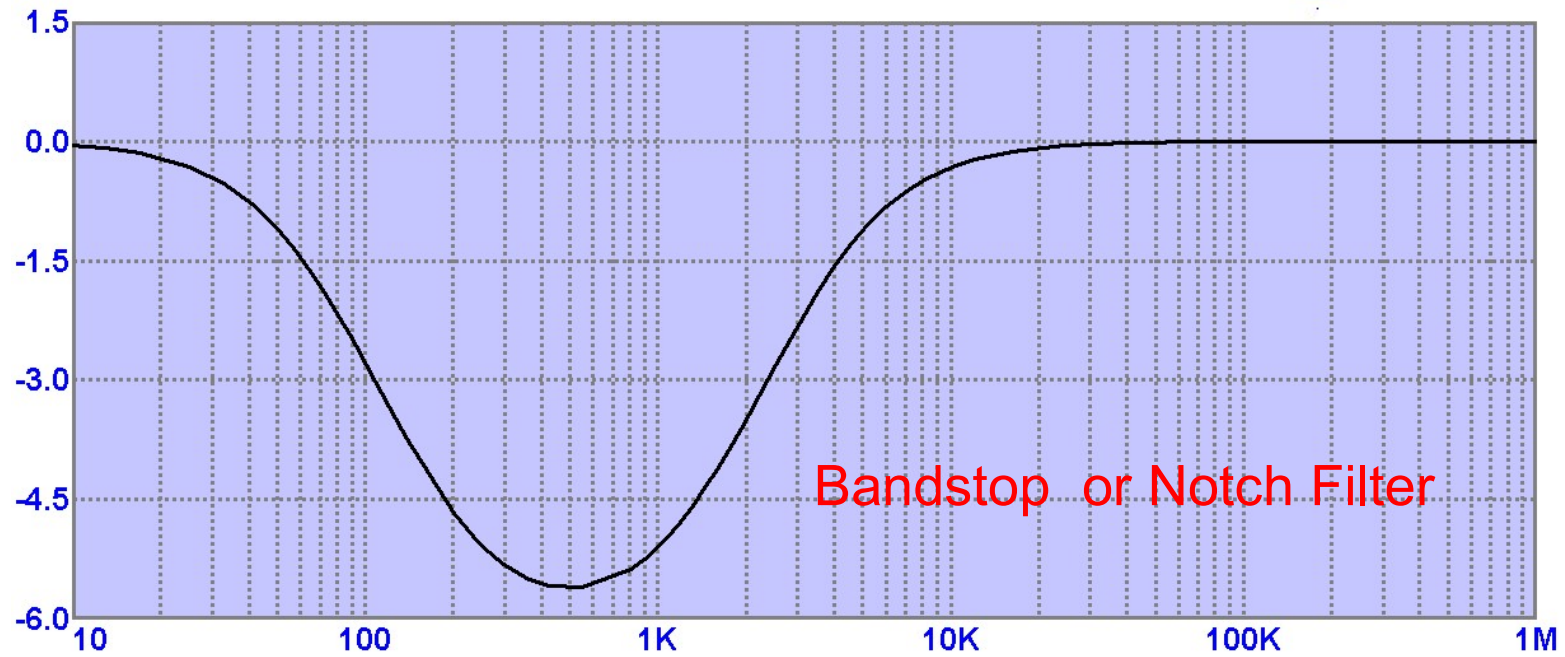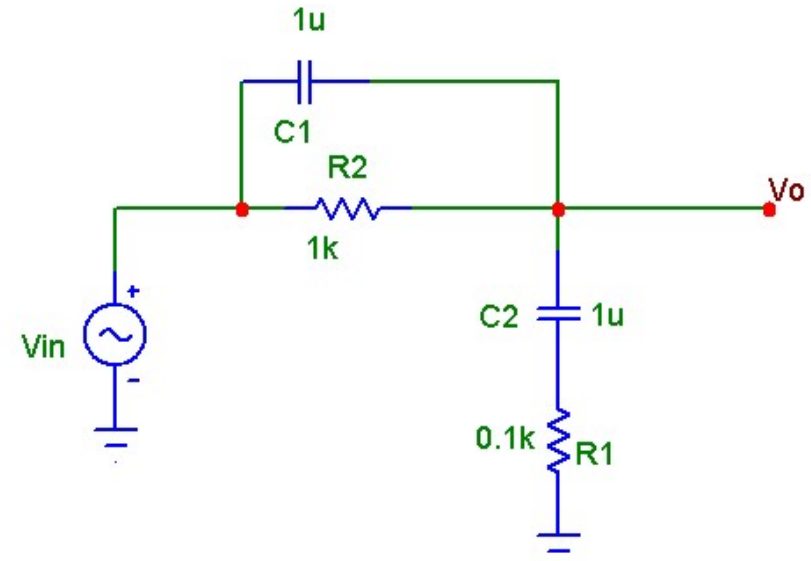


R-L Circuits (Filters)

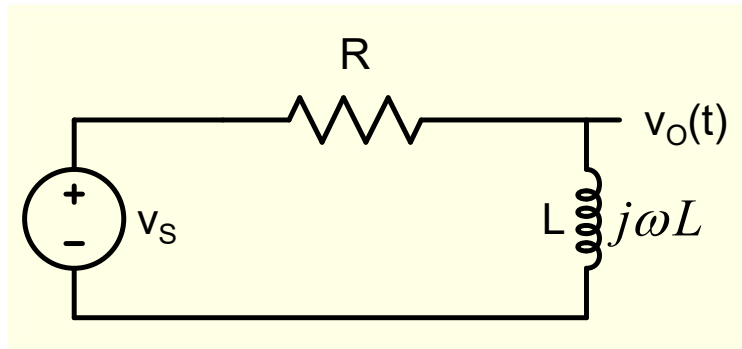


$$H(\omega) = \frac{V_o(\omega)}{V_s(\omega)}$$

$$H(\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j(\omega / \omega_{3dB})}{1 + j(\omega / \omega_{3dB})}$$

$$\omega_{3dB} = \frac{R}{L}$$

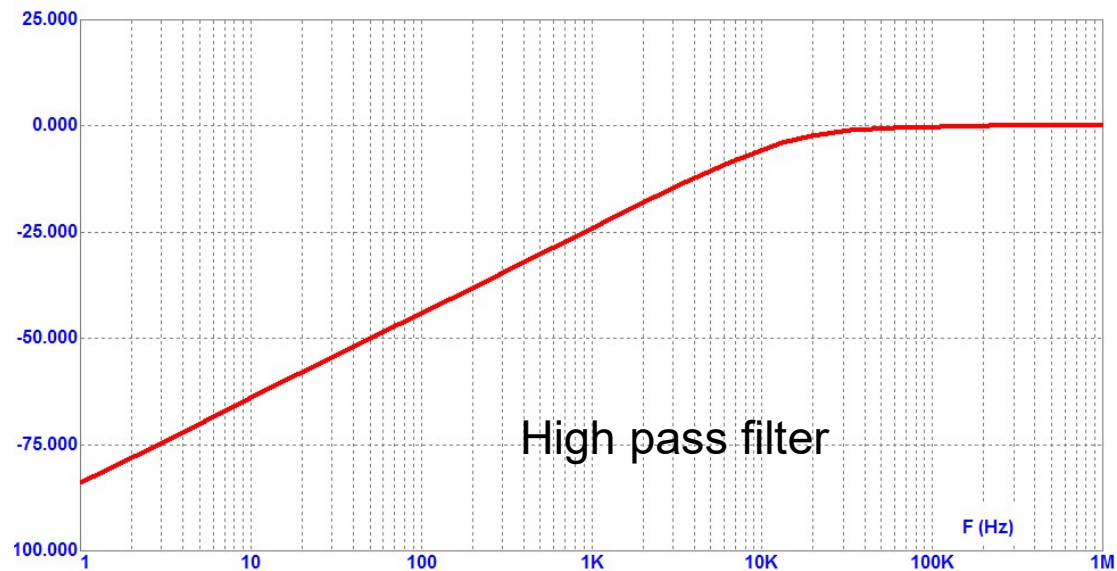

R-L Circuits

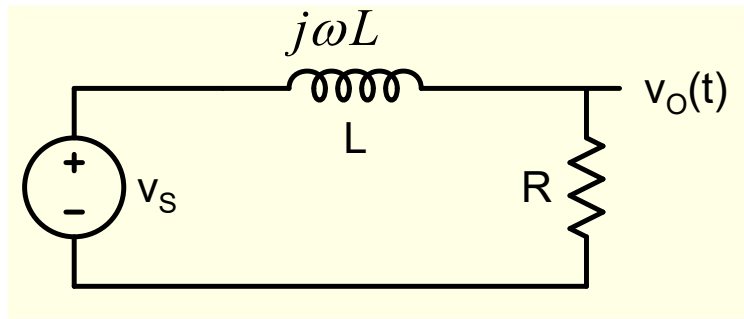

$$H(\omega) = \frac{V_o(\omega)}{V_s(\omega)}$$

$$H(\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + j(\omega / \omega_{3dB})}$$

$$\omega_{3dB} = \frac{R}{L}$$

