


ESC201T : Introduction to Electronics

Lecture 37: Sequential circuit design-1

B. Mazhari
Dept. of EE, IIT Kanpur


Digital Circuits

Combinational Circuits

 


Output is determined by current values of inputs only.

Sequential Circuits

 

Output is determined in general by current values of inputs and past values of inputs/outputs as well.

NOR SR Latch

 


$Q = 1; \overline{Q} = 0$ Set State

$Q = 0; \overline{Q} = 1$ Reset State

S	R	Q	\overline{Q}	State
1	0	1	0	SET

NOR SR Latch

 


$Q = 1; \bar{Q} = 0$ Set State


$Q = 0; \bar{Q} = 1$ Reset State

S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	1	0	1	RESET

HOLD State


 


S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\overline{Q}	HOLD
1	1	0	0	INVALID

 





Both the outputs are well defined and 0. the first problem is that we do not get complementary output.

  A more serious problem occurs when we switch the latch to the hold state by changing RS from 11 \rightarrow 00 . Suppose the inputs do not change simultaneously and we get the situation 11 \rightarrow 01* \rightarrow 00






Q = 1

 

   

Q = 1

  
 
Suppose the inputs change as $RS = 11 \rightarrow 10^* \rightarrow 00$




Q = 0

So although output is well defined when we apply $RS = 11$, it becomes unpredictable once we switch the latch to hold state by applying $RS = 00$. That is why $RS = 11$ is not used as an input combination.

  The error can occur also due to unequal gate delays.





Suppose gate-1 is faster

 


Q = 1

  On the other hand suppose that gate-2 is faster.




 Again the output is unpredictable in general




Q = 0

NAND Latch

 


S	R	Q	\overline{Q}	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\overline{Q}	HOLD
0	0	1	1	INVALID

RS NAND Latch with Enable

 


Hold State

 


Enable	S	R	Q	\overline{Q}	State
0	x	x	Q	\overline{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\overline{Q}	Hold
1	1	1	0	0	Invalid

D latch


 


Enable	S	R	Q	\bar{Q}	State
0	x	x	Q	\bar{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\bar{Q}	Hold
1	1	1	0	0	Invalid


 


If $EN = 1$ then $Q = D$ otherwise the latch is in Hold state



Synchronous Sequential Circuits

  


Example

  


Example

 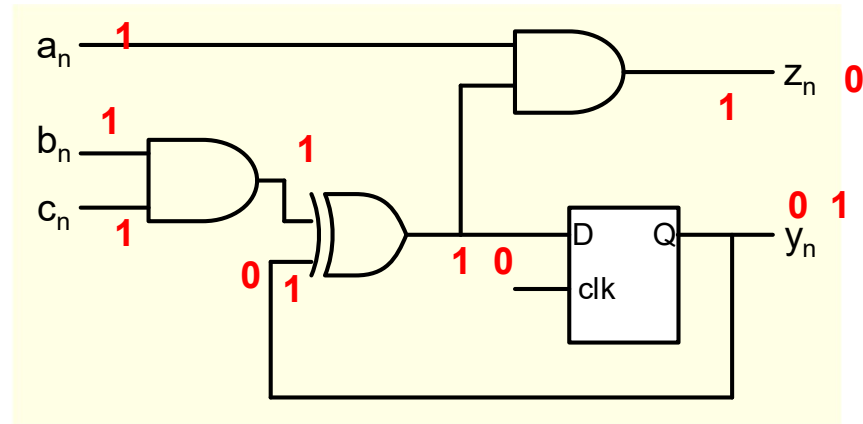



Problem with Latch

 

 Circuits are designed with the idea there would be single change in output or memory state in single clock cycle.





Edge Triggered Latch or Flip-flop

  


Positive edge triggered flipflop

  
Negative Edge Triggered Latch or Flip-flop




Master-Slave D Flip-flop

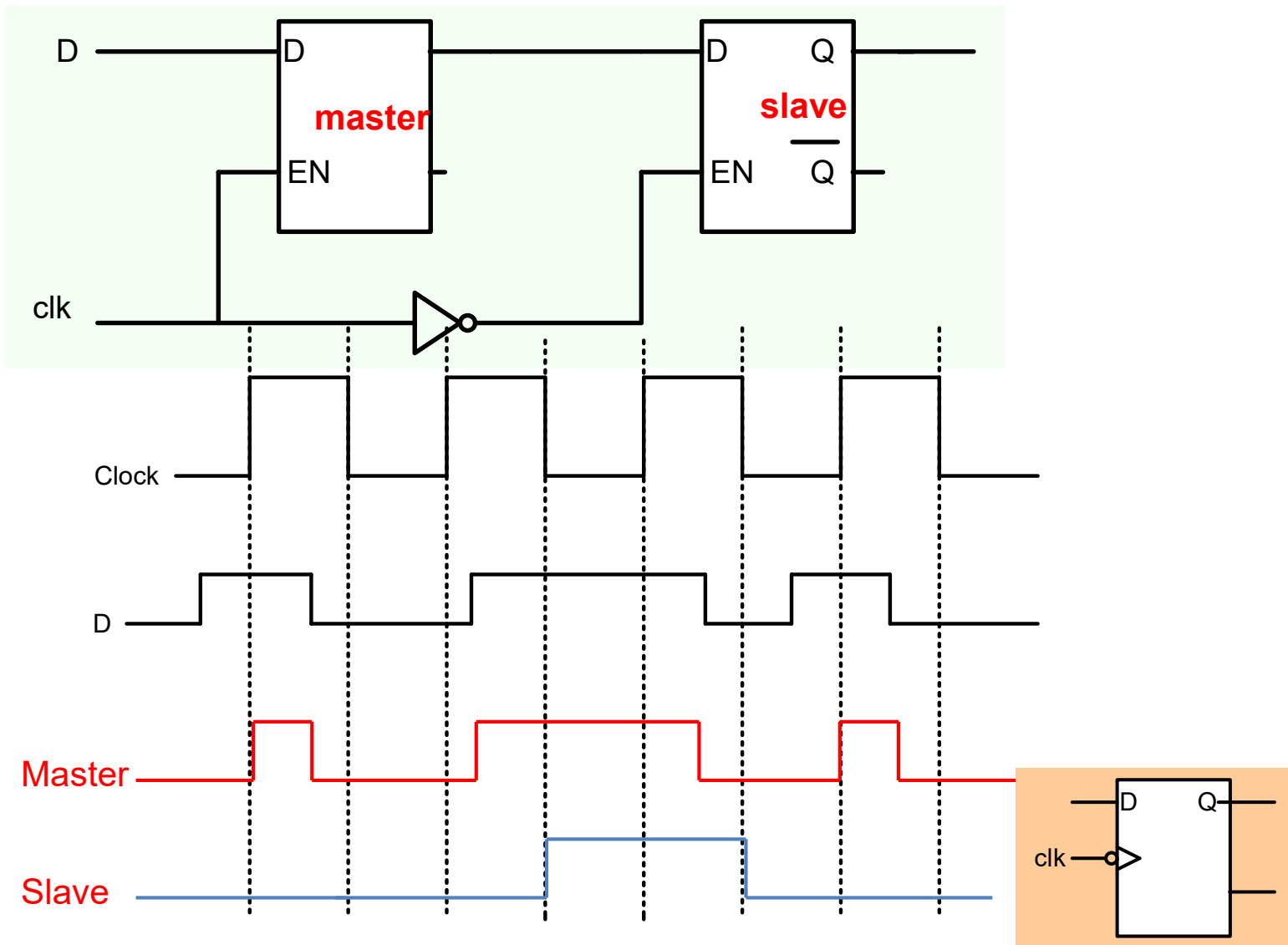

Positive edge triggered Flip-flop

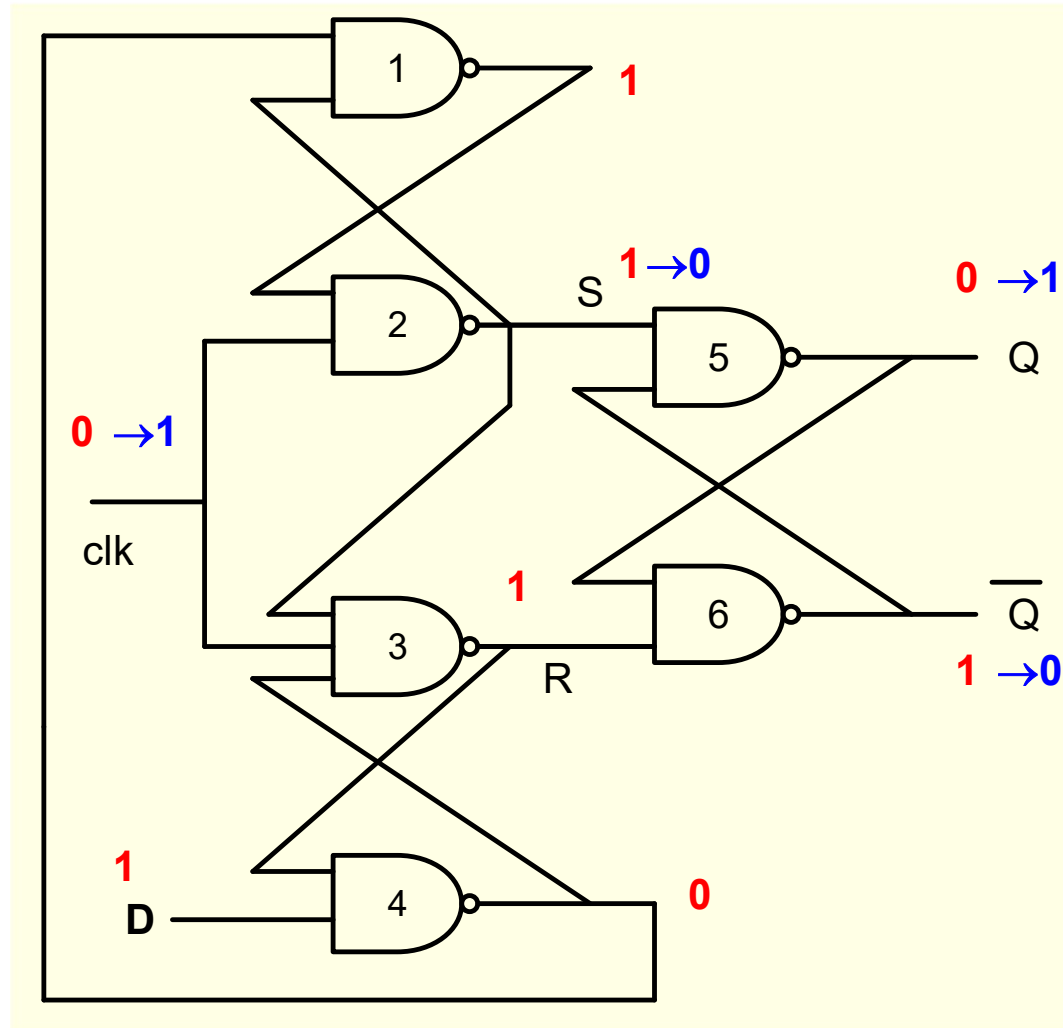


Positive edge triggered Flip-flop

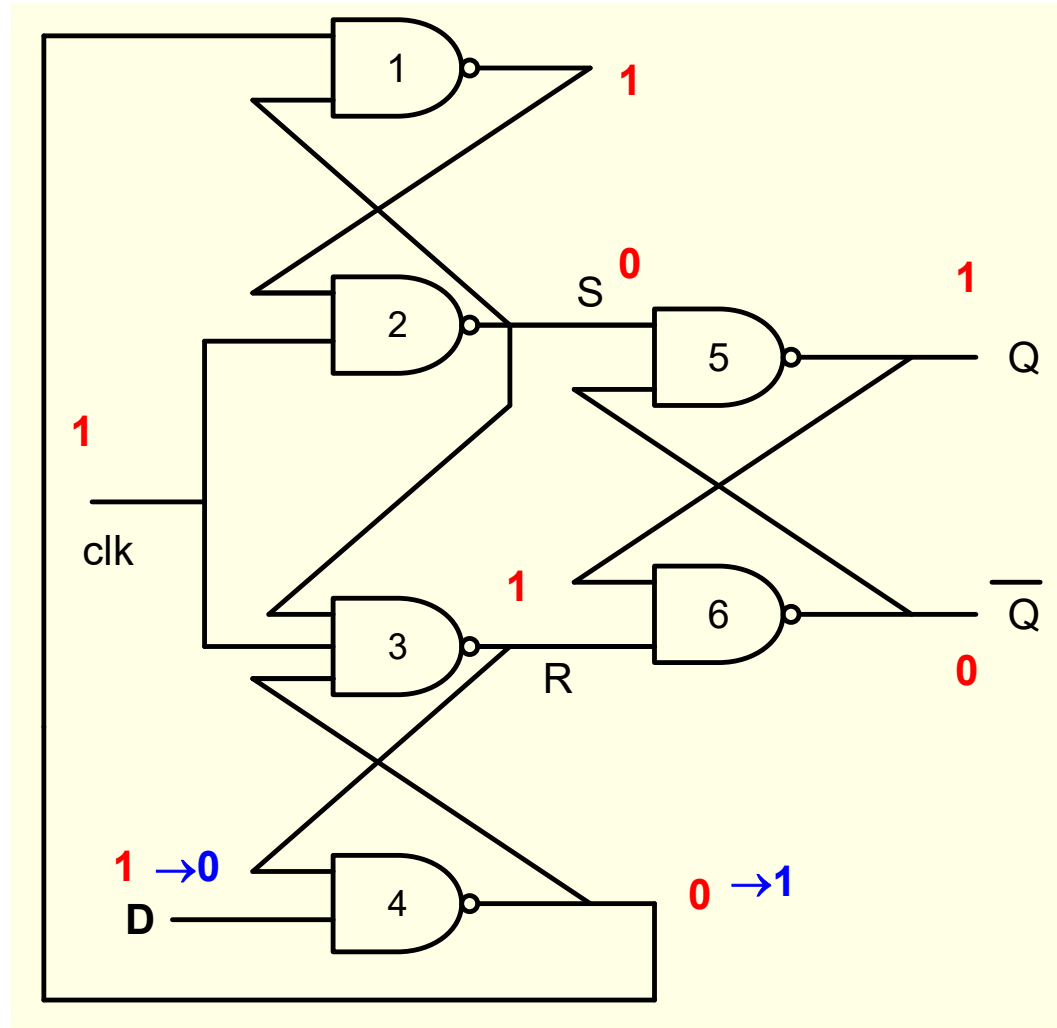


A change in input has no effect if it occurs after the clock edge

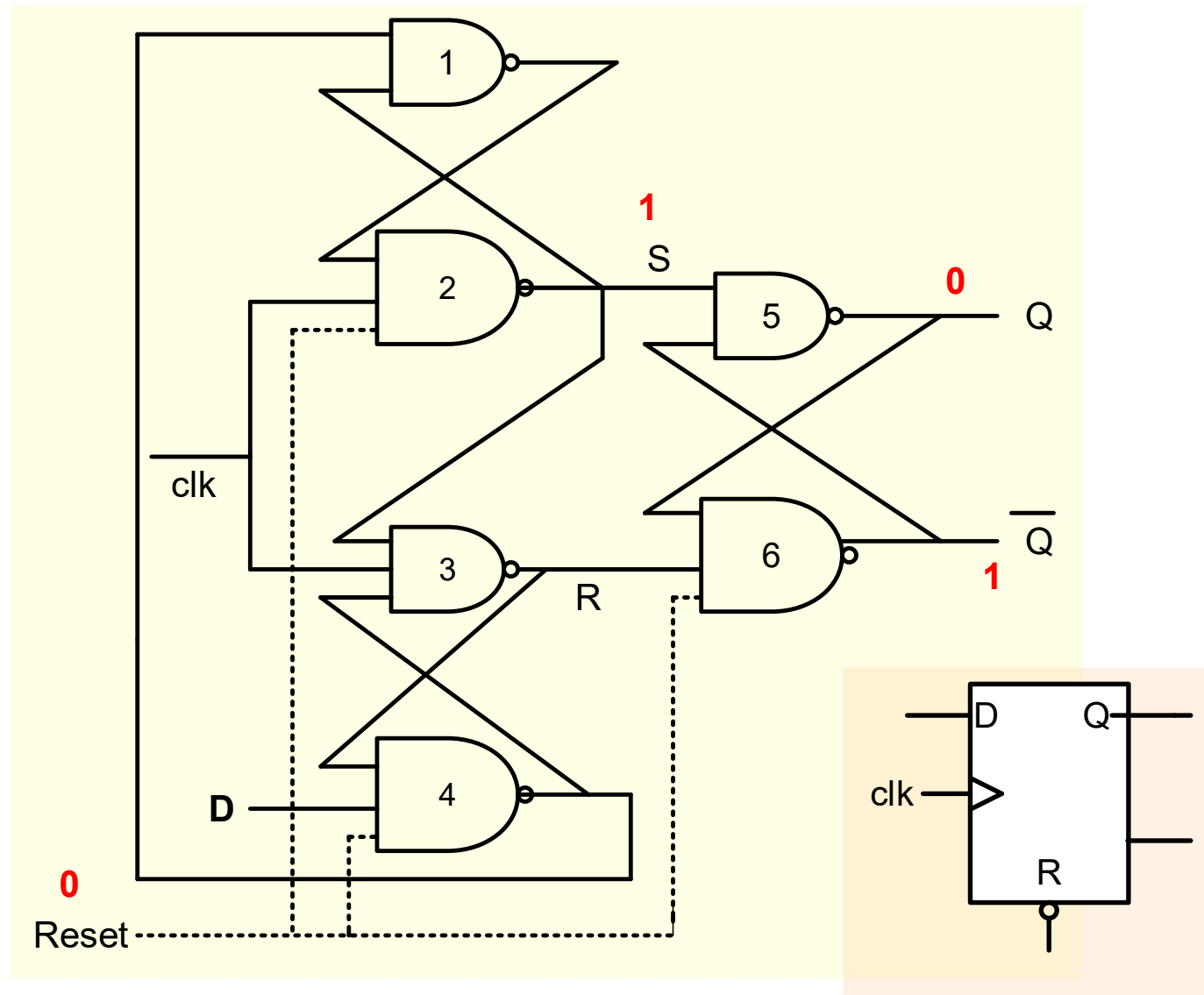Positive edge Triggered Flip-flop with Asynchronous Reset



Characteristic table

 
Given a input and the present state of the flip-flop, what is the next state of the flip-flop



Inputs (D)	Q(t+1)
0	0
1	1

$$Q(t+1) = D$$

JK Flip-flop

 


Inputs J K	Q(t+1)
0 0	Q(t)
0 1	0
1 0	1
1 1	$\overline{Q(t)}$

$$Q(t+1) = \overline{Q(t)}.J + Q(t).\overline{K}$$

→Characteristic equation

Toggle or T Flip-flop

 


Inputs (T)	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$

$$Q(t+1) = \overline{Q(t)}.T + Q(t).\overline{T}$$

Excitation Table What inputs are required to effect a particular state change

Inputs		
Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0


Excitation Table

 

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

Inputs

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

 


D	$Q(t+1)$
0	0
1	1

Inputs

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

Convert a D FF to JK FF

 

J	K	Q(t+1)	D
0	0	Q(t)	Q(t)
0	1	0	0
1	0	1	1
1	1	$\overline{Q(t)}$	$\overline{Q(t)}$

Q \ JK	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$D = \overline{Q}.J + Q.\overline{K}$$

