

# ESC201T : Introduction to Electronics


## L8: Circuit Analysis-Summary

B. Mazhari  
Dept. of EE, IIT Kanpur

## Circuit Analysis Tools

1. Nodal Analysis
2. Mesh Analysis
3. Re-use methodology
4. Superposition
5. Thevenin Equivalent circuit
6. Norton equivalent circuit
7. Source Transformation

## Mesh Analysis

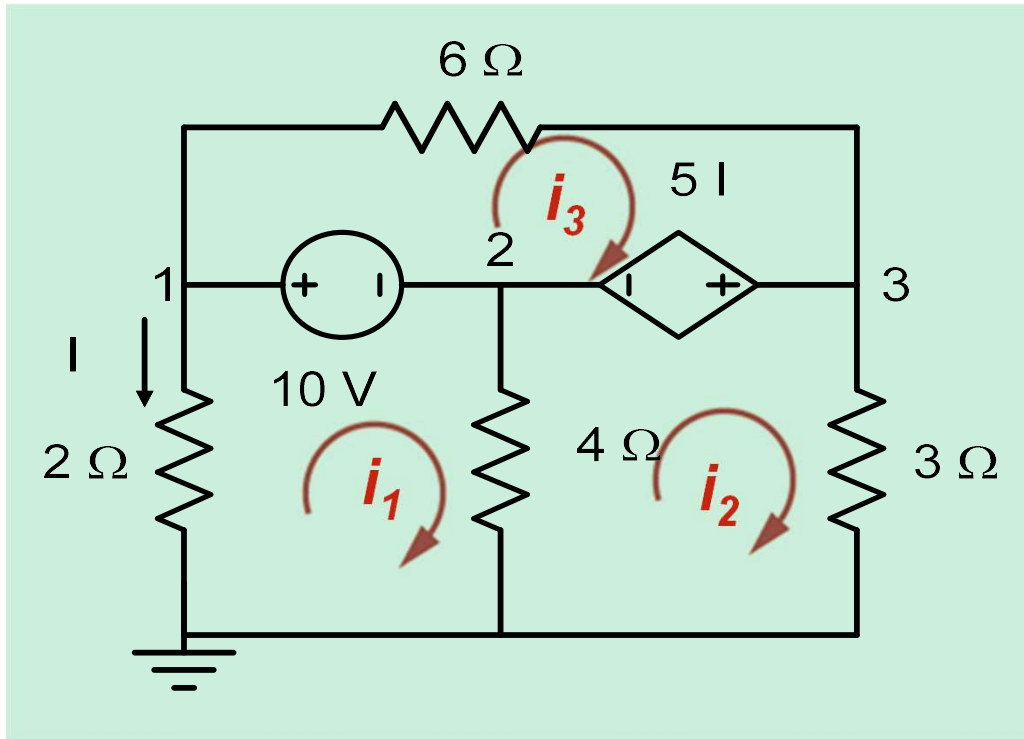

$$2i_1 + 10 + (i_1 - i_2) \times 4 = 0 \quad (1)$$

$$4 \times (i_2 - i_1) - 5 \times i + i_2 \times 3 = 0 \quad (2)$$


$$6i_3 + 5i - 10 = 0 \quad (3)$$

$$i = -i_1 \quad (4)$$

$$i_1 = -1.52\text{ A}; i_2 = 0.217\text{ A}; i_3 = 0.4\text{ A}$$

$$v_2 = 4 \times (i_1 - i_2) = -6.95\text{ V}$$

## Nodal Analysis

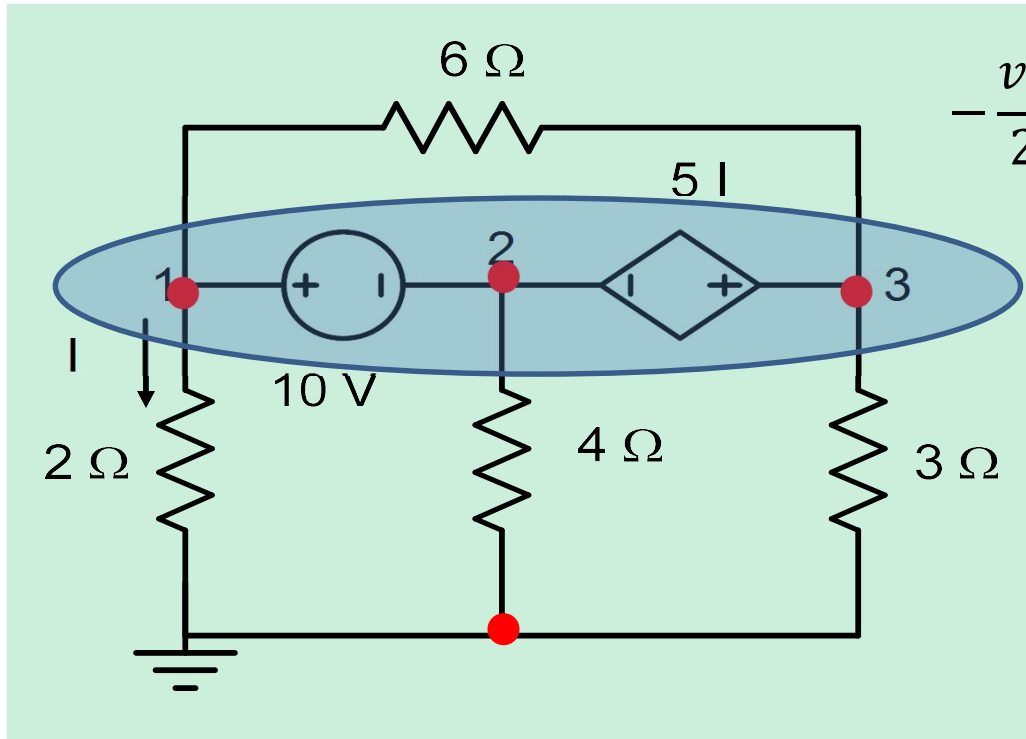

$$-\frac{v_1}{2} + \frac{v_3 - v_1}{6} - \frac{v_2}{4} - \frac{v_3}{3} + \frac{v_1 - v_3}{6} = 0$$


$$v_1 - v_2 = 10$$

$$v_3 - v_2 = 5i$$

$$i = \frac{v_1}{2} \Rightarrow v_3 - v_2 = 2.5v_1$$

$$\Rightarrow v_2 = -6.95\text{ V}$$

## Nodal Analysis

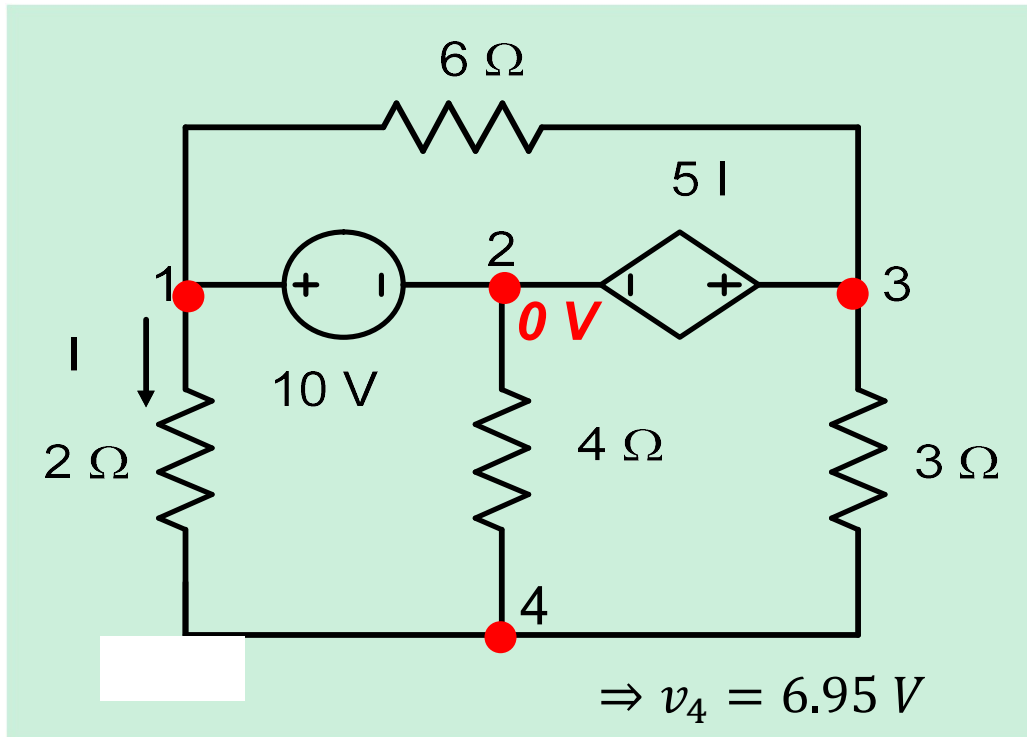

$$v_1 = 10 \text{ V} ; v_2 = 0 \text{ V}$$

$$v_3 = 5i = 5 \times \frac{10 - v_4}{2}$$



KCL at node 4

$$\frac{10 - v_4}{2} + \frac{0 - v_4}{4} + \frac{v_3 - v_4}{3} = 0$$

$$v_4 - v_2 = 6.95 \text{ V} \Rightarrow v_2 = v_4 - 6.95 = -6.95 \text{ V}$$

$$v_1 - v_4 = 10 - 6.95 \text{ V} = 3.04 \Rightarrow v_1 = v_4 + 3.04 = 3.04 \text{ V}$$

## Thevenin equivalent circuit

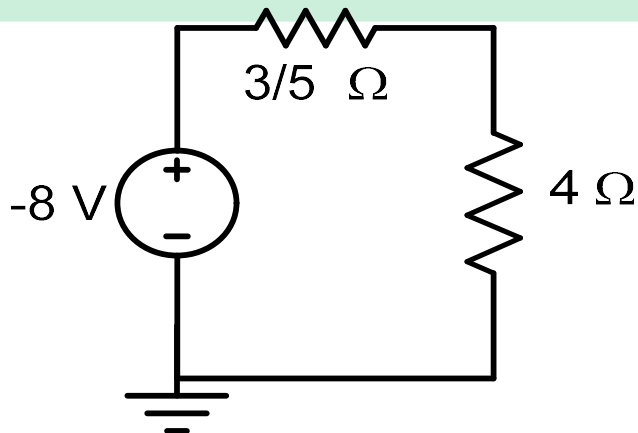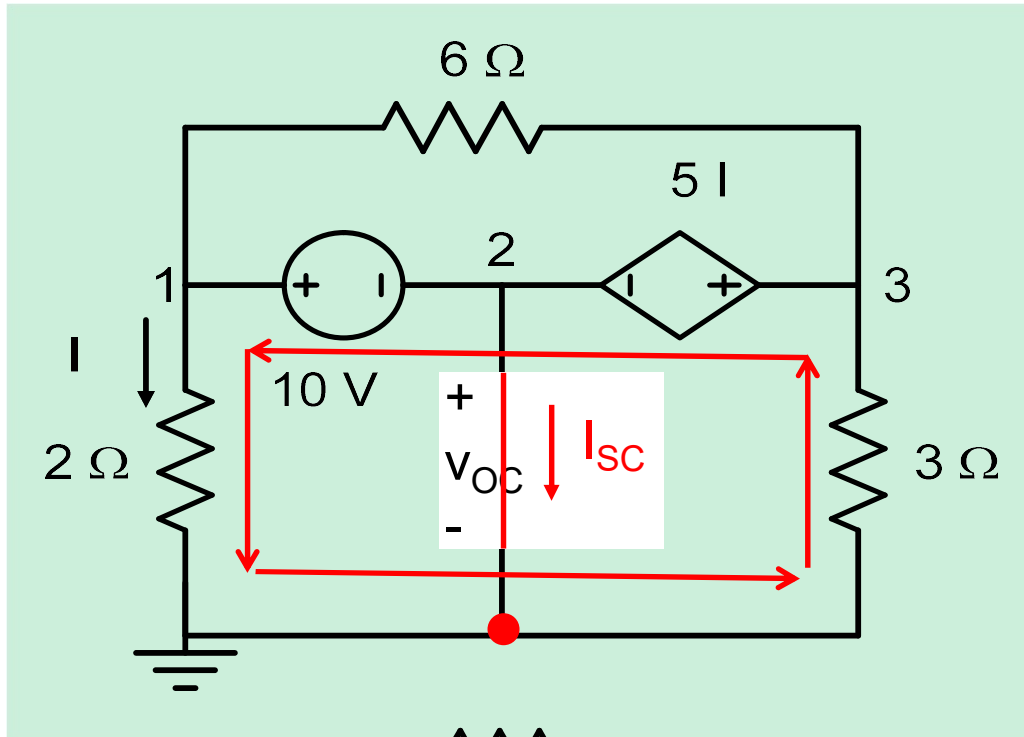

$$3i + 5i - 10 + 2i = 0$$

$$\Rightarrow i = 1$$

$$v_1 = 2V \Rightarrow v_{OC} = v_2 = -8V$$







$$\Rightarrow i = \frac{10}{2} = 5A$$

$$\frac{10}{2} + i_{SC} + \frac{25}{3} = 0$$

$$\Rightarrow i_{SC} = -\frac{40}{3}$$



$$R_{TH} = \frac{v_{OC}}{i_{SC}} = \frac{3}{5} \Omega$$
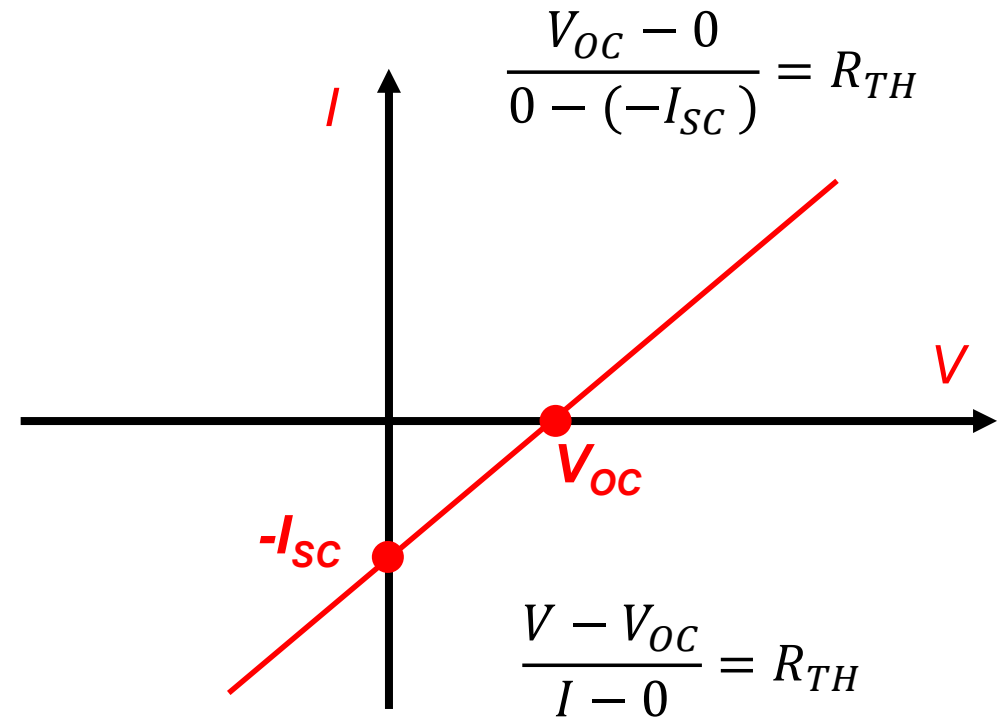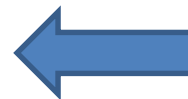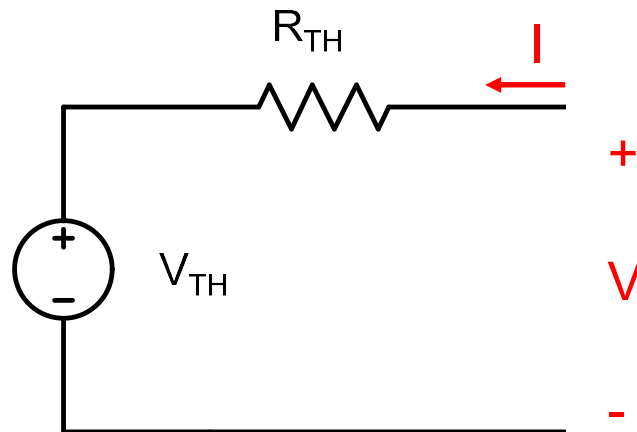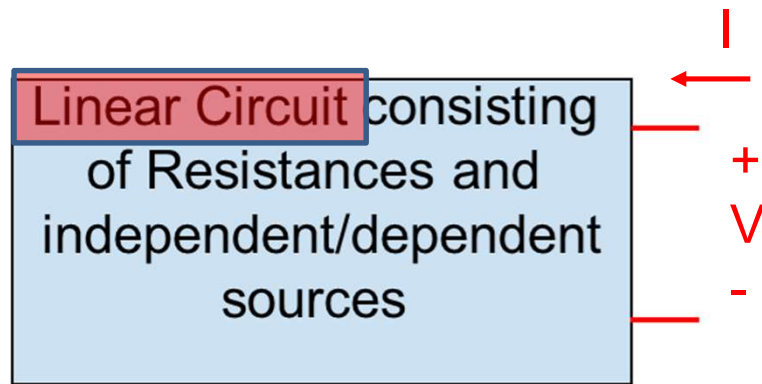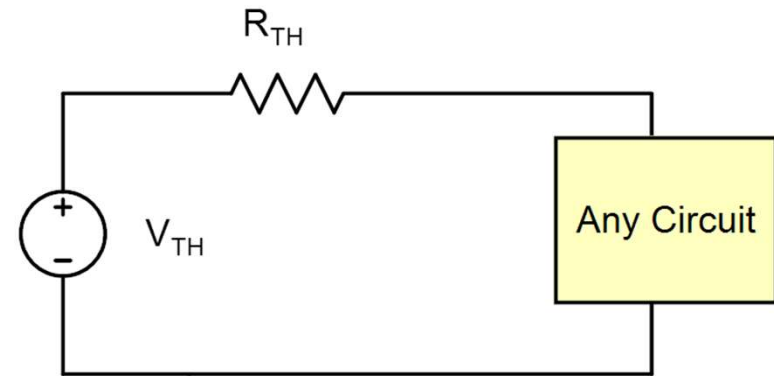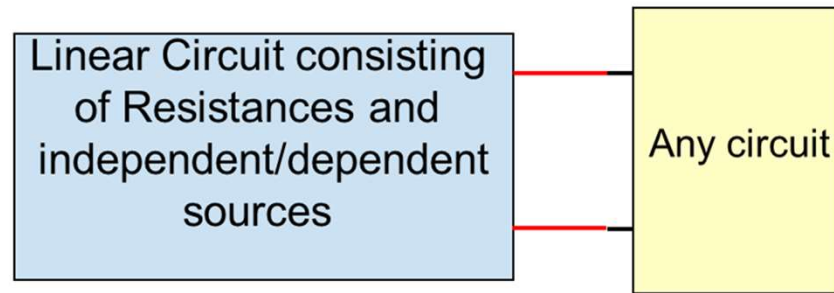
$$v_2 = -8 \times \frac{4}{4 + \frac{3}{5}} = -6.95 V$$



$$V = V_{OC} + I \times R_{TH}$$

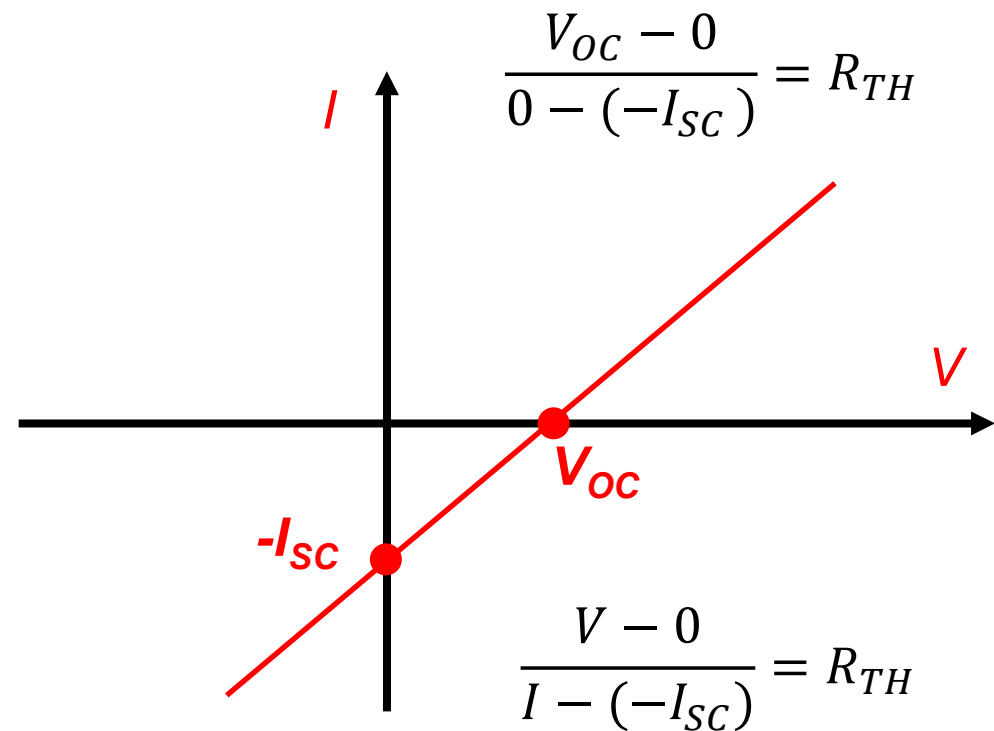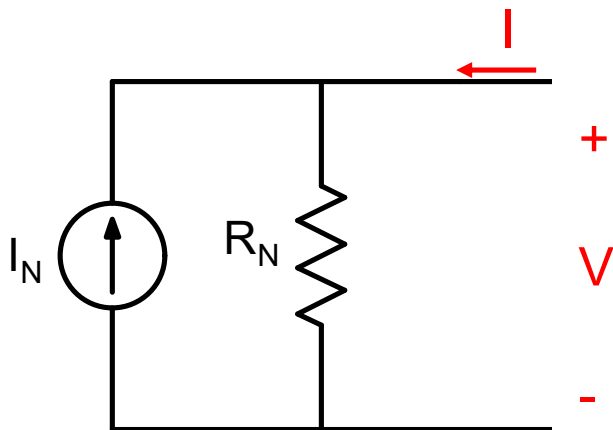Linear Circuit consisting  
of Resistances and  
independent/dependent  
sources



$$I = -I_{SC} + \frac{V}{R_{TH}}$$

$$I = -I_N + \frac{V}{R_{TH}}$$