
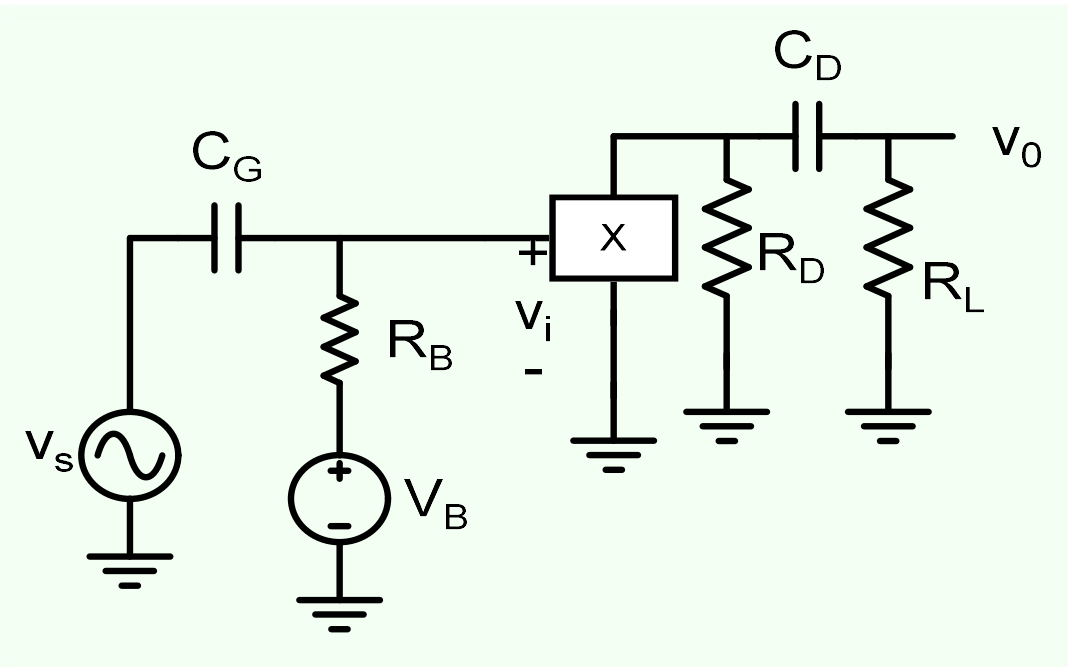


# ESC201T : Introduction to Electronics



## Lecture 26: Amplifiers-2

B. Mazhari  
Dept. of EE, IIT Kanpur


# Amplifier Schematic

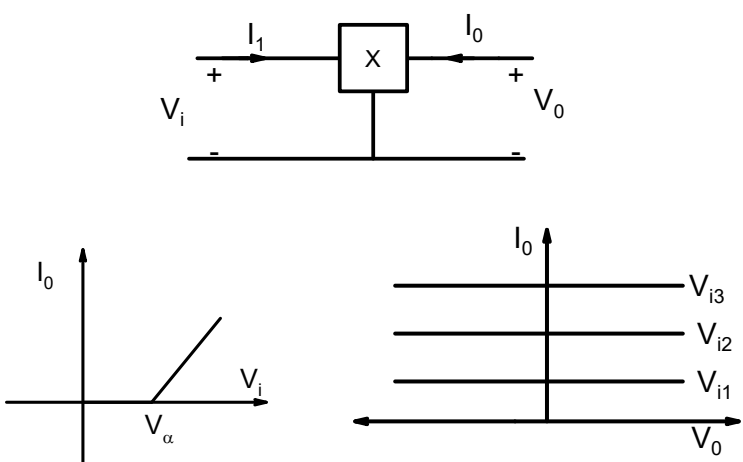



## Device Y

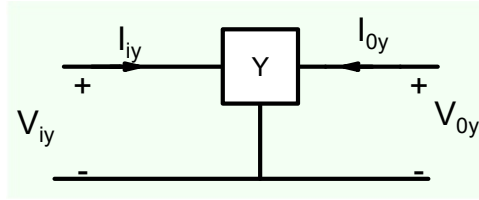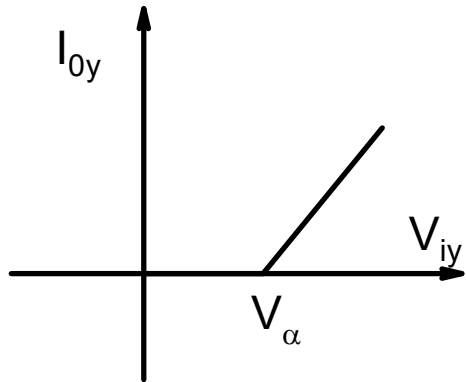


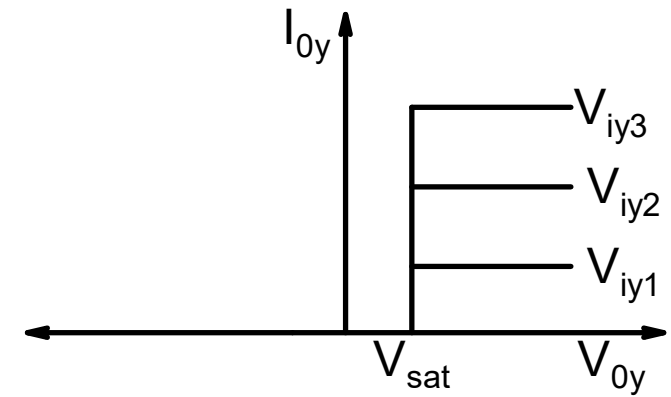
$$\begin{aligned}
 I_{oy} &= 0 \text{ for } V_{OY} < V_{sat} \\
 \text{for } V_{OY} &\geq V_{sat} \\
 I_{oy} &= 0 & \text{for } V_{iy} \leq V_{\alpha} \\
 &= g_m \times (V_{iy} - V_{\alpha}) & \text{for } V_{iy} > V_{\alpha}
 \end{aligned}$$



## Ideal Characteristics

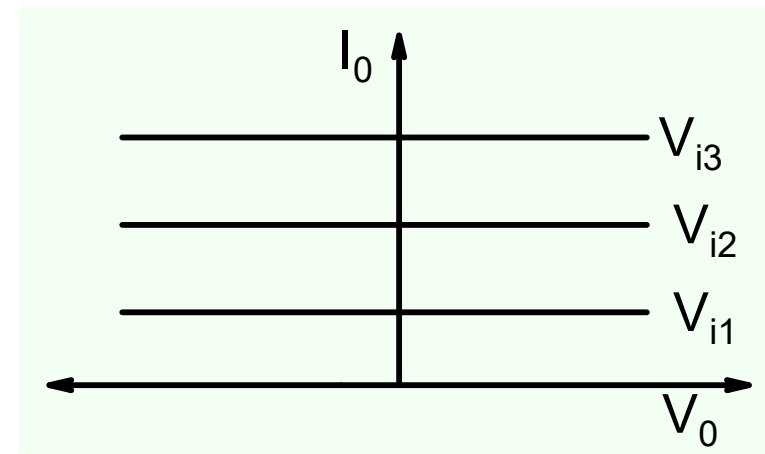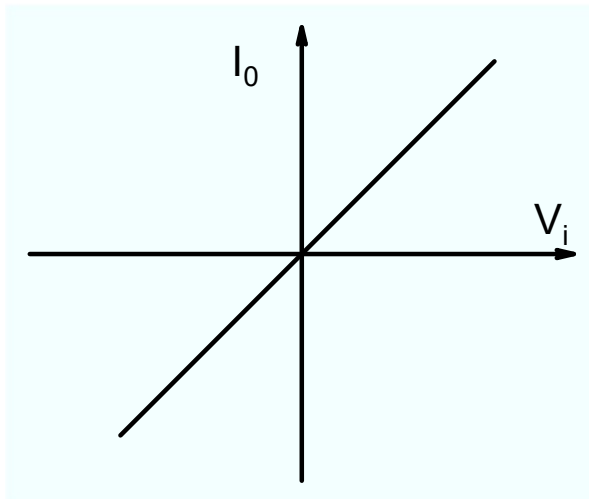
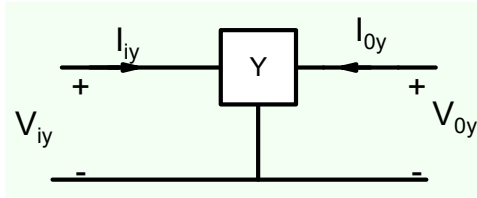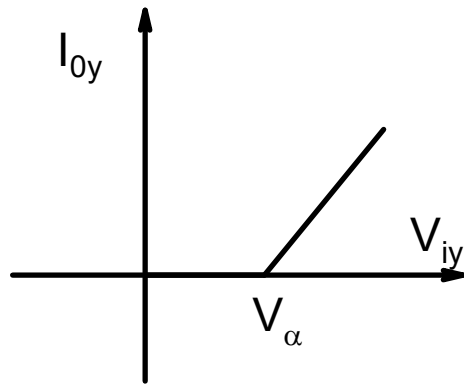
## How do we use device Y to make an amplifier?




$$I_{oy} = 0 \text{ for } V_{OY} < V_{sat}$$


$$\text{for } V_{OY} \geq V_{sat}$$

$$I_{oy} = 0 \quad \text{for } V_{iy} \leq V_{\alpha}$$



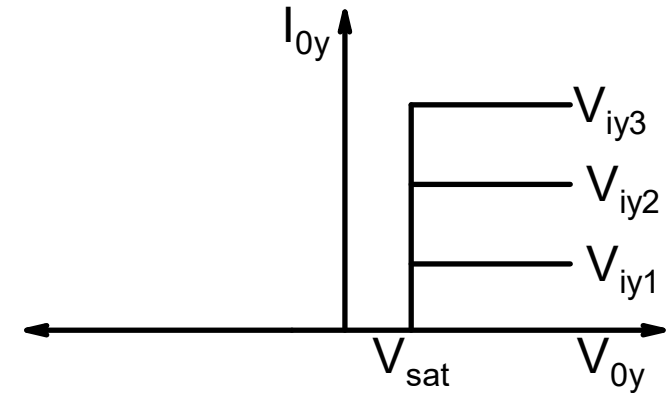
$$= g_m \times (V_{iy} - V_{\alpha}) \text{ for } V_{iy} > V_{\alpha}$$





Will the earlier solution work?

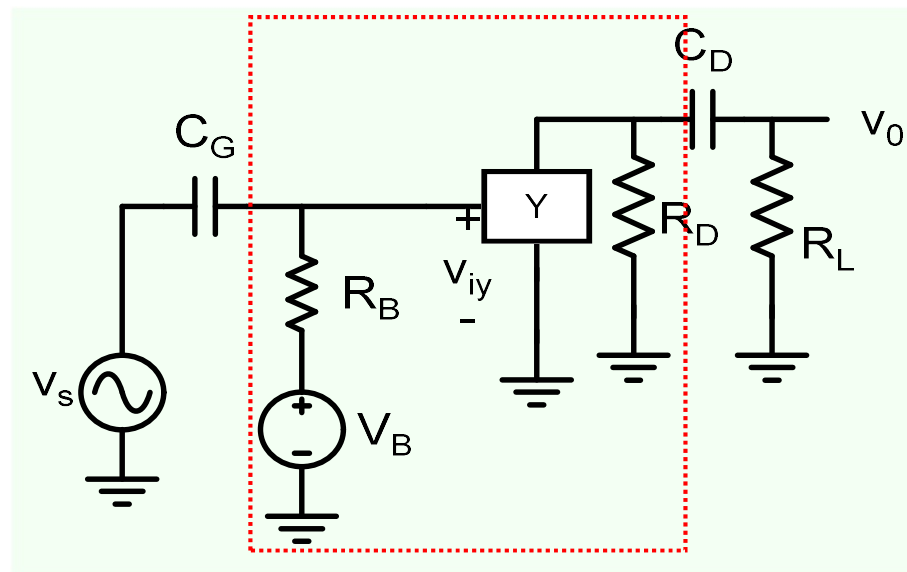


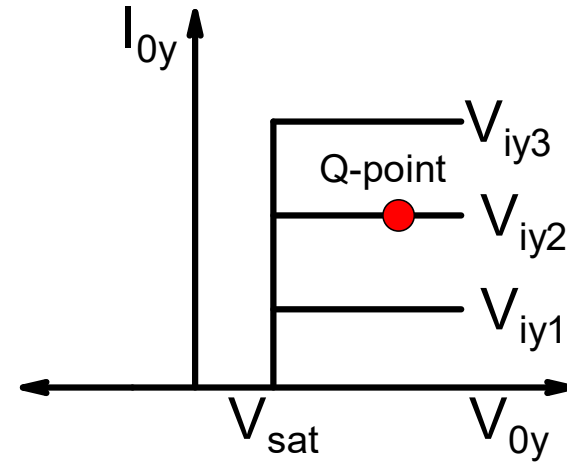
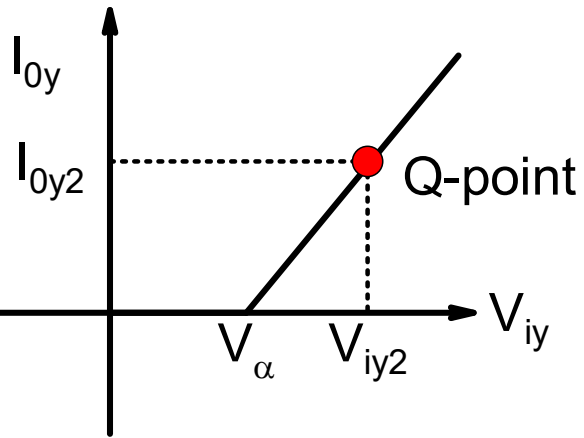
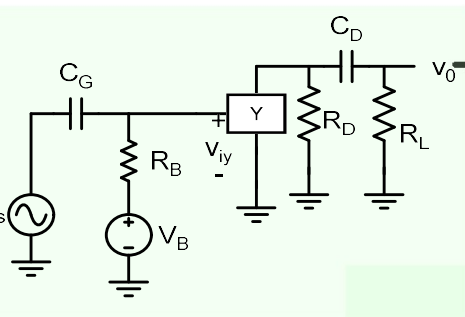
The purpose of biasing network is to operate the device in a region which resembles ideal transistor





$V_{Oy} = -ve$  which is not possible

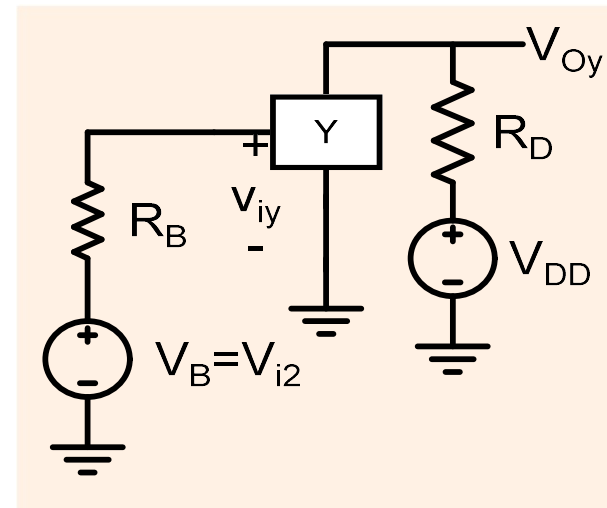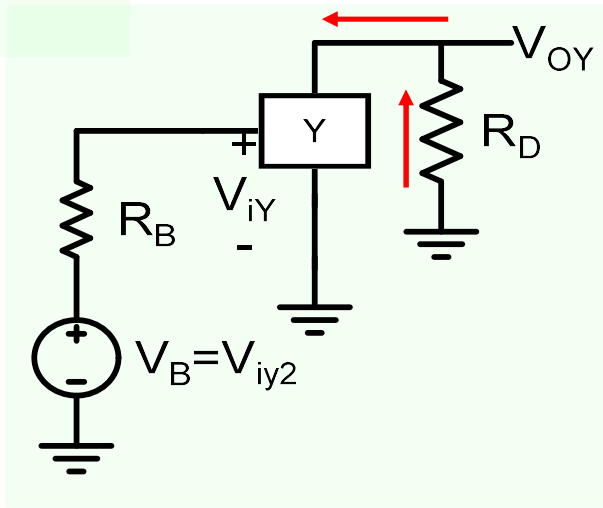



## Revised Amplifier Schematic

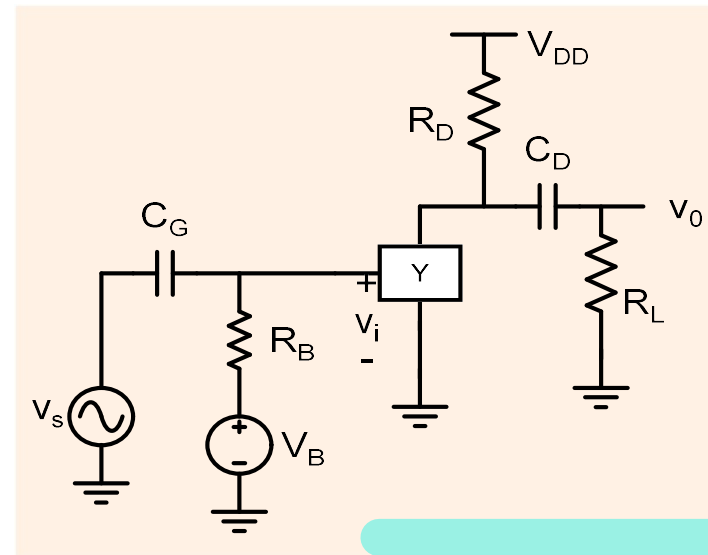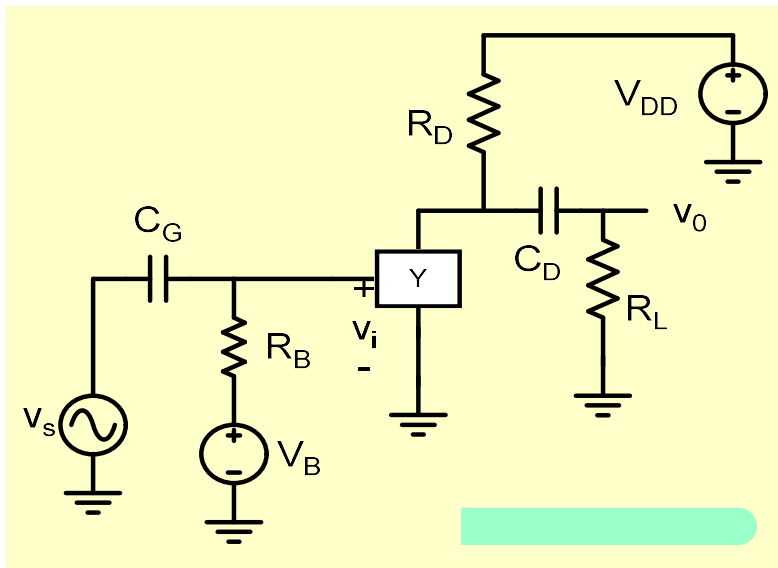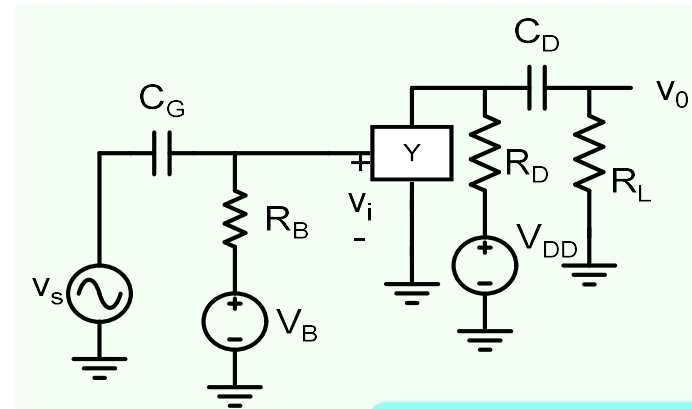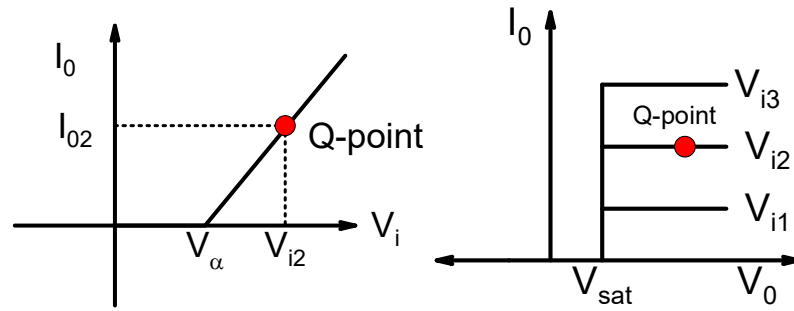

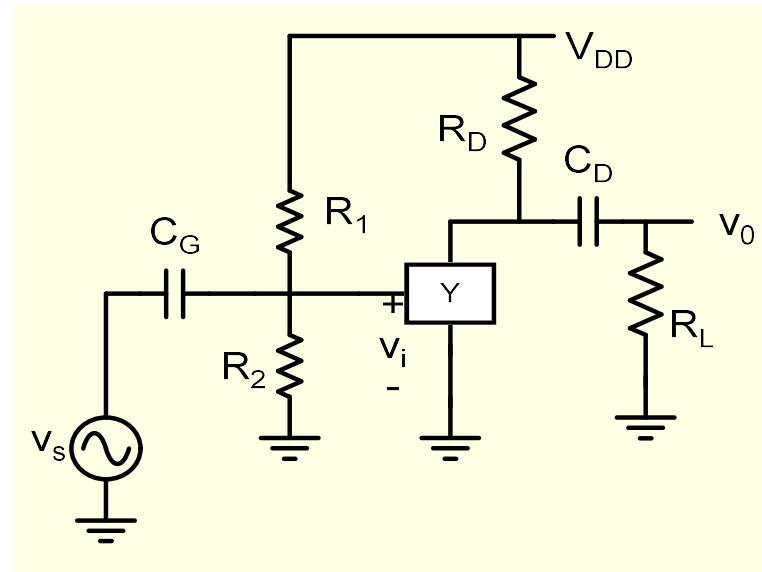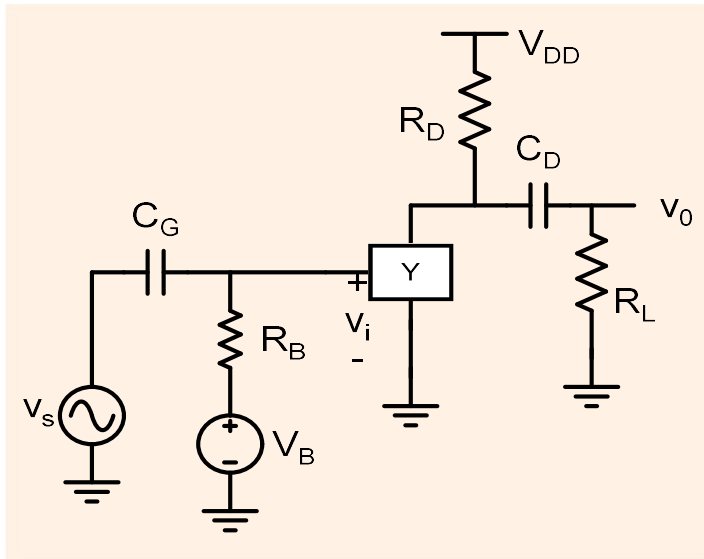Can we Bias using one dc voltage source only?


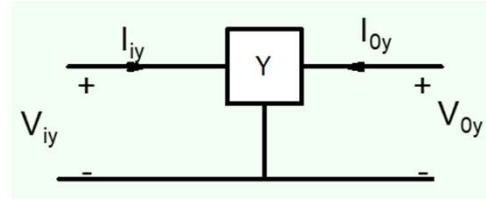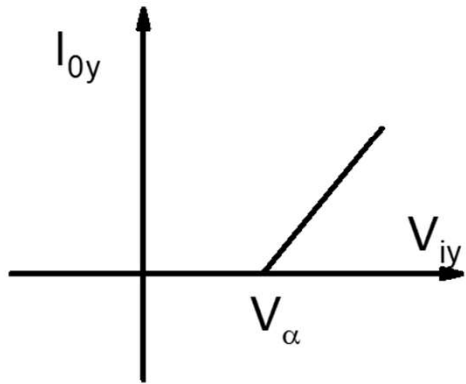
$$V_B = V_{DD} \times \frac{R_2}{R_1 + R_2}$$





$$I_{oy} = 0 \text{ for } V_{OY} < V_{sat}$$

$$\text{for } V_{OY} \geq V_{sat}$$



$$I_{oy} = 0 \quad \text{for } V_{iy} \leq V_{\alpha}$$
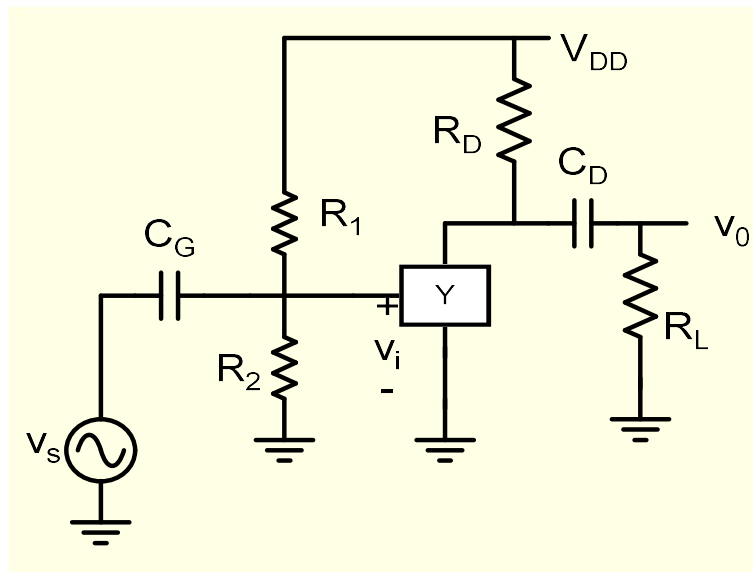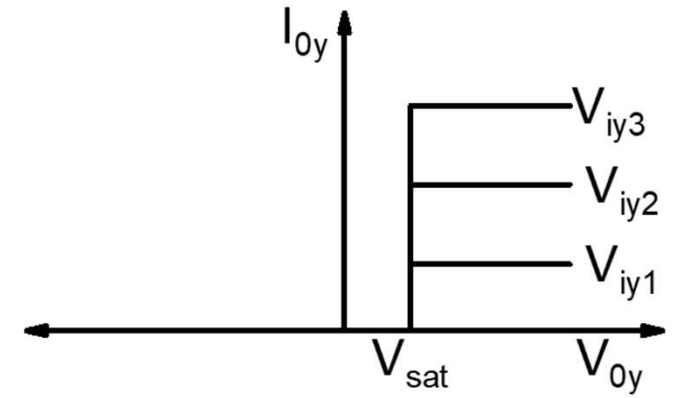
$$= g_m \times (V_{iy} - V_{\alpha}) \text{ for } V_{iy} > V_{\alpha}$$





## Device Z

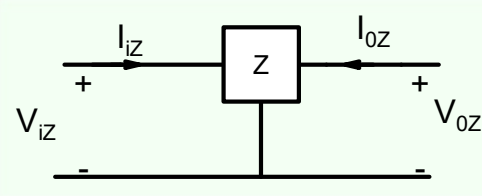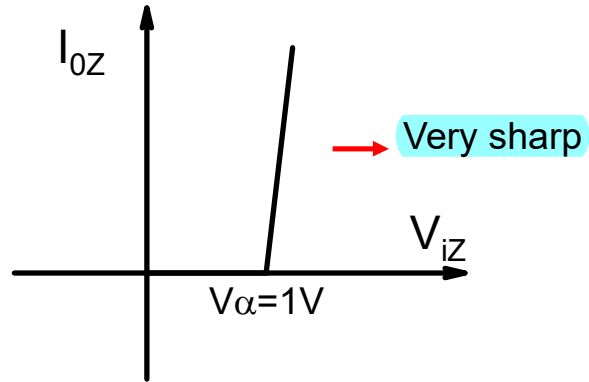


$$I_{OZ} = 0 \text{ for } V_{OZ} < 0.2V$$


$$\text{for } V_{OZ} \geq 0.2$$

$$I_{OZ} = 0 \quad \text{for } V_{IZ} \leq 1V$$
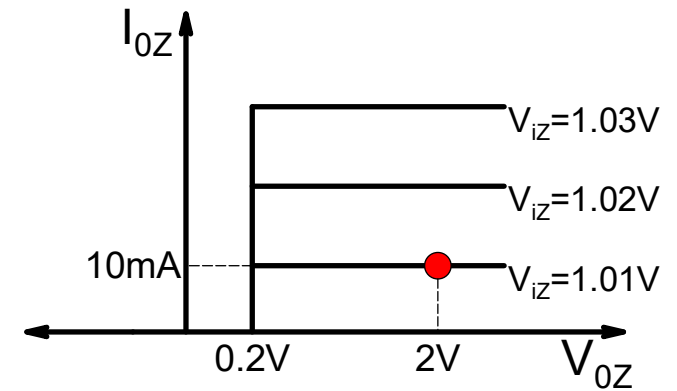
$$= 1 \times (V_{IZ} - 1V) \text{ for } V_{IZ} > 1V$$



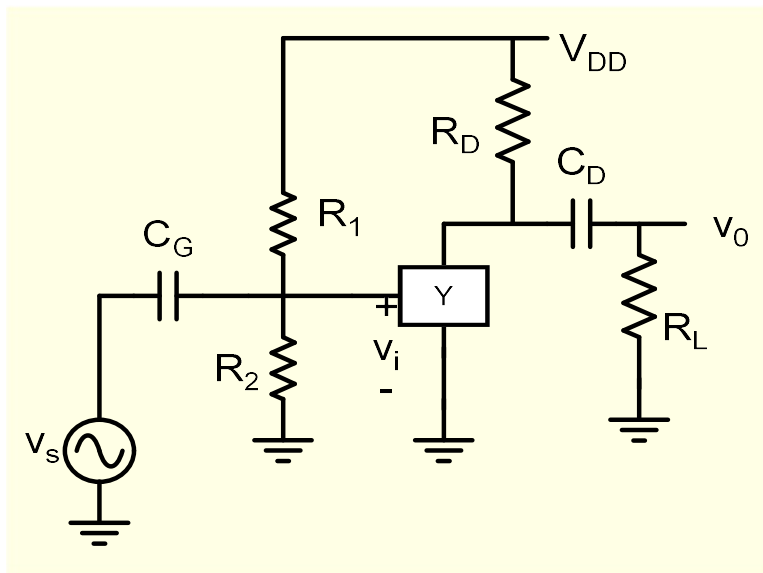Circuit is very sensitive to variations in resistor values, power supply, device parameters such as  $V_{\alpha}$



$$V_{DD} = 5V; R_2 = 1K; R_1 = 3.95K$$

$$\Rightarrow V_{IZ} = 1.01 \Rightarrow I_{OZ} = 10mA$$



$$V_{DD} = 5V; R_2 = 0.99K; R_1 = 3.95K$$

$$\Rightarrow V_{IZ} = 1.002 \Rightarrow I_{OZ} = 1.9mA$$




$$V_{DD} = 5V; R_2 = 0.98K; R_1 = 3.95K$$




$$\Rightarrow V_{IZ} = 0.994V \Rightarrow I_{OZ} = 0$$

## Solution

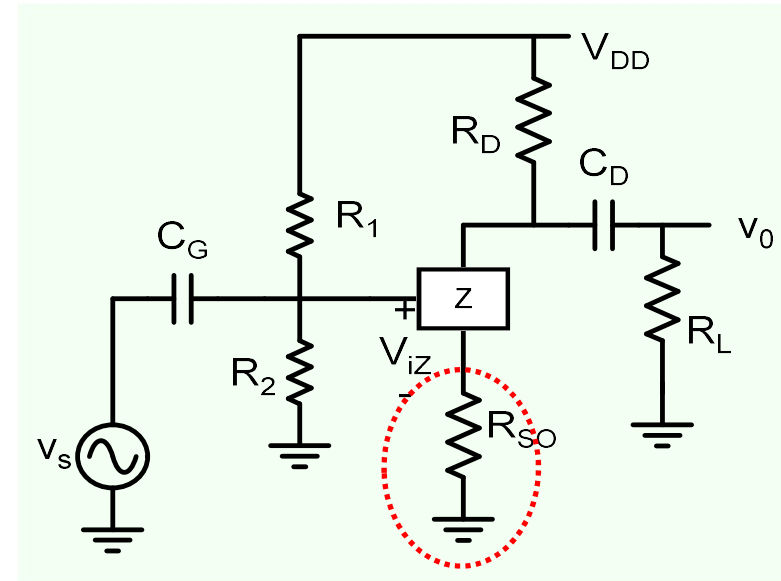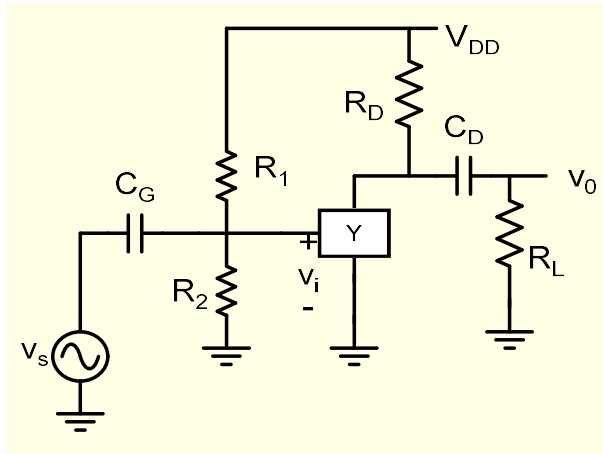

### dc Analysis

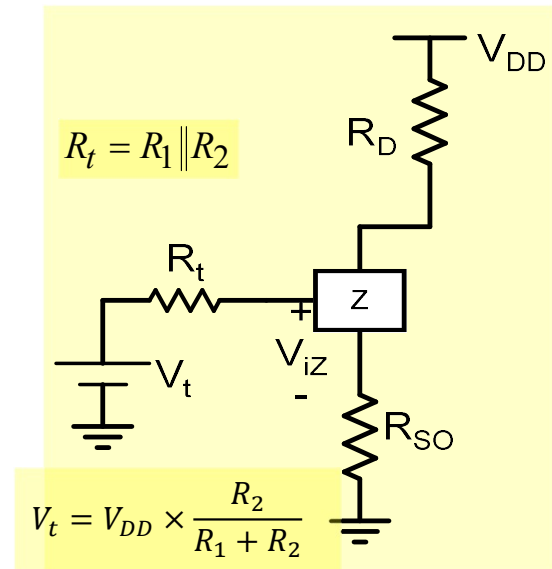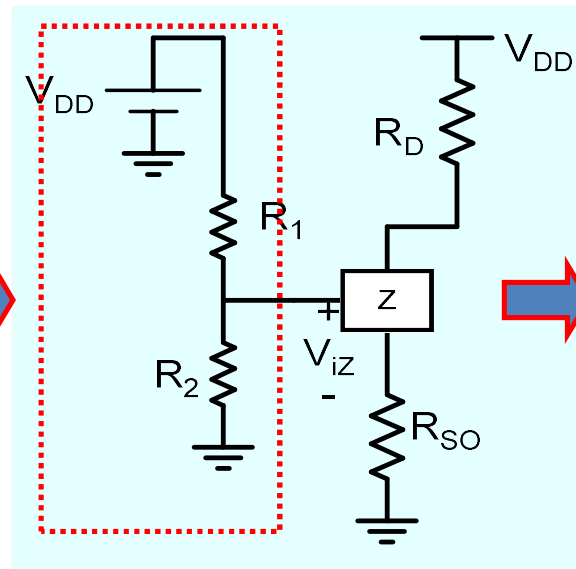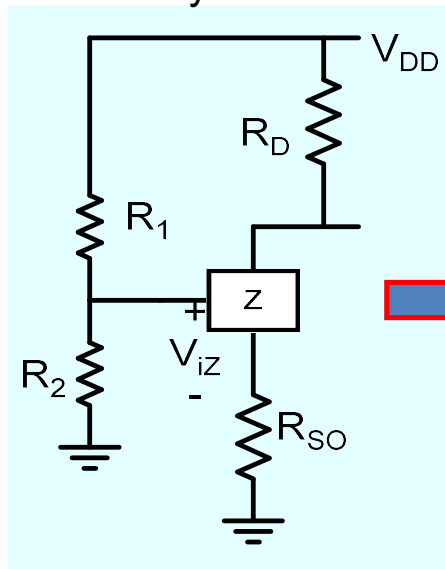

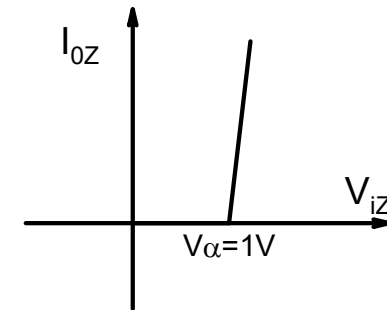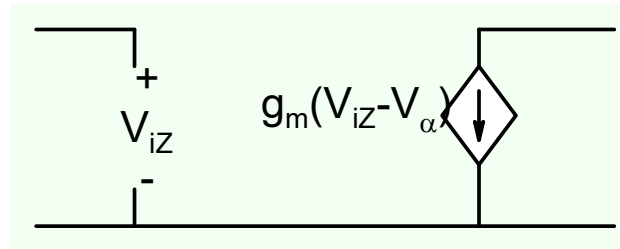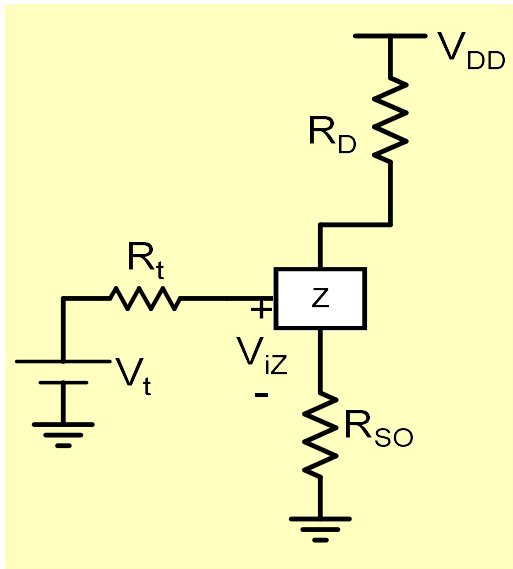

$$-V_t + 0 \times R_t + V_{iz} + I_{OZ}R_{SO} = 0$$


Since  $I_{OZ}$  vs.  $V_{iz}$  characteristics is very sharp,  $V_{iz} \sim V_\alpha = 1V$

$$I_{OZ} \cong \frac{V_t - V_\alpha}{R_{SO}}$$










If  $V_t$  changes by 1% due to variation in resistor values then the change in output current is proportional.

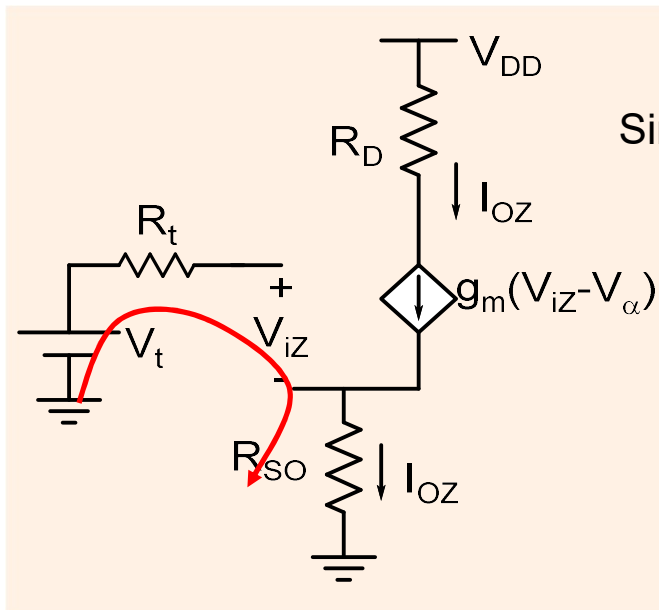Circuit is much less sensitive to variations in circuit parameters



## Ac analysis

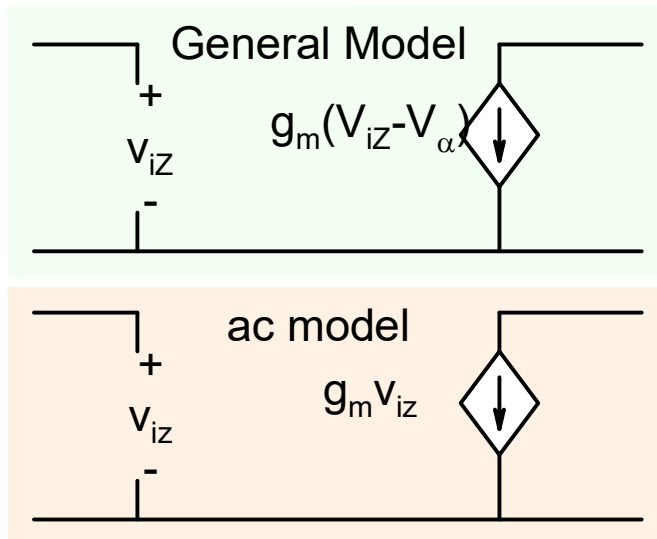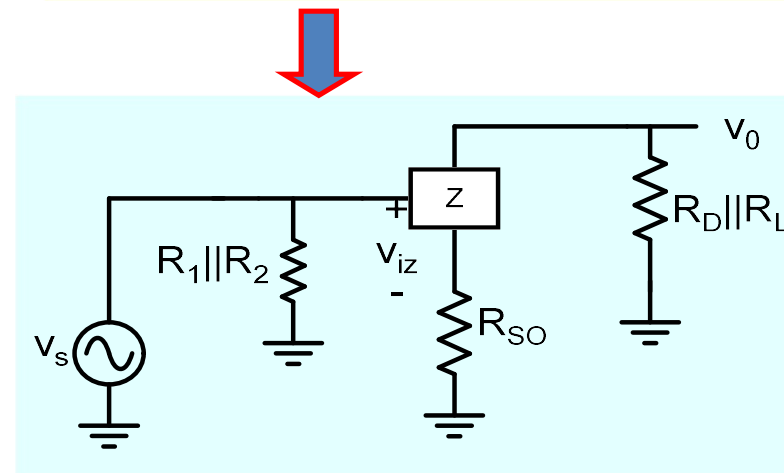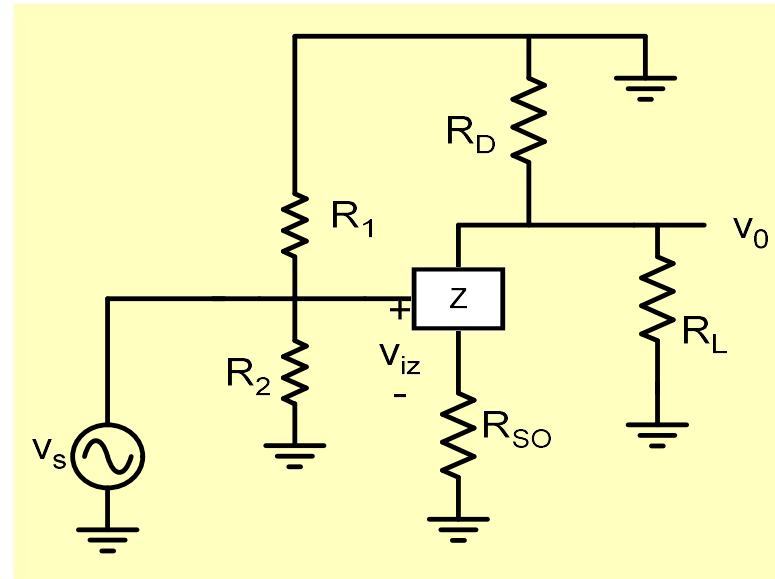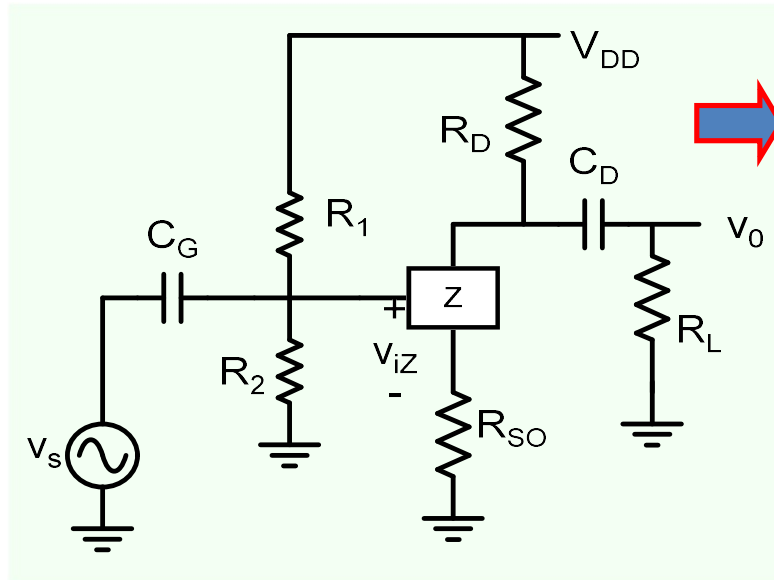


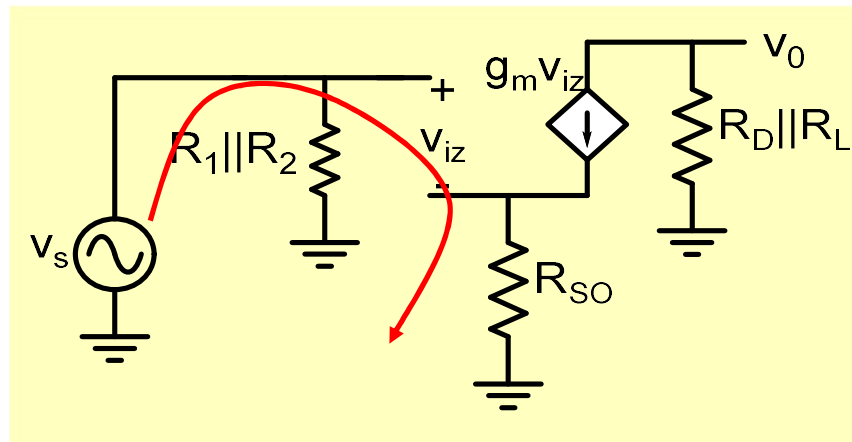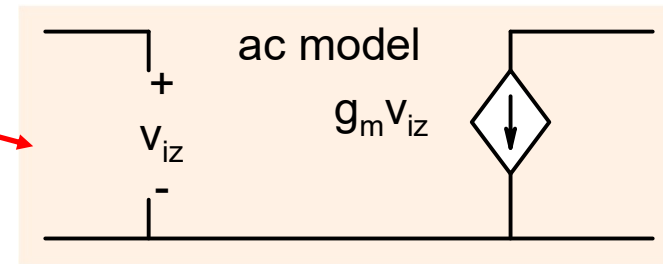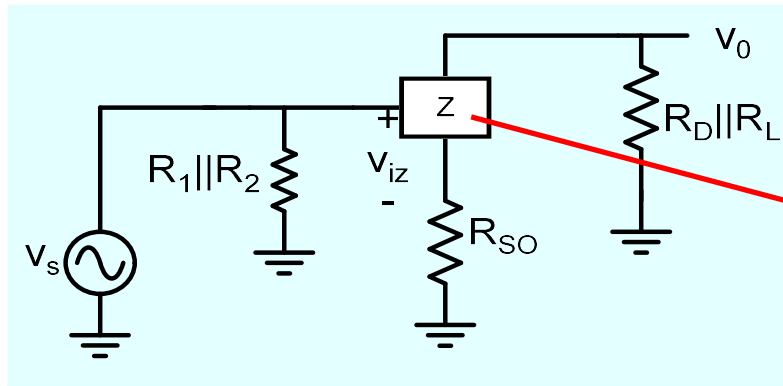

$$v_S = v_{iz} + g_m v_{iz} R_{SO}$$


$$v_O = -g_m \times R_D \parallel R_L v_{iz}$$
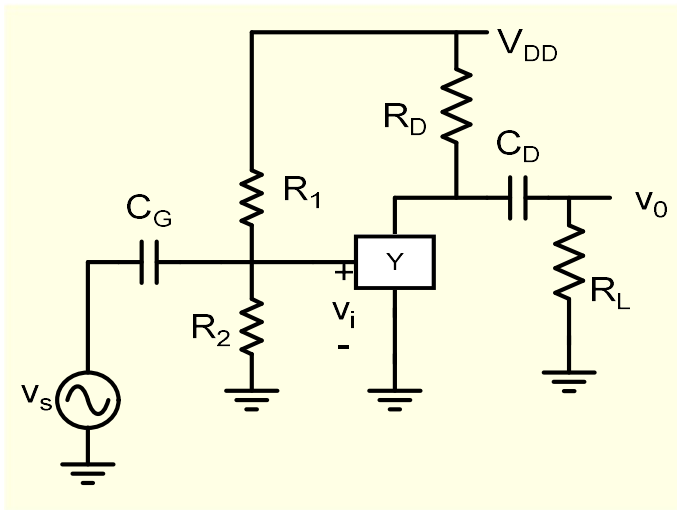
$$A_V = \frac{v_O}{v_S} = -\frac{g_m R_D \parallel R_L}{1 + g_m R_{SO}}$$



Circuit is very sensitive to variations in resistor values, power supply, device parameters such as  $V_{\alpha}$
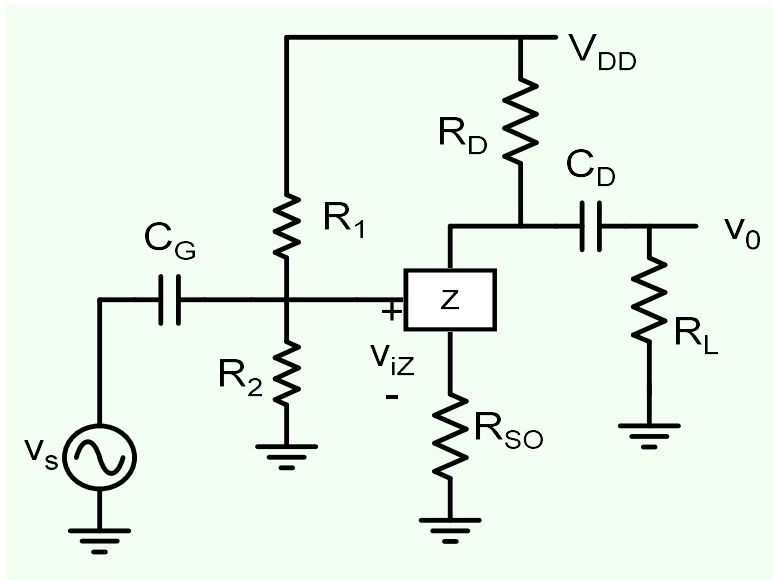
$$A_V = \frac{v_o}{v_s} = -g_m R_D \parallel R_L$$




Circuit is much less sensitive to variations in circuit parameters

$$A_V = \frac{v_o}{v_s} = -\frac{g_m R_D \parallel R_L}{1 + g_m R_{SO}}$$

But gain is smaller


## Simple Solution

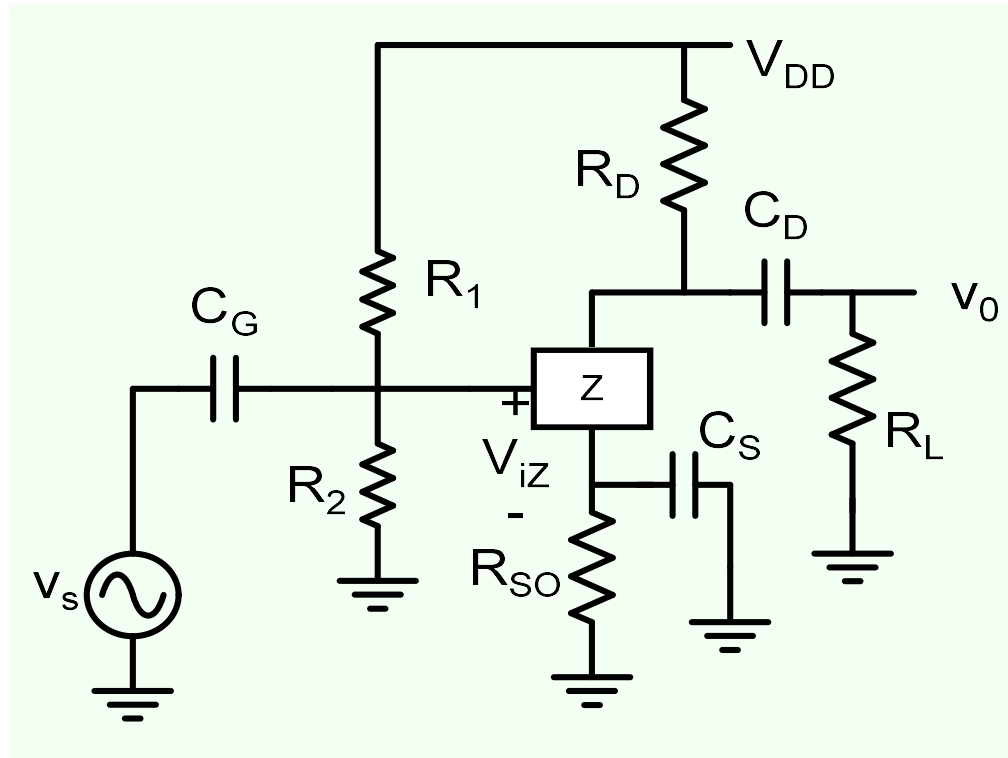

For dc, Capacitor  $C_S$  acts as open allowing  $R_{SO}$  to reduce variations in current

For ac, Capacitor  $C_S$  acts as a short circuit ( $1/j\omega C \sim 0$ ) allowing high voltage gain to be obtained

## Device NL:


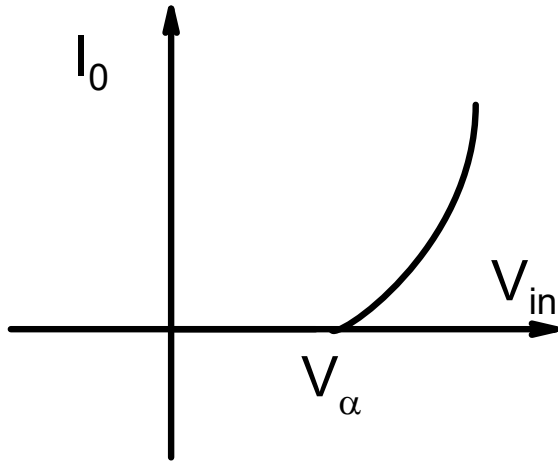


$$I_o = K \times (V_{in} - V_\alpha)^2 \text{ for } V_{in} \geq V_\alpha$$





$$V_\alpha = 1.0V ; K = 0.02$$




$$V_B = 1.5V$$

$$v_s = 0.3V \sin(\omega t)$$

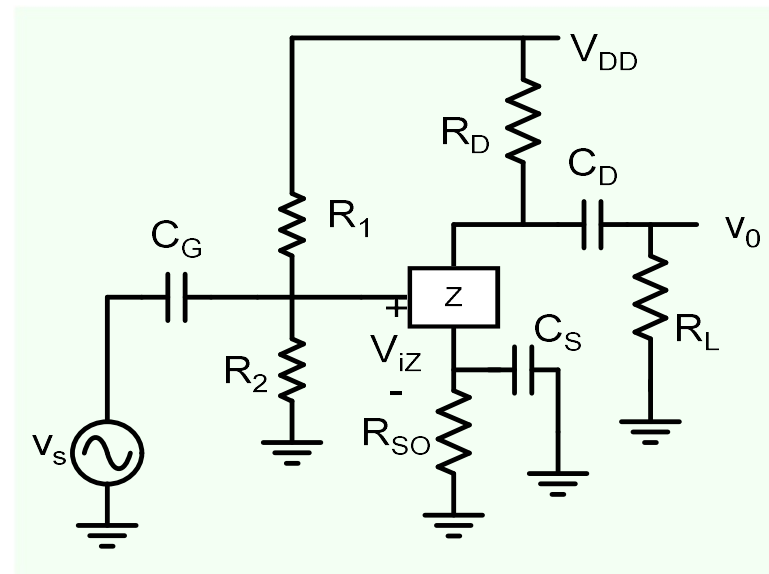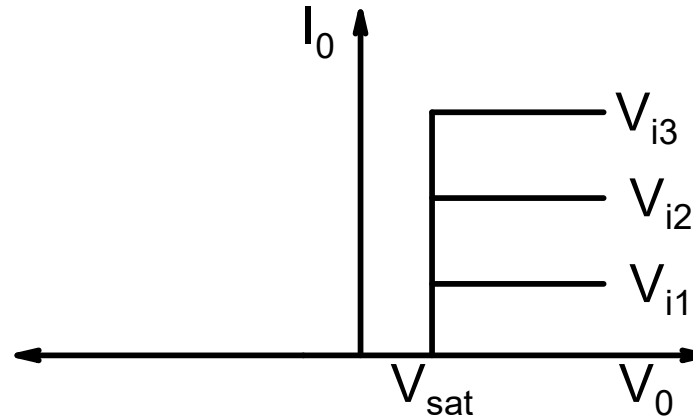




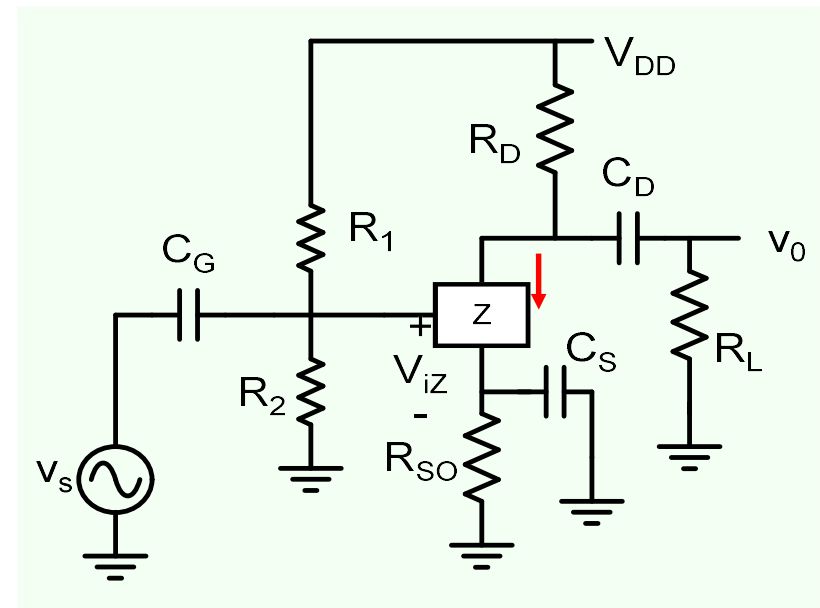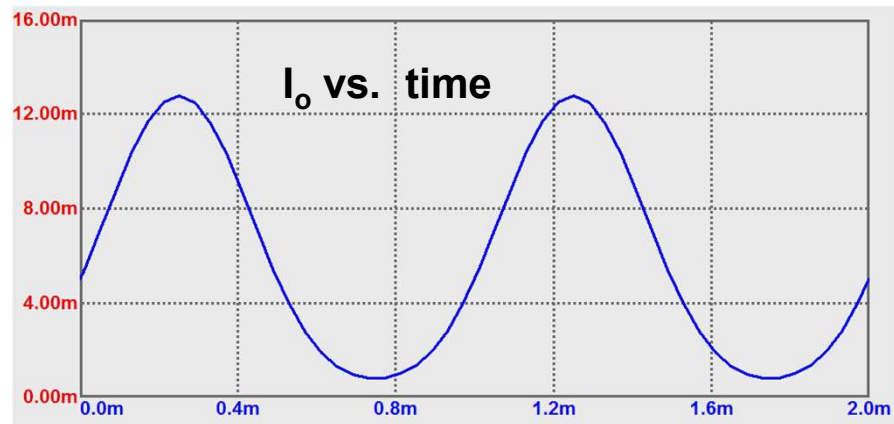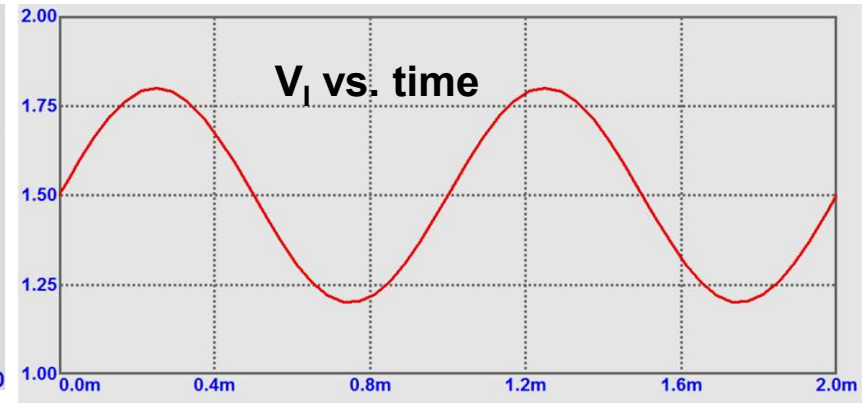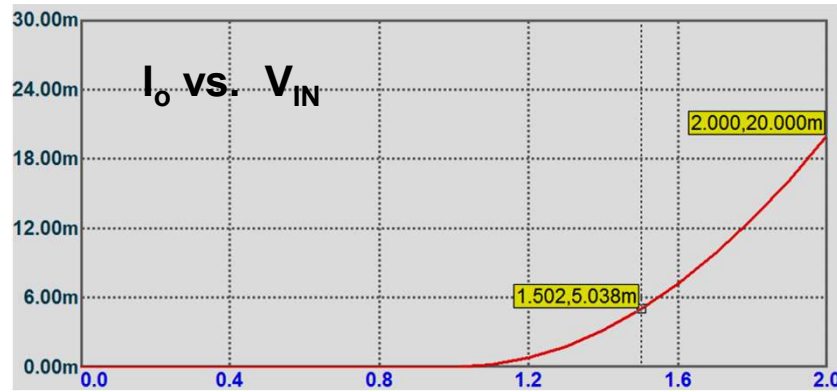

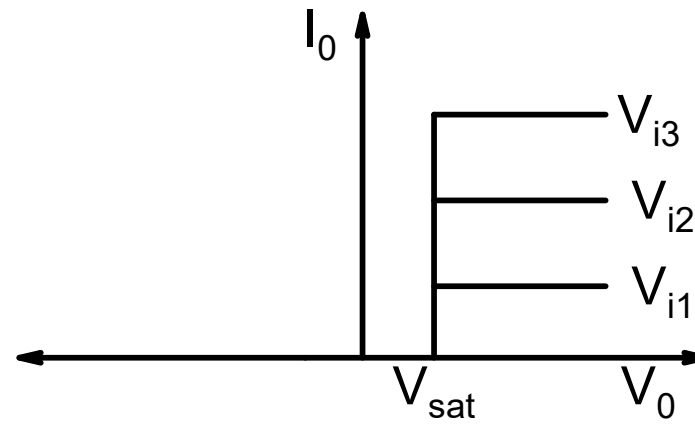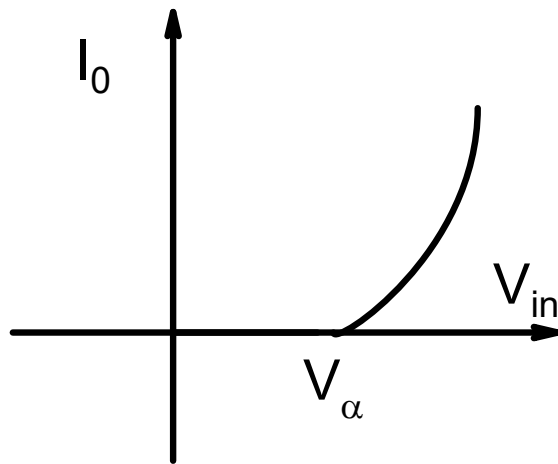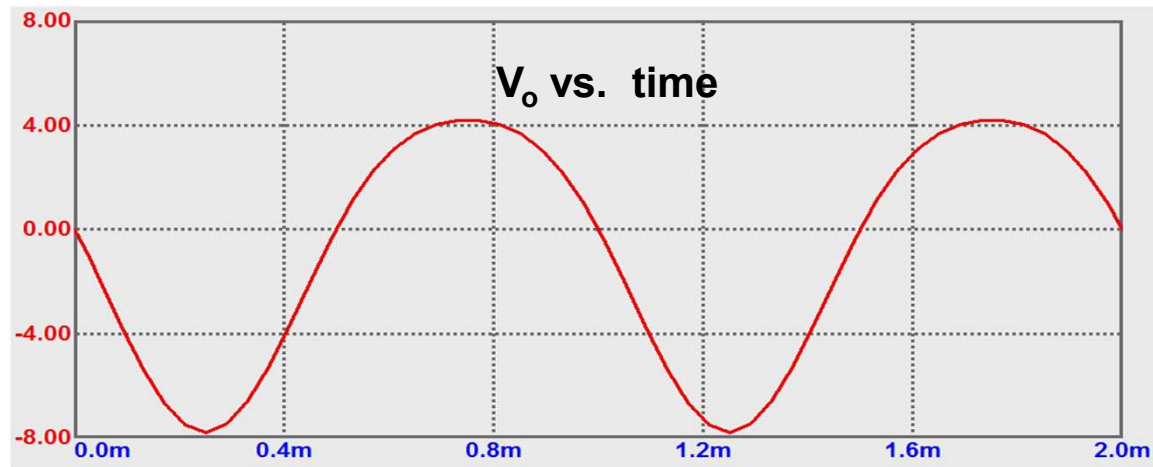




Because of Non-linearity the output waveform is distorted !

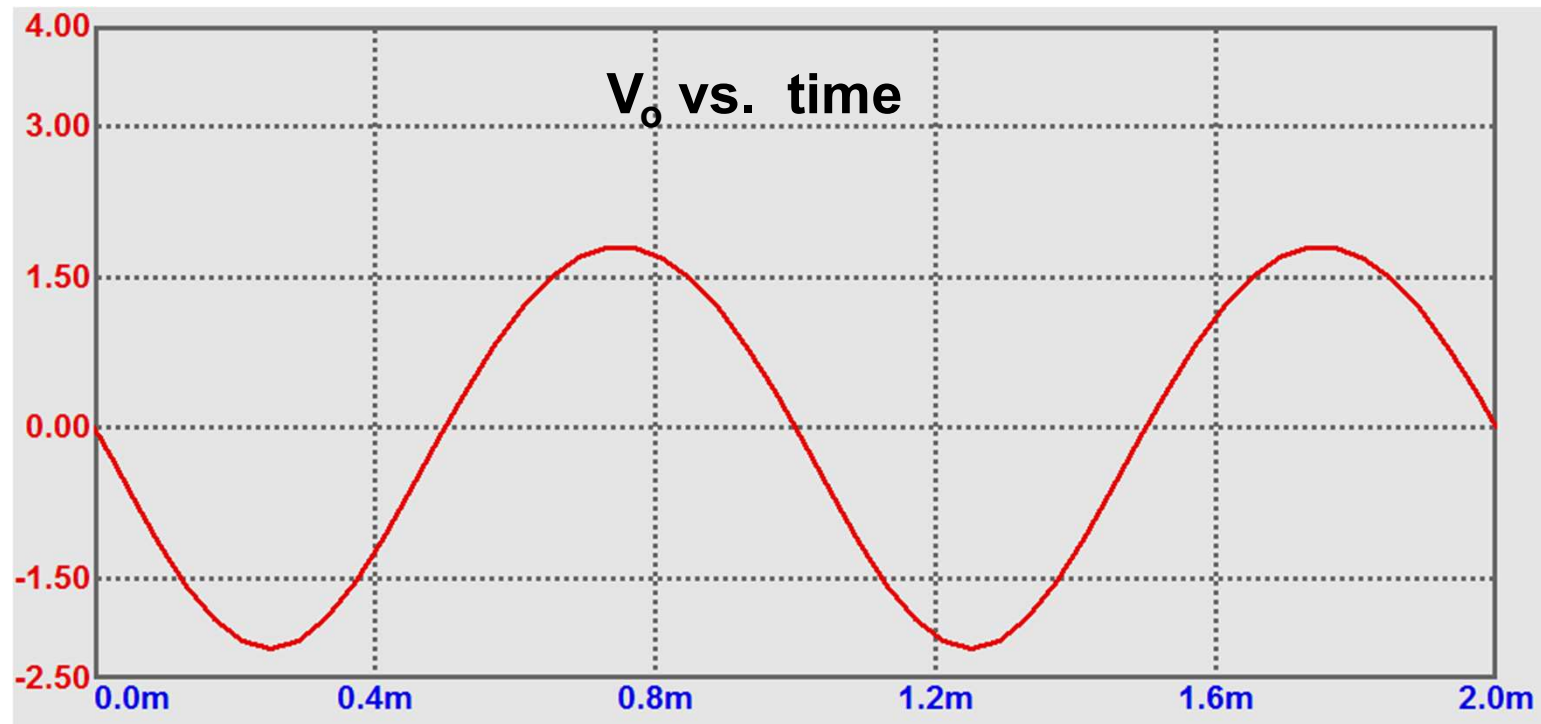Suppose input is reduced to  $v_s = 0.1V \sin(\omega t)$



**Distortion is much smaller if we restrict input voltage to a small value !**
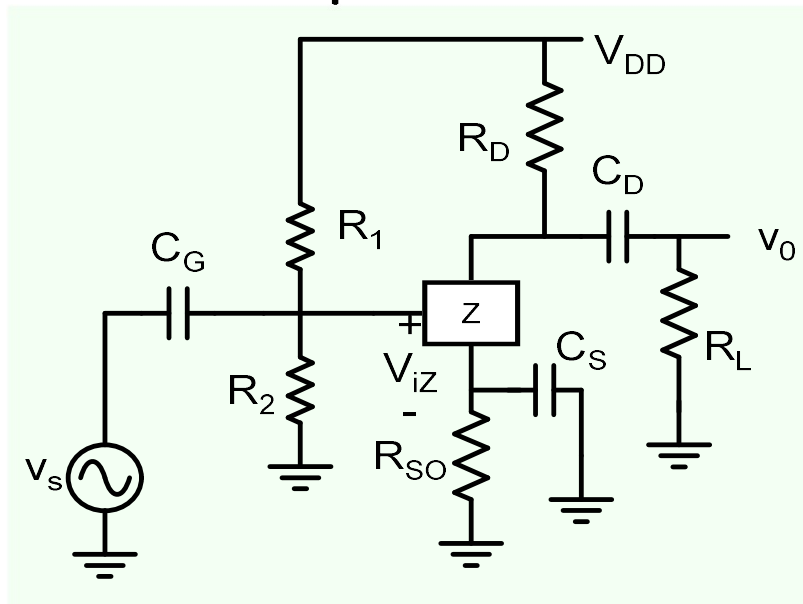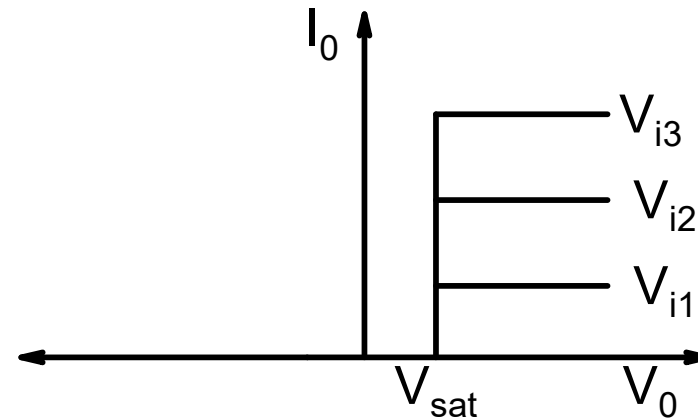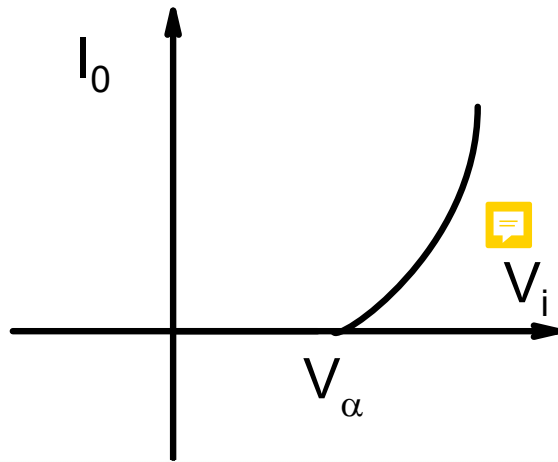
## Building Amplifiers with non-linear devices



Amplifier will work properly (with small distortion only if we restrict the amplitude of input signal to small values.

How small depends on the nature of non-linearity. The stronger the non-linearity the lesser the signal amplitude.