


# ESC201T : Introduction to Electronics

## HW9: Solution

B. Mazhari  
Dept. of EE, IIT Kanpur

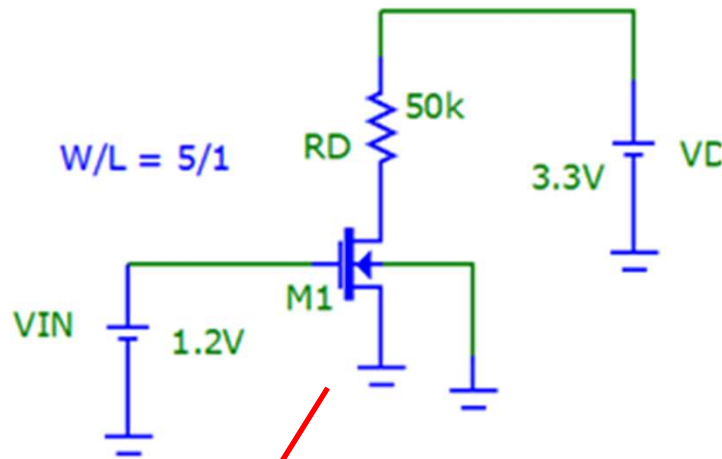Q.1 Determine the drain current and drain-source voltage for the two circuits shown below.

Assume that  $KP_N = 100\mu A/V^2$ ;  $V_{THN} = 1V$ ;  $\lambda_n = 0V^{-1}$



Assuming saturation mode :


$$ids(vgs) := kpn \times \frac{W}{L} \times \frac{(vgs - vthn)^2}{2}$$

$$ids(vgs) = 1 \times 10^{-5}$$

$$vds := vdd - ids(vgs) \times RD$$

$$vds = 2.8 \quad vdsat = 0.2$$

So assumption is correct

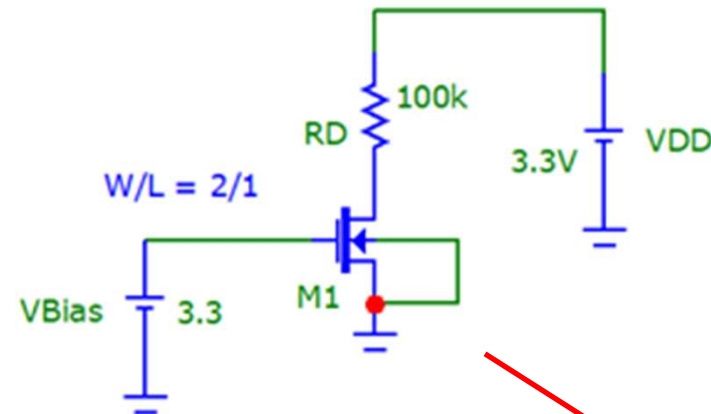

Assuming saturation mode :

$$ids(vgs) := kpn \times \frac{W}{L} \times \frac{(vgs - vthn)^2}{2}$$

$$ids(vgs) = 5.29 \times 10^{-4} \quad vds = -49.6$$


So Transistor is in Linear mode

$$ids := kpn \times \frac{W}{L} \times (vgs - vthn) \times (vdd - ids \times RD)$$

$$ids = 3.23 \times 10^{-5} \quad vds := vdd - ids \times RD = 0.07$$

(Units are Ampere and Volt)

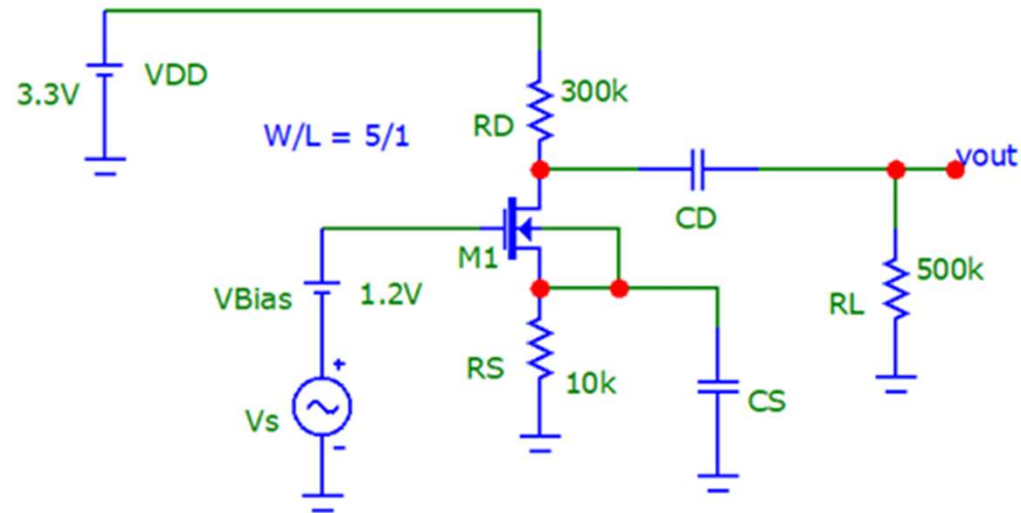Q.2 Analyze the circuit shown below to determine the voltage gain of the amplifier. Determine the gain if the capacitor  $C_S$  is removed from the circuit. Assume the same MOS parameters as in Q.1



### dc or Bias point or Quiescent point

(Units are Ampere and Volt)


Assuming saturation mode

$$i_{ds}(v_{gs}) := k_{pn} \times \frac{W}{L} \times \frac{(v_{gs} - v_{thn})^2}{2} \quad v_{gs} := V_{bias} - i_{ds} \times R_D \quad \text{We will get 2 values}$$

$$i_{ds1} = 7.464 \times 10^{-5} \quad v_{gs1} := v_{thn} + \sqrt{\frac{2 \times i_{ds1}}{k_{pn} \times \frac{W}{L}}} \quad v_{gs1} = 1.546 \quad \text{Not possible since } V_{Bias} = 1.2$$

$$i_{ds2} = 5.359 \times 10^{-6} \quad v_{gs2} := v_{thn} + \sqrt{\frac{2 \times i_{ds2}}{k_{pn} \times \frac{W}{L}}} \quad v_{gs2} = 1.146 \quad \text{This is fine } V_{DSAT} = 0.146V$$
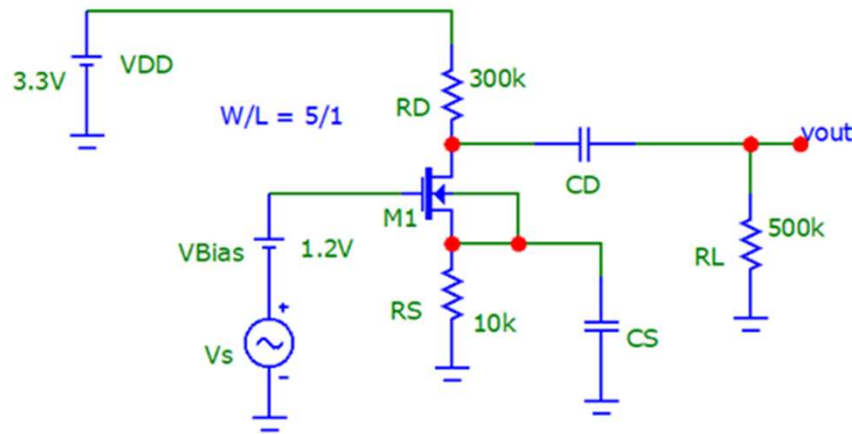
$$v_{dd} - i_{ds2} \times R_D = 1.692 \quad \text{So Tr. Is in SAT}$$



### Bias point:


$$v_{gs2} = 1.146 \text{ V} \quad i_{ds2} = 5.359 \times 10^{-6} \text{ A}$$

$$v_{dd} - i_{ds2} \times R_D = 1.692 \text{ V}$$

$$g_m = \sqrt{2I_{DS} \times KP_N \times \frac{W}{L}} = 7.3 \times 10^{-5} \Omega^{-1}$$


ac or small signal analysis

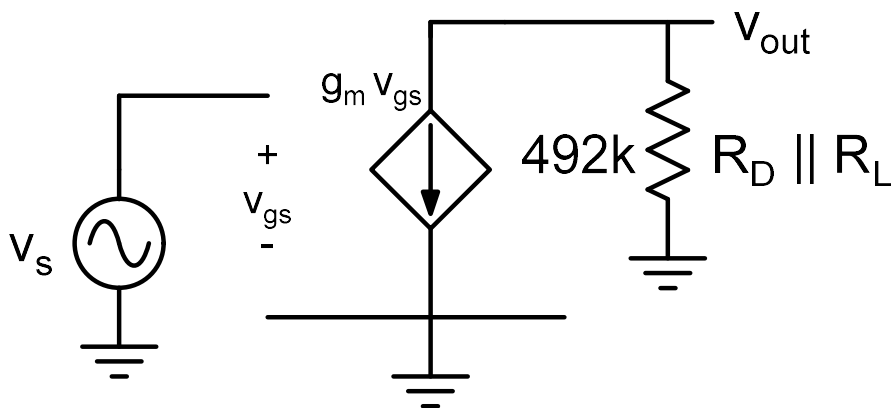Capacitors acts as short resulting in the following equivalent circuit




$$A_V = -g_m \times R_D \parallel R_L = -36$$

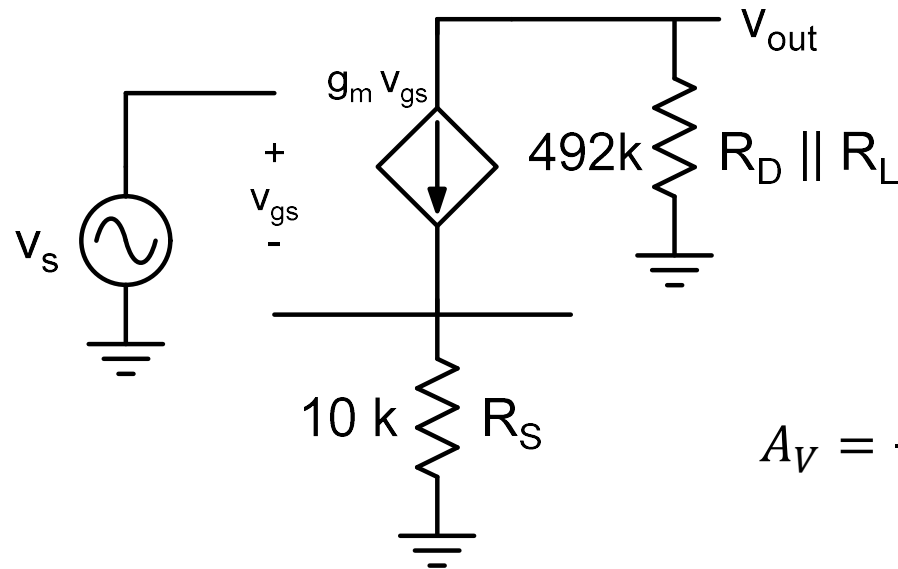Removing the capacitor  $C_s$  does not alter the bias point and thus  $g_m$  also remains same. The ac equivalent circuit now becomes




$$A_V = -\frac{g_m}{1 + g_m \times R_S} \times R_D \parallel R_L = -20.78$$

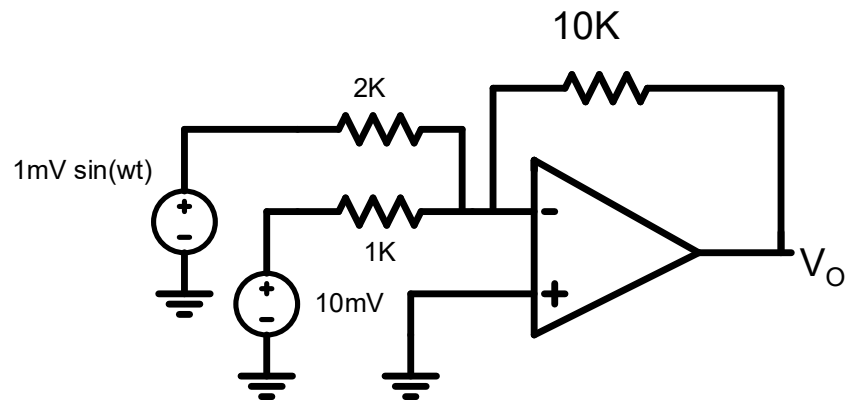Q.3 Determine the output of the ideal opamp circuits shown below





$$v_o = -\left\{\frac{10K}{1K} \times 10mV + \frac{10K}{2K} \times 1mV \sin(\omega t)\right\}$$
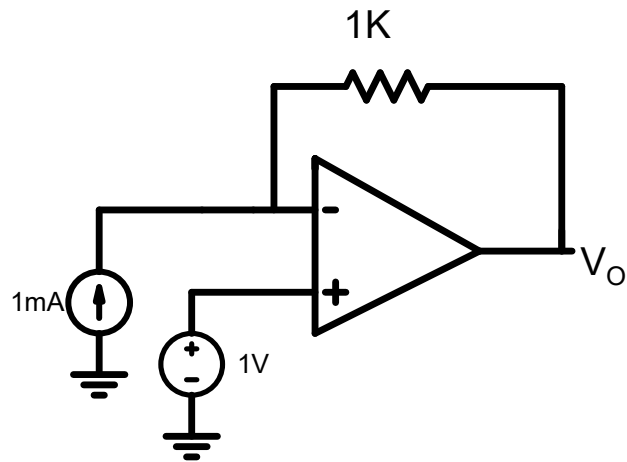
$$= -\{0.1 + 5 \times 10^{-3} \sin(\omega t)\}$$




$$v_+ = v_- = 1V$$
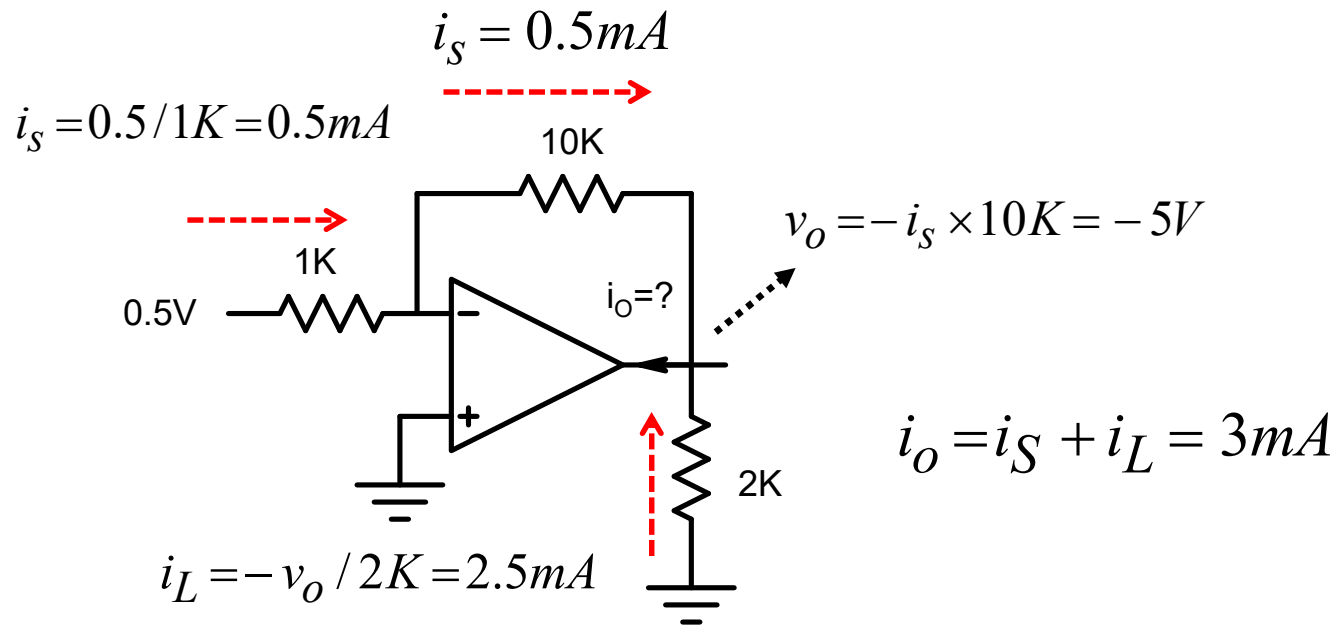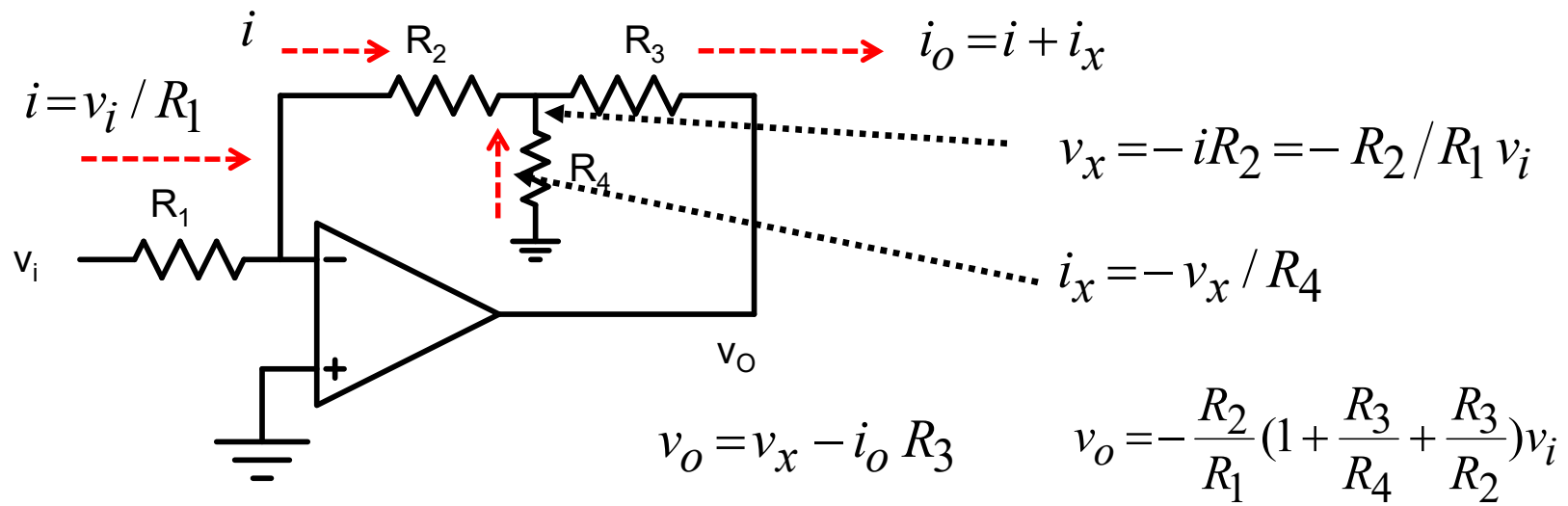
$$\frac{1 - v_o}{1K} = 1mA \quad v_o = 0V$$



Q.4 Design an opamp circuit that would generate the following output voltage where  $V_{s1}$ ,  $V_{s2}$ ,  $V_{s3}$  and  $V_{s4}$  are input voltages
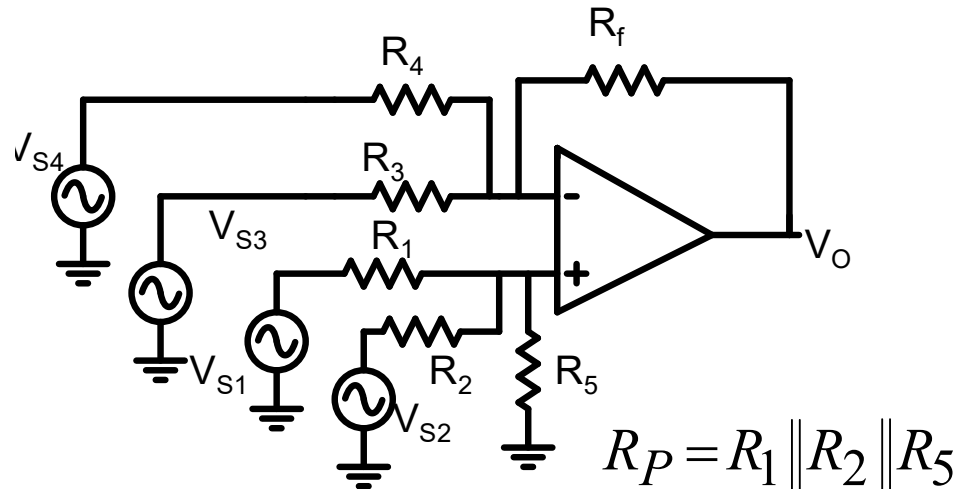
$$V_O = 2v_{s1} + 4v_{s2} - 8v_{s3} - 10v_{s4}$$


$$v_o = -\left(\frac{R_f}{R_3}\right)v_{s3} - \left(\frac{R_f}{R_4}\right)v_{s4} + \left(1 + \frac{R_f}{R_3 \parallel R_4}\right) \times \frac{R_P}{R_1}v_{s1} + \left(1 + \frac{R_f}{R_3 \parallel R_4}\right) \times \frac{R_P}{R_2}v_{s2}$$


Choose :  $R_f = 10K \Rightarrow R_3 = 1.25K \Rightarrow R_4 = 1K$

$\Rightarrow \frac{R_P}{R_1} = 0.105 \quad \Rightarrow \frac{R_P}{R_2} = 0.211 \quad \Rightarrow \frac{R_1}{R_2} = 2$


Choose :  $R_2 = 1K \Rightarrow R_1 = 2K \Rightarrow R_P = 0.211K \Rightarrow R_5 = 0.308K$




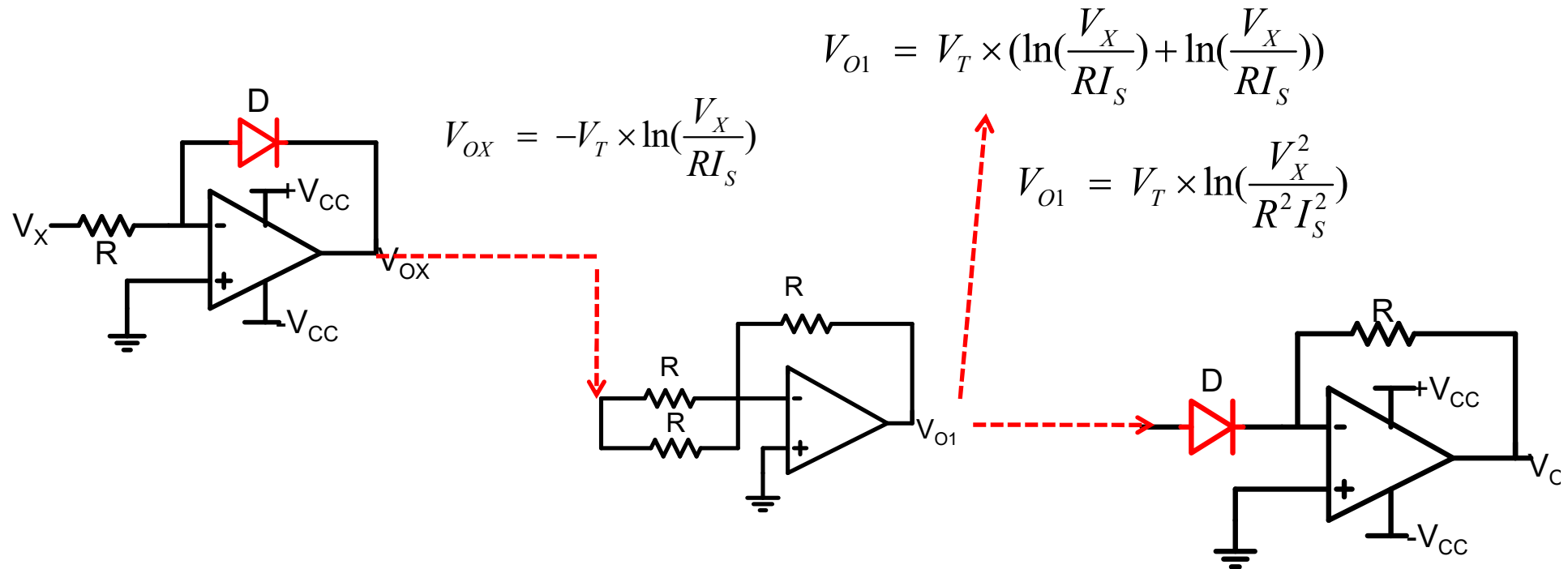Q.5 Design an opamp circuit that can produce  $V_O = K \times V_{IN}^2$  where  $V_{in}$  is the input voltage.



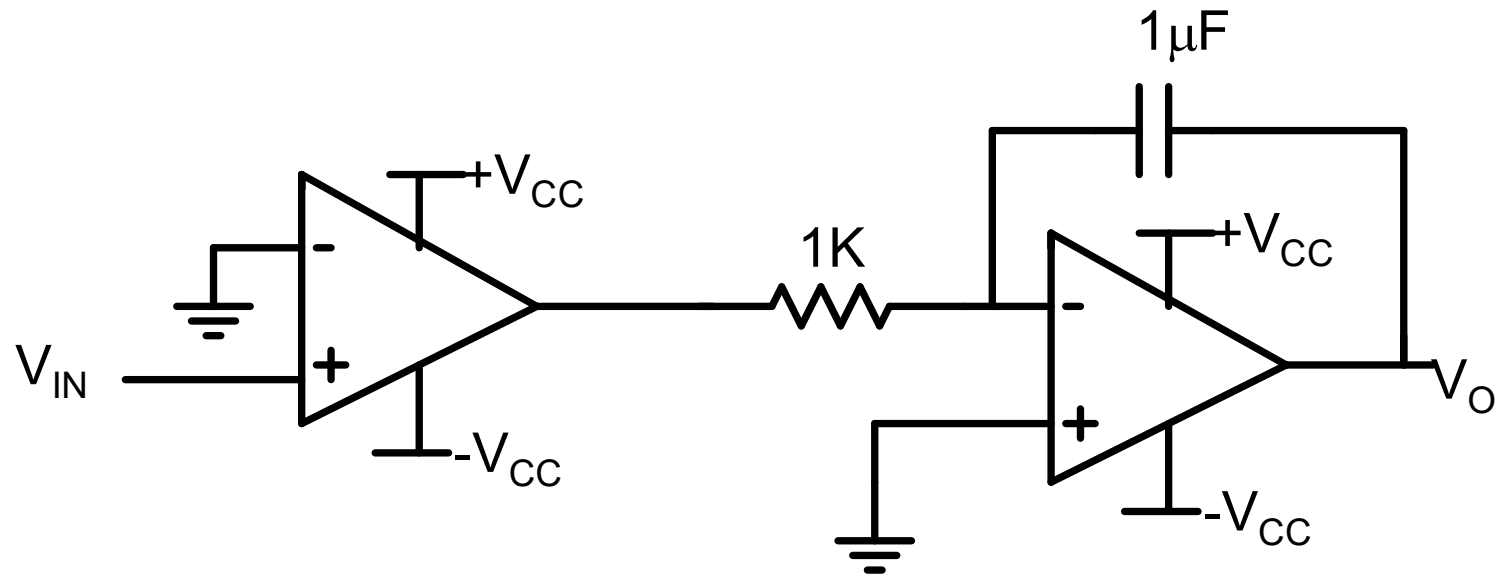Q.6 Sketch the output voltage of the circuit shown below for  $V_{in} = 1V \sin(2\pi ft)$ ;  $f = 1KHz$  and supply voltages of  $\pm 5V$




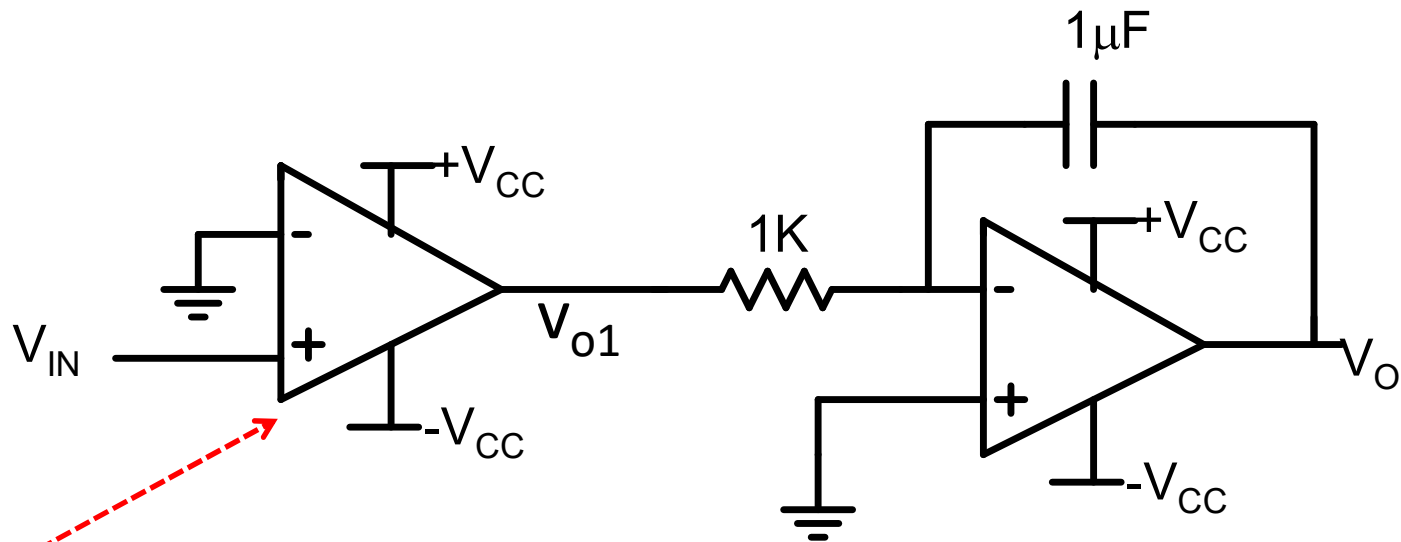


comparator

$$V_{O1} = +5V \text{ if } v_{in} > 0$$


$$= -5V \text{ if } v_{in} < 0$$

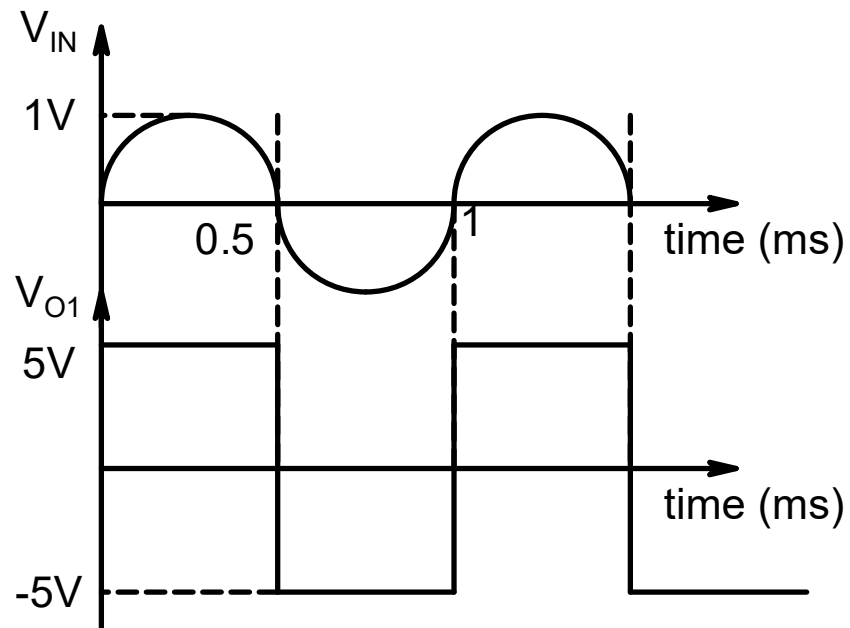

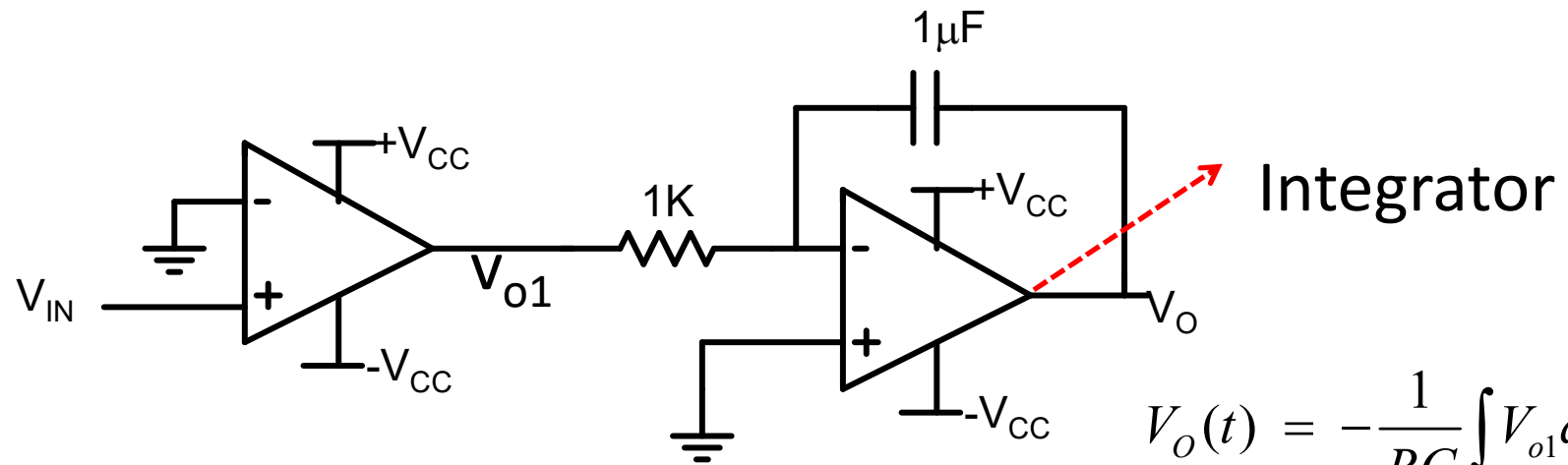

$$V_O(t) = -\frac{1}{RC} \int V_{o1} dt$$



$$= -10^3 \int V_{o1} dt$$

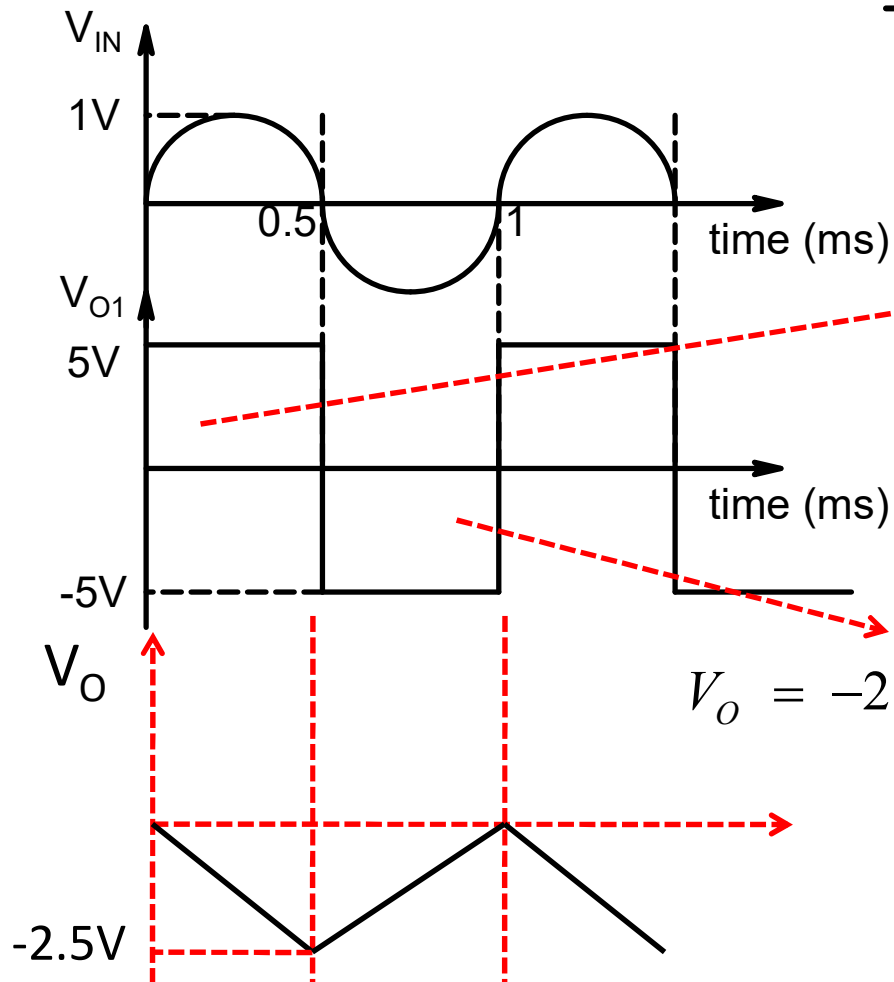


$$V_O = -5 \times 10^3 \times t \text{ for } 0 \leq t \leq 0.5 \text{ ms}$$

$$V_O = -2.5 + 5 \times 10^3 \times (t - 0.5 \text{ ms}) \text{ for } 0.5 \text{ ms} \leq t \leq 1 \text{ ms}$$

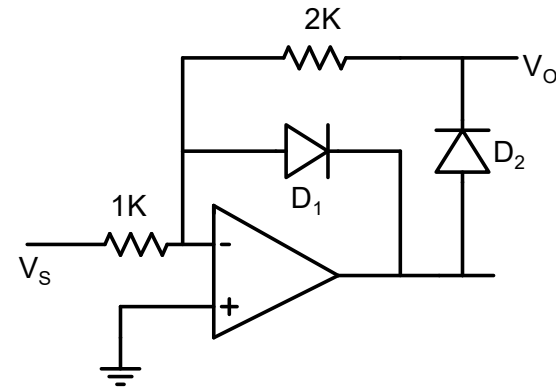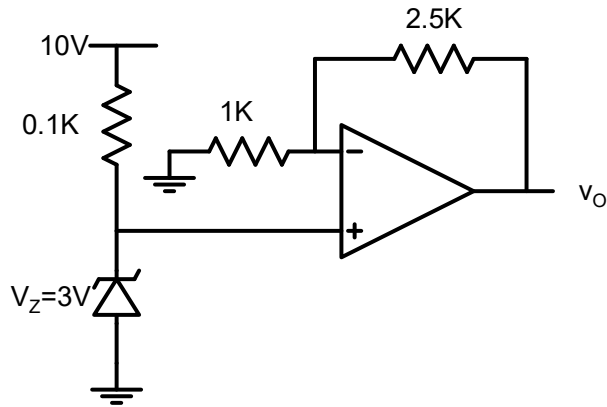Q.7 Determine the output for the ideal opamp circuits shown below. For the circuit on the right assume that diodes have cut-in voltage of 0.7V. Analyze the circuit for  $V_s = 1V$  and  $V_s = -1V$ . For the transistor assume a current gain of 100. What is the usefulness of each of the circuits?





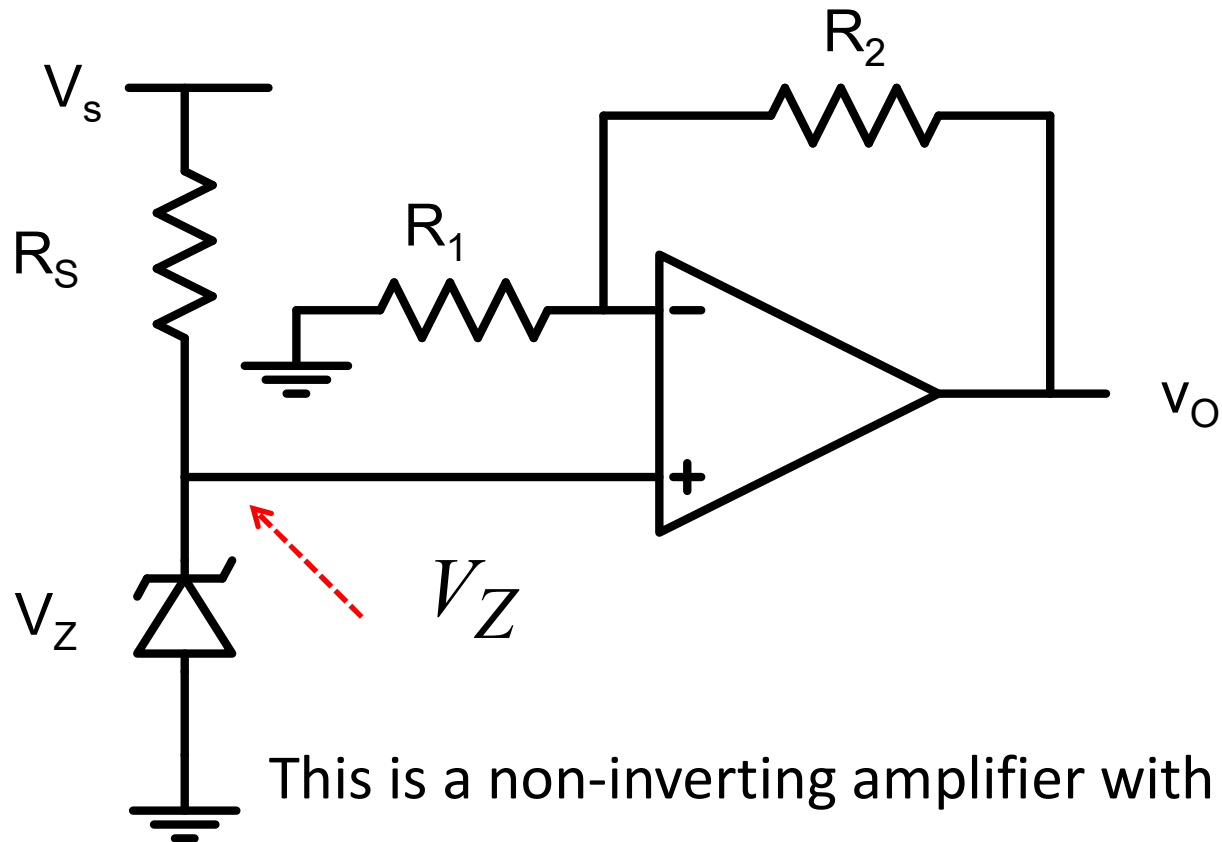

This is a non-inverting amplifier with  $V_Z$  as input

$$v_o = V_Z \left( 1 + \frac{R_2}{R_1} \right)$$

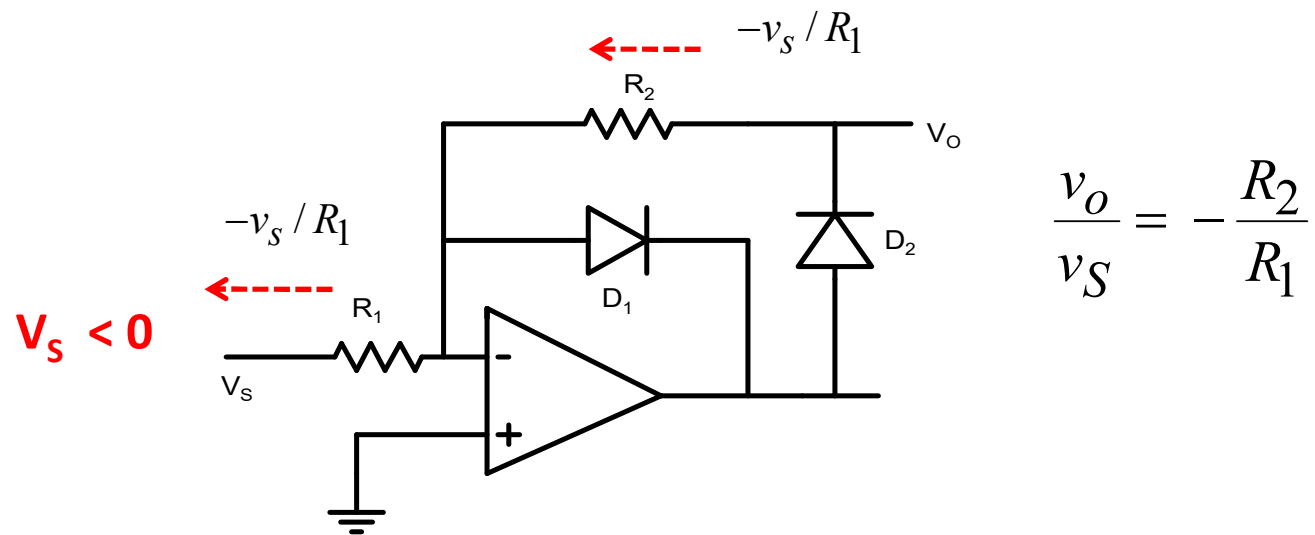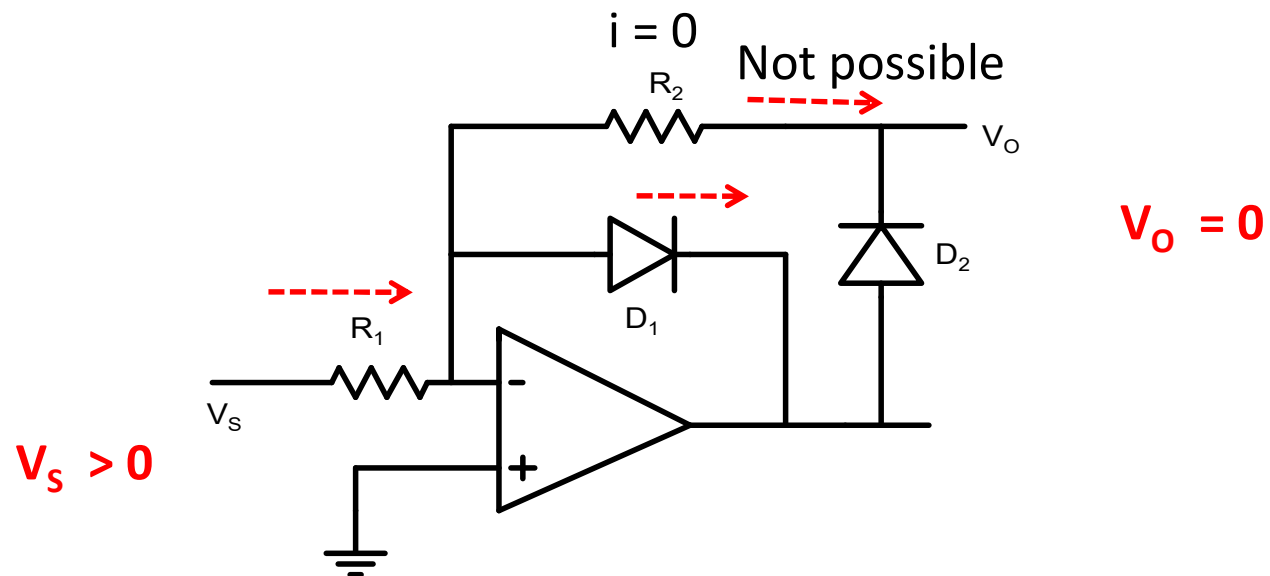The circuit produces a constant output voltage  $V_o$  even though supply voltage may vary and thus acts like a voltage regulator.



The circuit acts like a rectifier