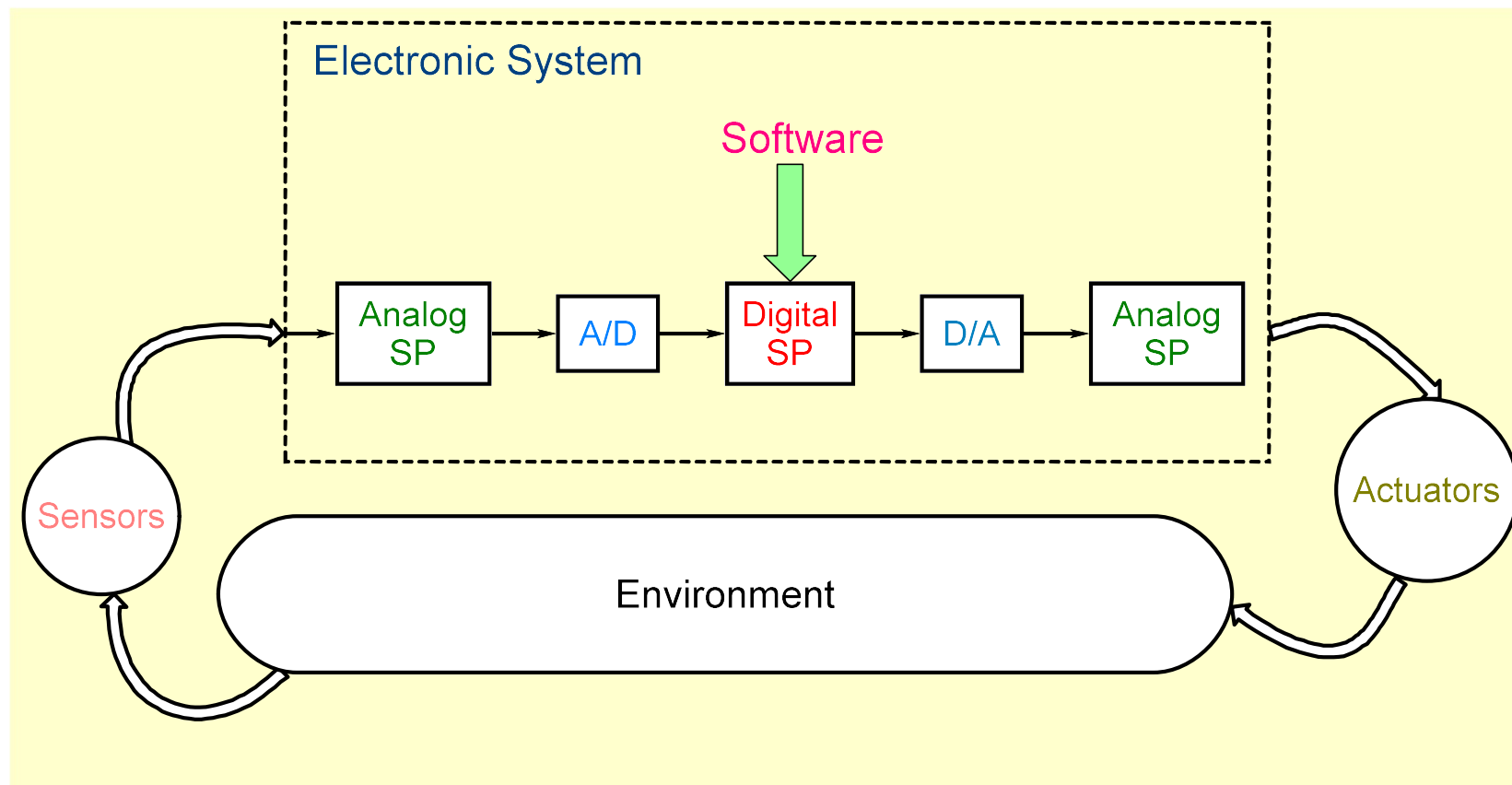


# **ESC201AT : Introduction to Electronics**

## **Lecture-3 : Tools For Circuit Analysis-1**

B. Mazhari  
professor, Dept. of EE  
IIT Kanpur

# Problem Solving Using Electronics



In ESC201A we learn by analyzing and designing analog and digital circuits


# Toolbox



We need to equip ourselves with tools for circuit analysis
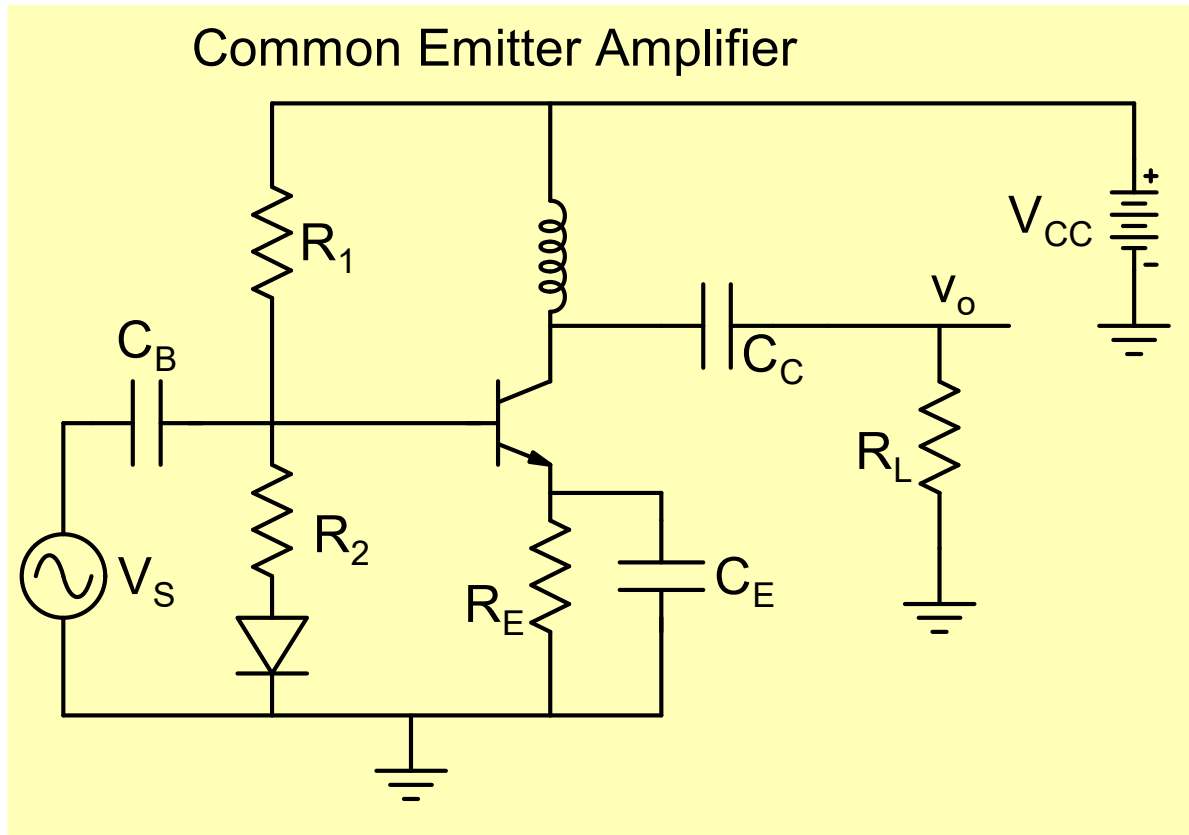
## Electrical Circuit

Connection of several circuit elements in closed paths by conductors




Before we learn how to analyze and design circuits, we must become familiar with some basic circuit elements.
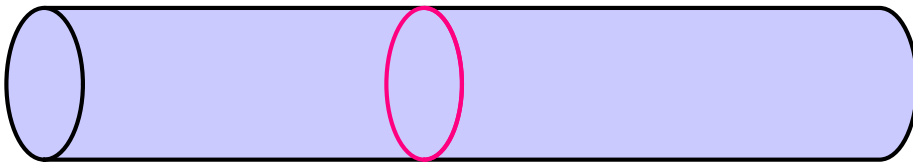
# Electrical Current

The time rate of flow of electrical charge

– The units are amperes (A), which are equivalent to coulombs per second (C/s)




$$i(t) = \frac{dq(t)}{dt}$$

Flow of electrons through a wire or other electrical conductor gives rise to current

- Electrons are negatively charged particles

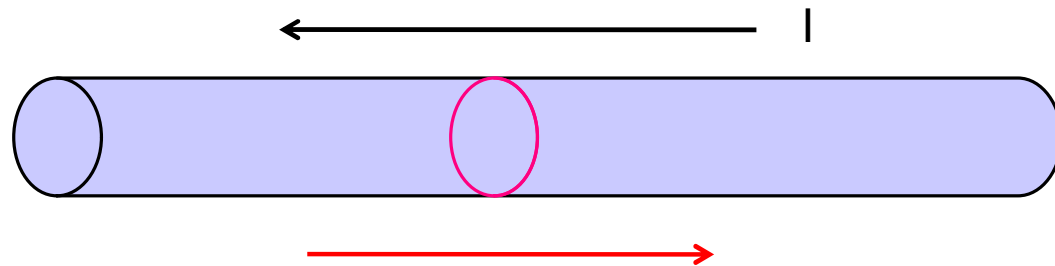The charge per electron is  **$-1.602 \times 10^{-19} \text{ C}$**



$10^{16}$  electrons flow per second



Large number of electrons have to flow for appreciable current

How much current flows?  $i(t) = \frac{dq(t)}{dt}$

$$I = \frac{Q}{t} = \frac{-1.6 \times 10^{-19} \times 10^{16}}{1} = -1.6 \times 10^{-3} \text{ A}$$
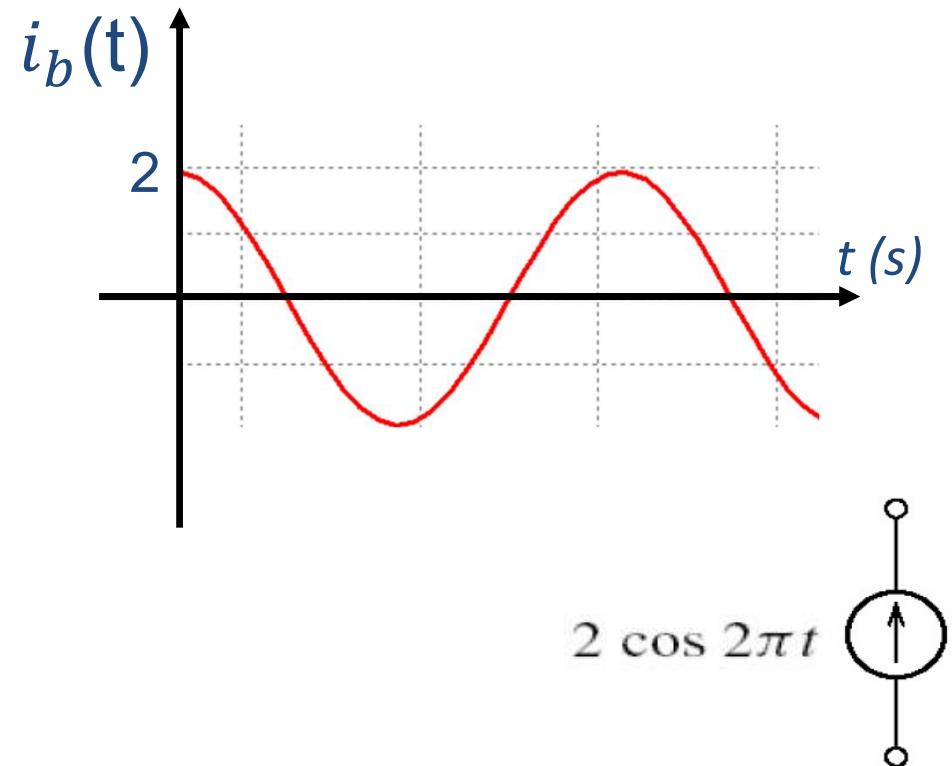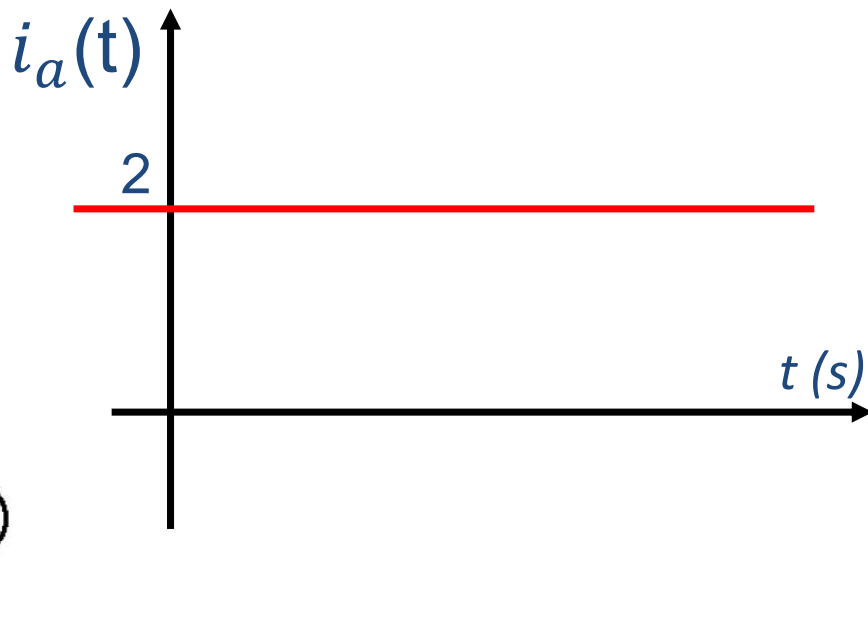
## Direct Current (DC) & Alternating Current (AC)

When current is constant with time, we say that we have direct current, abbreviated as DC.




On the other hand, a current that varies with time, reversing direction periodically, is called alternating current, abbreviated as **AC**

# Voltage


Voltage difference is a Source of current flow

Units of Voltage: Volts (V)


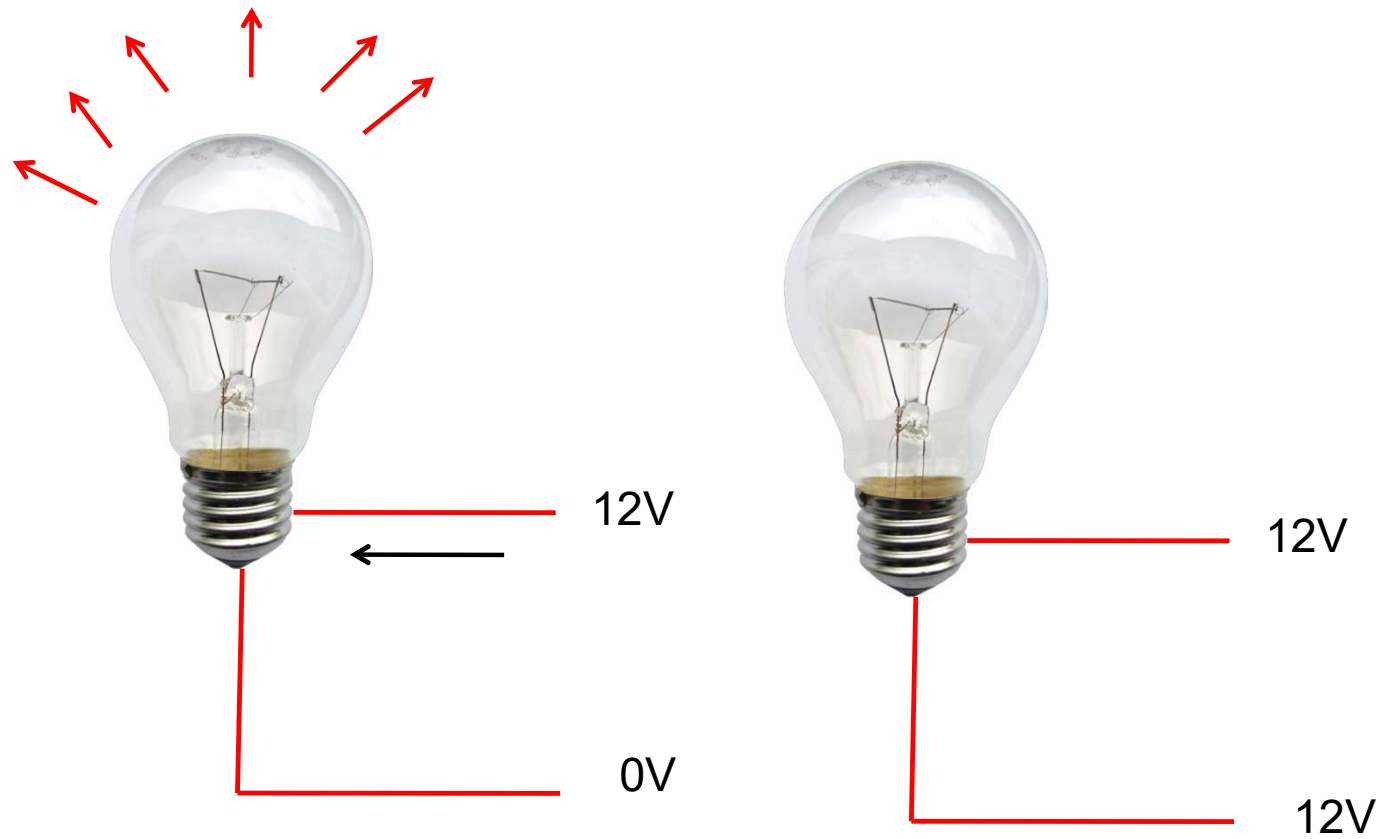





# DC and AC voltages

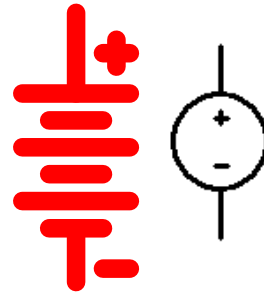


$$V_{+} - V_{-} = 12V$$

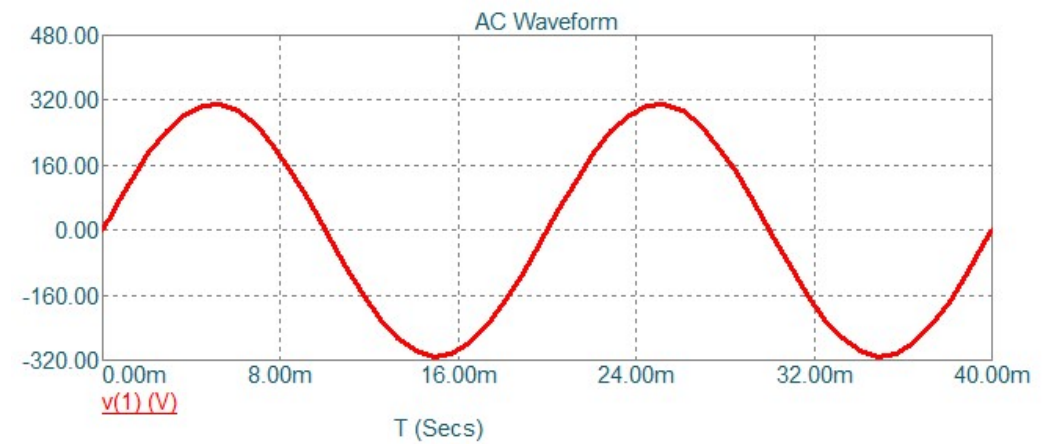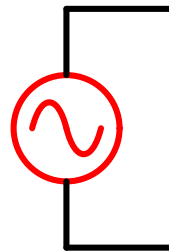


# Voltage Sources

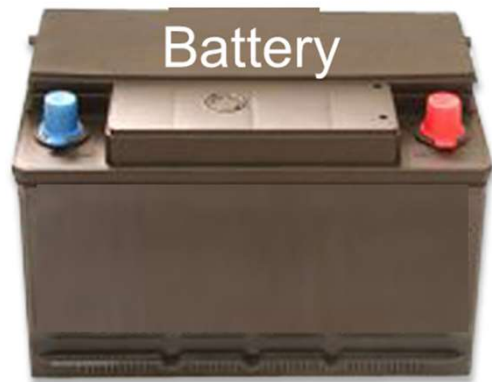

## Common Emitter Amplifier

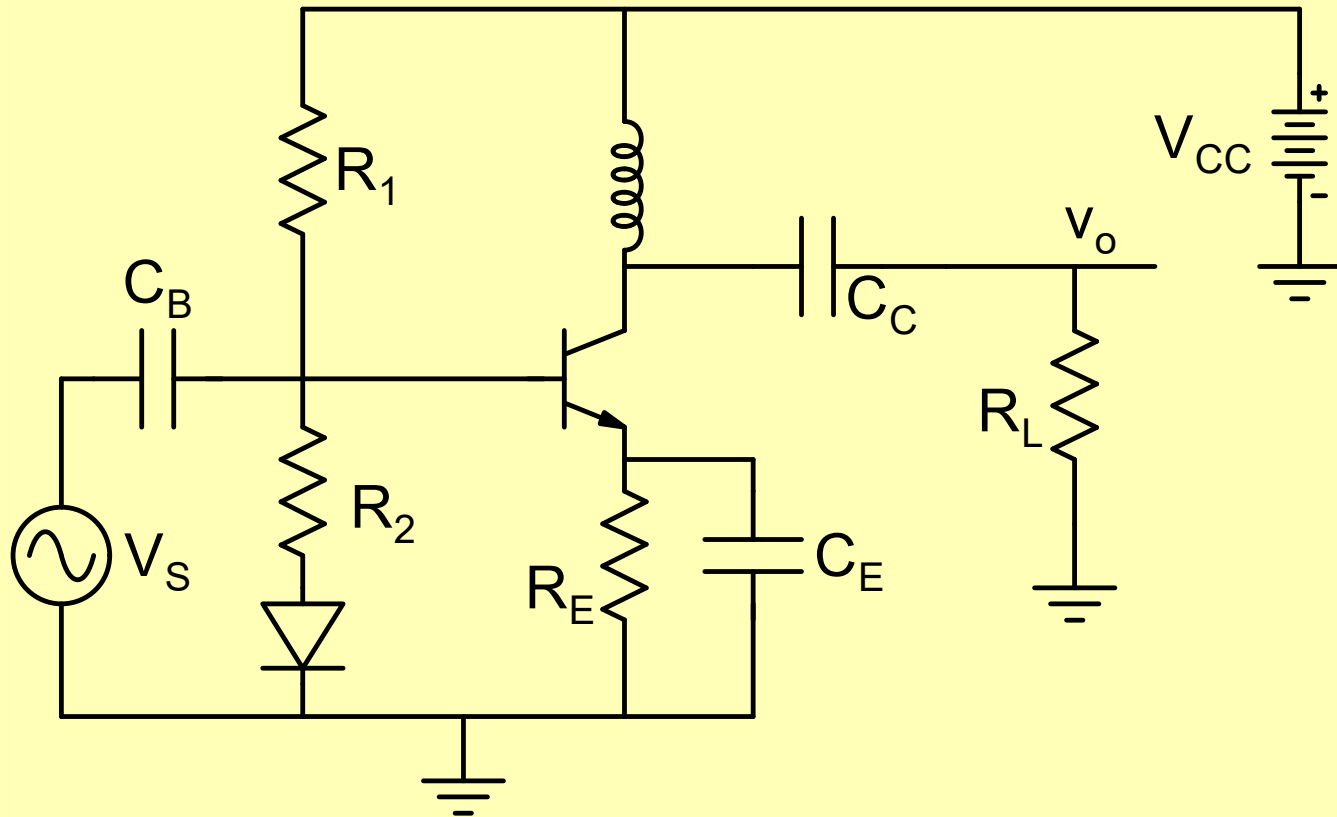

## Resistance

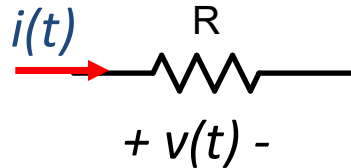

$$v(t) = R \times i(t)$$

Ohm's law

The constant,  $R$ , is called the resistance and is measured in units of Ohm ( $\Omega$ )

Standard Multiples of Ohm


$M\Omega$  Mega Ohm ( $10^6 \Omega$ )

$k\Omega$  Kilo Ohm ( $10^3 \Omega$ )

$$i(t) = \frac{v(t)}{R} = G \times v(t)$$

$G = 1/R$  is called conductance and its unit is Siemens (S)
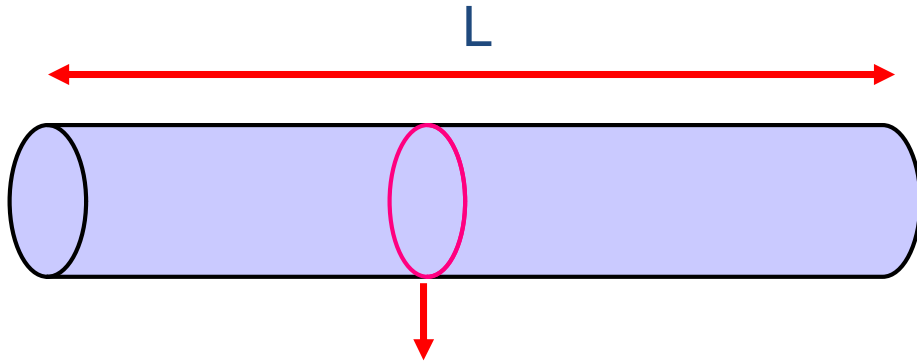
## Resistance Related to Physical Parameters



Cross-sectional Area A



$$R = \rho \times \frac{L}{A}$$

Resistance is affected by the **dimensions** and **geometry** of the resistor as well as the **particular material** used



$\rho$  is the resistivity of the material in ohm meters [ $\Omega\cdot\text{m}$ ]

- Conductors (Aluminum, Carbon, Copper, Gold)
- Insulators (Glass, Teflon)
- Semiconductors (Silicon)


## Two special resistors

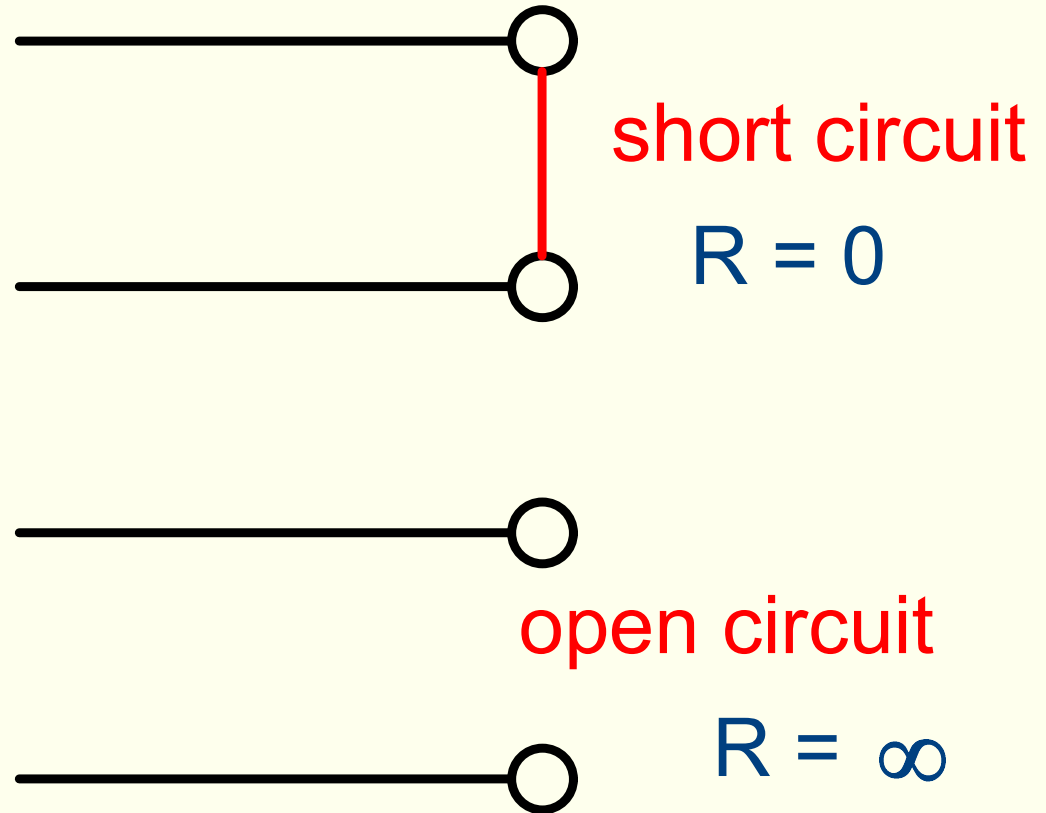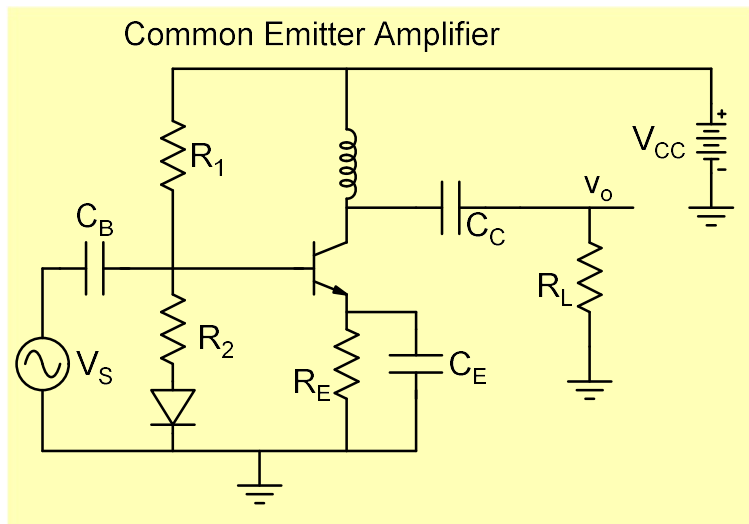

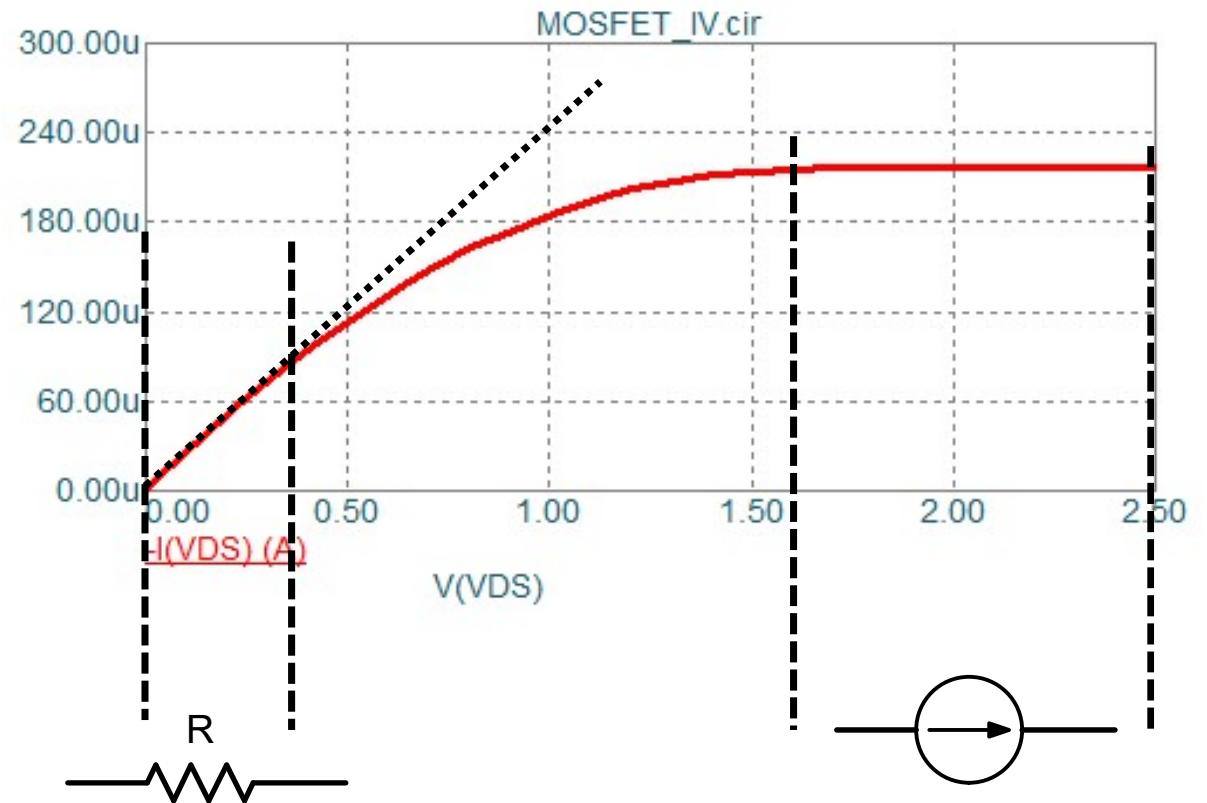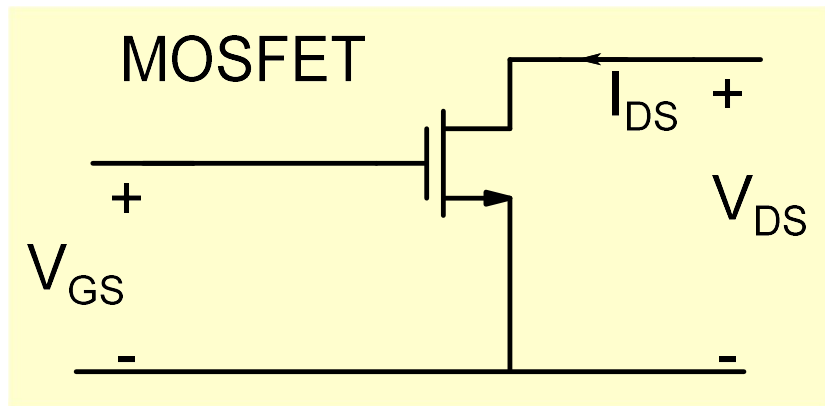Any electrical element which has linear current voltage characteristics over a certain voltage range can be **modeled** as a resistor in that range



# Power

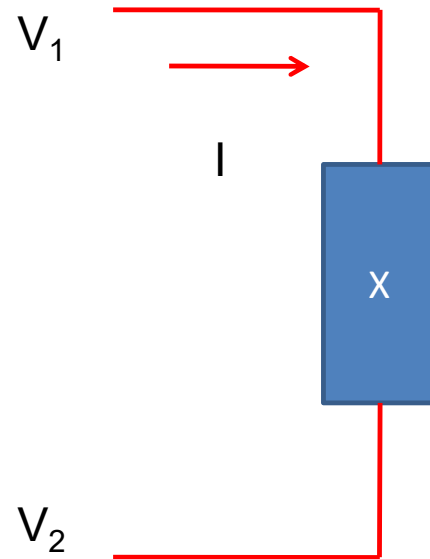


$$P = (V_1 - V_2) \times I$$

If  $V_1 > V_2$  then  $P$  is positive and it means that power is being delivered to the electrical element  $X$

If  $V_1 < V_2$  then  $P$  is negative and it means that power is being extracted from the electrical element  $X$ .  $X$  is a source of power !




## Examples

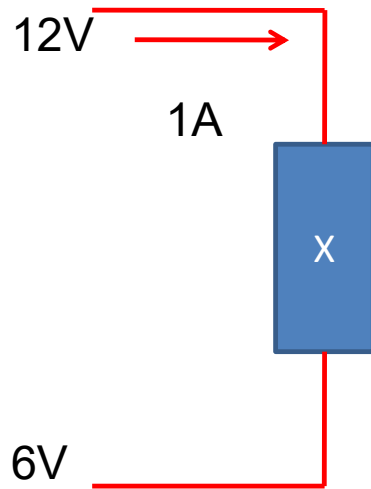

$P = ?$

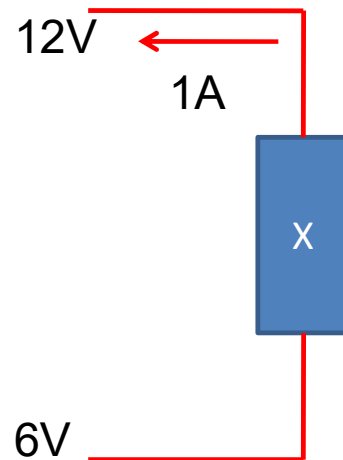
$$\begin{aligned} P &= (V_1 - V_2) \times I \\ &= (12 - 6) \times 1 = 6W \end{aligned}$$



$P = ?$

$$\begin{aligned} P &= (V_1 - V_2) \times I \\ &= (12 - 6) \times -1 = -6W \end{aligned}$$

## Power dissipated in a Resistor

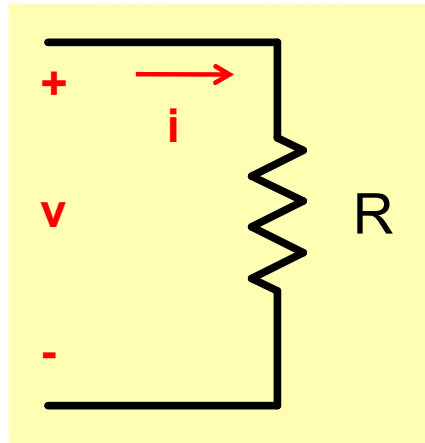

$$v = i \times R$$

$$i = \frac{v}{R}$$


$$P = v \times i$$

$$P = i^2 \times R$$


$$P = \frac{v^2}{R}$$
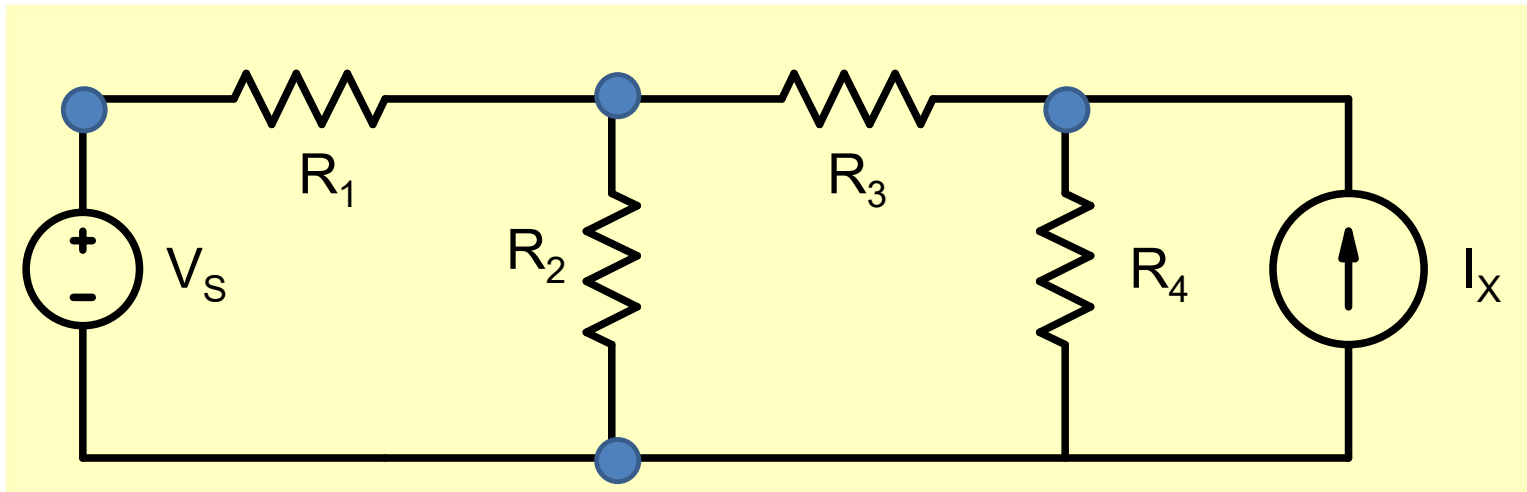
# Nodes and loops

**Node:** A point where 2 or more circuit elements are connected.




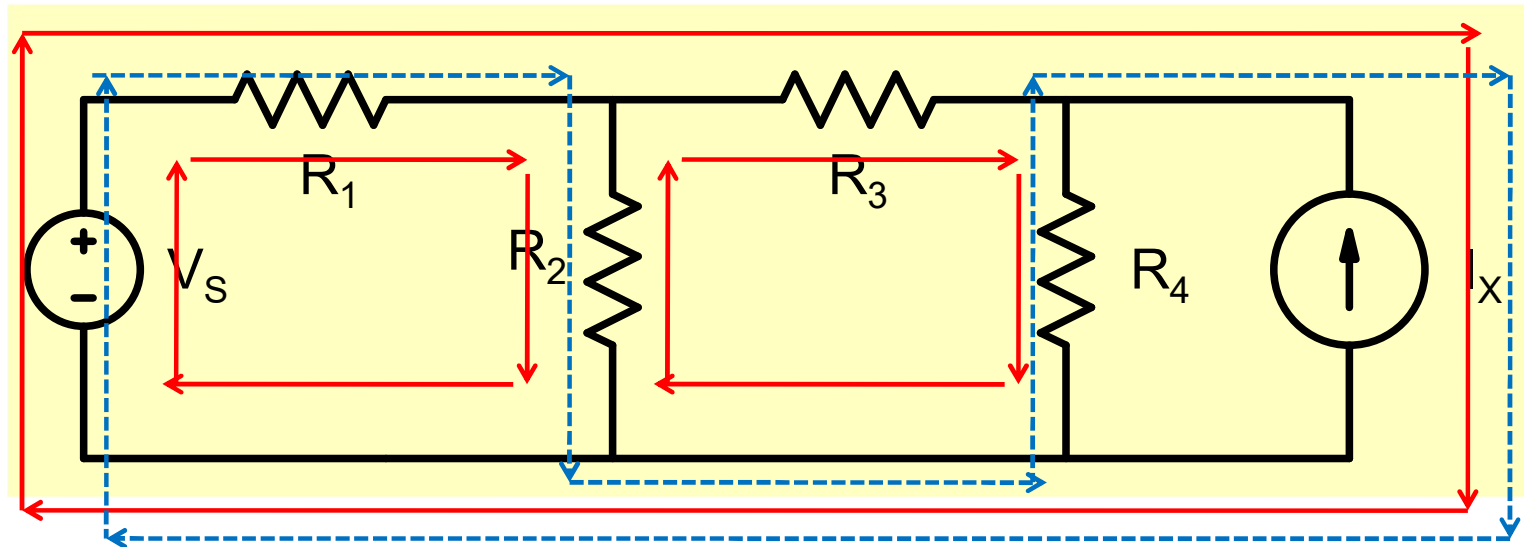A **loop is formed by tracing a closed path** through circuit elements without passing through any intermediate node more than once



This is not a valid loop !

## Circuit Analysis

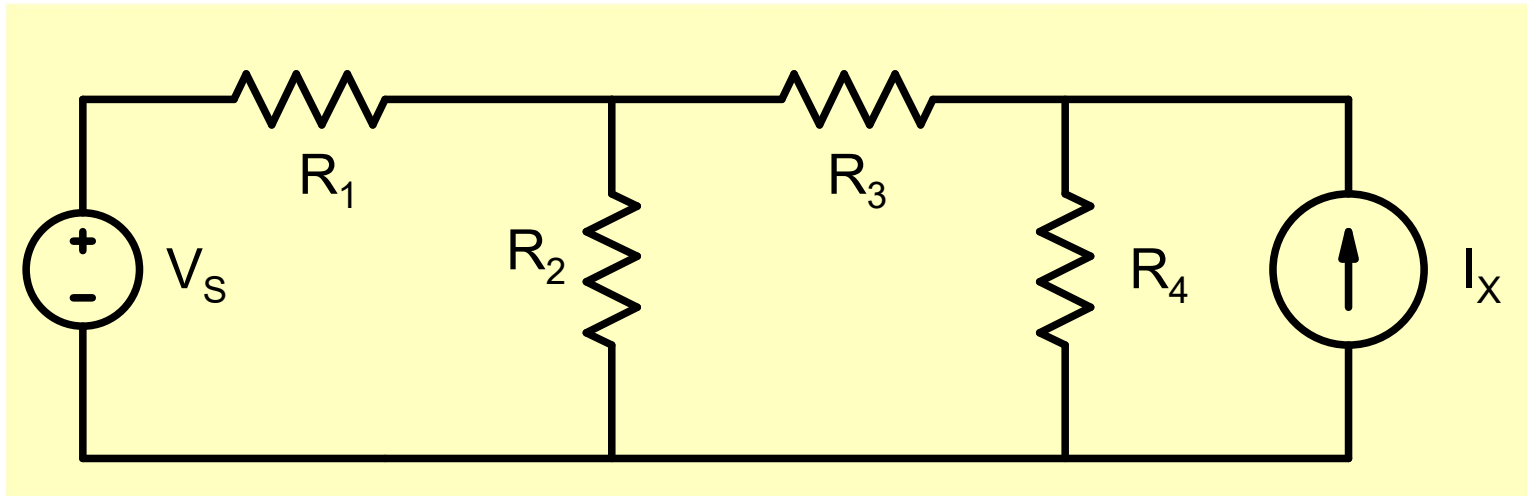

What is current in  $R_2$  ?

Procedure:


Use Kirchhoff's voltage law (KVL) and Kirchhoff's Current law (KCL) to transform the circuit into a set of equations whose solution gives the required voltage or current value

## Kirchhoff's Current Law (KCL)


Net current entering a node is zero

$$\sum_{j=1}^N i_j = 0$$

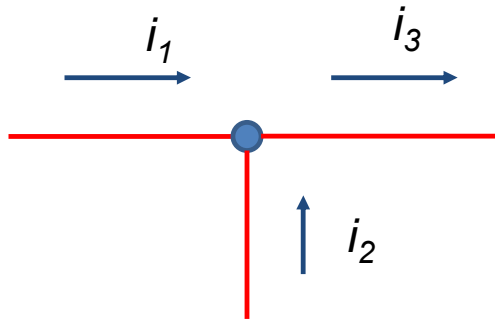
Current entering a node is considered positive and current leaving a node is considered as negative



$$i_1 + i_2 - i_3 = 0$$

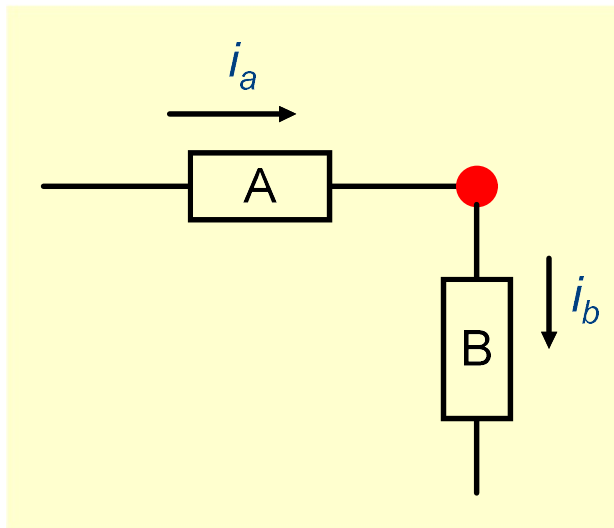

$$i_a = i_b$$

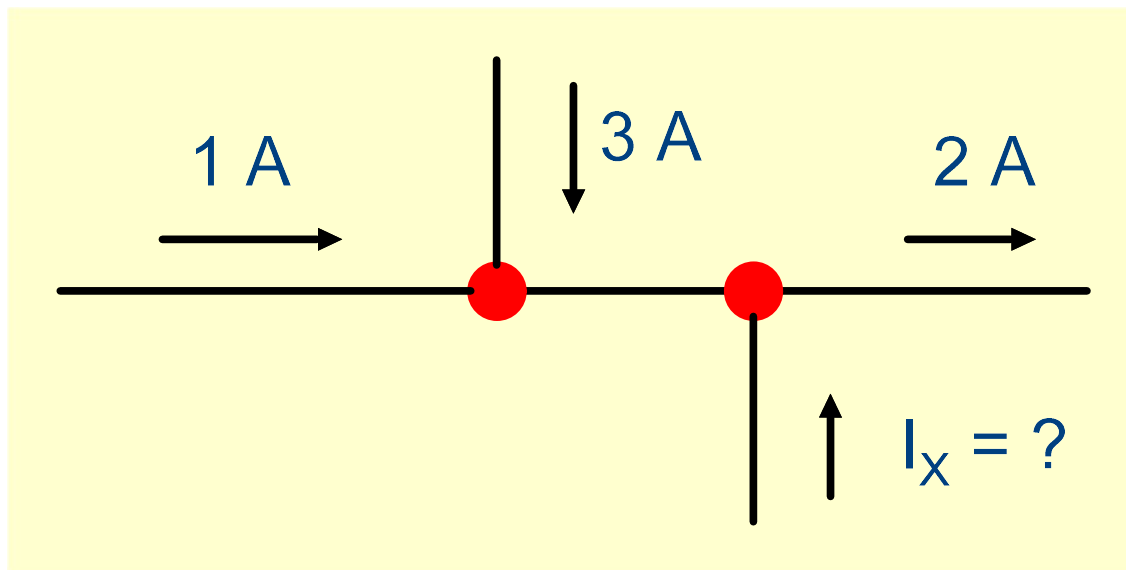


$$1 + 3 + I_x - 2 = 0$$


$$I_x = -2$$
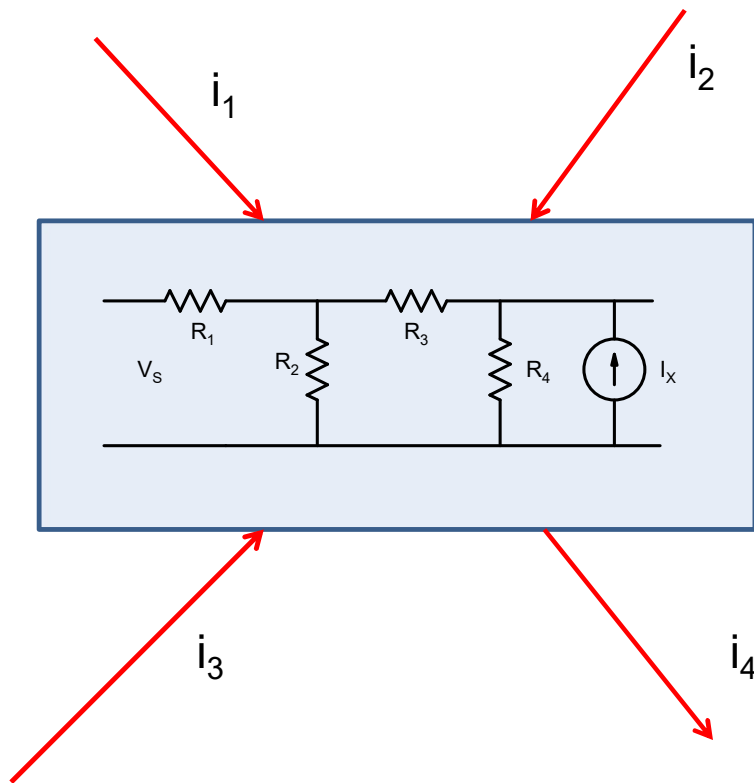
## KCL: More general formulation

The sum of currents entering/leaving a **closed surface** is zero.




$$i_1 + i_2 + i_3 - i_4 = 0$$

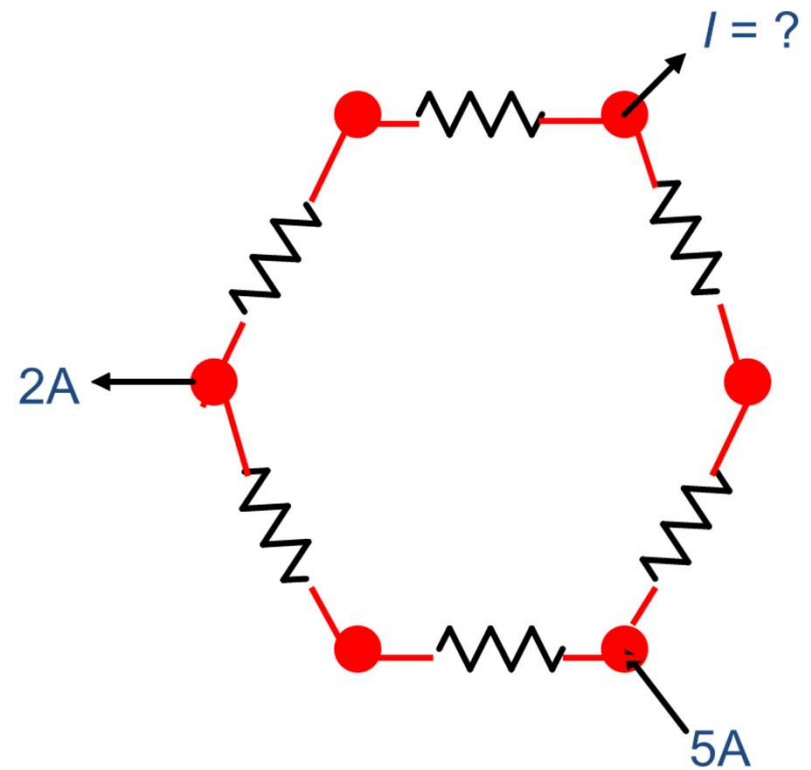


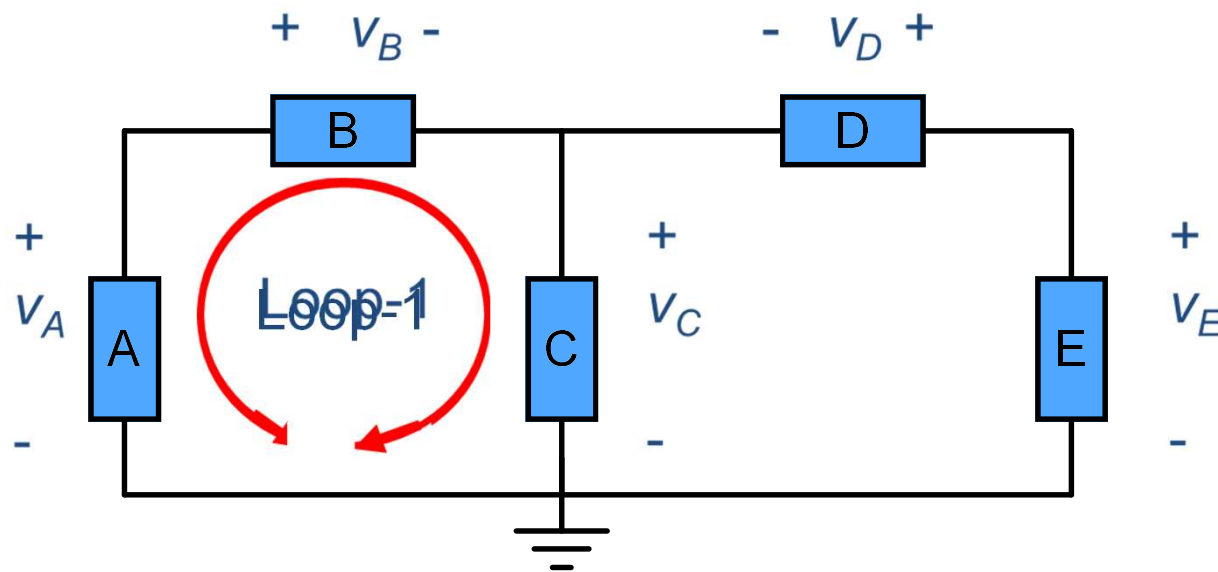
## Kirchhoff's Voltage Law (KVL)

The sum of the voltages for any closed path (loop) in an electrical circuit equals zero




$$\text{Loop1: } -v_a + v_b + v_c = 0$$

$$\text{Loop1: } -v_c - v_b + v_a = 0$$

Voltages are added or subtracted depending on their reference polarities relative to direction of travel around the loop

## Example

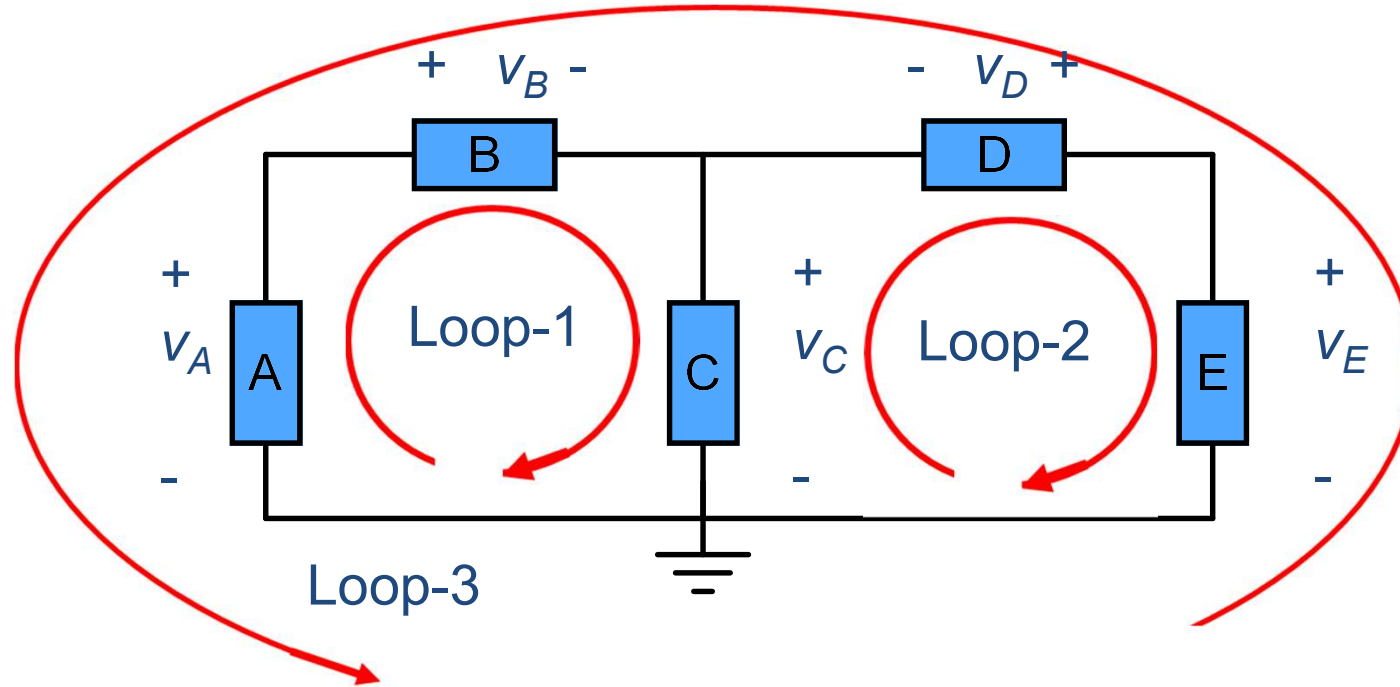


$$\text{Loop1: } -v_a + v_b + v_c = 0$$


$$\text{Loop2: } -v_c - v_d + v_e = 0$$

$$\text{Loop3: } -v_e + v_d - v_b + v_a = 0$$

## KVL and Conservation of Energy

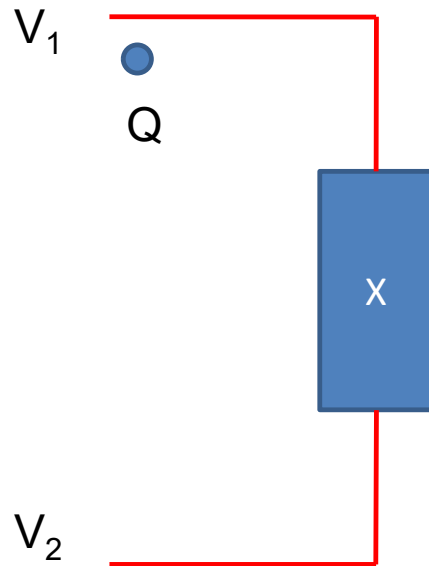

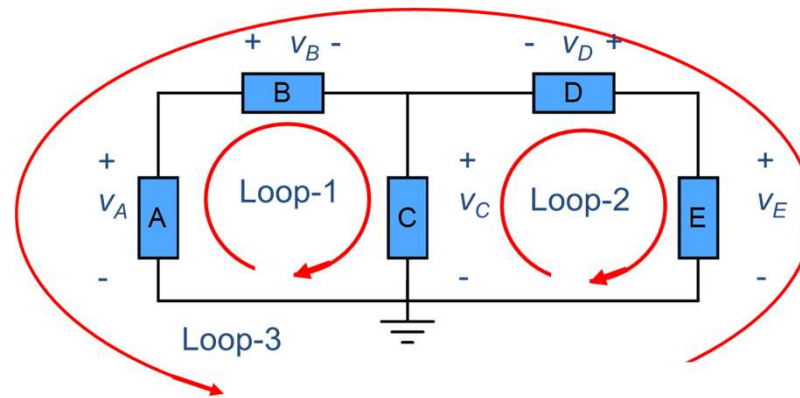The charge loses energy =  $Q \times (V_1 - V_2)$  Joules



$$\text{Loop 1: } -v_a + v_b + v_c = 0$$


**KVL: law of conservation of Energy**

Energy gained

Energy lost
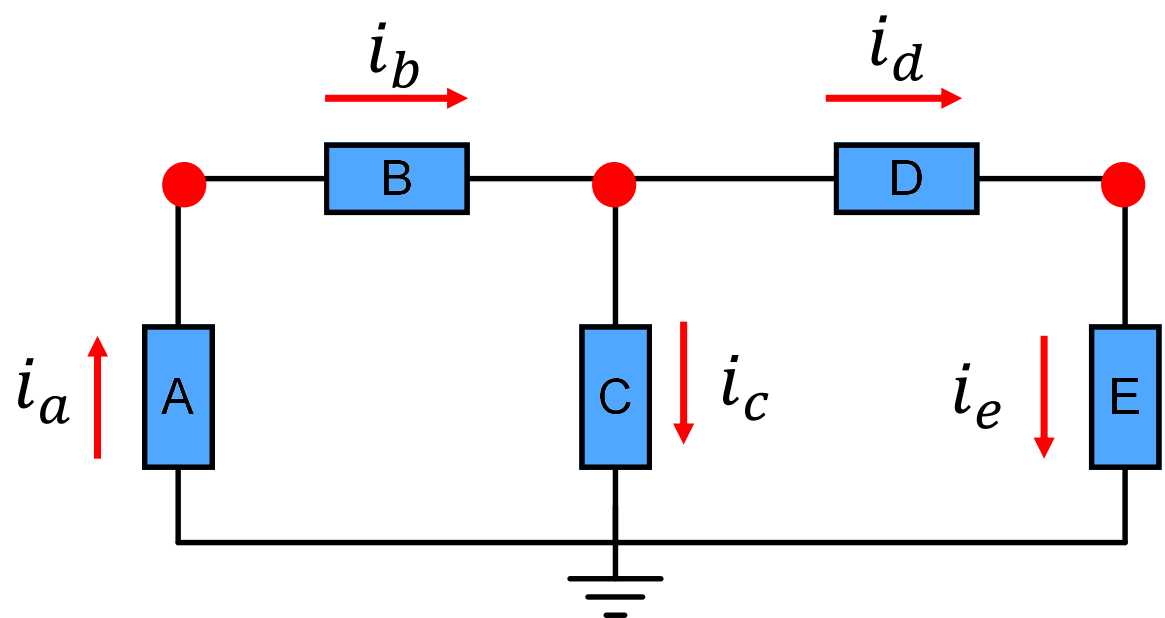
# Series Connected Elements

Two elements are connected in series if there is no other element connected to the node joining them



A, B are in series

The elements have the same current going through them


$$i_a = i_b$$

E and D are in series       $i_d = i_e$

B and C are not in series       $i_b \neq i_c$
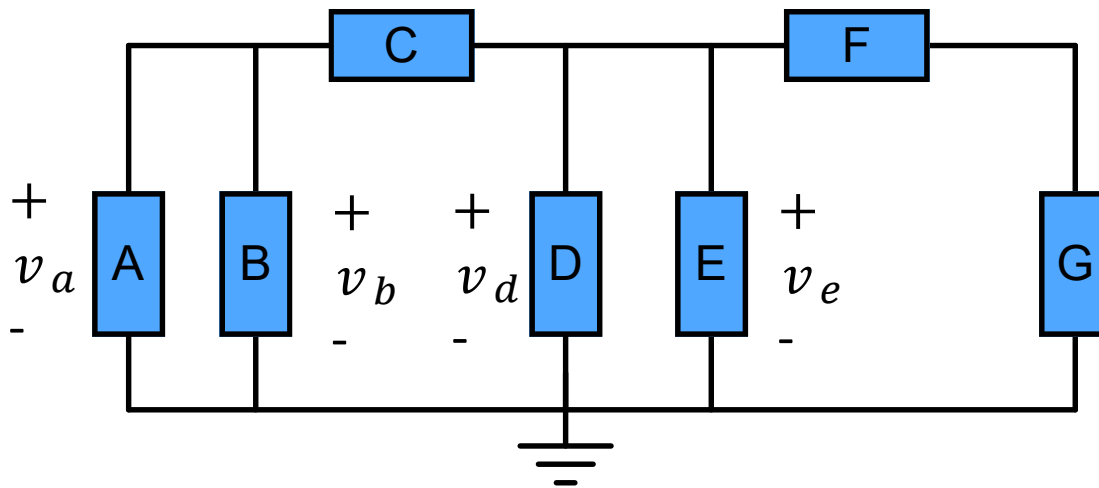
## Parallel Connected Circuit Elements

Two elements are connected in parallel if both ends of one element are connected directly to corresponding ends of the other



A and B are connected in parallel



D, E are connected in parallel

$$v_a = v_b$$

$$v_d = v_e$$


The voltage across parallel elements are equal (both magnitude and polarity)

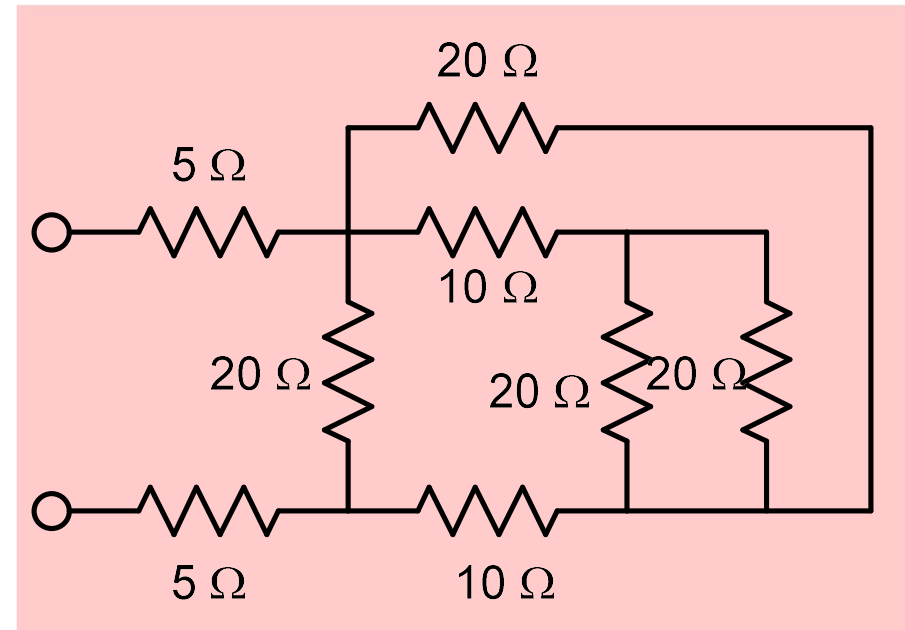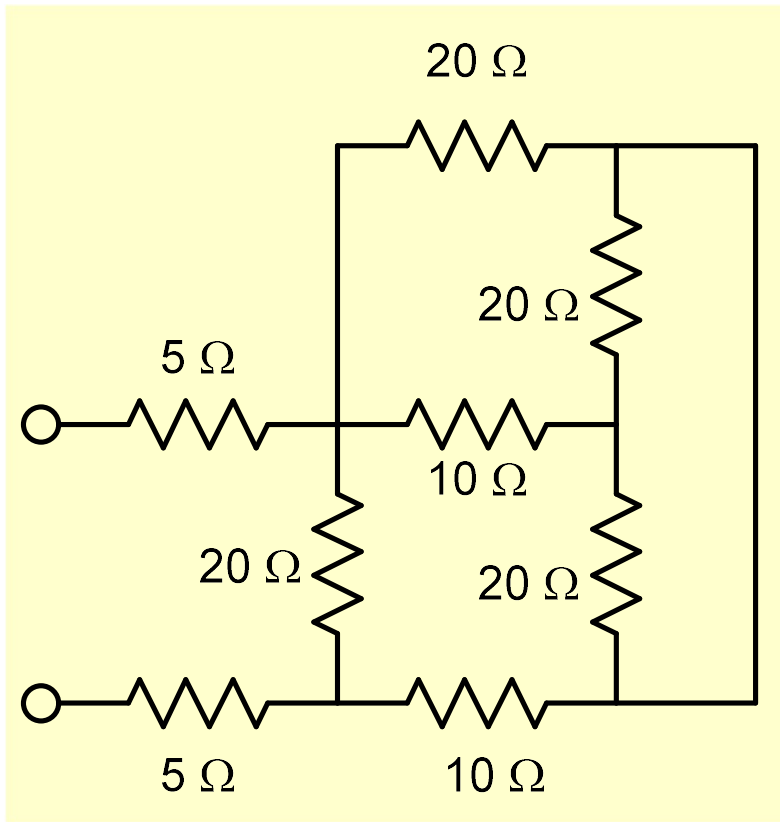Identification of series or parallel connected elements may not be straightforward



Re-drawing of circuit often helps in visualization of simplification opportunities

# Circuit Analysis

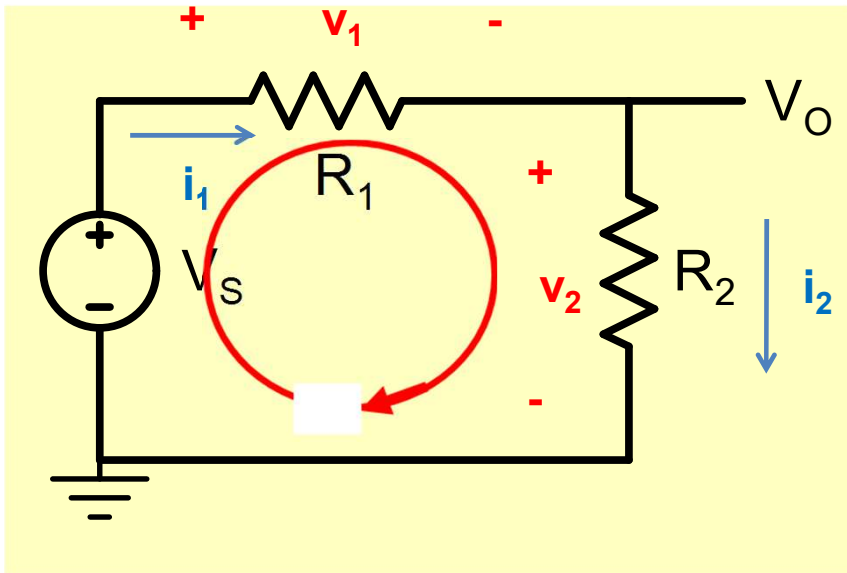

What is expression for current  $i_2$  ?

**Procedure:**

Use **Kirchhoff's voltage law (KVL)** and **Kirchhoff's Current law (KCL)** to transform the circuit into a set of equations whose solution gives the required voltage or current value

$$KVL : -V_S + v_1 + v_2 = 0 \Rightarrow V_S = v_1 + v_2$$

$$KCL : i_1 - i_2 = 0 \Rightarrow i_1 = i_2 = i$$

$$Model\ of\ Resistor : v_1 = i_1 \times R_1; v_2 = i_2 \times R_2$$

$$V_S = i \times (R_1 + R_2) \quad V_O = i \times R_2$$


$$V_O = V_S \times \frac{R_2}{R_2 + R_1}$$

# Circuit Analysis

Apply KVL and KCL

Use mathematical model of circuit elements

Solve the resulting system of Equations

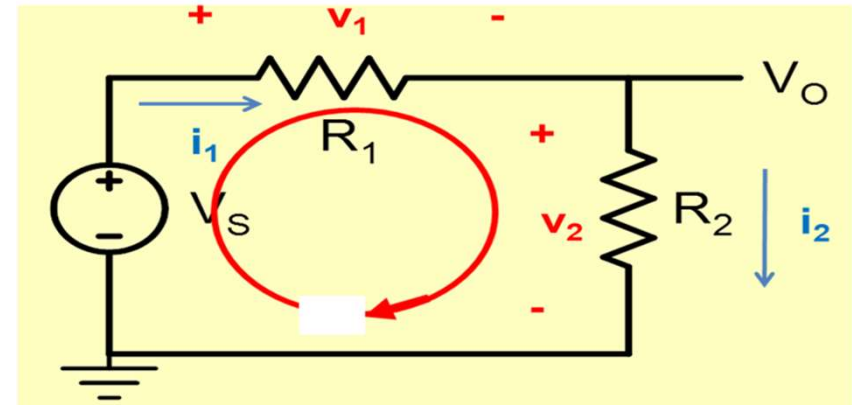

$$\text{KVL : } -V_S + v_1 + v_2 = 0 \Rightarrow V_S = v_1 + v_2$$

$$\text{KCL : } i_1 - i_2 = 0 \Rightarrow i_1 = i_2 = i$$

$$\text{Model of Resistor : } v_1 = i_1 \times R_1; v_2 = i_2 \times R_2$$

$$V_S = i \times (R_1 + R_2) \quad V_O = i \times R_2$$

$$V_O = V_S \times \frac{R_2}{R_2 + R_1}$$




## Circuit Analysis

Apply KVL and KCL

Use mathematical model of circuit elements

Solve the resulting system of Equations

Find  $I_x$  in the circuit shown:

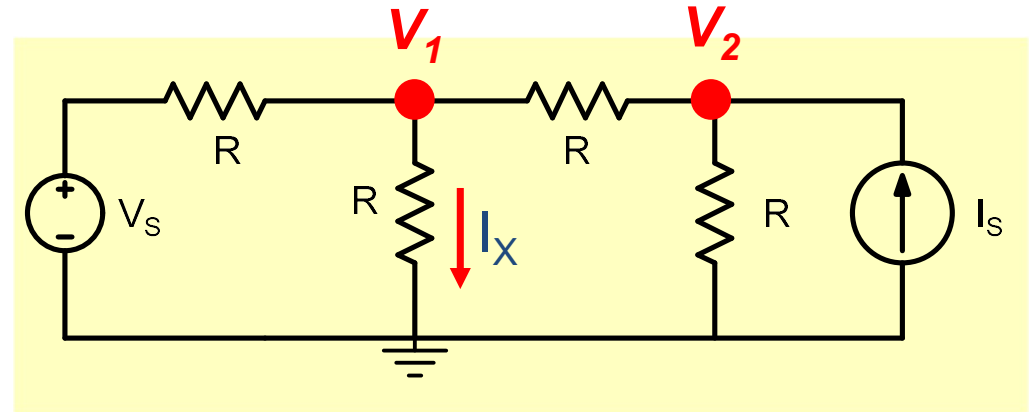


$$\frac{V_s - V_1}{R} - \frac{V_1}{R} + \frac{V_2 - V_1}{R} = 0$$

$$\frac{V_1 - V_2}{R} - \frac{V_1}{R} + I_s = 0$$


# Summary

## Circuit Analysis

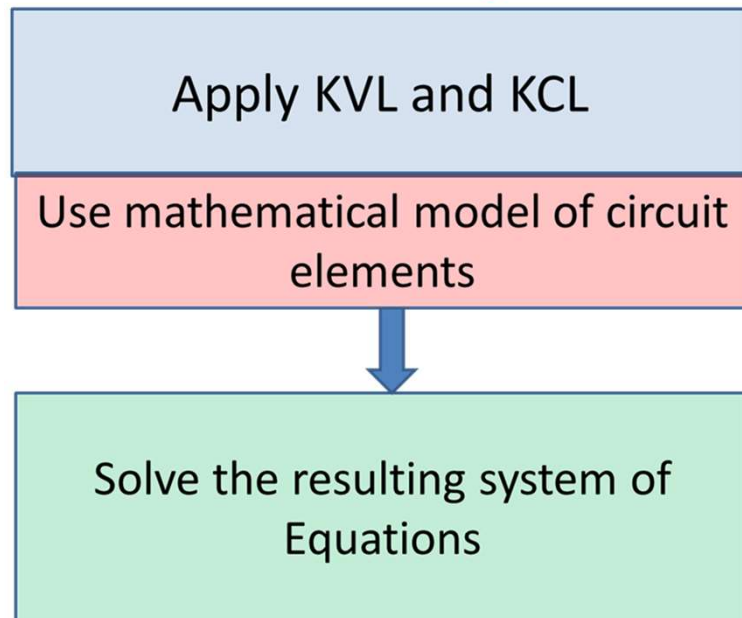

## Resistor

$$v(t) = R \times i(t)$$

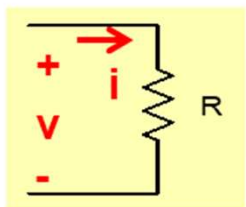

$$P = i^2 \times R$$

$$P = \frac{v^2}{R}$$

## Kirchhoff's Current Law (KCL)

Sum of currents entering a node is equal to sum of currents leaving a node

## Kirchhoff's Voltage Law (KVL)

The algebraic sum of the voltages equals zero for any closed path (loop) in an electrical circuit

Two elements are connected in series if there is no other element connected to the node joining them. **Same current flows**

Two elements are connected in parallel if both ends of one element are connected directly to corresponding ends of the other. **Same voltage**