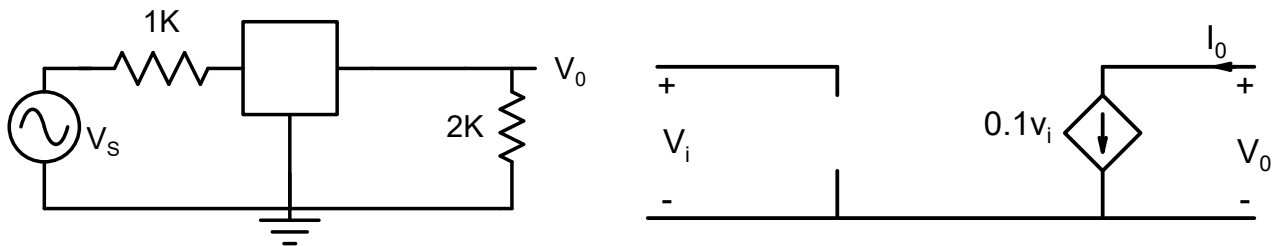


## ESC201T: Introduction to Electronics


### HW -8

Date: 04.11.2020



Q.1 Determine the voltage gain of the amplifier for the ideal transistor model shown below:



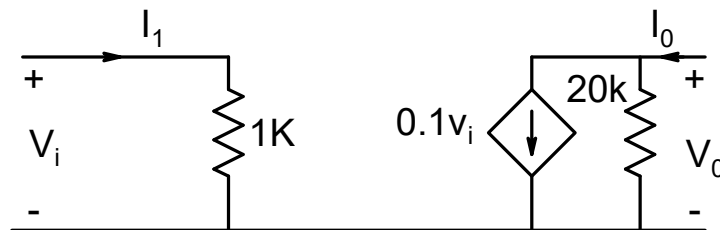
Q.2 Determine the voltage and power gain of the amplifier shown above for the transistor model shown below



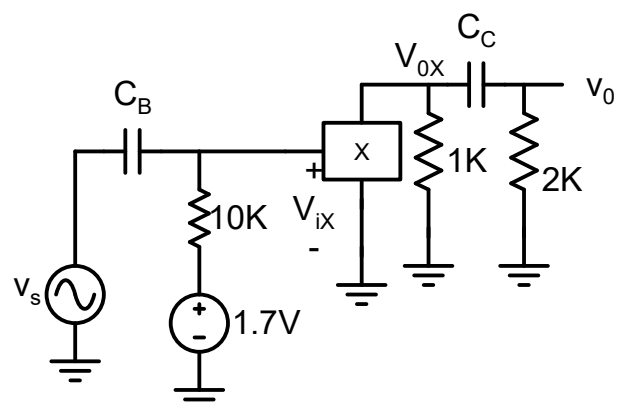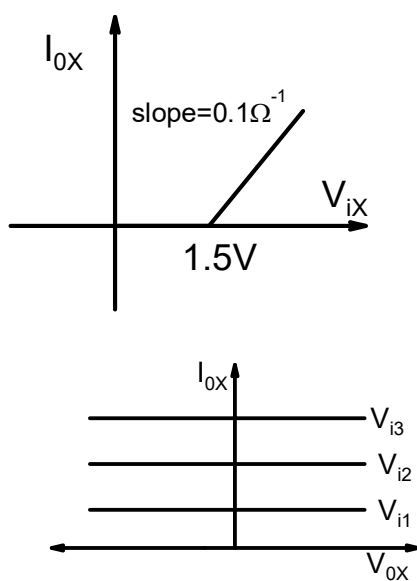Q.3 Carry out dc and ac analysis of the amplifier circuit shown below on the right for the device X characteristics shown below on the left. Sketch  $V_{ix}$ ,  $V_{ox}$  and  $v_o$  for  $v_s = 0.2\sin(\omega t)$ .



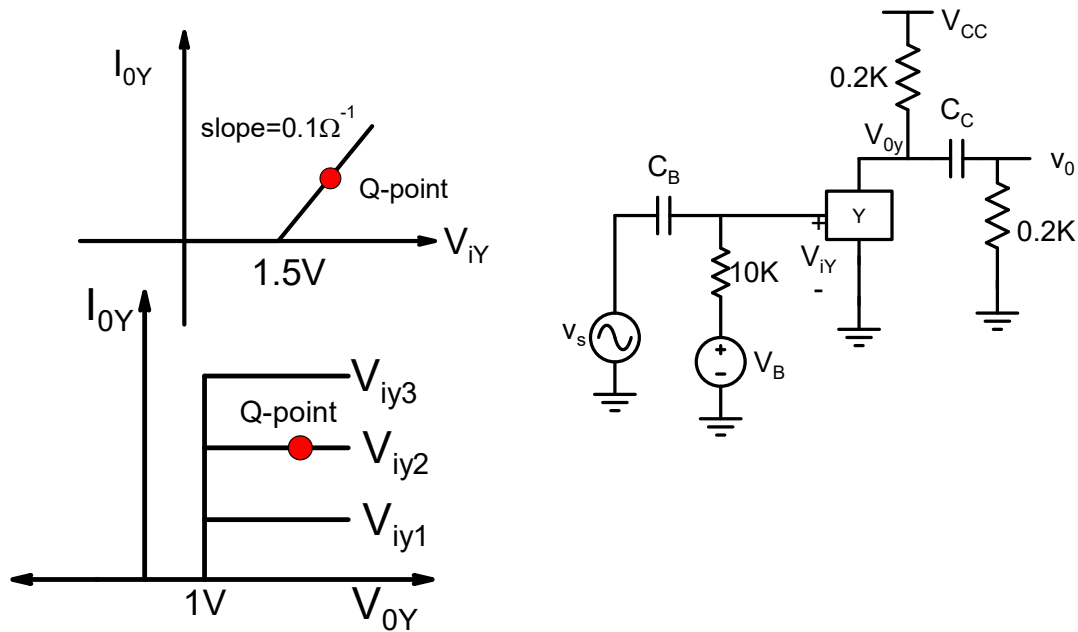**Q.4** Determine appropriate Q point (dc value of  $V_{iY}$  and  $V_{oY}$ ) so that the amplifier shown below on the right would properly amplify an input voltage of  $v_s = 0.2\sin(\omega t)$ . Determine minimum supply voltage  $V_{CC}$  for which the amplifier would work properly.



**Q.5** Carry out dc and ac analysis of the amplifier circuit shown below on the right to determine bias or Q- point (dc value of  $I_{oZ}$  and  $V_{oZ}$ ) and ac voltage gain.

