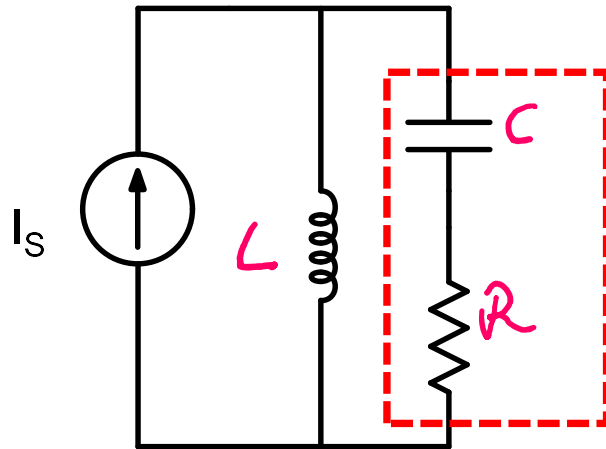


# **ESC201T : Introduction to Electronics**

## **HW6: Solution**

B. Mazhari  
Dept. of EE, IIT Kanpur

Q.1 Determine unity power factor frequencies for the circuit shown below




$$Z = R + \frac{1}{j\omega C} = \frac{1 + j\omega CR}{j\omega C}$$

$$Y = \frac{j\omega C}{1 + j\omega CR} = \frac{\omega^2 C^2 R}{1 + \omega^2 C^2 R^2} + \frac{j\omega C}{1 + \omega^2 C^2 R^2}$$

$$C_P = \frac{C}{1 + \omega^2 C^2 R^2}$$
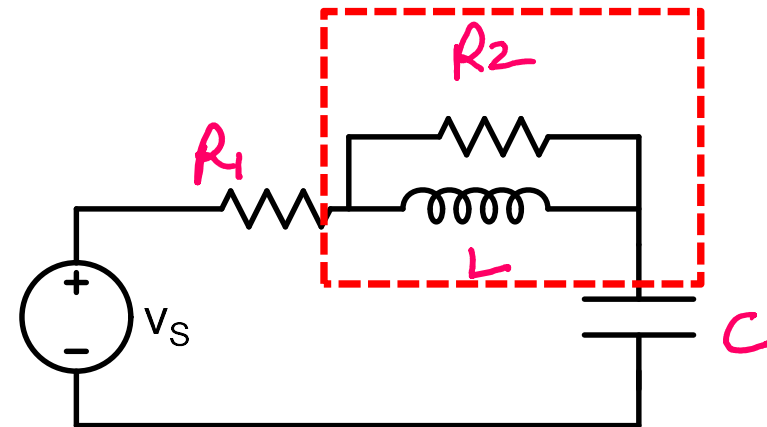
$$\omega_0 L = \frac{1}{\omega_0 C_P} \Rightarrow \text{zero power factor frequency}$$




$$Y = \frac{1}{R_2} + \frac{1}{j\omega L} = \frac{R_2 + j\omega L}{j\omega L R_2}$$

$$Z = \frac{j\omega L R_2}{R_2 + j\omega L} = R_S + j\omega L_S$$

$$L_S = L \times \frac{R_2^2}{R_2^2 + \omega^2 L^2}$$

$$\omega_0 L_S = \frac{1}{\omega_0 C}$$

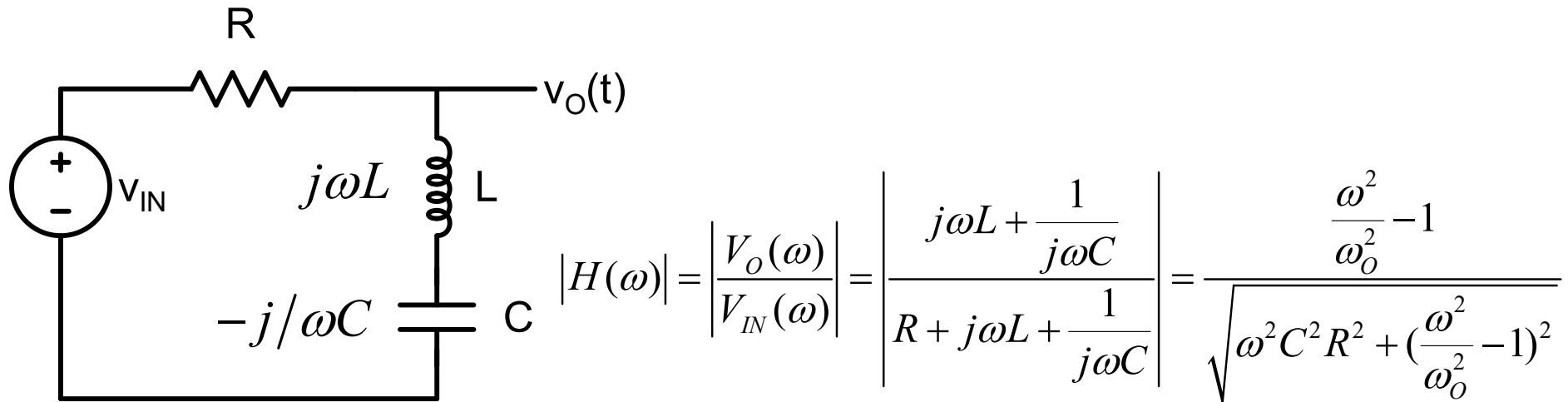Q.2 Design a bandstop (or a notch filter) to remove a 50Hz noise from a 60Hz signal using a series RLC circuit. Assume  $L = 1\text{H}$ . The attenuation of 60Hz signal should be less than 3dB



Assuming  $V_{IN} = 1\text{V}$  and noting that  $Q = 1/\omega_o CR$

$$|V_O(\omega)| = \frac{Q \times (\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega})}{\sqrt{1 + Q^2 (\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega})^2}}$$


For  $\omega = \omega_o$ ,  $V_O = 0$  so the signal is rejected

$$\omega_o = 2 \times \pi \times 50 = 314.16 \text{ rad/s} = \frac{1}{\sqrt{LC}} \Rightarrow C = 10.13 \mu\text{F}$$


Less than 3dB attenuation for 60Hz signal implies

$$|V_o(\omega_1)| = \frac{Q \times \left( \frac{\omega_1}{\omega_o} - \frac{\omega_o}{\omega_1} \right)}{\sqrt{1 + Q^2 \left( \frac{\omega_1}{\omega_o} - \frac{\omega_o}{\omega_1} \right)^2}} \geq \frac{1}{\sqrt{2}} \quad \omega_1 = 2\pi \times 60 \quad \Rightarrow Q \geq 2.7$$

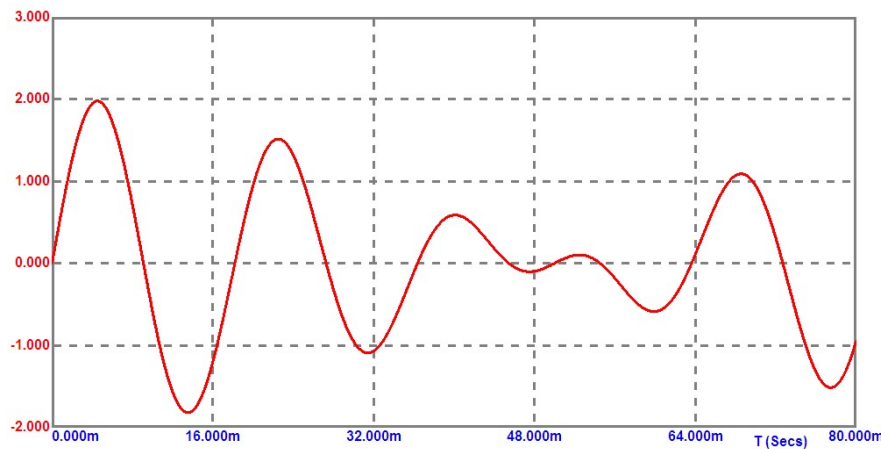Let  $Q = 5$ .  $Q = \frac{\omega_o L}{R} \Rightarrow R \cong 63\Omega$





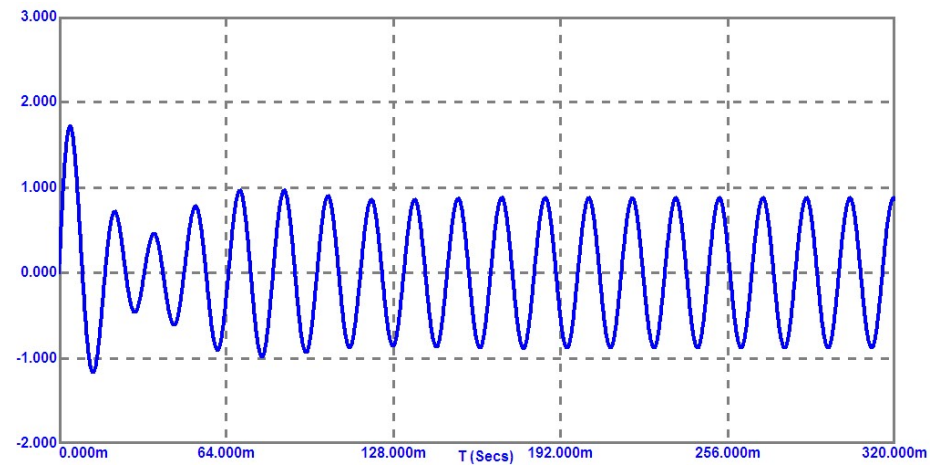
$$V_{in} = 1\sin(2\pi 50t) + 1\sin(2\pi 60t)$$



Output has only 60Hz component

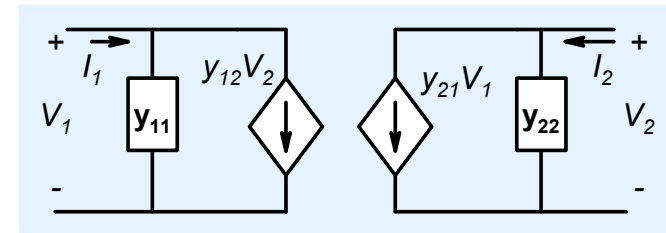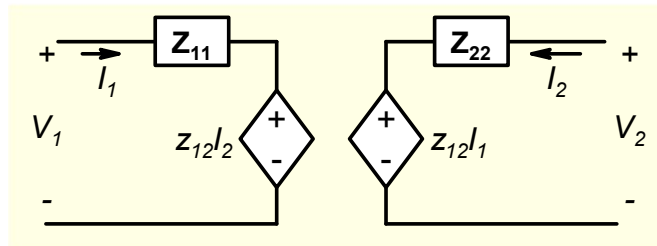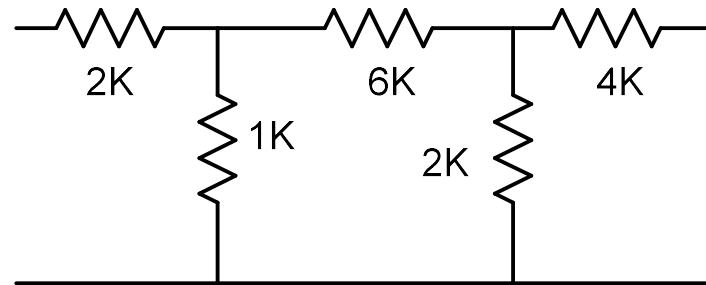Q.3 Determine Z, Y, H and G parameters for the circuit shown below



$$Z_{11} = \frac{V_1}{I_1} | I_2 = 0 \Rightarrow 2k + 1k \parallel 8k = 2.89k\Omega$$

$$Z_{12} = \frac{V_1}{I_2} | I_1 = 0 \Rightarrow \frac{2k}{9k} \times 1k = 0.22\Omega$$

$$Z_{21} = \frac{V_2}{I_1} | I_2 = 0 = Z_{12} = 0.22k\Omega$$




$$Z_{22} = \frac{V_2}{I_2} | I_1 = 0 \Rightarrow 4k + 2k \parallel 7k = 5.55 k\Omega$$

$$Y_{11} = \frac{I_1}{V_1} | V_2 = 0 \Rightarrow \frac{10^{-3}}{2 + 1 \parallel (6 + 2 \parallel 4)} = 3.4 \times 10^{-4} \Omega^{-1}$$

$$Y_{12} = \frac{I_1}{V_2} | V_1 = 0 \Rightarrow = 13.88 \times 10^{-6} \Omega^{-1}$$

$$Y_{21} = \frac{I_2}{V_1} | V_2 = 0 \Rightarrow = 13.88 \times 10^{-6} \Omega^{-1}$$

$$Y_{22} = \frac{I_2}{V_2} | V_1 = 0 \Rightarrow = 1.8 \times 10^{-4} \Omega^{-1}$$

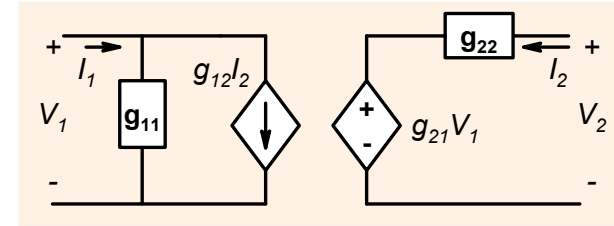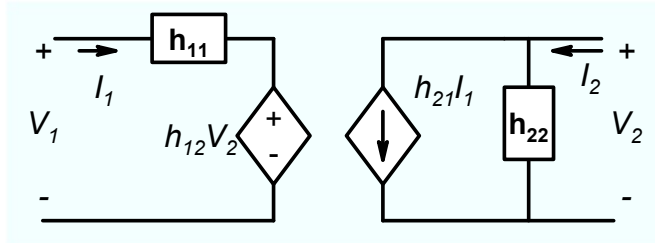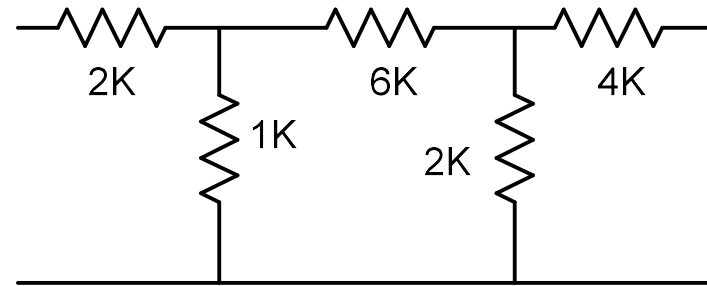

$$h_{11} = \frac{V_1}{I_1} | V_2 = 0 \Rightarrow = 2.88 \times 10^3 \Omega$$

$$h_{12} = \frac{V_1}{V_2} | I_1 = 0 \Rightarrow = 4 \times 10^{-2}$$

$$h_{21} = -h_{12} = -4 \times 10^{-2}$$

$$h_{22} = \frac{I_2}{V_2} | I_1 = 0 \Rightarrow = 1.8 \times 10^{-4} \Omega^{-1}$$


$$g_{11} = \frac{I_1}{V_1} | I_2 = 0 \Rightarrow = 3.46 \times 10^{-4} \Omega^{-1}$$

$$g_{12} = \frac{I_1}{I_2} | V_1 = 0 \Rightarrow = -0.077$$

$$g_{21} = -g_{12} = 0.077$$

$$g_{22} = \frac{V_2}{I_2} | V_1 = 0 \Rightarrow = 5.53 k \Omega$$

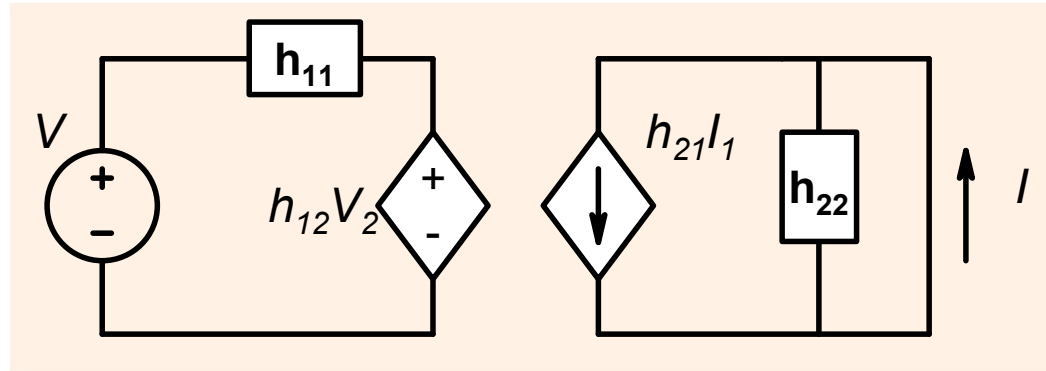
Q.4 Stating from the definition of a reciprocal network, show that  $h_{21} = -h_{12}$



$$I = h_{21}I_1$$

$$I_1 = \frac{V}{h_{11}}$$



$$I = \frac{h_{21}}{h_{11}}V$$

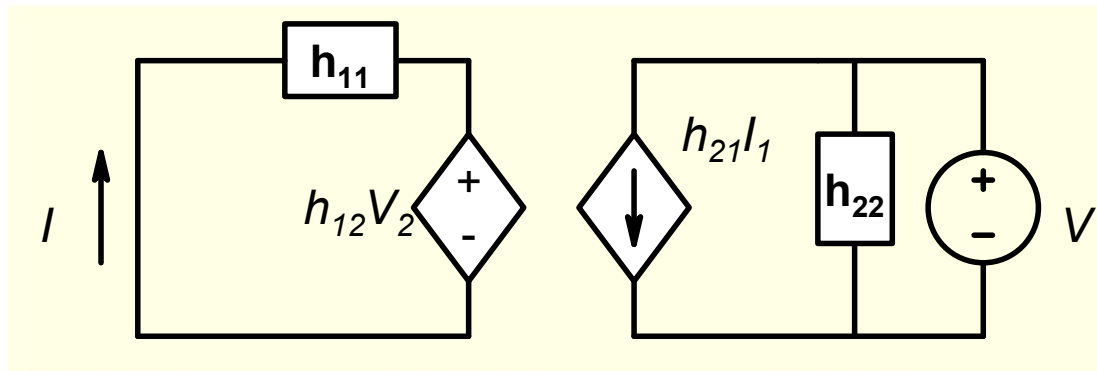

$$I = -\frac{h_{12}V}{h_{11}}$$

$$\Rightarrow h_{12} = -h_{21}$$

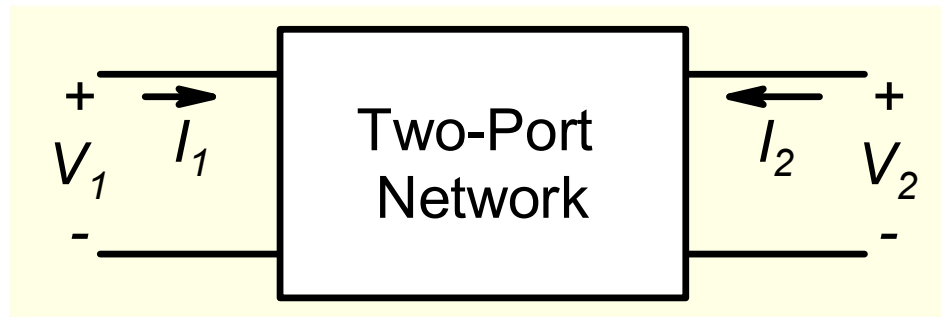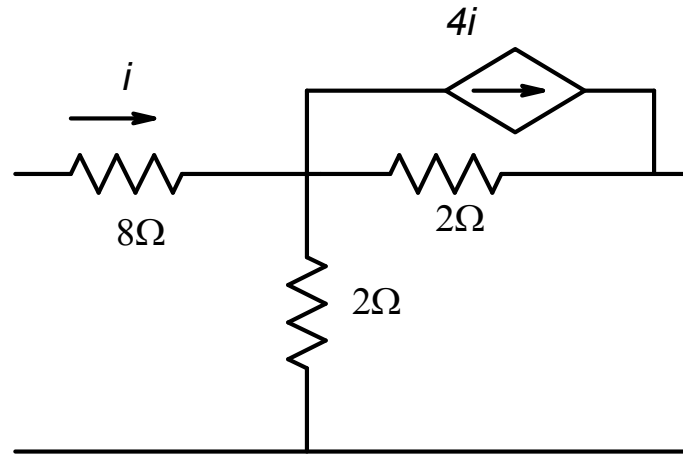Q.5 Determine the Y parameters for the circuit shown below




$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$



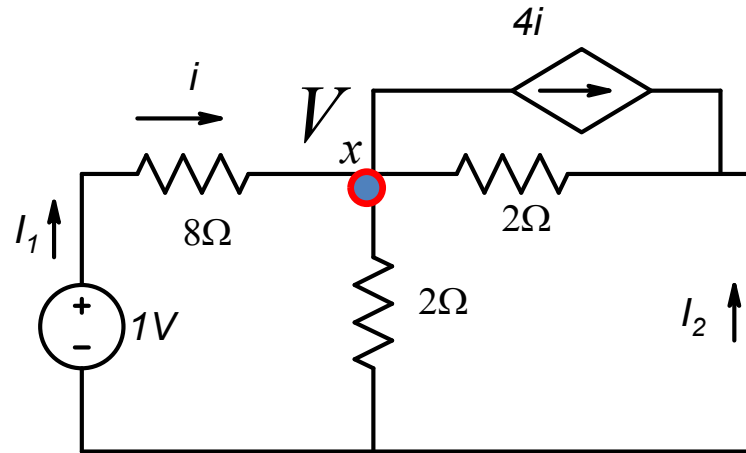

Nodal analysis gives: 
$$\frac{V_x - 1}{8} + \frac{V_x}{2} + \frac{V_x}{2} + 4i = 0 \quad i = \frac{1 - V_x}{8}$$


$$V_x = -\frac{3}{5}V \quad i = 0.2A$$

$$i_2 = -4i - \frac{V_x}{2} = -0.5A$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = 0.2\Omega^{-1} \quad y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = -0.5\Omega^{-1}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

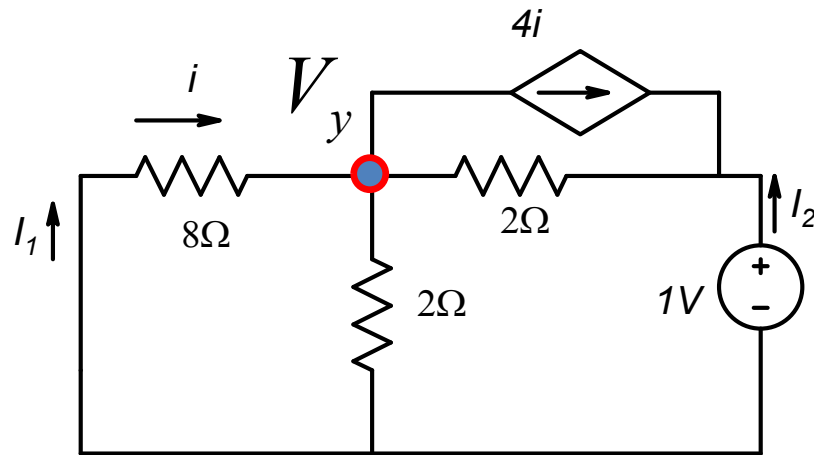




Nodal analysis gives:

$$\frac{V_y - 1}{2} + \frac{V_y}{2} + \frac{V_y}{8} + 4i = 0 \quad i = \frac{0 - V_y}{8}$$

$$V_y = \frac{4}{5} V \quad i = -0.1 A$$

$$i_2 = -4i + \frac{1 - V_y}{2} = 0.5 A$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = 0.5 \Omega^{-1} \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -0.1 \Omega^{-1}$$

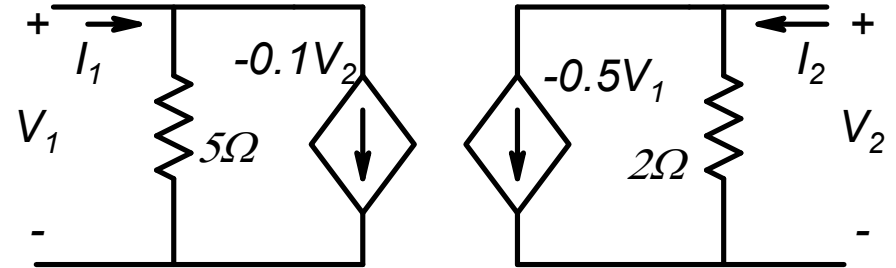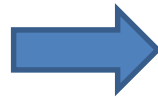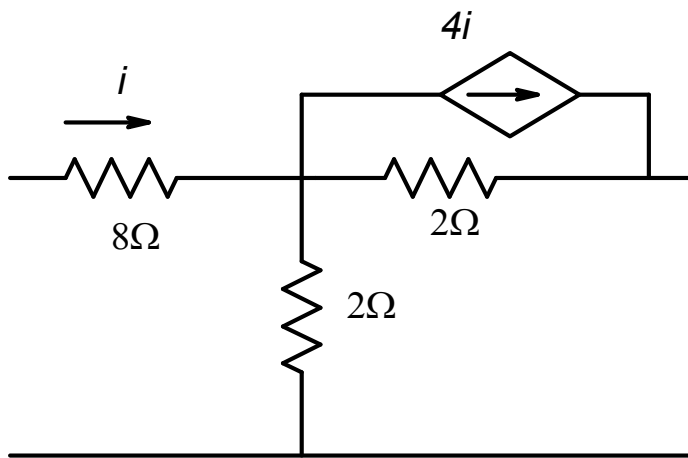




$$y_{11} = 0.2\Omega^{-1}$$

$$y_{22} = 0.5\Omega^{-1}$$

$$y_{21} = -0.5\Omega^{-1}$$

$$y_{12} = -0.1\Omega^{-1}$$

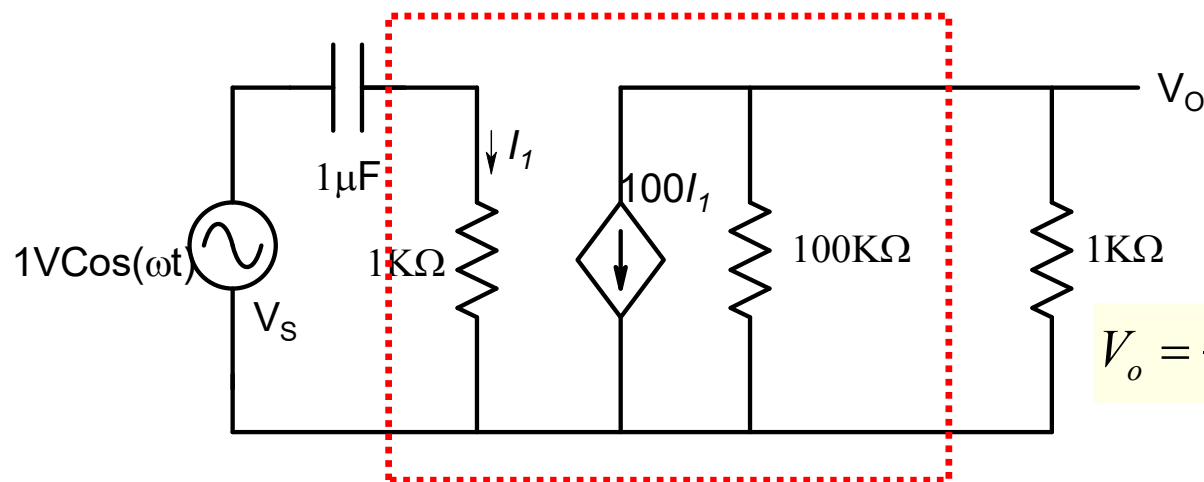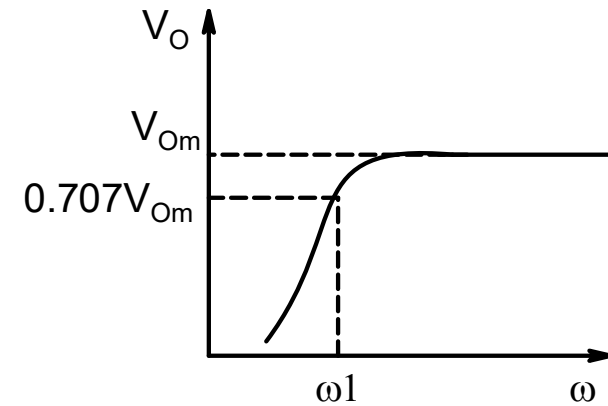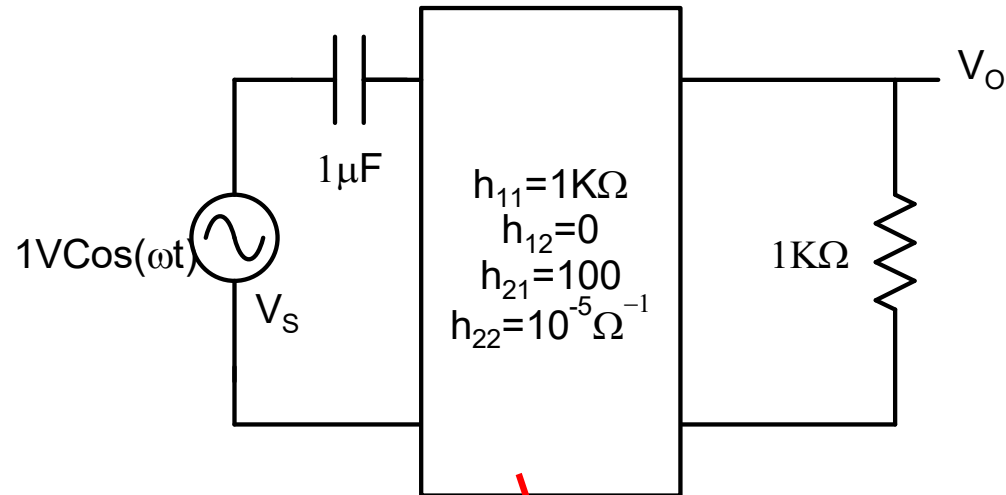Q.6 For the circuit shown below on the left, the variation of magnitude of output voltage with frequency is shown on the right. Determine the voltage  $V_{om}$  and frequency  $\omega_1$ .



$$I_1 = \frac{1 \angle 0}{10^3 - \frac{j}{\omega C}}$$

$$V_o = -100 I_1 \times 10^5 \parallel 10^3 = -9.9 \times 10^4 I_1$$

$$V_o = -\frac{9.9 \times 10^4}{10^3 - \frac{j}{\omega C}}$$


$$|V_o| = \frac{9.9 \times 10^4 \omega C}{\sqrt{10^6 \omega^2 C^2 + 1}}$$

One notes that for  $\omega = 0$ , output voltage is zero and increases as frequency increases.



For very large  $\omega$ ,  $V_o$  can be approximated as

$$|V_{om}| \cong \frac{9.9 \times 10^4 \omega C}{10^3 \omega C} \cong 99$$
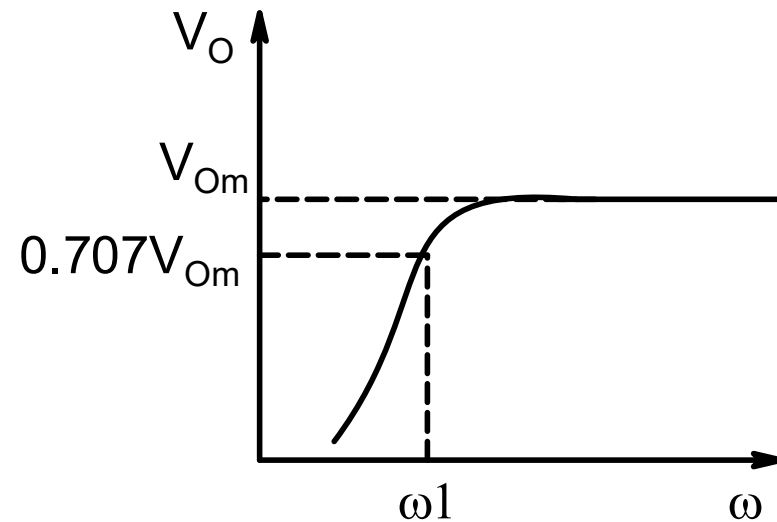
$$\frac{99}{\sqrt{2}} = \frac{9.9 \times 10^4 \omega_1 C}{\sqrt{10^6 \omega_1^2 C^2 + 1}} \Rightarrow \omega_1 = 10^3 \text{ rad/s}$$



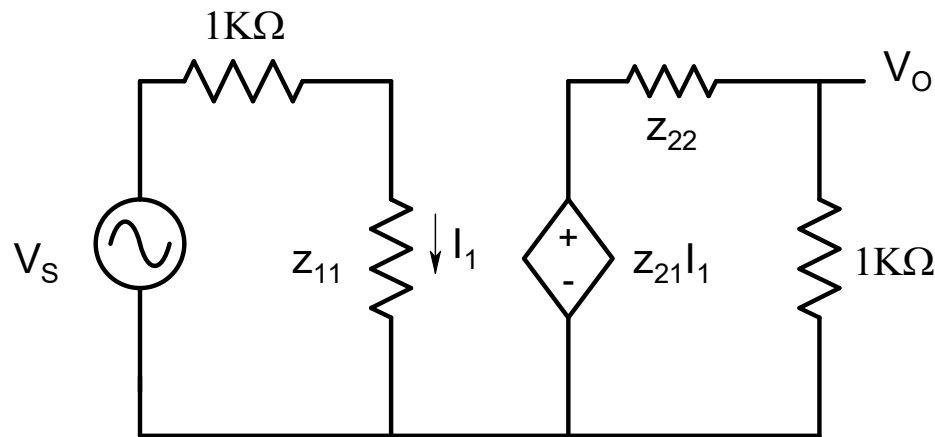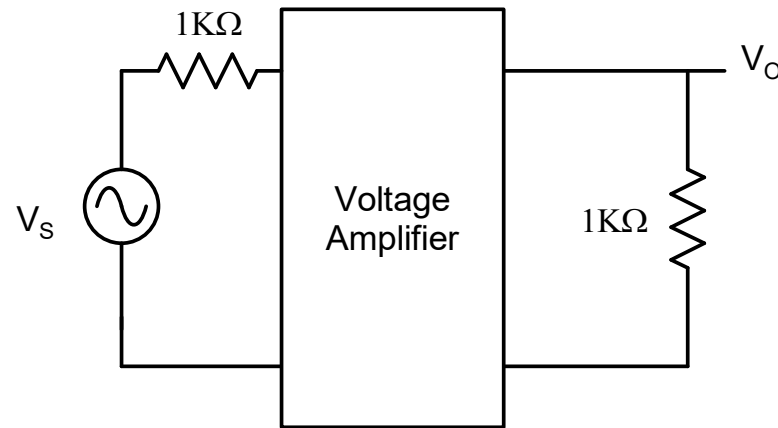Q.7 The two port network shown below is a voltage amplifier. One can design the amplifier for different values of  $z$  parameters under the constraint  $\frac{z_{21}}{z_{22}} = 100$  and  $z_{12} = 0$ . Determine suitable values for the  $z$  parameters such that voltage gain  $\frac{V_O}{V_S}$  is maximized.





$$I_1 = \frac{V_S}{z_{11} + 1K} \quad V_O = \frac{1K}{z_{22} + 1K} z_{21} I_1$$

$$\frac{V_O}{V_S} = \frac{1K}{z_{22} + 1K} \times z_{21} \times \frac{1}{z_{11} + 1K}$$

$$\frac{V_O}{V_S} = \frac{z_{22}}{z_{22} + 1K} \times \frac{1K}{z_{11} + 1K} \times 10^2$$

$$\Rightarrow z_{22} \gg 1K; z_{11} \ll 1K \quad \text{Choose } z_{22} = 10K, z_{11} = 0.1K \rightarrow z_{21} = 10^6$$

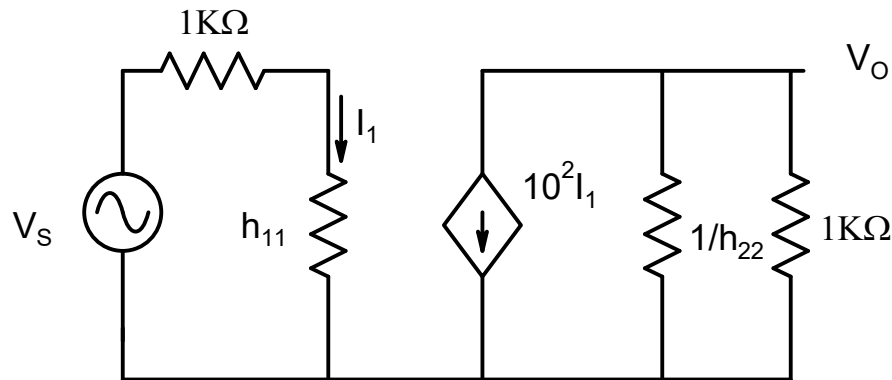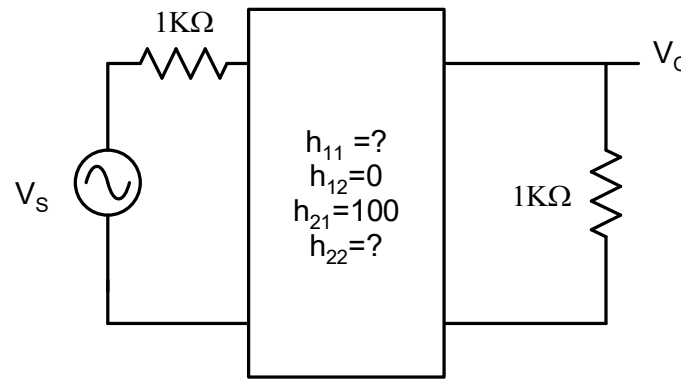Q.8 Determine the values of  $h_{11}$  and  $h_{22}$  for the amplifier shown below such power delivered to the load is maximized



To maximize power we need to maximize current in the 1K load resistor

$$I_L = 10^2 \frac{V_s}{h_{11} + 1K} \times \frac{1}{1 + h_{22} \times 10^3}$$

$$\Rightarrow h_{11} \ll 1K ; h_{22} 10^3 \ll 1$$

Choose  $h_{11} = 0.1K$ ,  $h_{22} = 10^{-4}$