



# ESC201T : Introduction to Electronics





## Lecture 15: Frequency Response

B. Mazhari  
Dept. of EE, IIT Kanpur





Time domain vs. Frequency domain analysis

Signal

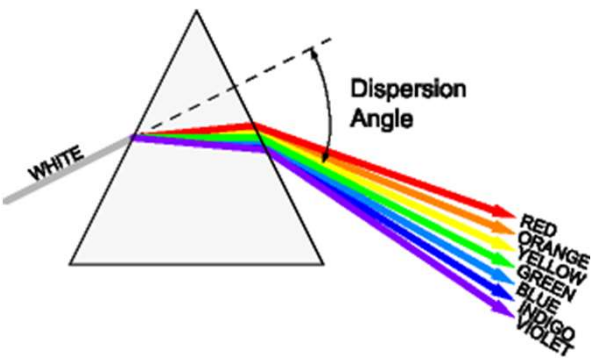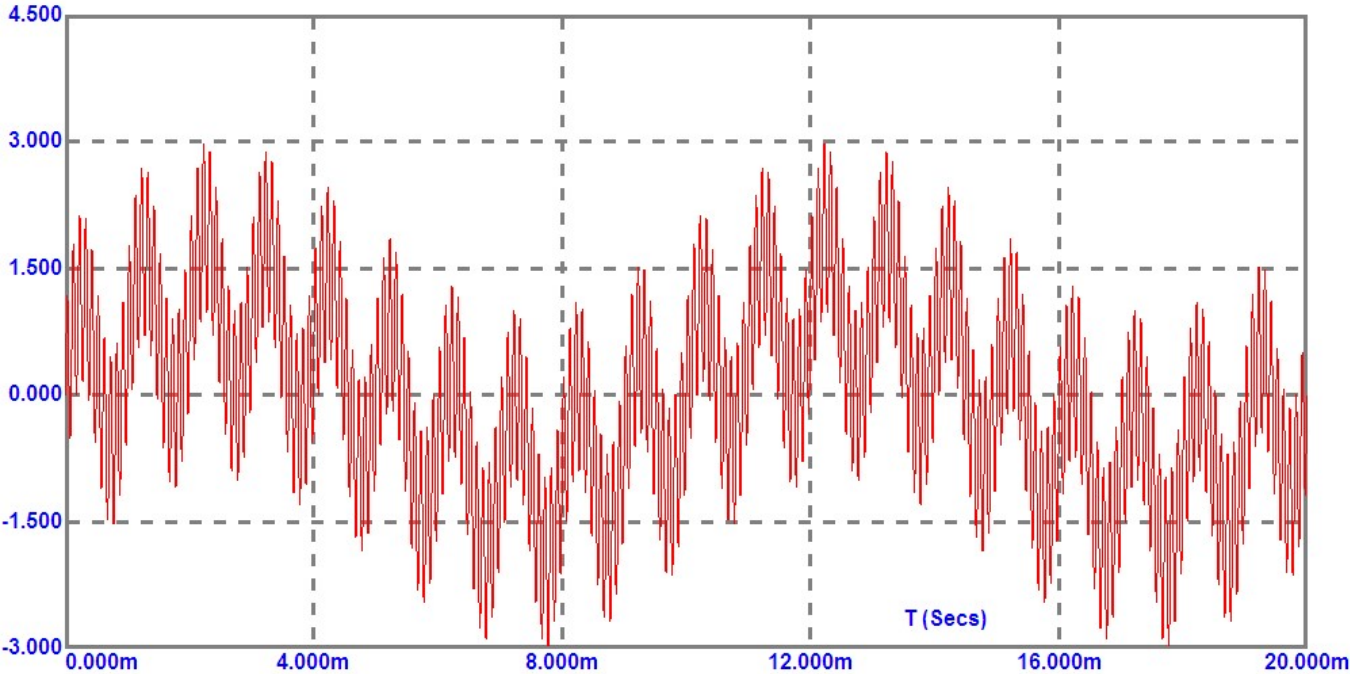

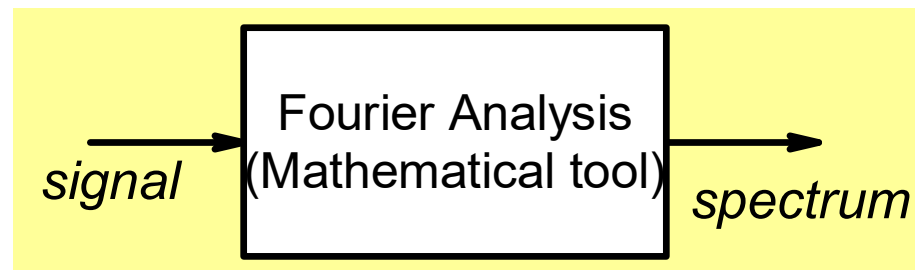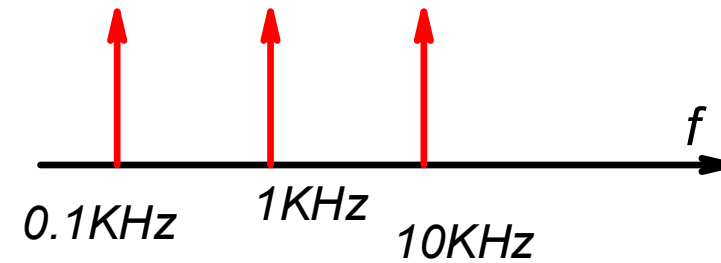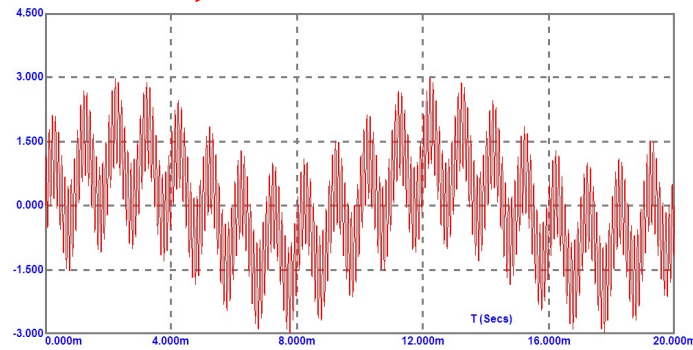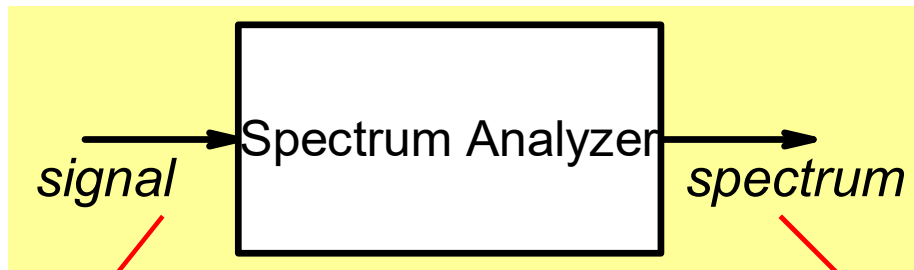



# Speech signal

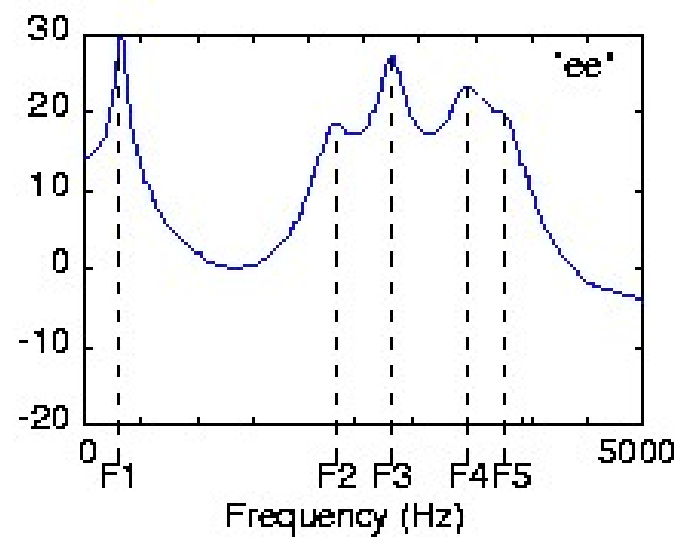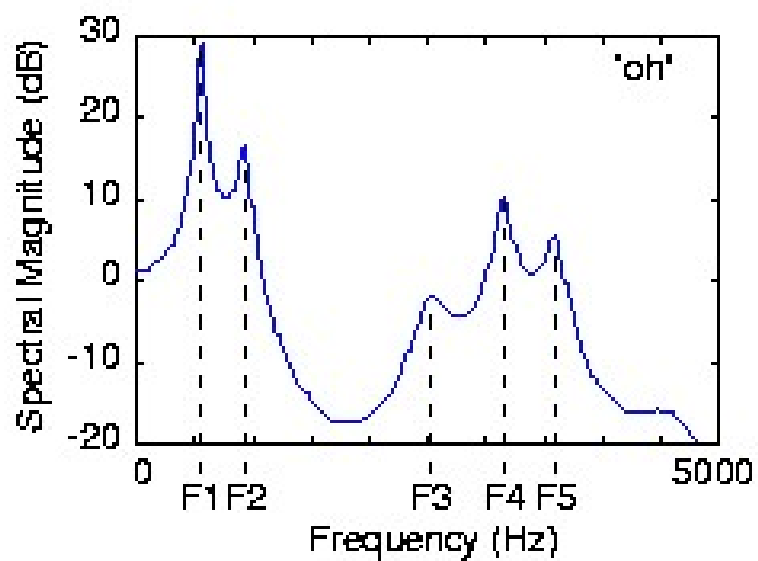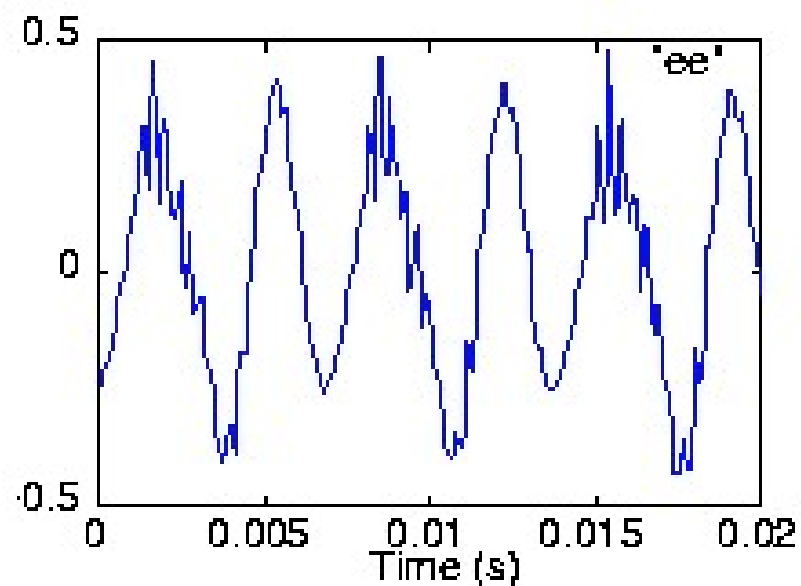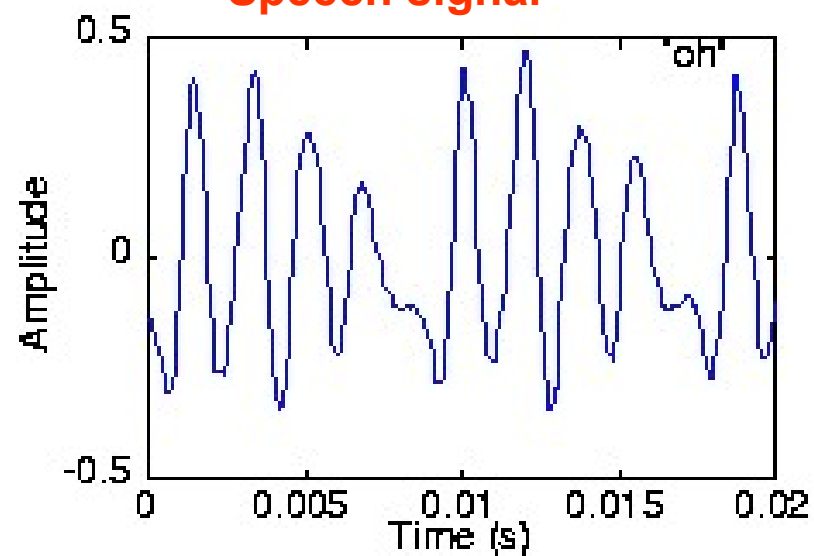



Don Johnson

# System

What does this circuit do ?

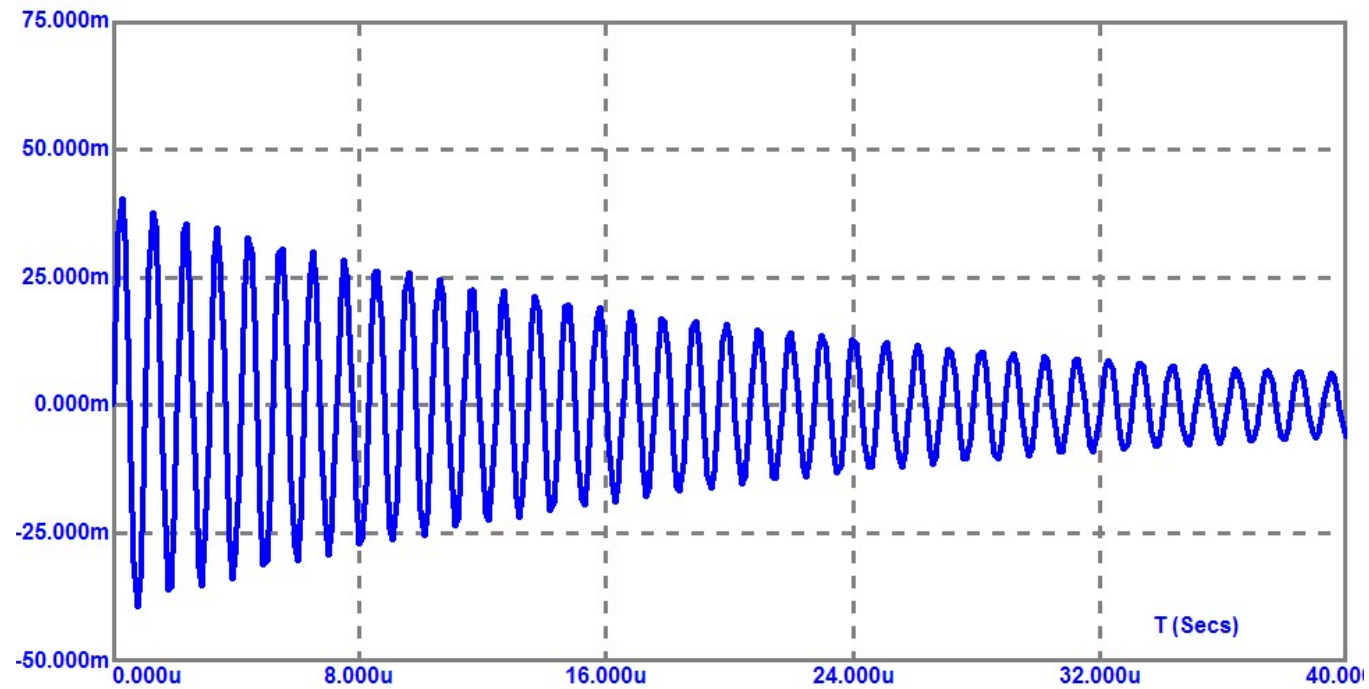
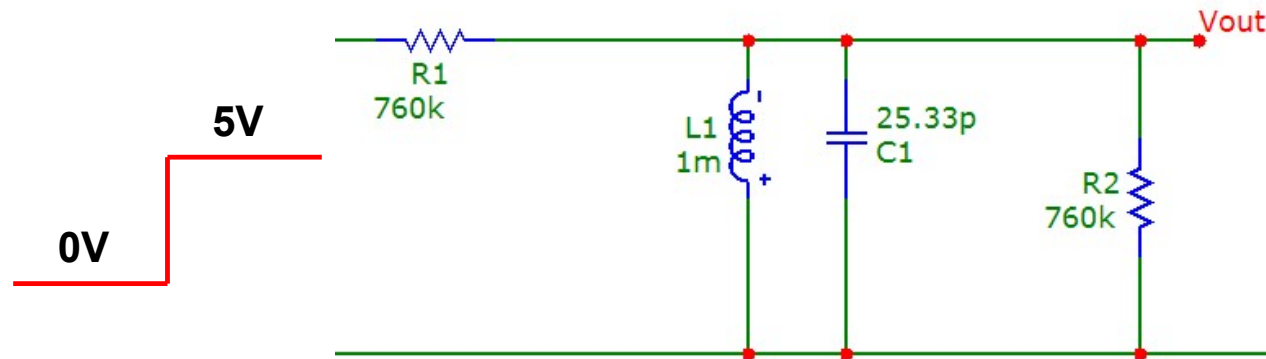


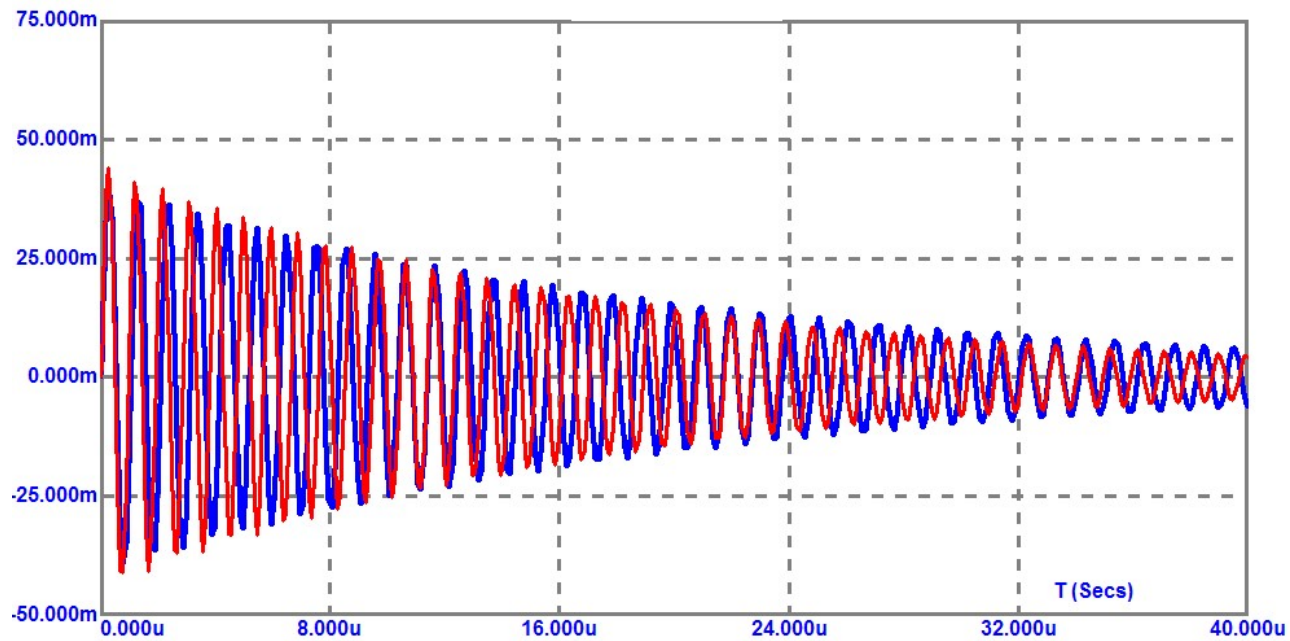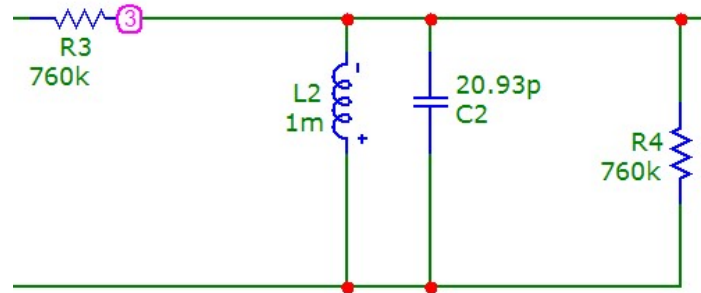Suppose the capacitor is reduced to  $\sim 21\text{pF}$ .




It is hard to find out what impact the change in capacitor has on circuit behavior


## Frequency domain analysis

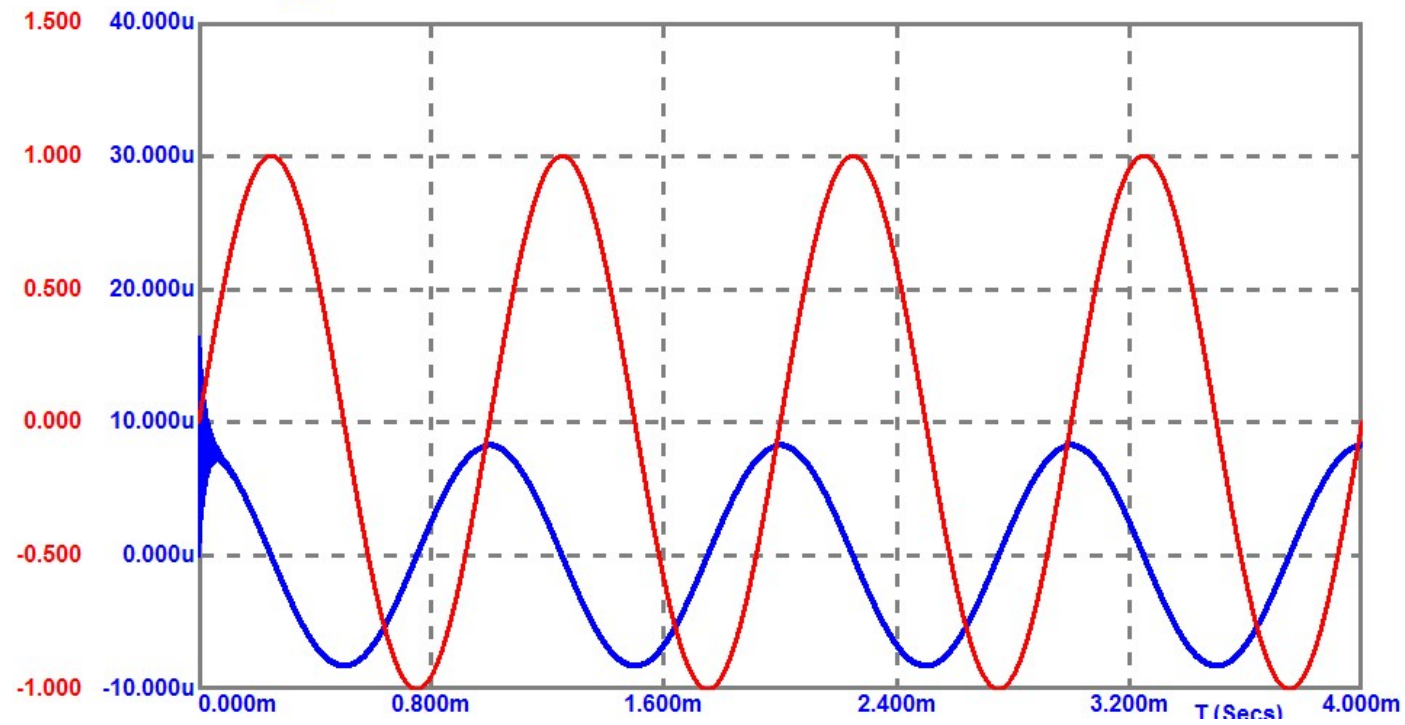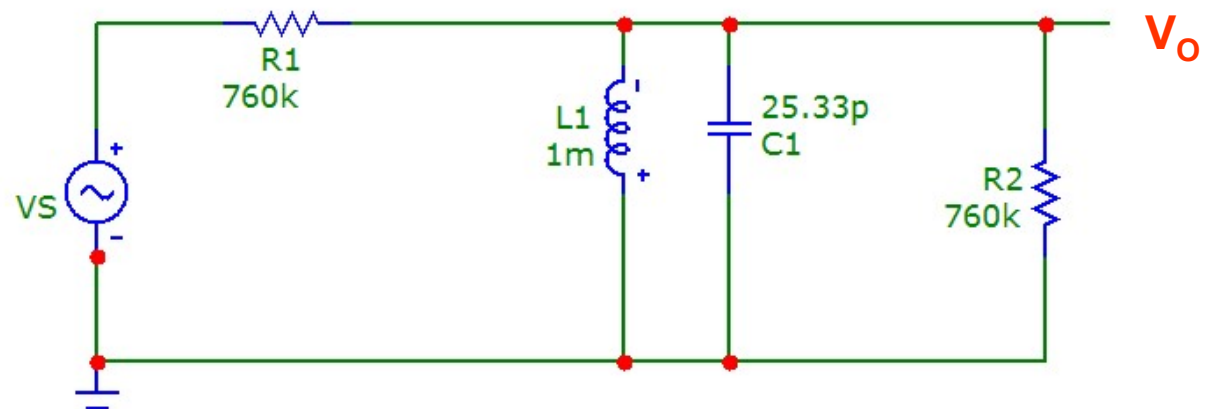

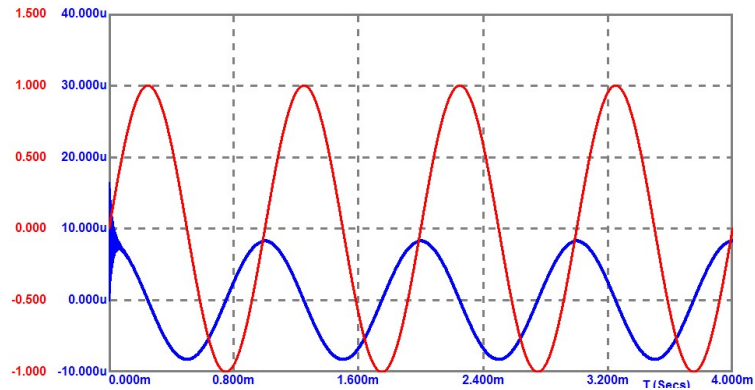
Measure response at many different frequencies for a constant input amplitude




$f=1\text{KHz}$

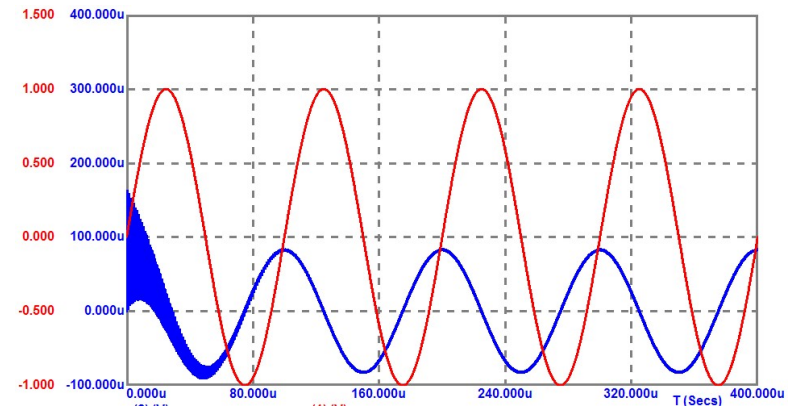

$f=10\text{KHz}$

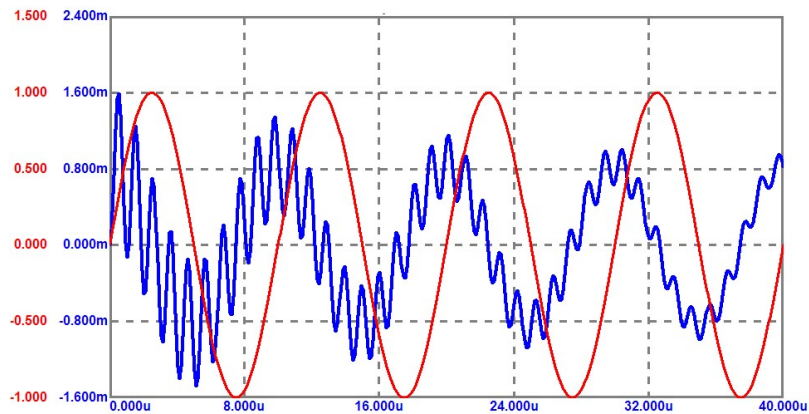



$f=100\text{KHz}$

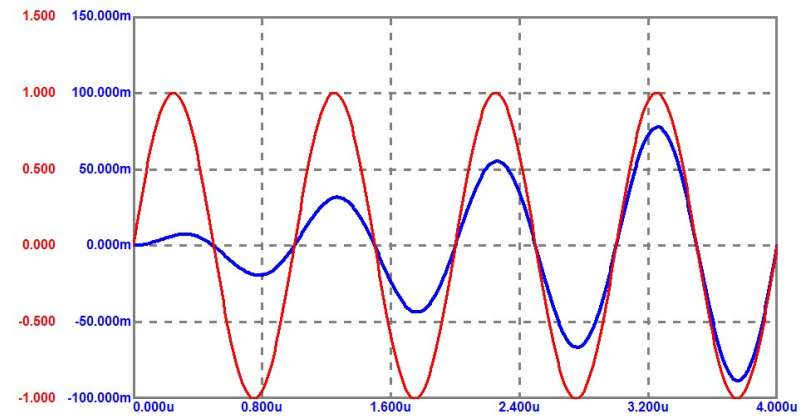

$f=1000\text{KHz}$





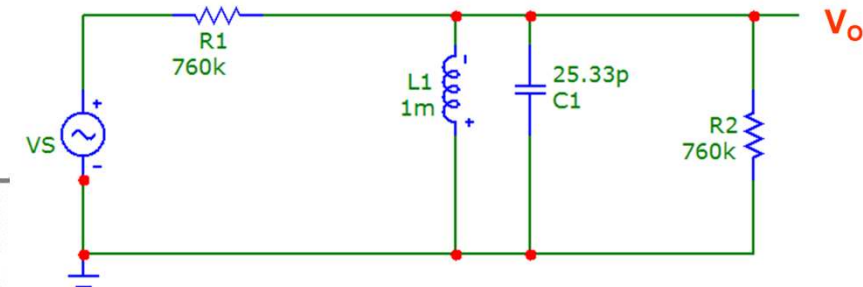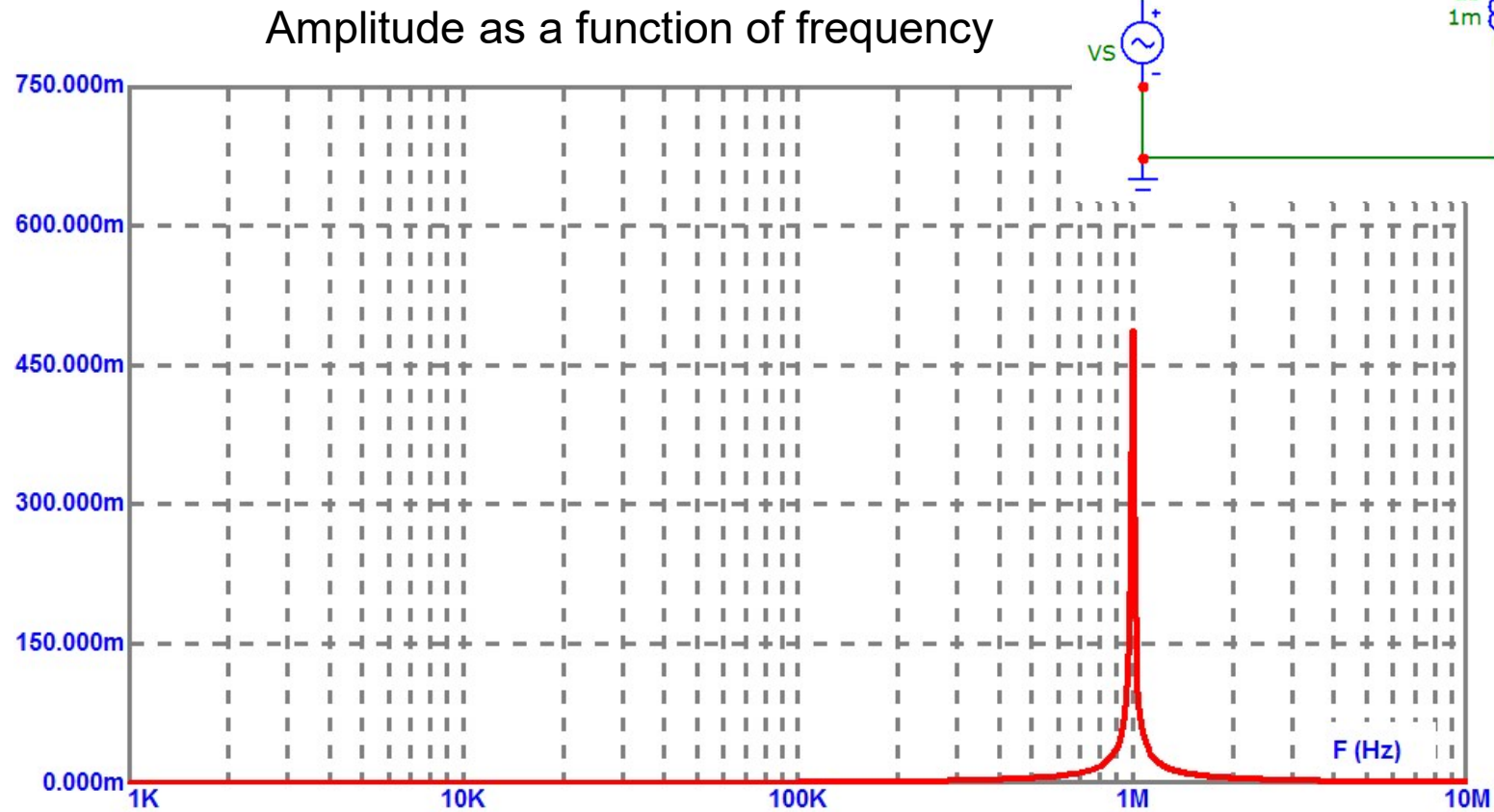Plot the amplitude and phase as a function of frequency





One can clearly see the frequency selective (often called a filter) nature of the circuit


## Phase as a function of frequency

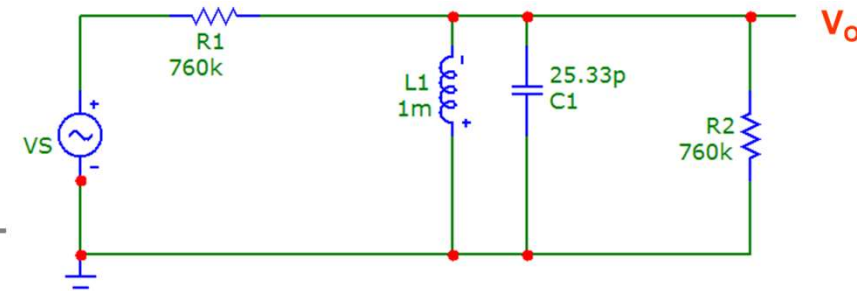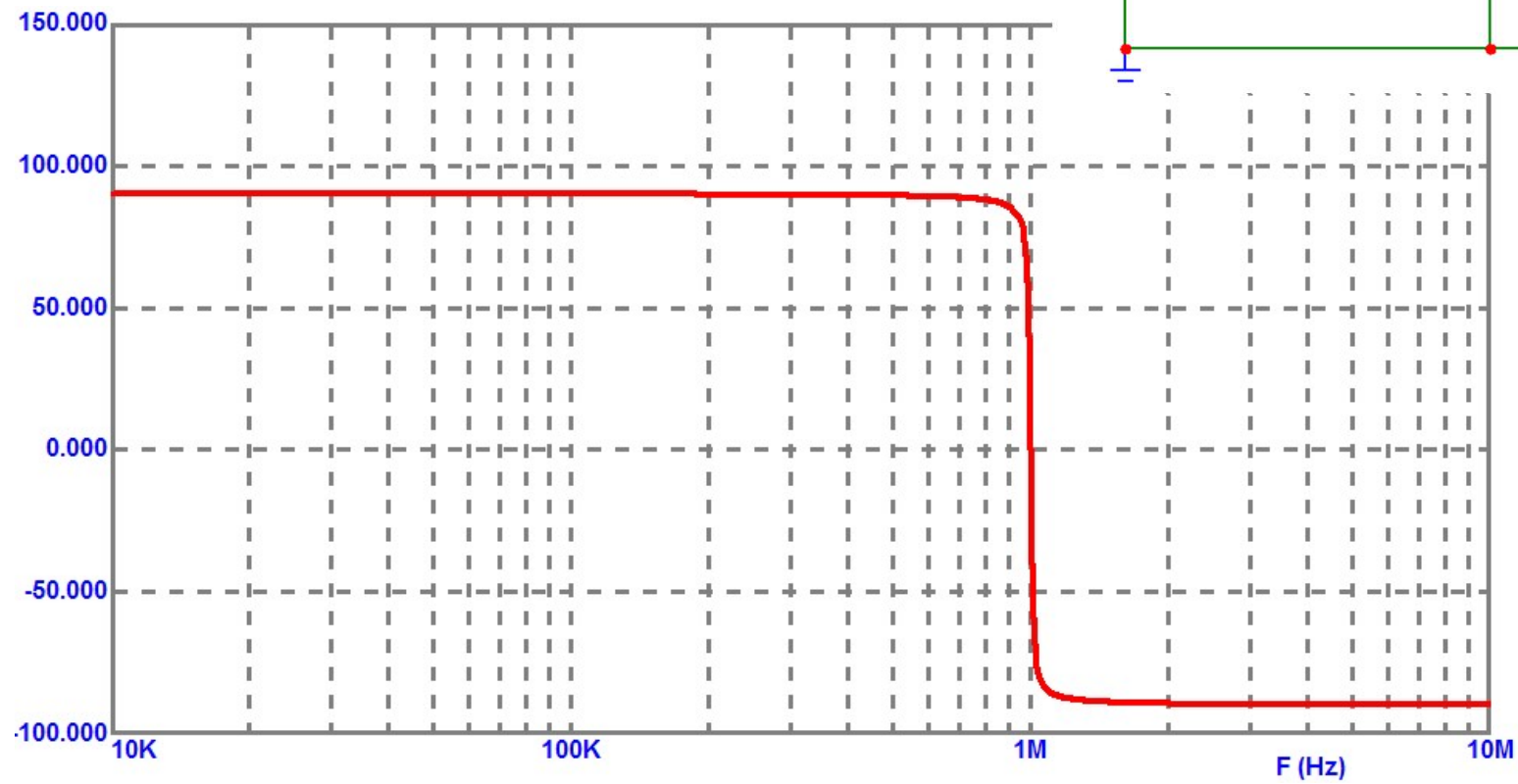

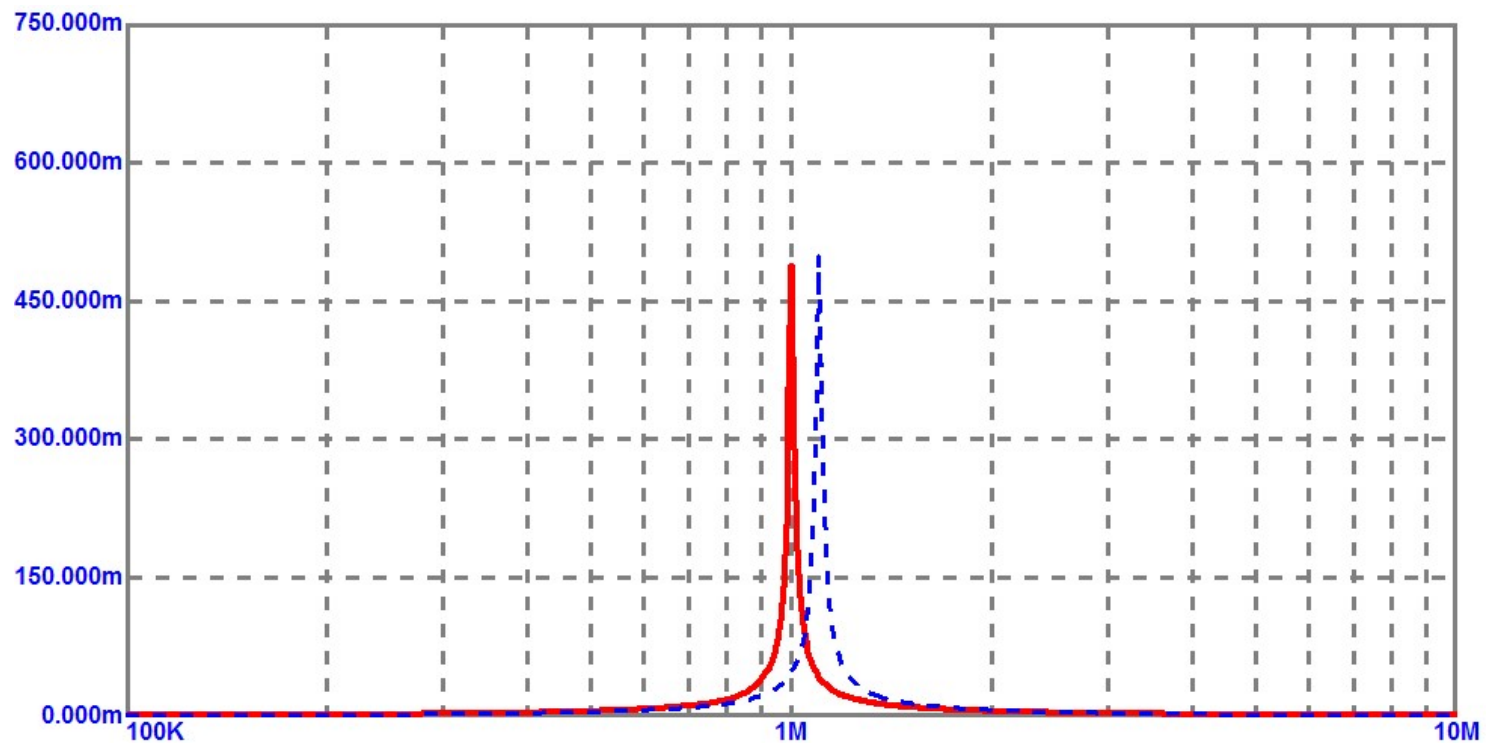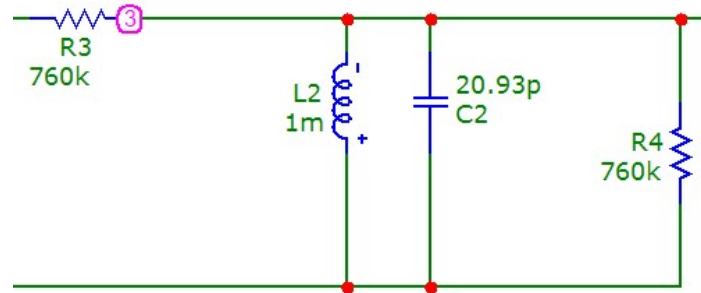
Suppose the capacitor is reduced to  $\sim 21\text{pF}$ .



## Absorption Spectroscopy

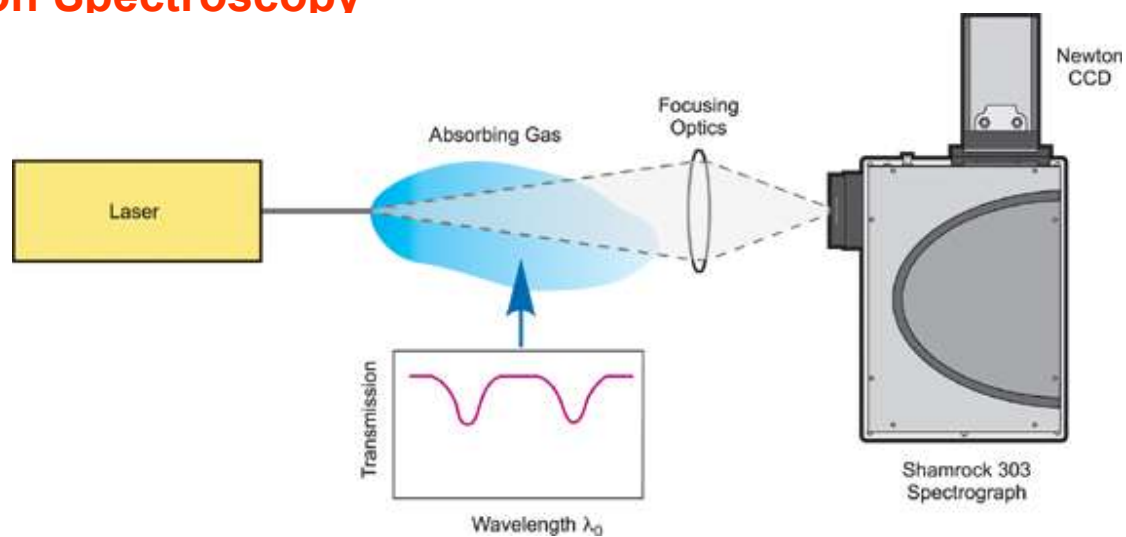

## Vibration-Rotation Spectrum of HCl

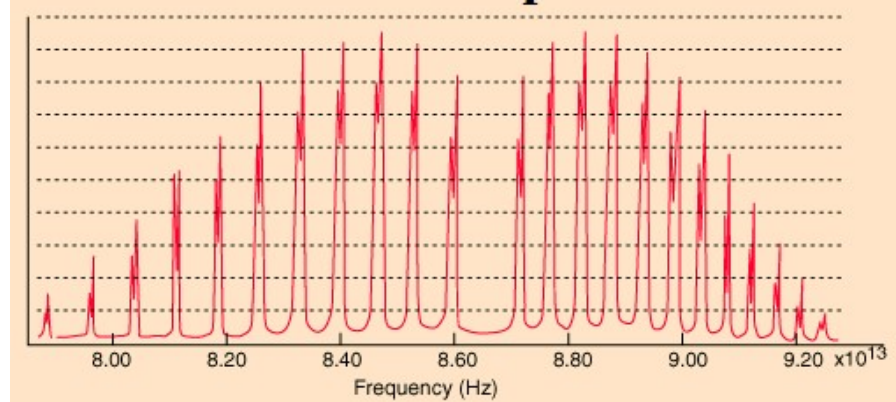


Bond length can be estimated from the spectra

***Analysis of signals and systems in frequency domain often provides useful insight into their behavior.***
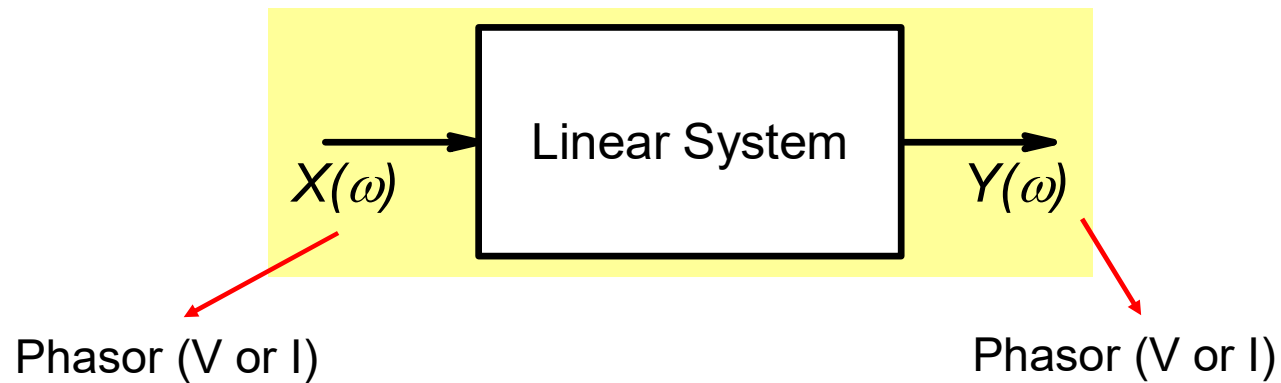
## Frequency domain analysis



Transfer function is a useful tool for finding the frequency response of a system



$$\text{Transfer Function: } H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

Transfer function has a magnitude and a phase

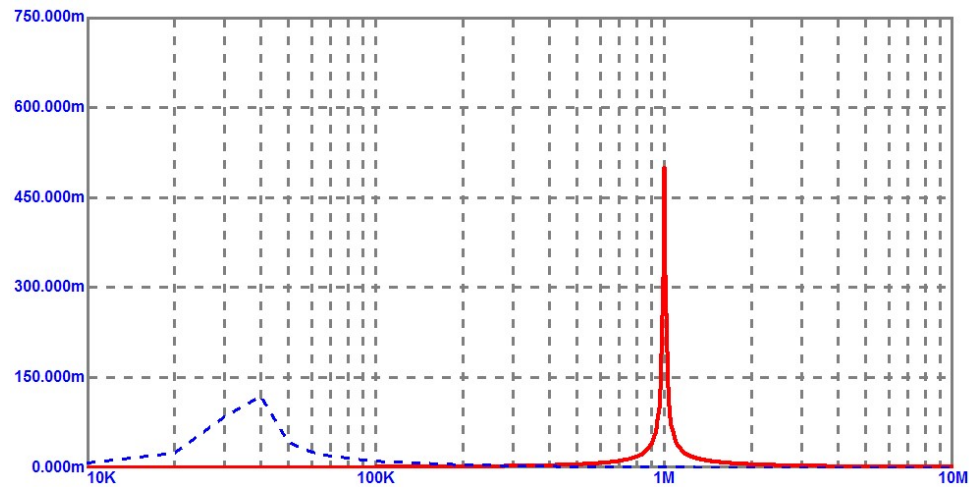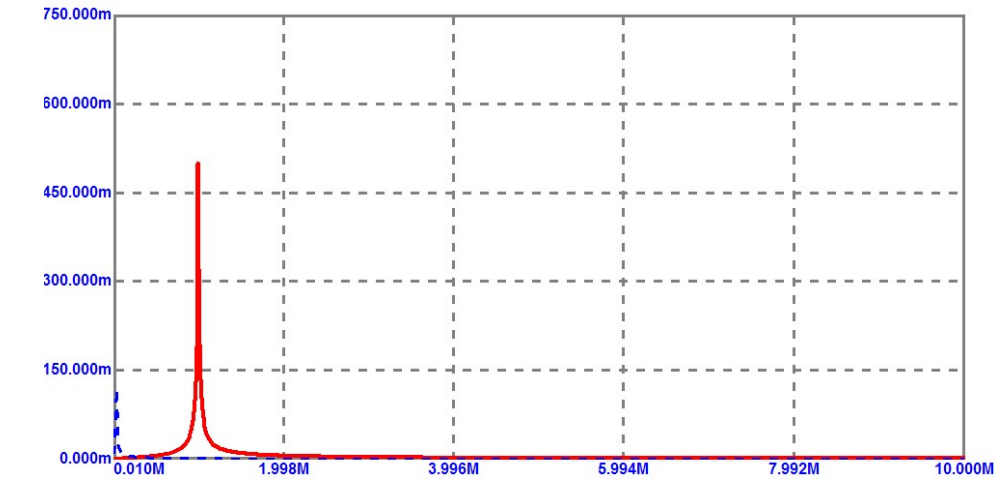Because of the wide dynamic range of frequency, plotting frequency on log axis is often more revealing !



**Insight is a strong function of  
information representation**

The magnitude of transfer function is often specified in **decibels**

$$G_{dB} = 10 \log_{10} \left( \frac{P_2}{P_1} \right)$$

Because power is proportional to  $V^2$  or  $I^2$ , voltage gain and current gain in decibels is specified as

$$G_{dB} = 20 \log_{10} \left( \frac{V_2}{V_1} \right)$$

$$G_{dB} = 20 \log_{10} \left( \frac{I_2}{I_1} \right)$$

Decibel scale is more convenient for our perception of hearing


Change in Sound Pressure Level	Apparent Change in Loudness
3 dB	Just noticeable
5 dB	Clearly noticeable
10 dB	Twice or half as loud
20 dB	4 times or 1/4 as loud




## Decibel Scale

G	$20\text{Log}_{10}(G)$
1000	60
100	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
0.5	-6
0.1	-20
0.01	-40

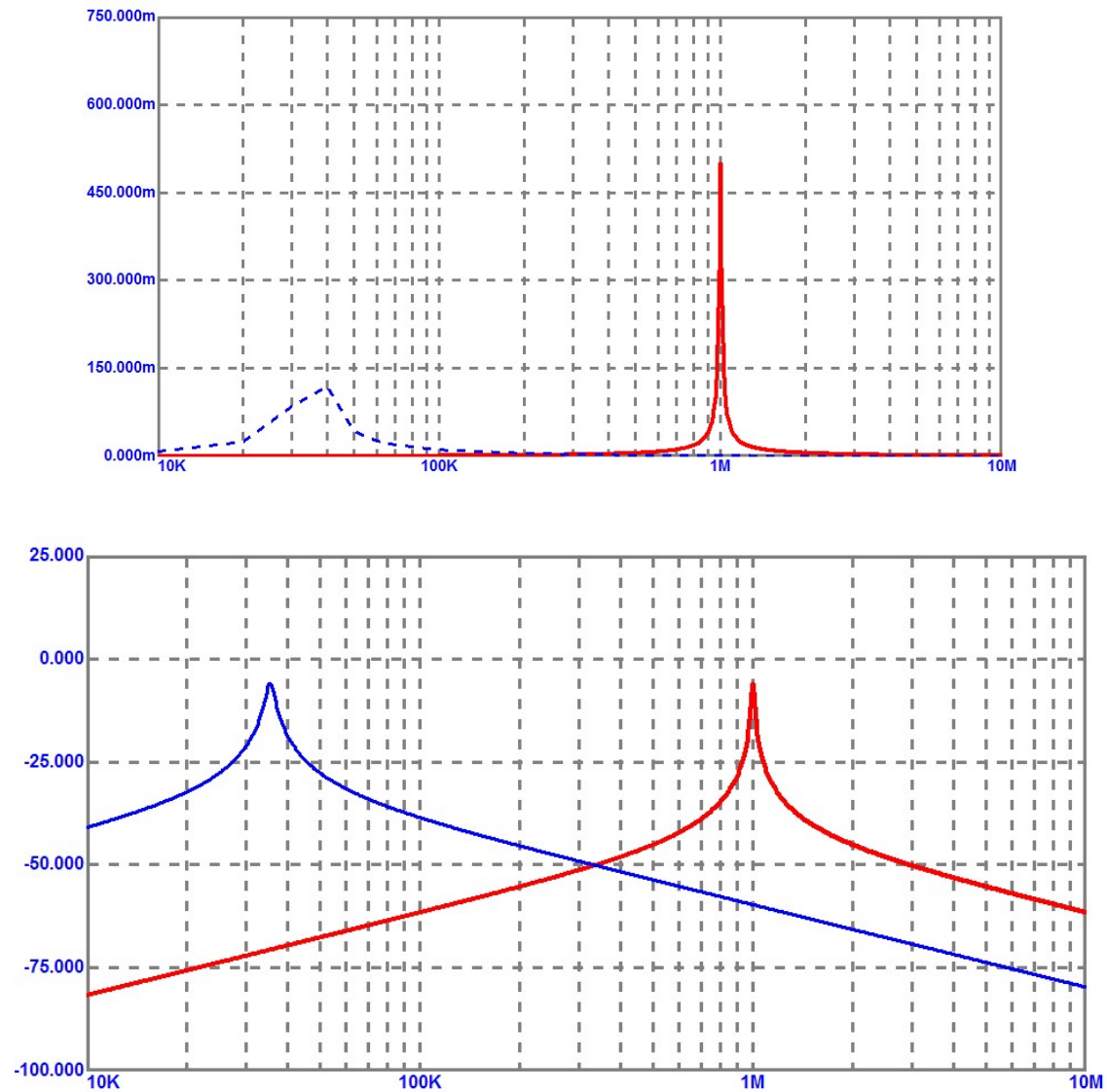Decibel scale often reveals more information about behavior




dB Scale

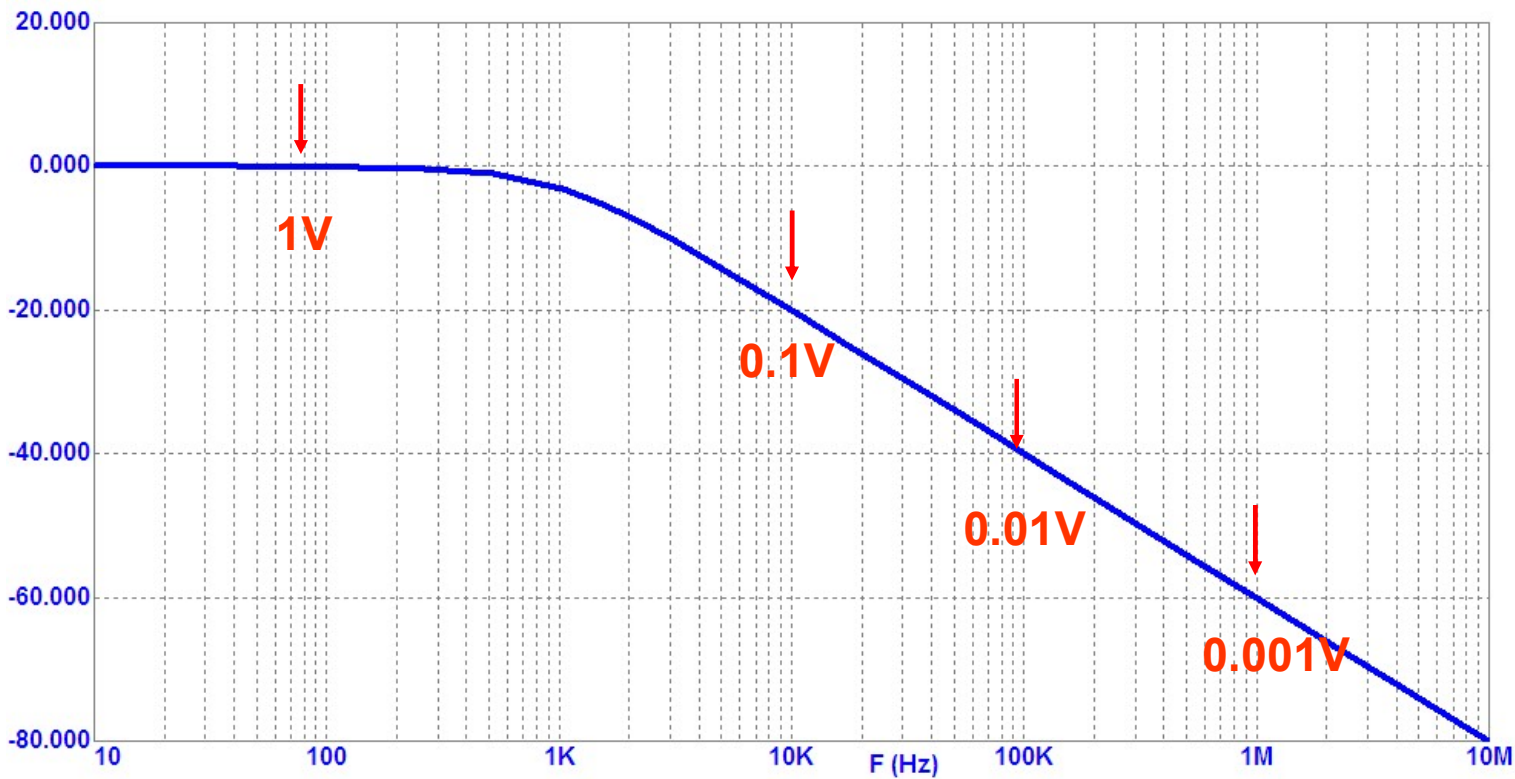

G	20Log <sub>10</sub> (G)
1000	60
100	40
10	20
2	6
√2	3
1	0
1/√2	-3
0.5	-6
0.1	-20
0.01	-40

A plot of the decibel magnitude of transfer function versus frequency using a logarithmic scale for frequency is called a **Bode plot**


## Logarithmic frequency scale

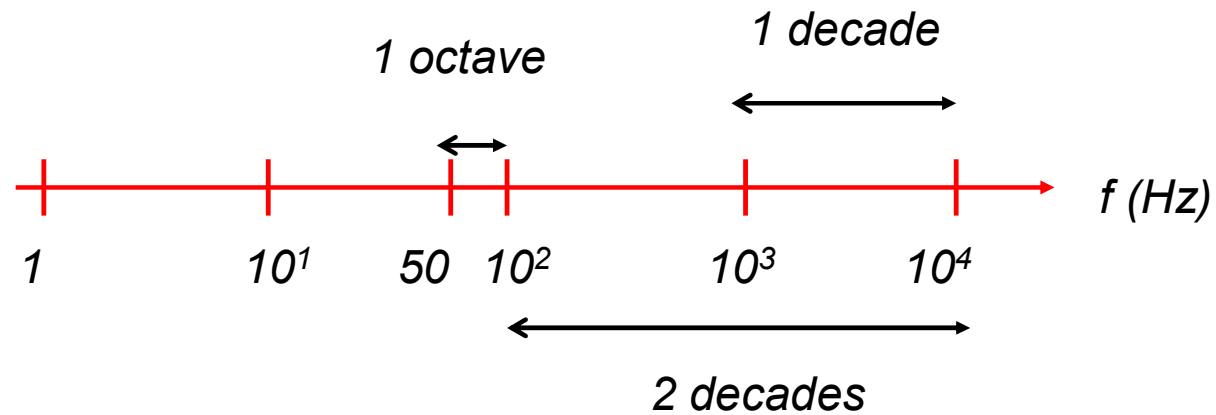

$$\text{No. of decades} = \log\left(\frac{f_2}{f_1}\right)$$


$$\text{No. of octaves} = \log_2\left(\frac{f_2}{f_1}\right) = \frac{\log\left(\frac{f_2}{f_1}\right)}{\log(2)}$$
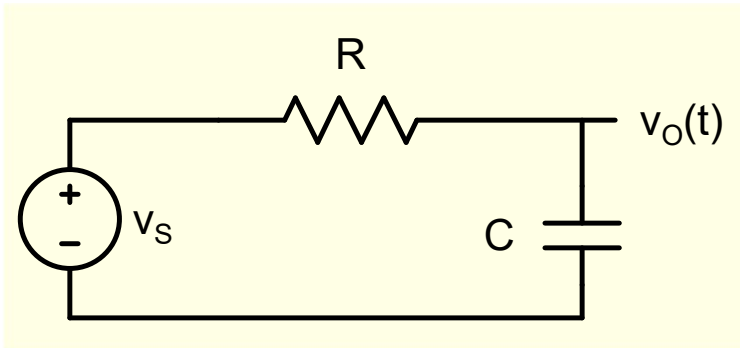
## How do we determine transfer function?



$$v_s(t) = v_{s0} \cos(\omega t)$$
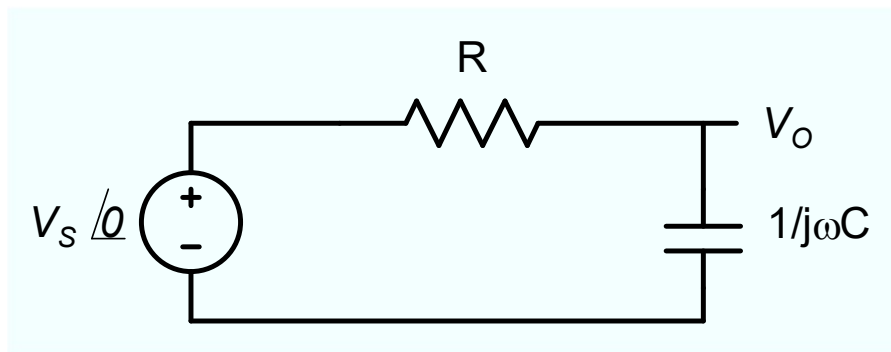
$$H(\omega) = \frac{V_o(\omega)}{V_s(\omega)}$$



$$H(\omega) = \frac{1}{1 + j\omega CR}$$



$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$$

$$\phi(\omega) = -\tan^{-1}(\omega CR)$$

## Magnitude plot

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$$

$$20\text{Log}_{10}(|H(\omega)|) = -10\text{Log}_{10}(1 + \omega^2 C^2 R^2)$$

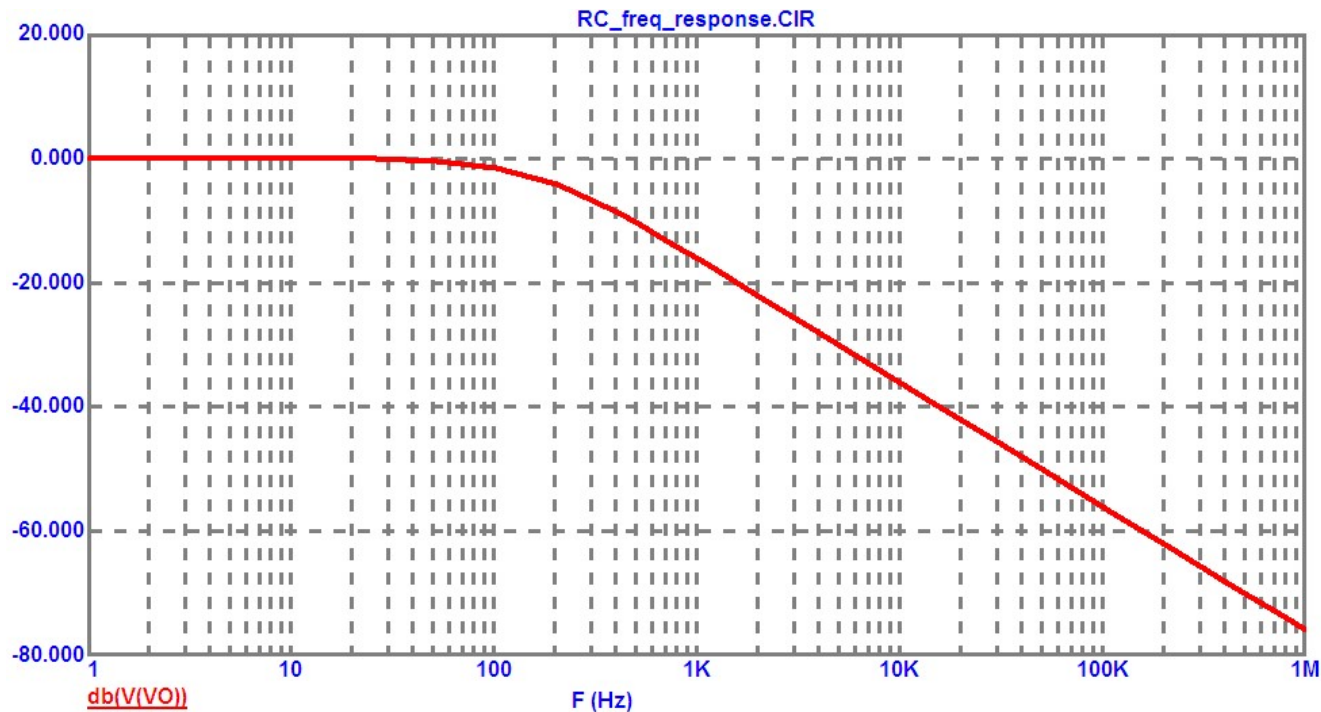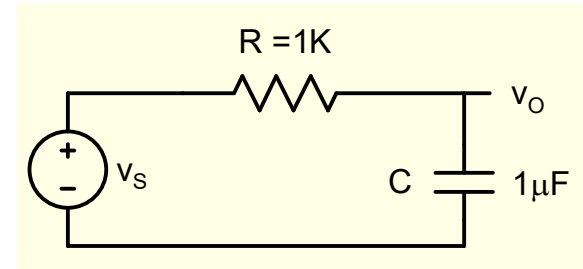


$$20\text{Log}_{10}(|H(\omega)|) = -10\text{Log}_{10}(1 + \omega^2 C^2 R^2)$$

$$= -10\text{Log}_{10}\left(1 + \frac{\omega^2}{\omega_{3dB}^2}\right)$$

$$\omega_{3dB} = \frac{1}{RC} \quad ; \quad f_{3dB} = \frac{1}{2\pi RC}$$


For  $\omega = \omega_{3dB}$   $20\text{Log}_{10}(|H(\omega_{3dB})|) = -3dB$

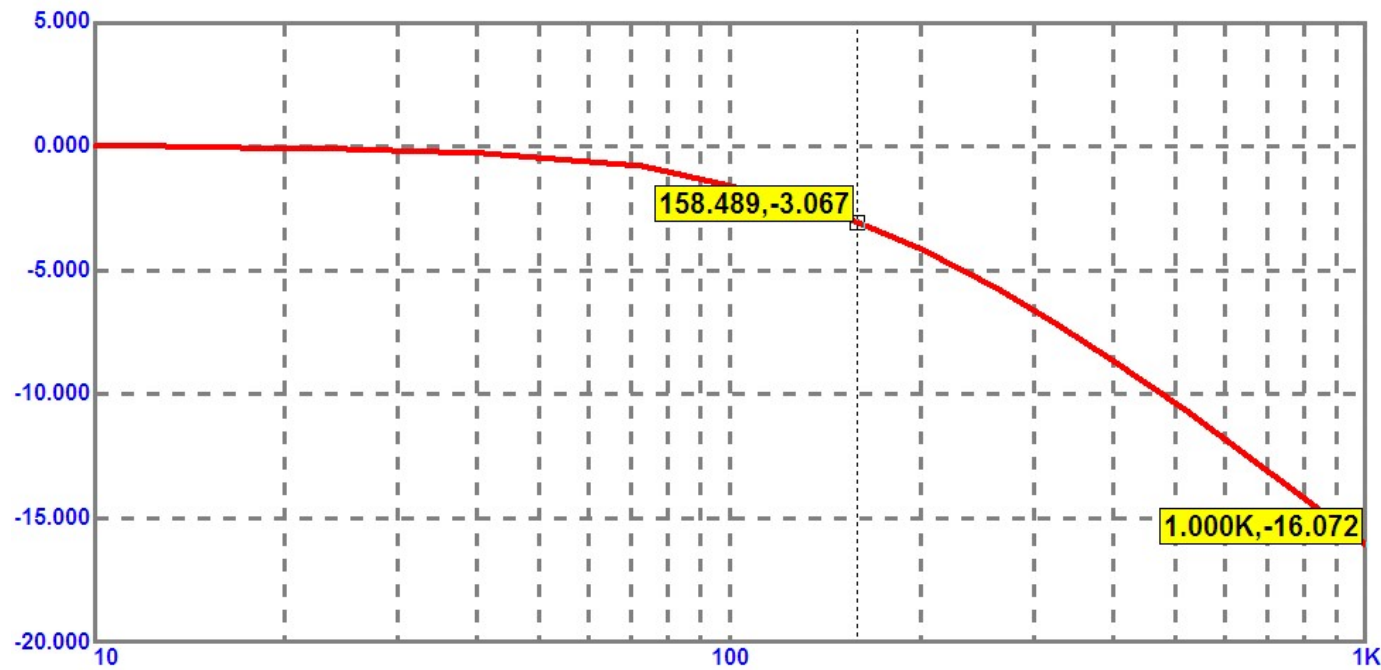

$$H(\omega) = \frac{1}{1 + j\omega CR}$$


$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$$

$$20\text{Log}_{10}(|H(\omega)|) = -10\text{Log}_{10}\left(1 + \frac{\omega^2}{\omega_{3dB}^2}\right)$$

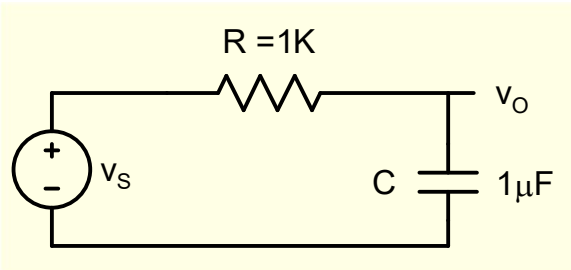

$$\text{For } \omega \gg \omega_{3dB} \quad 20\text{Log}_{10}(|H(\omega)|) \cong -20\text{Log}_{10}\left(\frac{\omega}{\omega_{3dB}}\right)$$

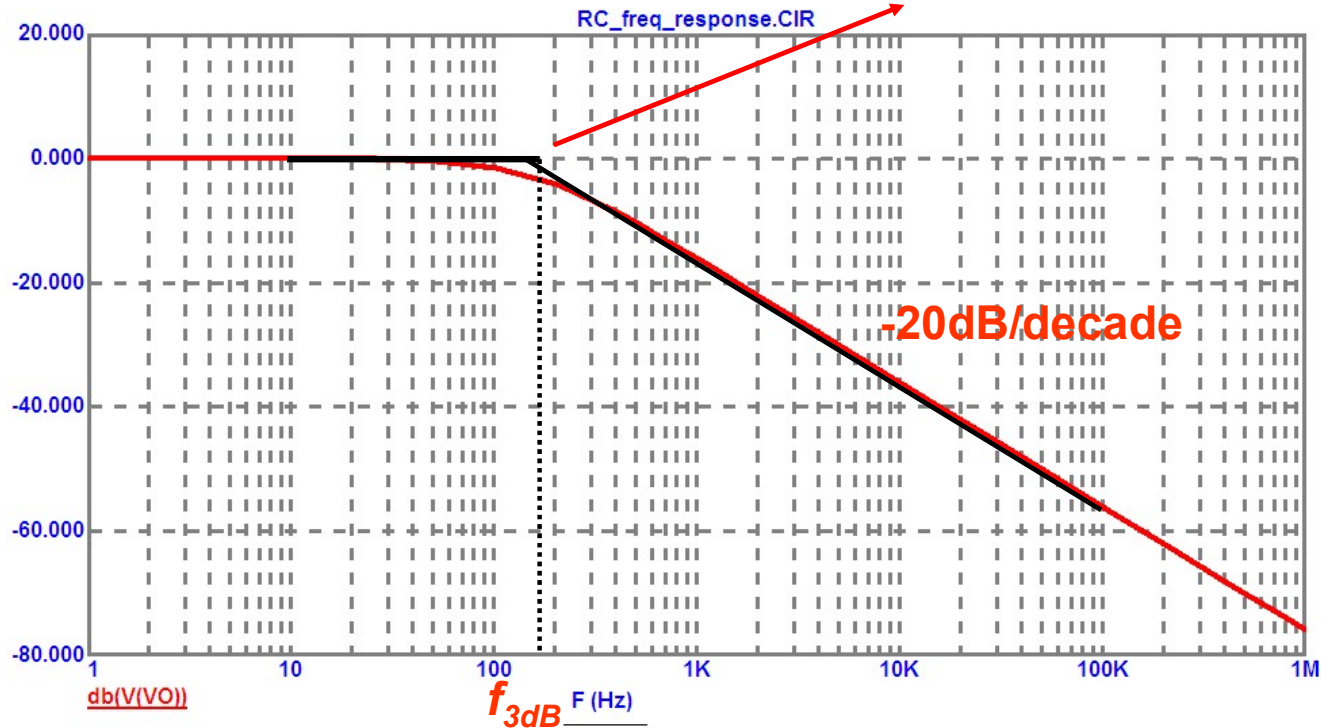Also called corner frequency  
or half power frequency






## Example





$$H(\omega) = \frac{10}{1 + j\omega 10^{-3}}$$

$$20\text{Log}_{10}(|H(\omega)|) = 20 - 10\text{Log}_{10}\left(1 + \frac{\omega^2}{\omega_{3dB}^2}\right)$$

$$\omega_{3dB} = 10^3$$

$$20\text{Log}_{10}(|H(\omega)|) \cong 20 - 20\text{Log}_{10}\left(\frac{\omega}{\omega_{3dB}}\right)$$

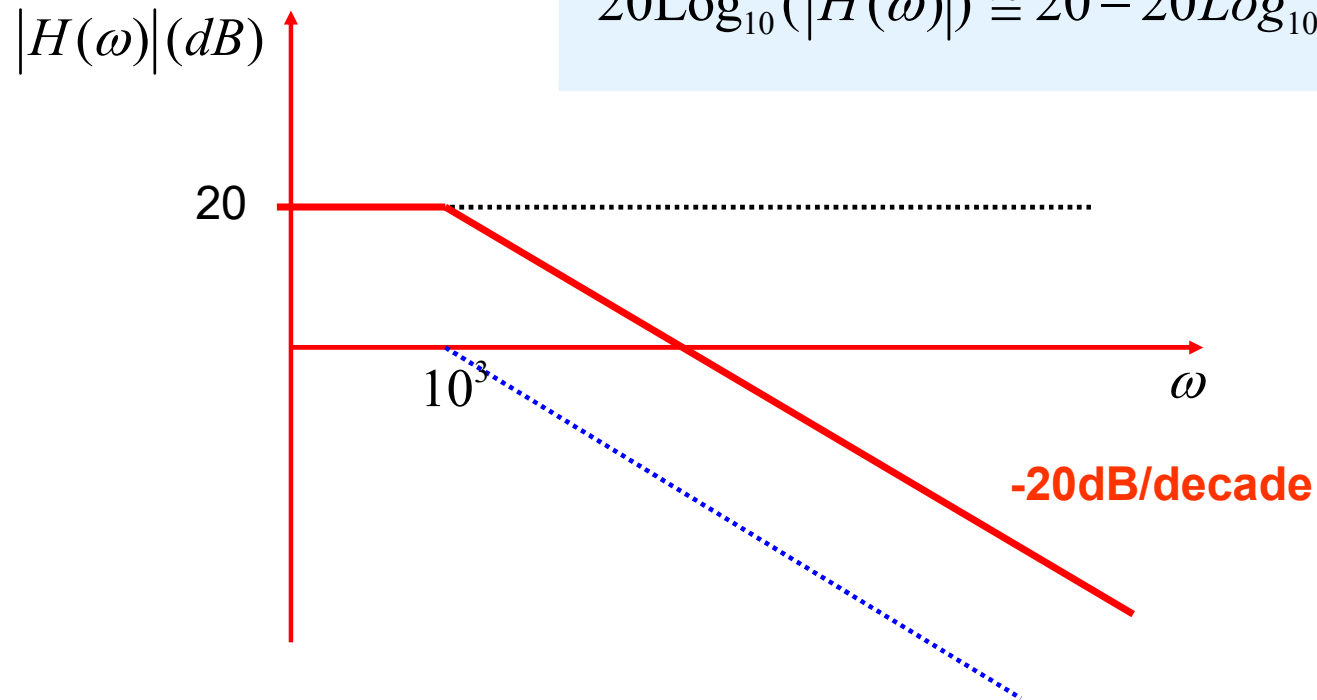


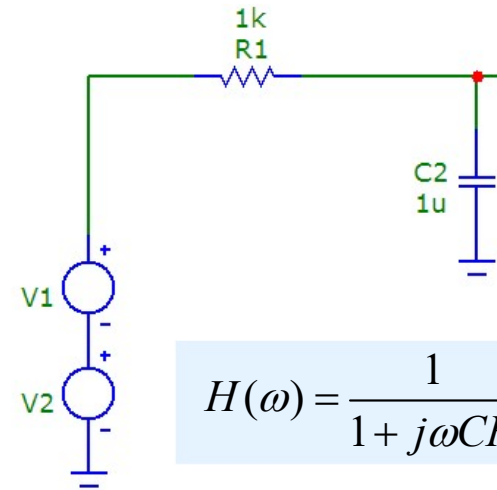
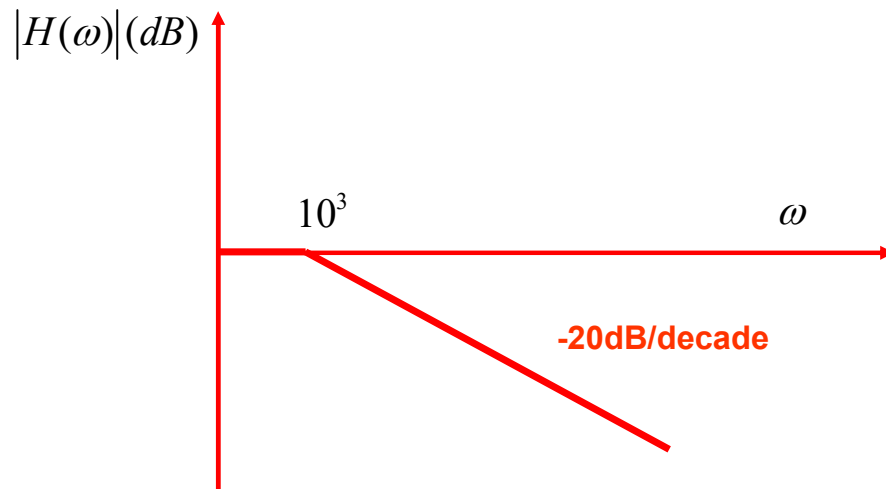
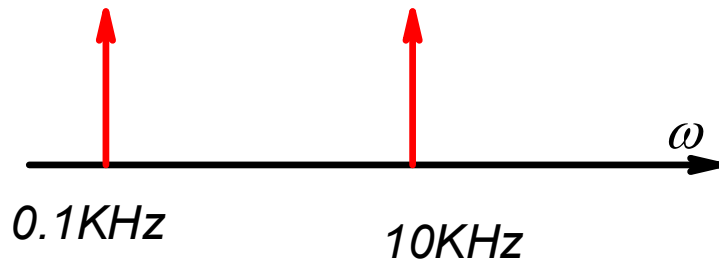
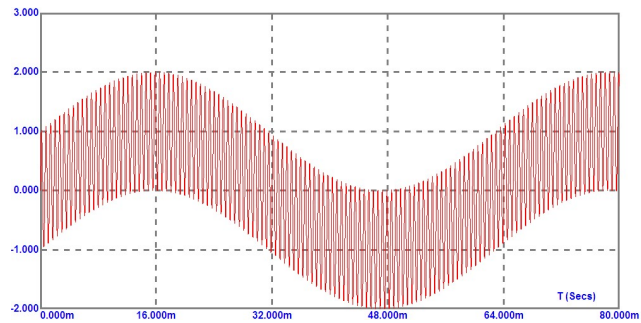




$$H(\omega) = \frac{1}{1 + j\omega CR}$$

$$H(\omega) = \frac{1}{1 + j\omega 10^{-3}} = \frac{1}{1 + j \frac{\omega}{10^3}}$$
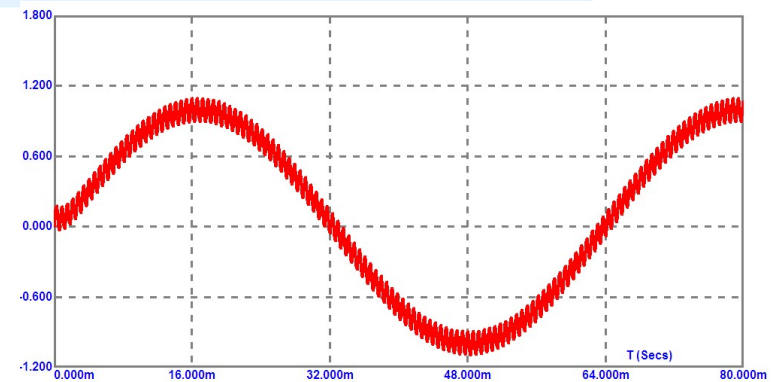
$$V_o(t) = 1\sin(100t) + 0.1\sin(10^3 t)$$



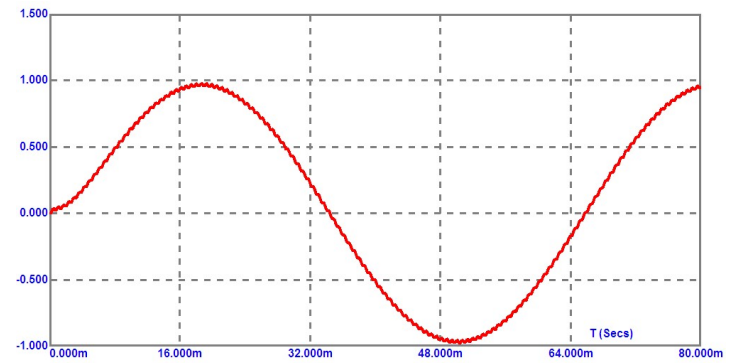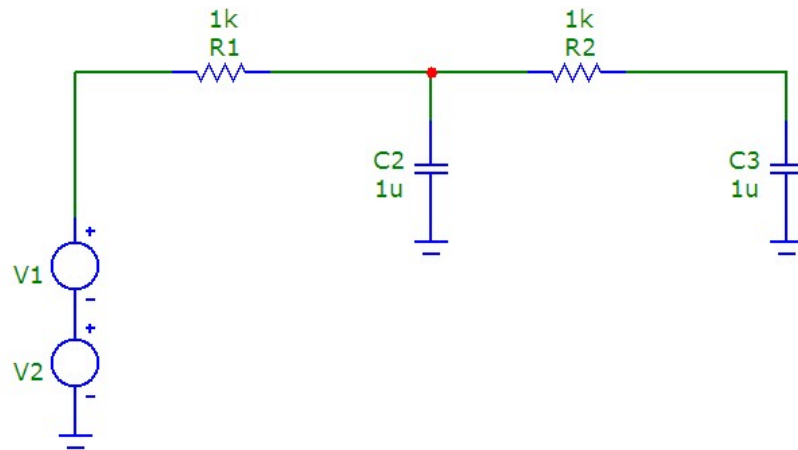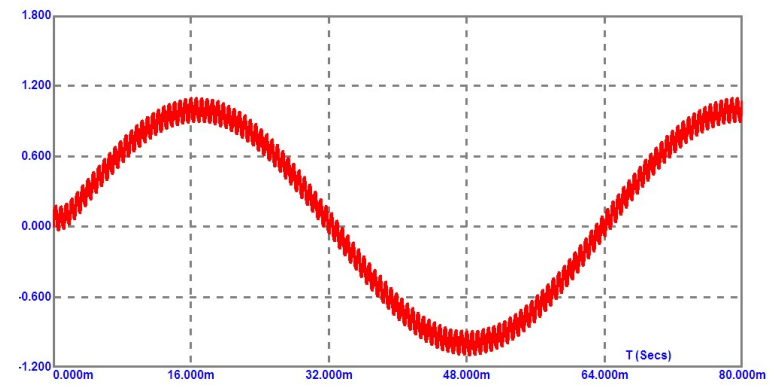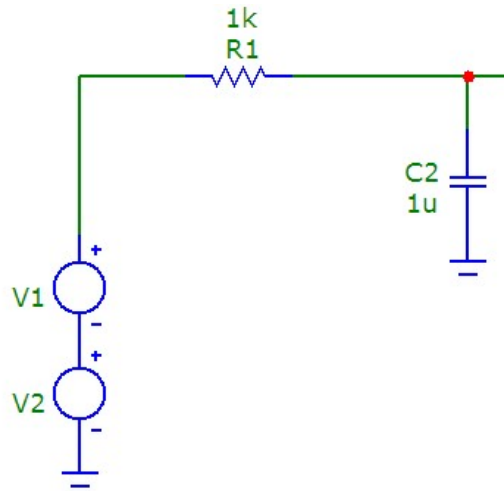

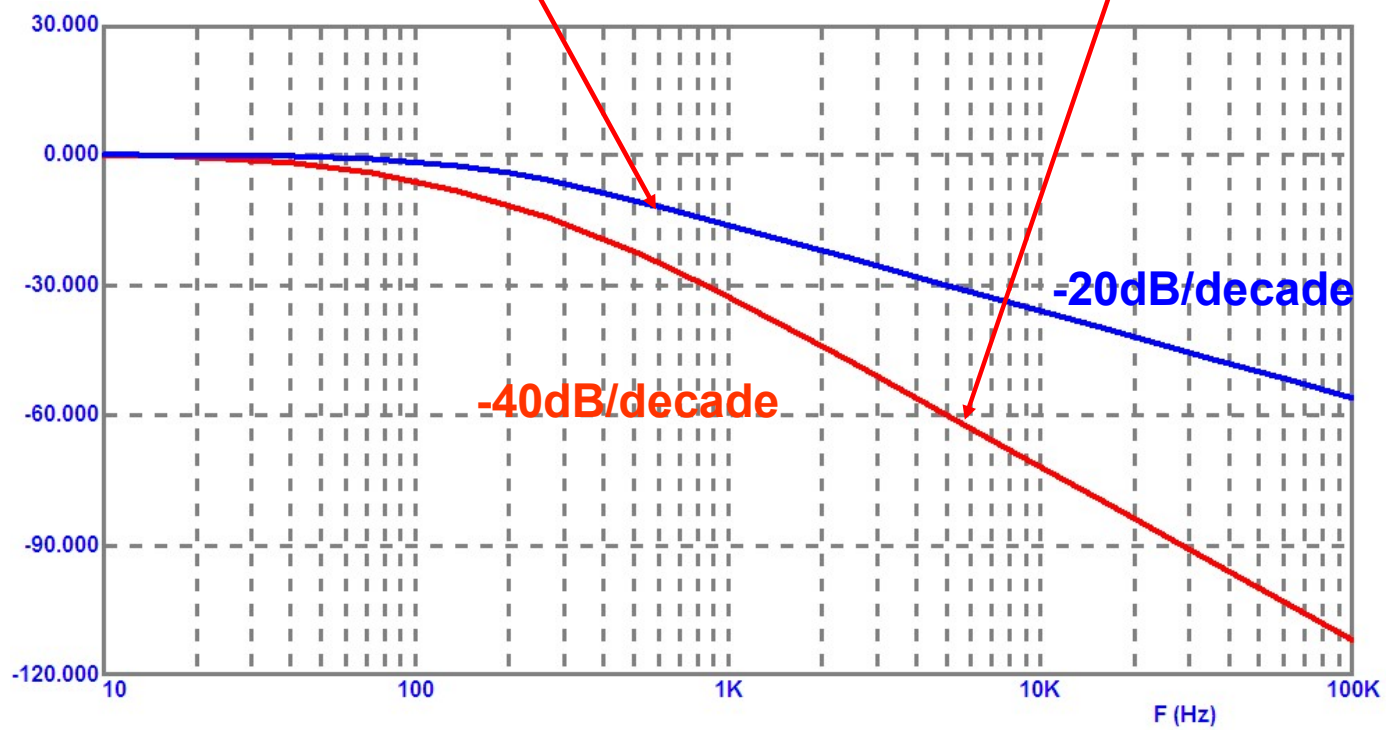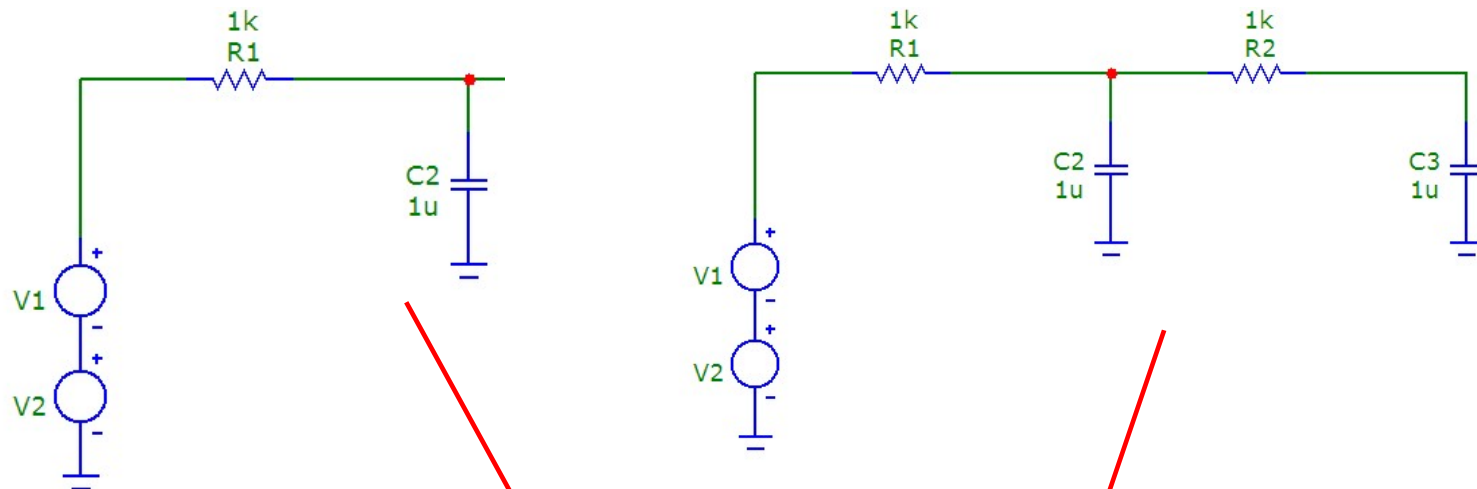

Adding more RC stages, makes the characteristics sharper

