

ESC 201T: Introduction to Electronics


Lecture 7: Toolbox For Circuit Analysis-4

**Thevenin and Norton equivalent circuits
Source Transformation**

B. Mazhari
professor, Dept. of EE
IIT Kanpur

- ❖ Mesh and Nodal analysis are “brute-force” techniques that are not only time consuming and error prone to use but also yield **unstructured** expressions that are often unsuitable for gaining **insight** into operation of circuits and **modifying or designing** them.
- ❖ Need techniques that yield relatively simpler structured expressions that **reveal the role of different components** and that require less **effort** and are less **error prone**

Maximum Power Transfer for dc circuits

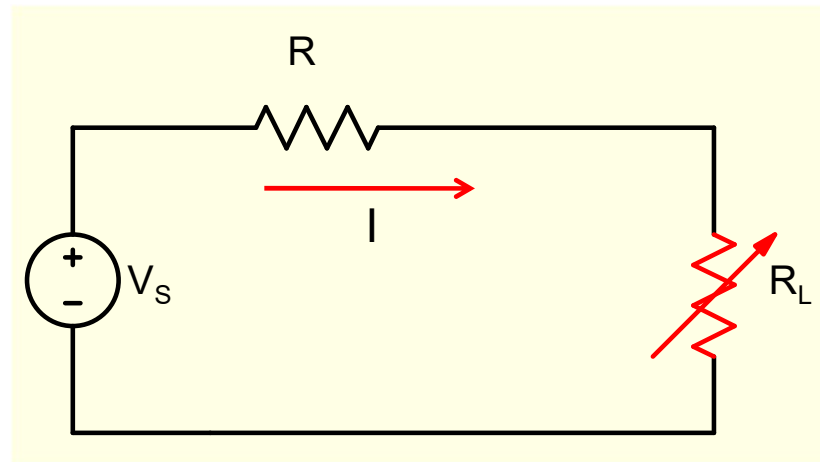

$$P_L = i^2 \times R_L$$

What value of R_L will give rise to maximum load power ?


$$I = \frac{V_s}{R + R_L}$$

$$P_L = I^2 R_L = V_s^2 \times \frac{R_L}{(R + R_L)^2}$$

$$\frac{\partial P_L}{\partial R_L} = 0$$

$$R_L = R$$

$$P_{L \max} = \frac{V_s^2}{4 R_L}$$

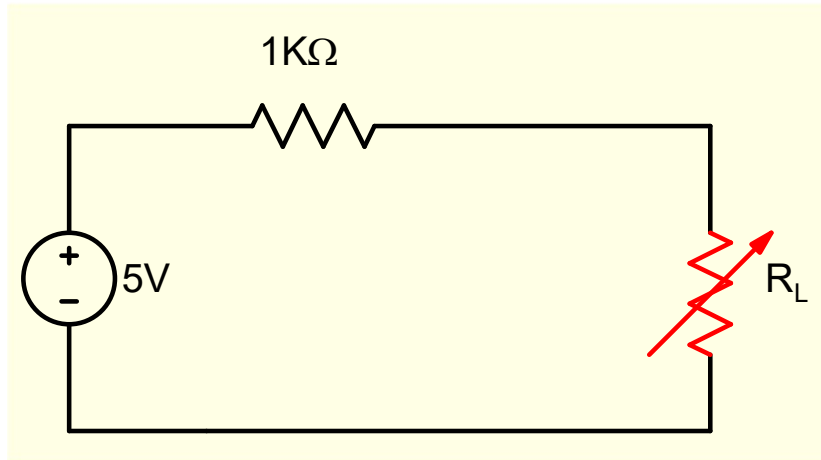


$$R_L = 1K \Rightarrow P_L = 6.25 mW$$

$$R_L = 10K \Rightarrow P_L = 2 mW$$

$$R_L = 0.2K \Rightarrow P_L = 3.47 mW$$

Maximum power is delivered to the load when **$R_L = R$**

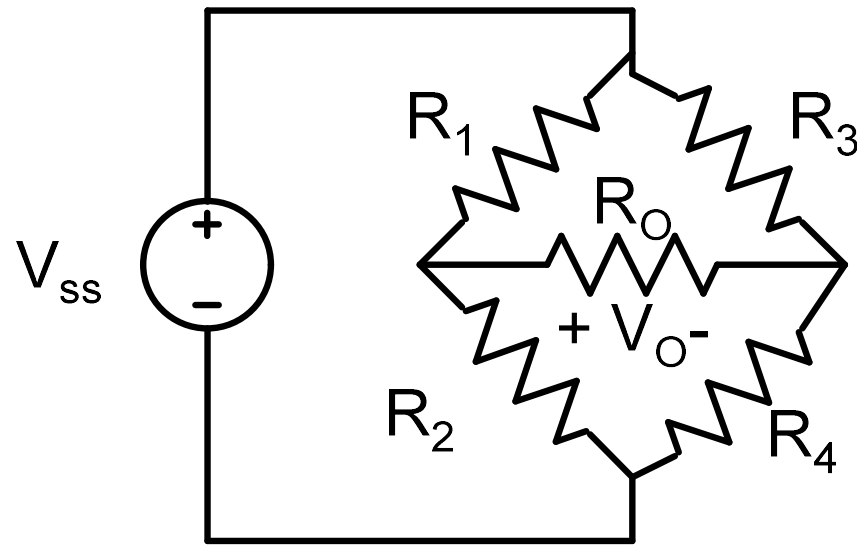
After deriving this useful result, how do we re-use it with other complicated circuits?



$$P_O = \frac{V_O^2}{R_O}$$

$$V_O = \frac{V_{SS} \times R_O \times (R_2 R_3 - R_1 R_4)}{R_2 R_4 R_O + R_2 R_3 R_O + R_1 R_4 R_O + R_1 R_3 R_O + R_2 R_3 R_4 + R_1 R_3 R_4 + R_1 R_2 R_4 + R_1 R_2 R_3}$$

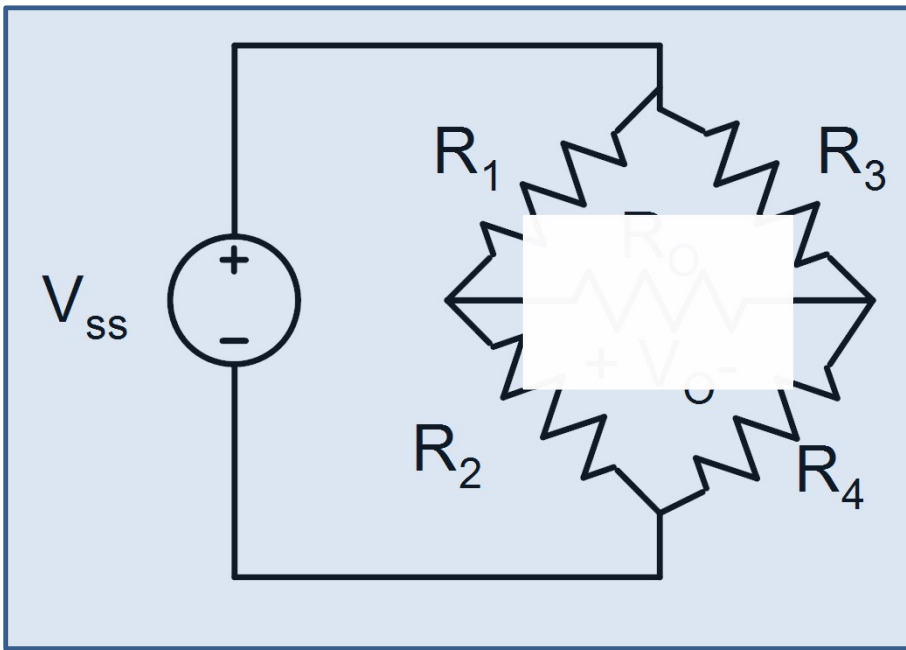
For what value of R_O is maximum power transferred to it?



$$V_O = V_{TH} \times \frac{R_O}{R_O + R_{TH}}$$

$$V_{TH} = V_{SS} \times \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right)$$
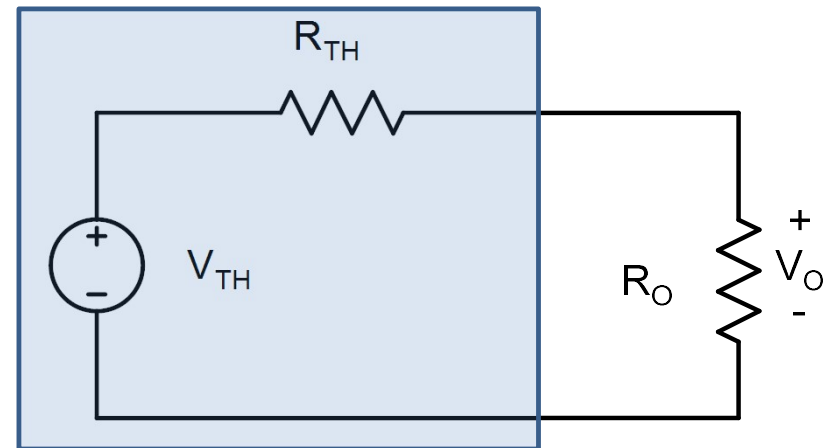
$$R_{TH} = (R_1 \parallel R_2) + (R_3 \parallel R_4)$$






$$V_O = V_{SS} \times \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right) \times \left\{ \frac{R_O}{R_O + \{(R_1 \parallel R_2) + (R_3 \parallel R_4)\}} \right\}$$

Maximum power will be transferred when R_O is chosen equal to R_{TH}





Thévenin Equivalent Circuit

Linear Circuit consisting
of Resistances and
independent/dependent
sources


Any circuit

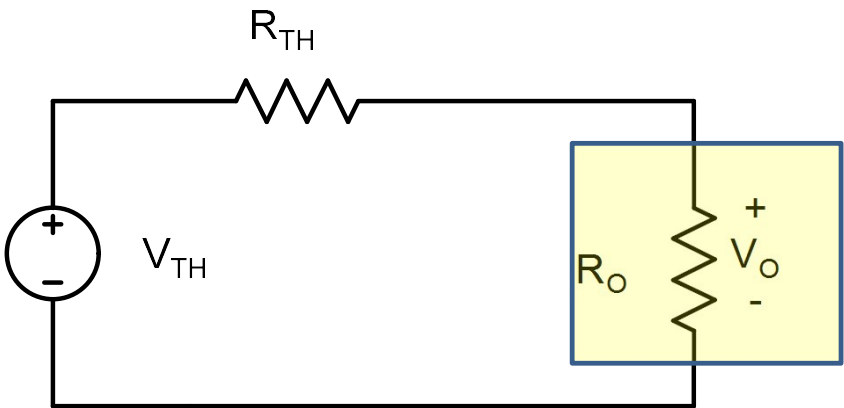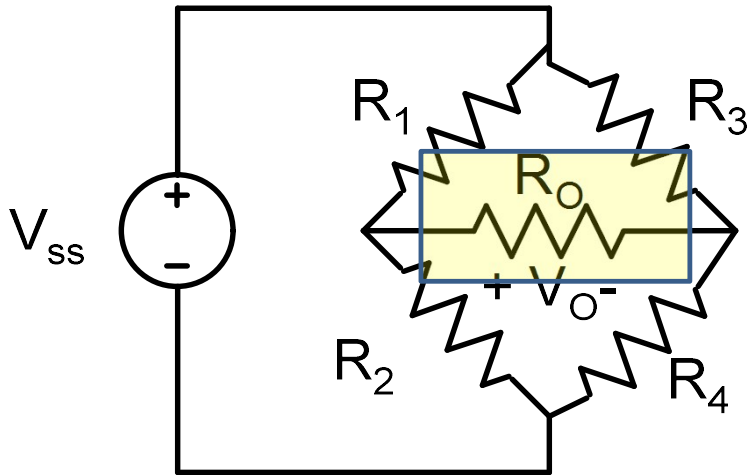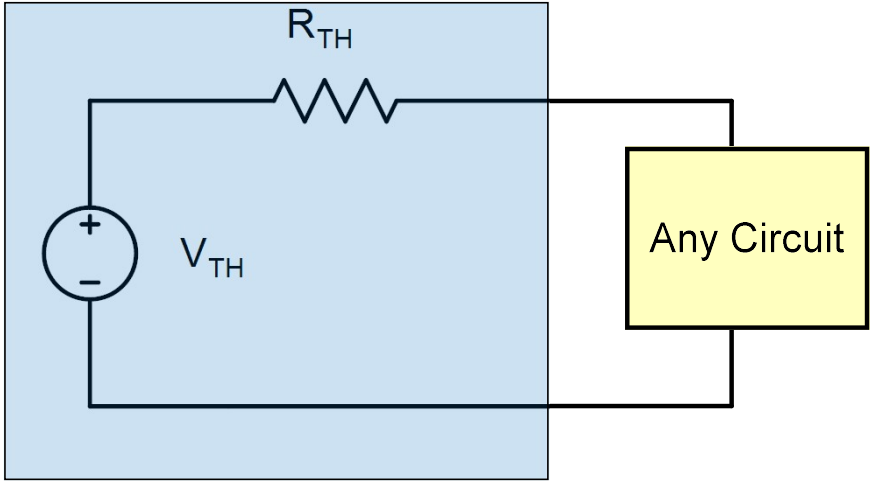

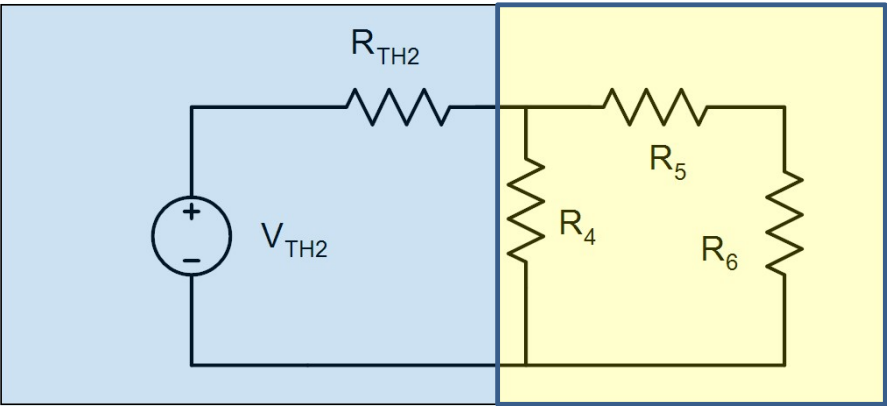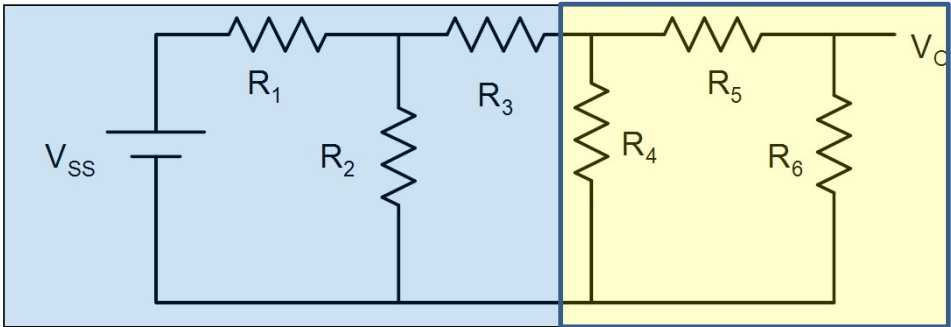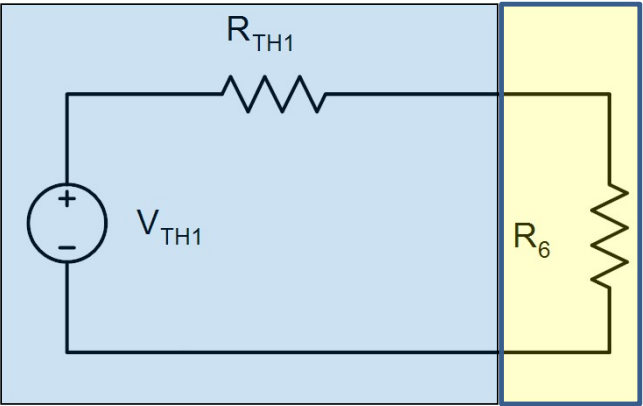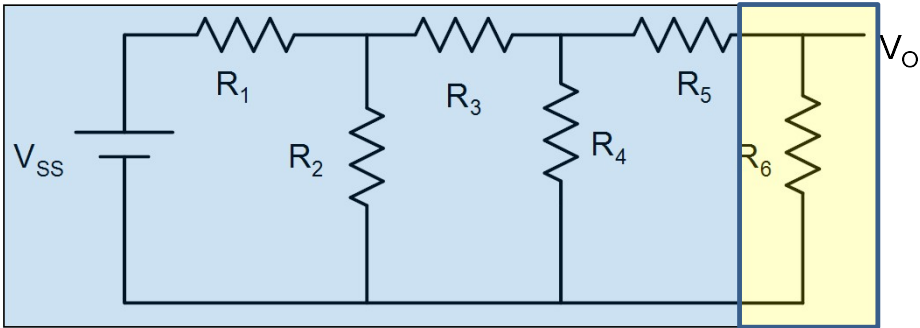
We can create Thevenin's equivalent for any part of the circuit



Thévenin Voltage



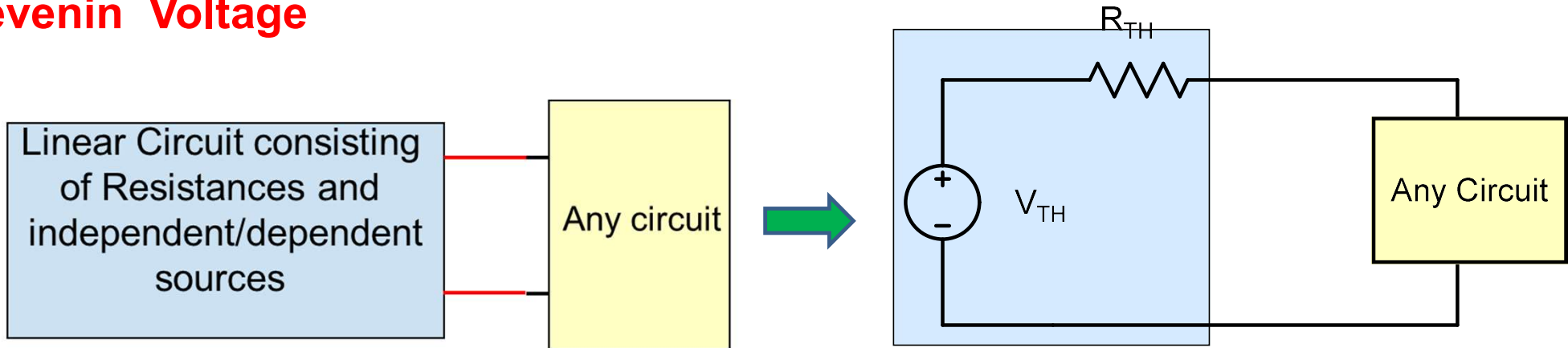


What is V_{TH} ?

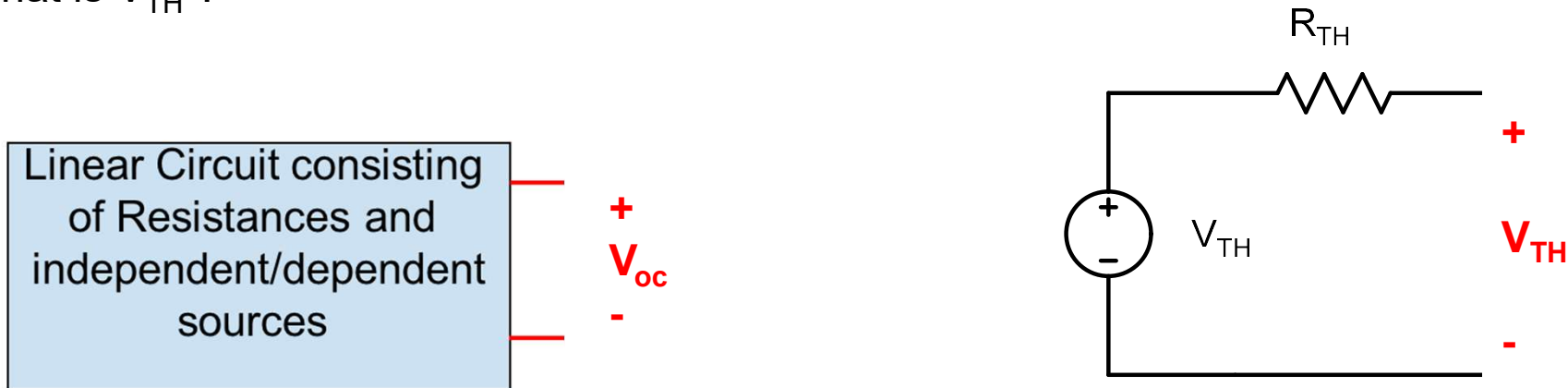


$$V_{TH} = V_{OC}$$

Example

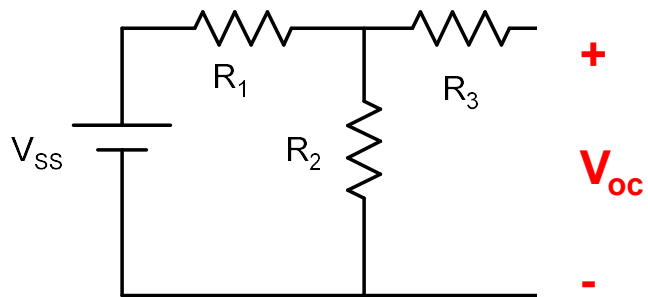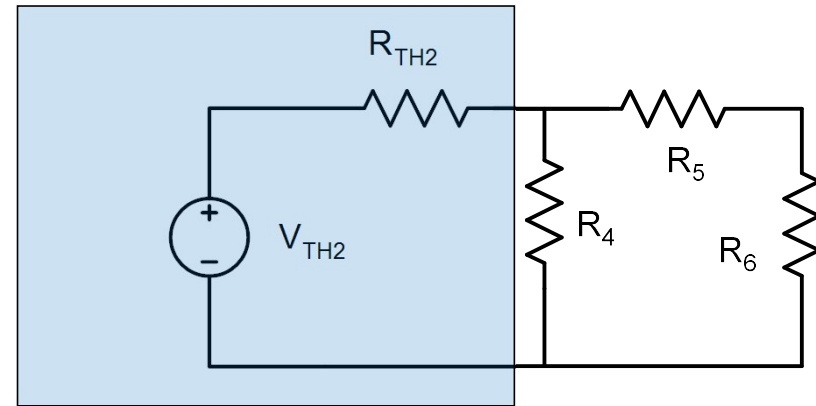
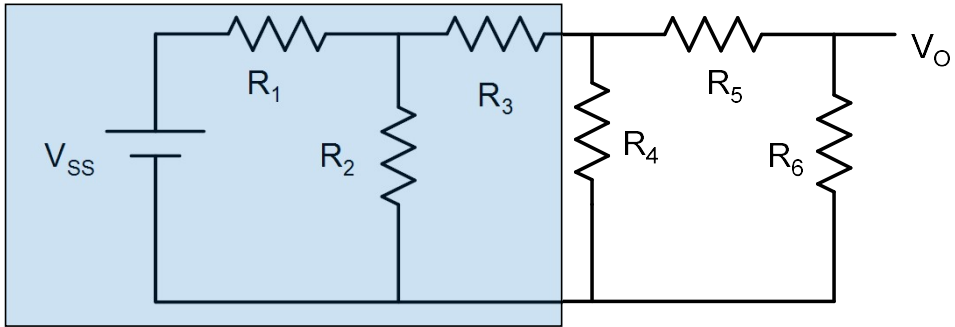


$$V_{TH2} = V_{OC} = V_{SS} \times \frac{R_2}{R_1 + R_2}$$

Thévenin Resistance


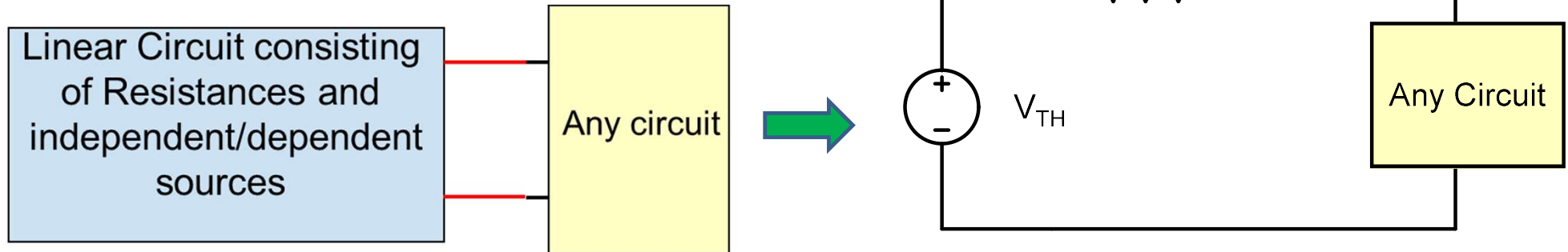


What is R_{TH} ?

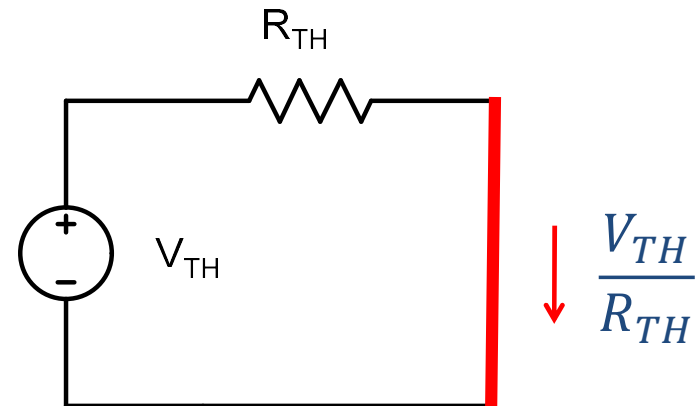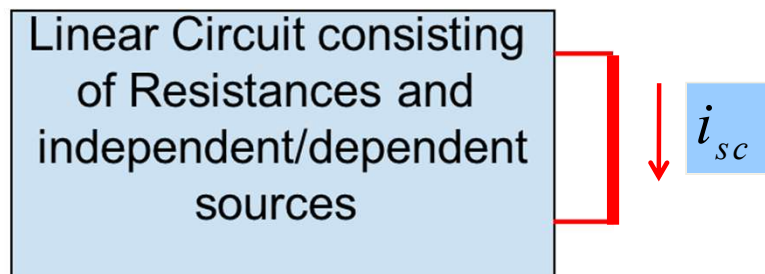


$$I_{SC} = \frac{V_{TH}}{R_{TH}} \Rightarrow R_{TH} = \frac{V_{OC}}{I_{SC}}$$

Summary


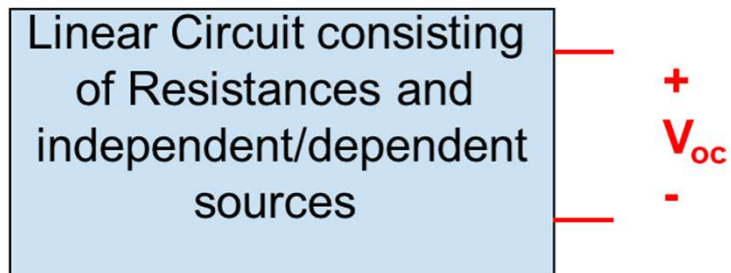
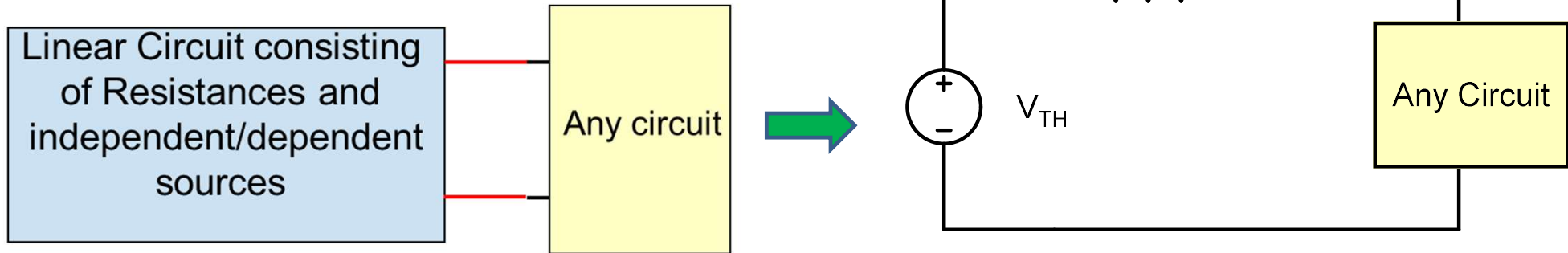


$$V_{TH} = V_{OC}$$

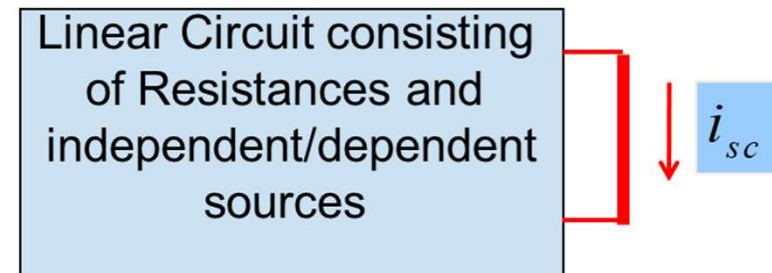


$$R_{TH} = \frac{V_{OC}}{I_{SC}}$$

Example

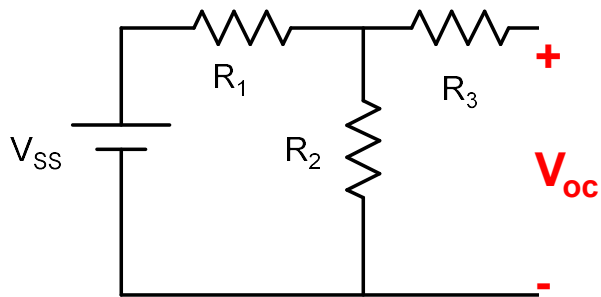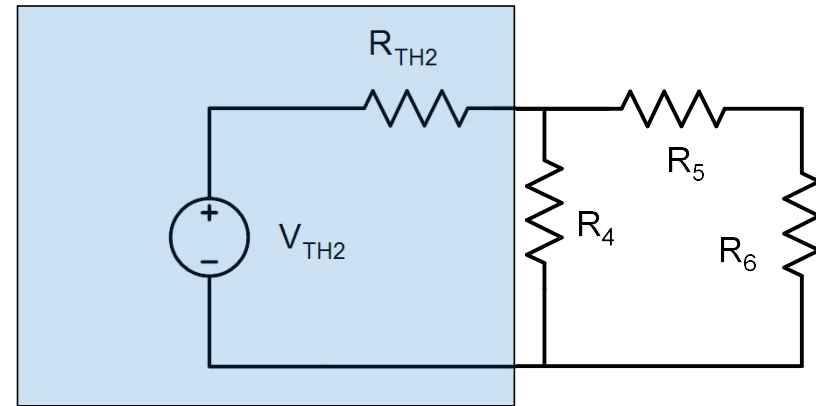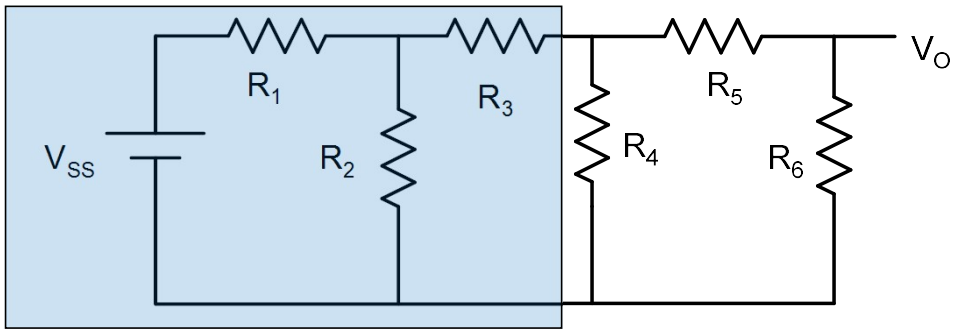

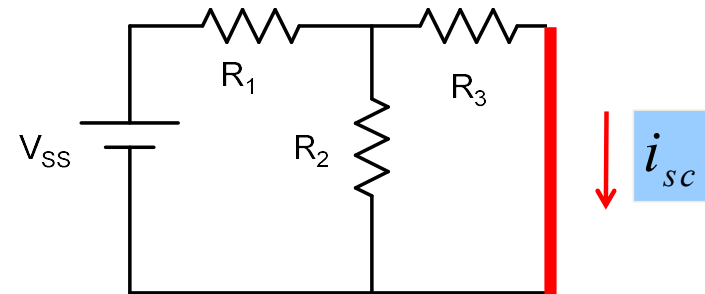
$$V_{TH2} = V_{OC} = V_{SS} \times \frac{R_2}{R_1 + R_2}$$




$$I_{SC} = \frac{V_{SS}}{R_1 + R_2 \parallel R_3} \times \frac{R_2}{R_2 + R_3}$$



$$R_{TH2} = \frac{V_{OC}}{I_{SC}} = \frac{R_2 + R_3}{R_1 + R_2} \times (R_1 + R_2 \parallel R_3)$$

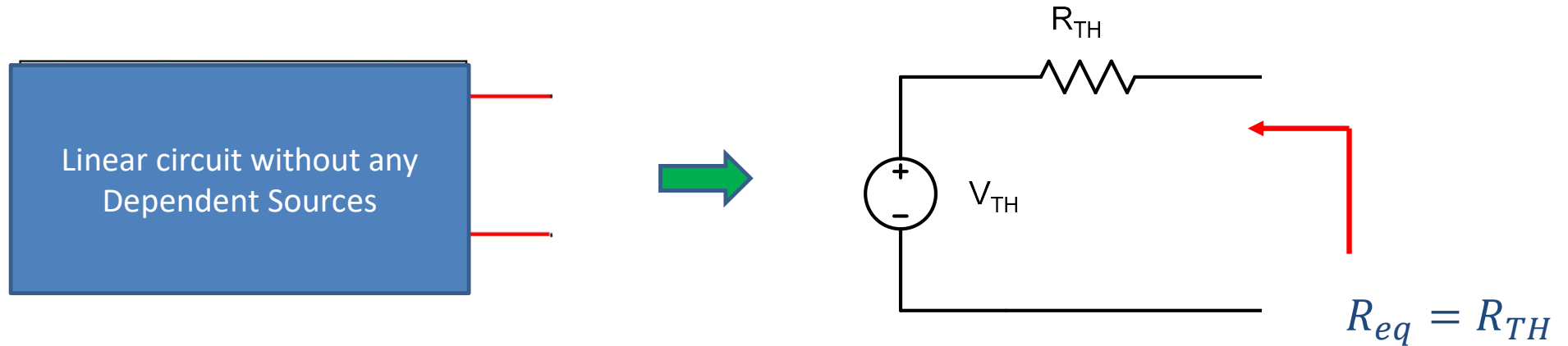Thévenin Resistance: Alternative Method in the absence of dependent sources



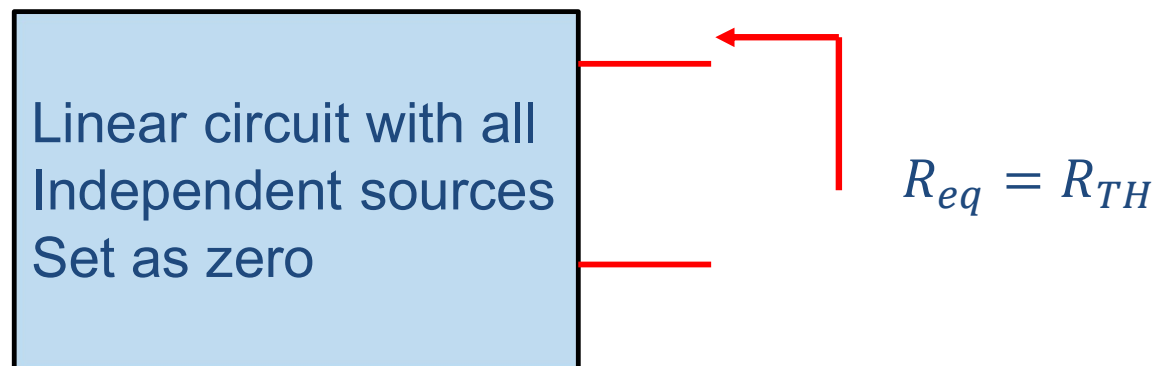If we make all independent sources zero, then $V_{TH} = 0$







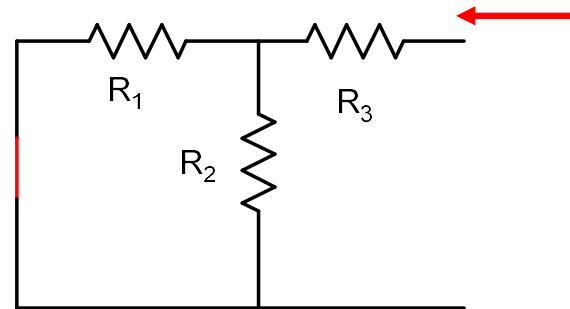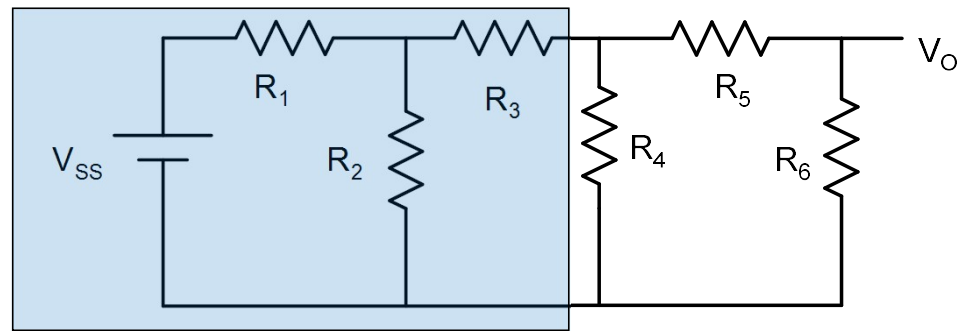




$$R_{eq} = R_{TH2} = R_1 \parallel R_2 + R_3$$

$$R_{TH2} = \frac{V_{OC}}{I_{SC}} = \frac{R_2 + R_3}{R_1 + R_2} \times (R_1 + R_2 \parallel R_3)$$




Norton Equivalent Circuit

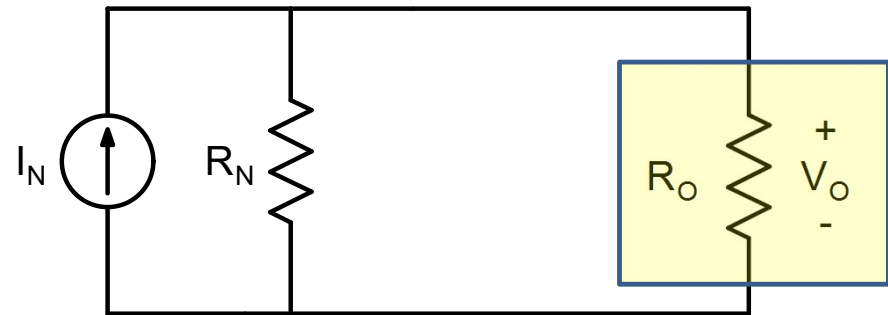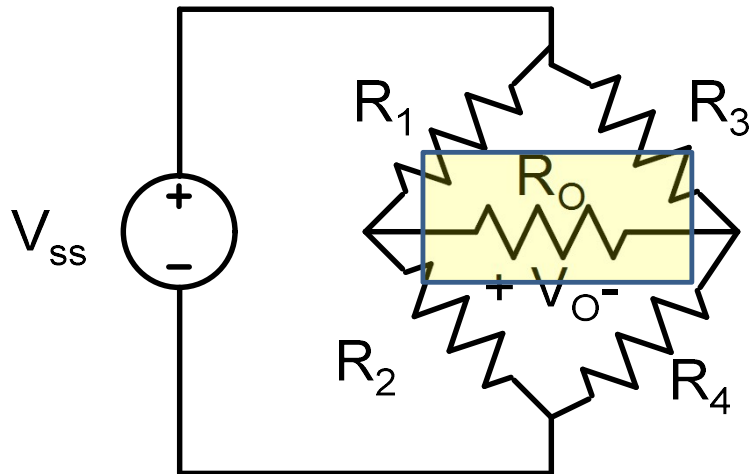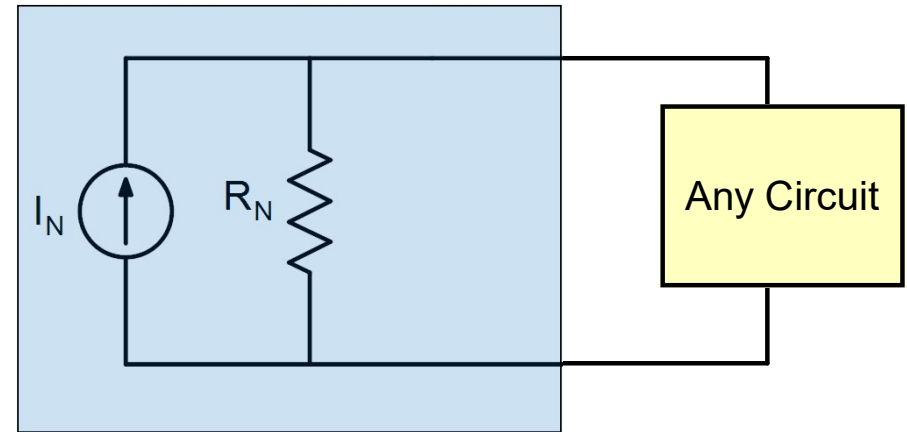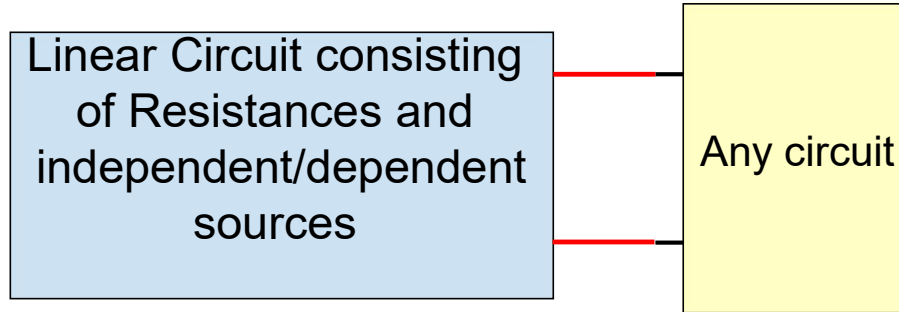

Norton's Current

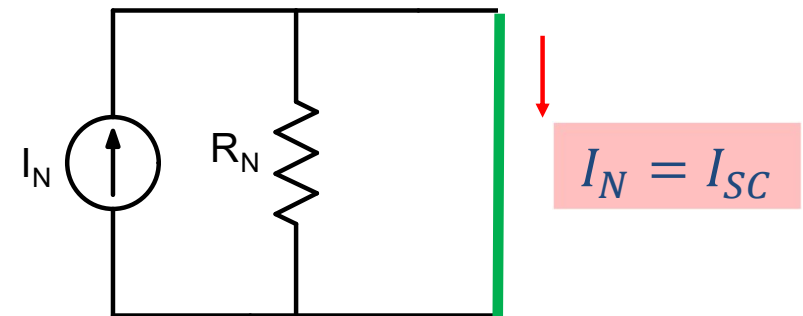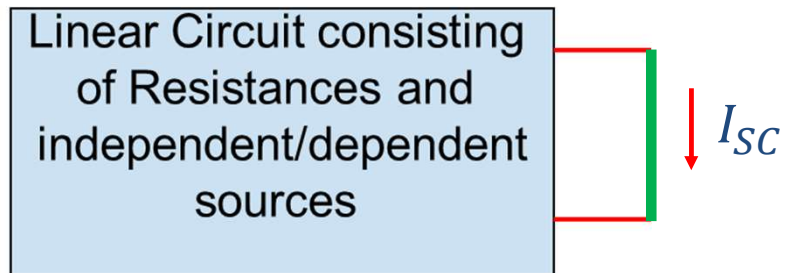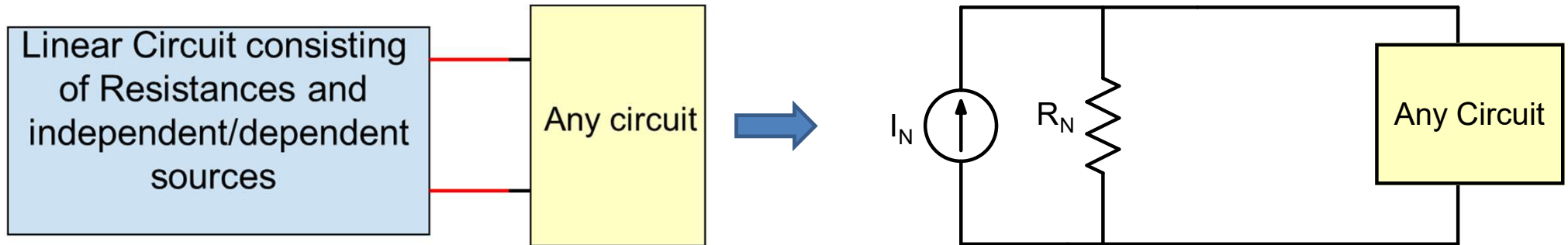


Norton's Resistance

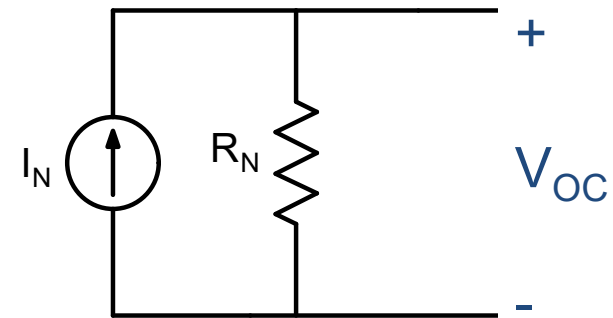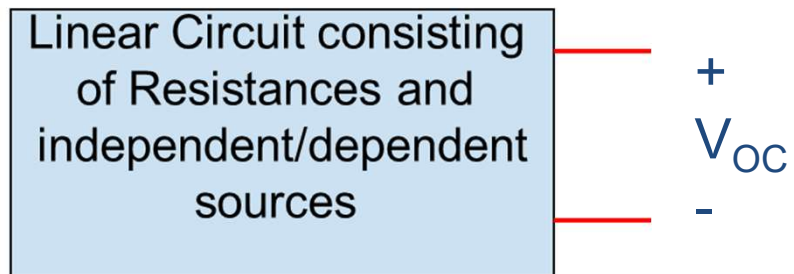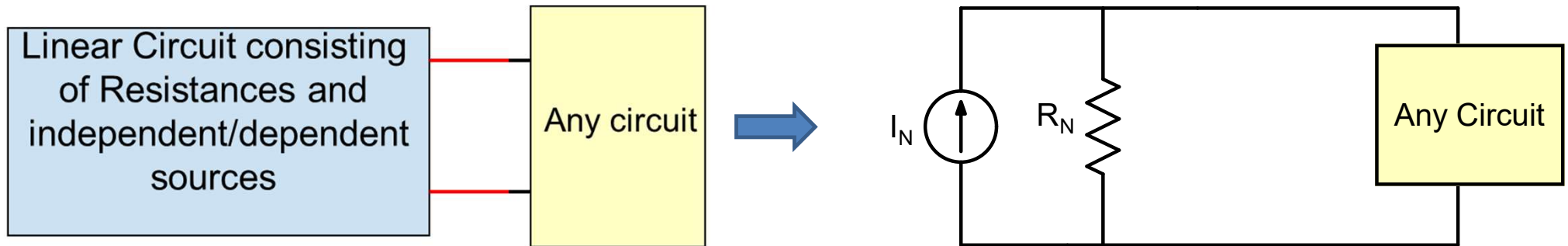


$$R_N = \frac{V_{OC}}{I_{SC}}$$

$$V_{OC} = I_N \times R_N$$



$$I_N = I_{SC}$$

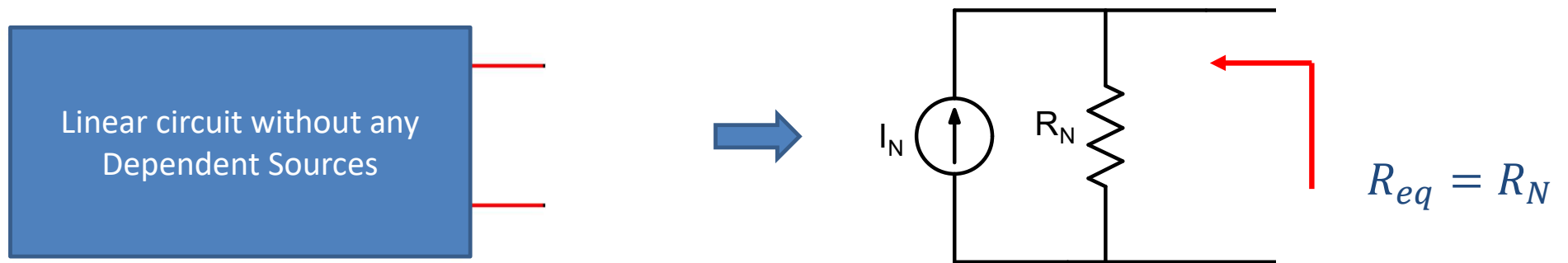

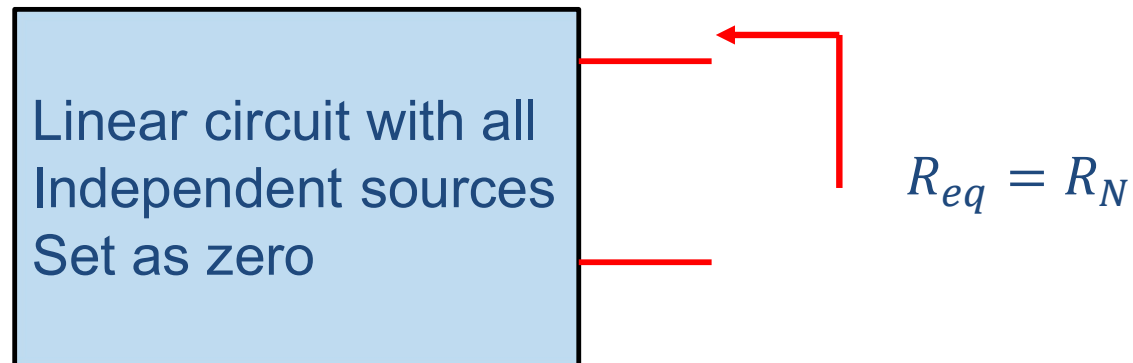
If we make all independent sources zero, then $I_N = 0$



Example

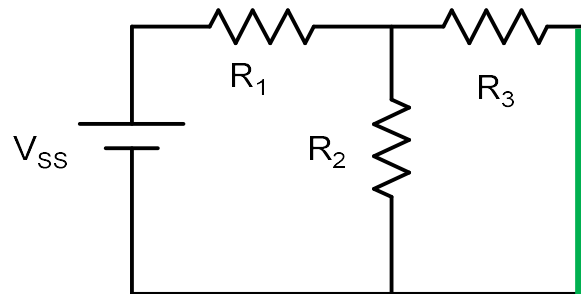
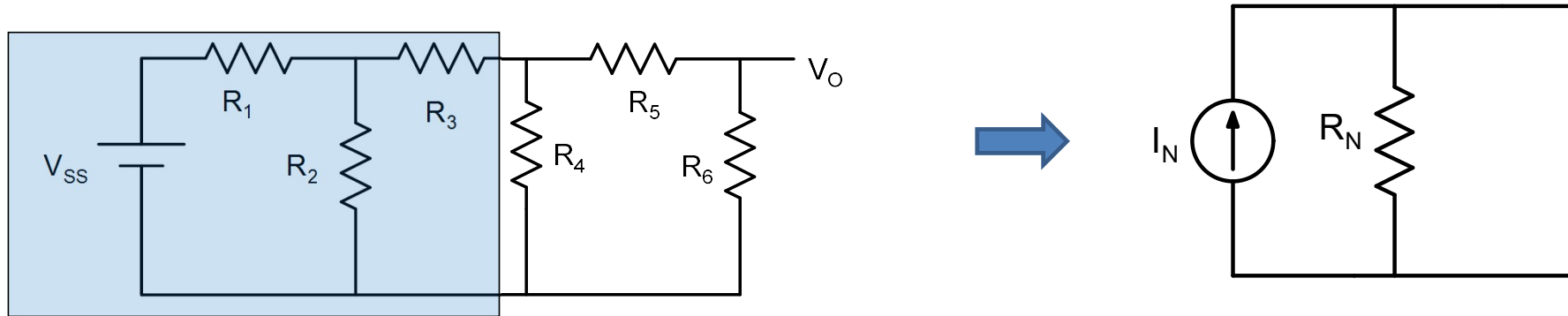

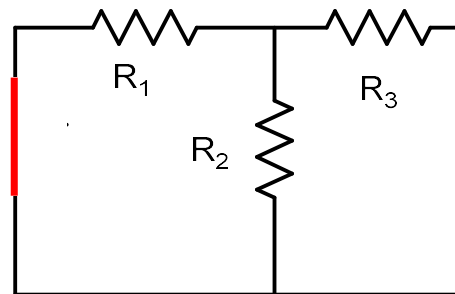
$$I_N = I_{SC} = \left(\frac{V_{SS}}{R_1 + R_2 \parallel R_3} \right) \times \left(\frac{R_2}{R_2 + R_3} \right)$$







$$R_{eq} = R_N = (R_1 \parallel R_2) + R_3$$

Maximum Power Transfer : General Case


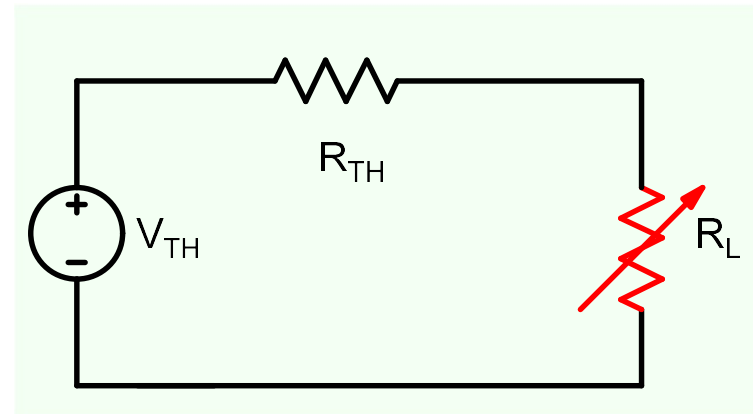
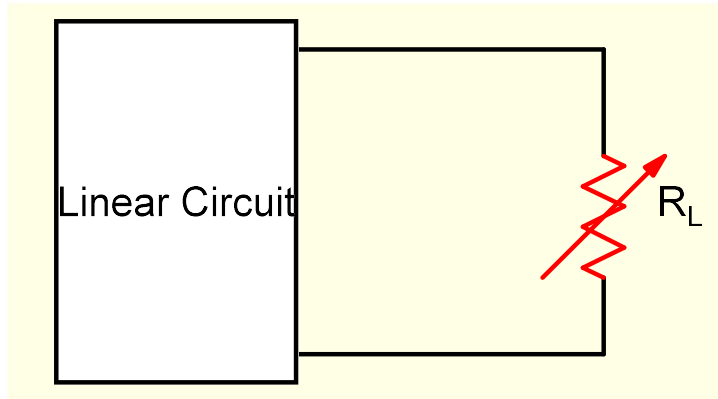


Maximum power is delivered to the load when $R_L = R_{TH}$

Source Transformation

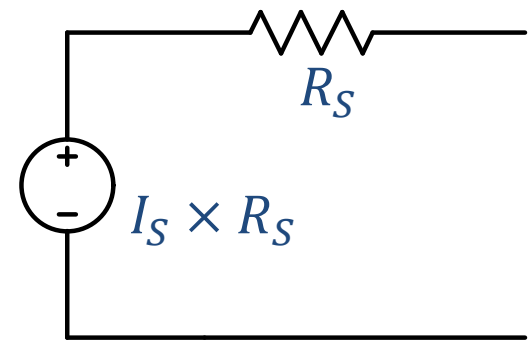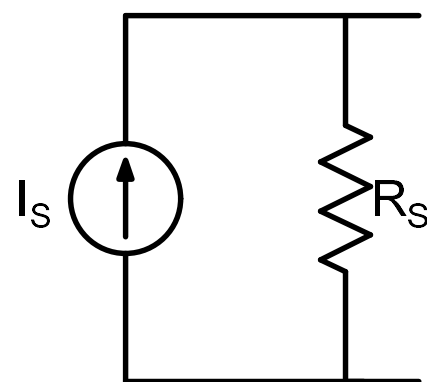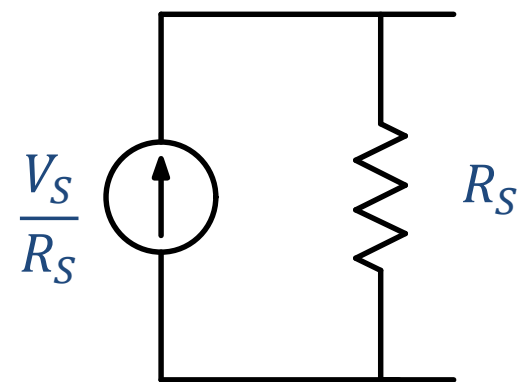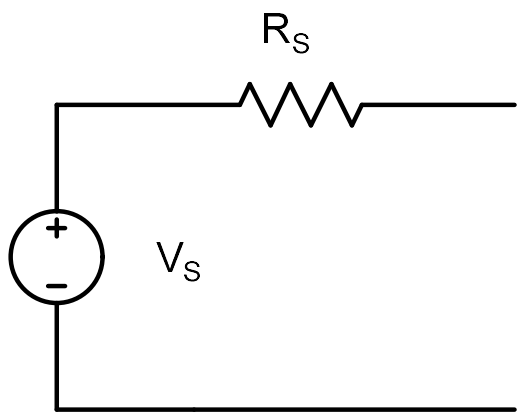

Example

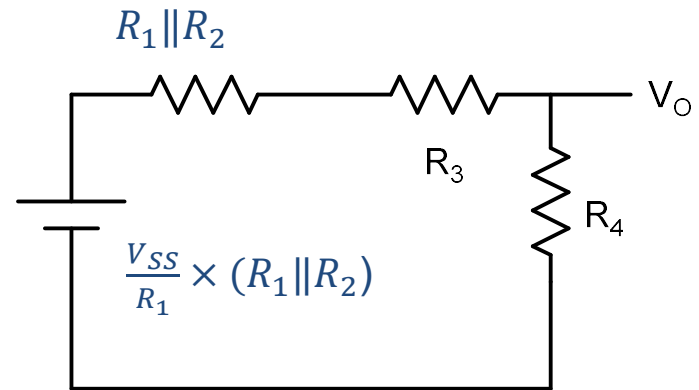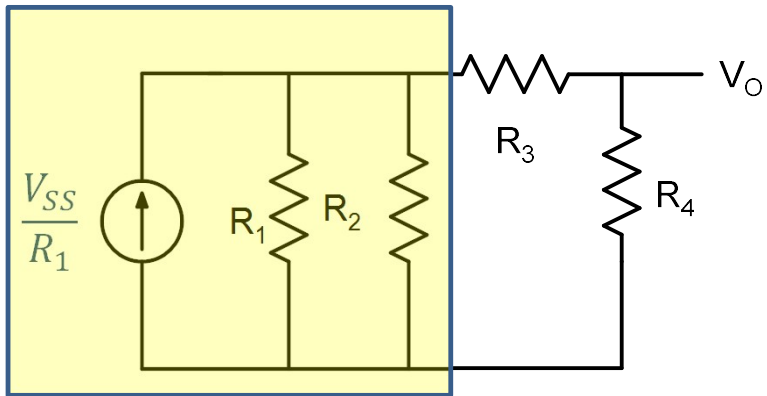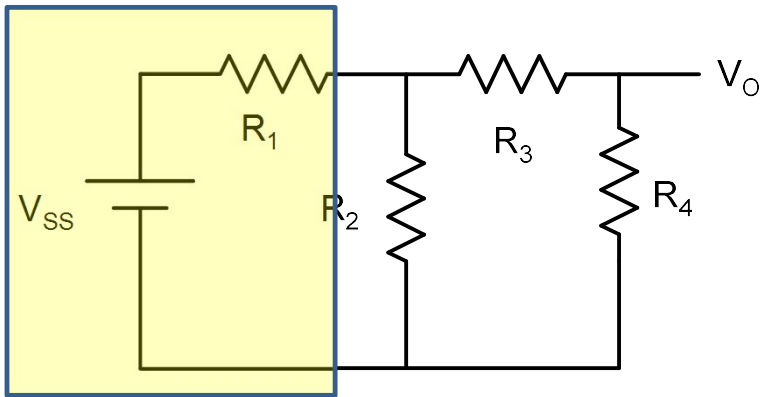

$$\frac{V_{SS}}{R_1} \times R_1 \parallel R_2 \times \frac{R_4}{R_4 + R_3 + (R_1 \parallel R_2)}$$

