

# ESC201T : Introduction to Electronics

## HW5: Solution

B. Mazhari  
Dept. of EE, IIT Kanpur


Q.1 An amplifier has a transfer function of the form

$$G(\omega) = \frac{V_O(\omega)}{V_{in}(\omega)} = \frac{100 \times j(\omega / \omega_L)}{\{1 + j(\omega / \omega_L)\} \{1 + j(\omega / \omega_H)\}}.$$

$$\omega_H > \omega_L$$

Sketch Bode plot of the transfer function and determine suitable values for corner frequencies such that amplifier can amplify audio frequencies in the range 20-20KHz equally well.

$$20\text{Log}_{10}(|G(\omega)|) = 40 + 10\text{Log}_{10}\left(\frac{\omega}{\omega_L}\right) - 10\text{Log}_{10}\left(1 + \left(\frac{\omega}{\omega_L}\right)^2\right) - 10\text{Log}_{10}\left(1 + \left(\frac{\omega}{\omega_H}\right)^2\right)$$

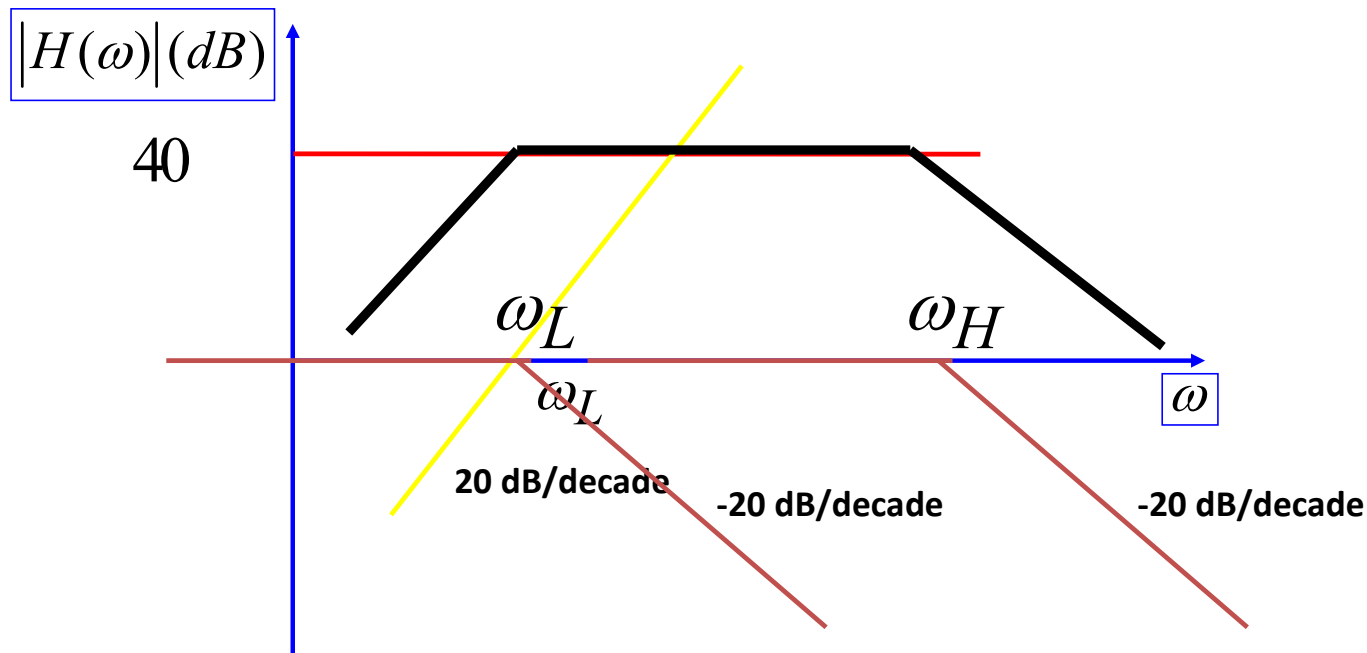


$$\omega_L < 2\pi \times 20\text{Hz}; \omega_H > 2\pi \times 20\text{KHz}$$

Q.2 There is a low pass filter whose transfer function is of the form

$$|H(f)| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_o}\right)^{2N}}}$$

There is a signal with 1KHz and 10KHz sinusoids of equal

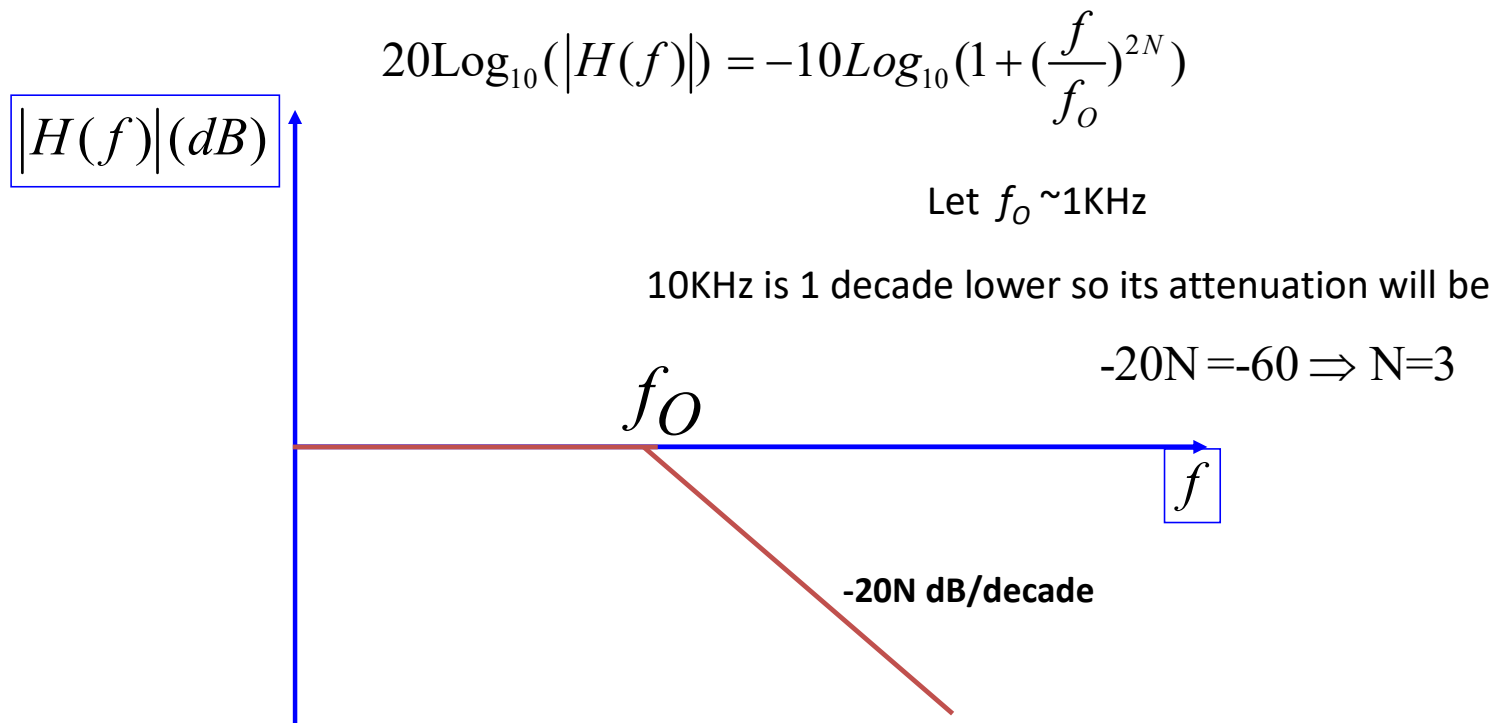magnitude. We would like to reject the 10KHz sinusoid. Determine suitable value for  $f_o$  and  $N$  such that magnitude of 10KHz is -60dB lower as compared to 1KHz signal after passing through the filter.



Q3 Draw the magnitude and phase Bode plots of the transfer function given below, for  $\omega$  ranging between 0.01 rad/sec to 100 rad/sec.


$$H(j\omega) = 2j\omega / [10(j\omega)^2 + 25(j\omega) + 10]$$

$$H(\omega) = \frac{2}{10} \times \frac{j\frac{\omega}{1}}{1 - \left(\frac{\omega}{1}\right)^2 + 2.5 \times j\left(\frac{\omega}{1}\right)}$$

$$H(\omega) = \frac{1}{1 - \left(\frac{\omega}{1}\right)^2 + 2.5 \times j\left(\frac{\omega}{1}\right)}$$


$$|H(1)| = -7.96 \text{ dB}$$
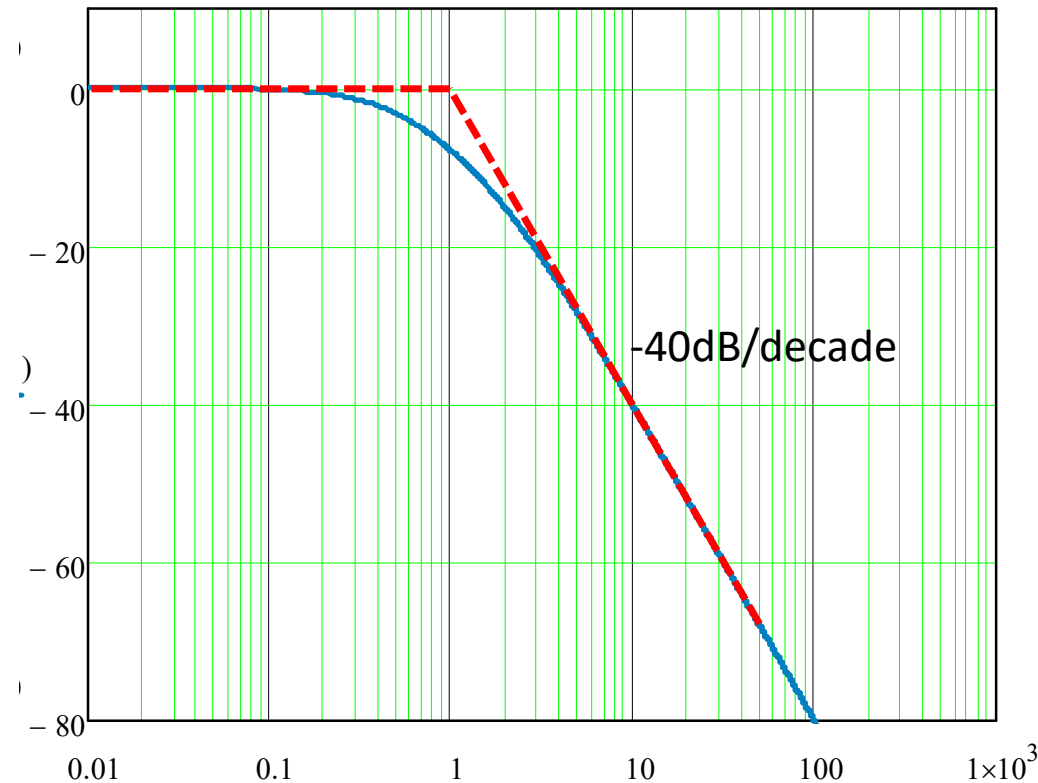
$$H(\omega) \approx \frac{-1}{\left(\frac{\omega}{1}\right)^2} \text{ for } \omega \gg 1$$




$$H(\omega) = \frac{1}{1 - \left(\frac{\omega}{1}\right)^2 + 0.5 \times j\left(\frac{\omega}{1}\right)}$$

$$|H(1)| = +6 \text{ dB}$$

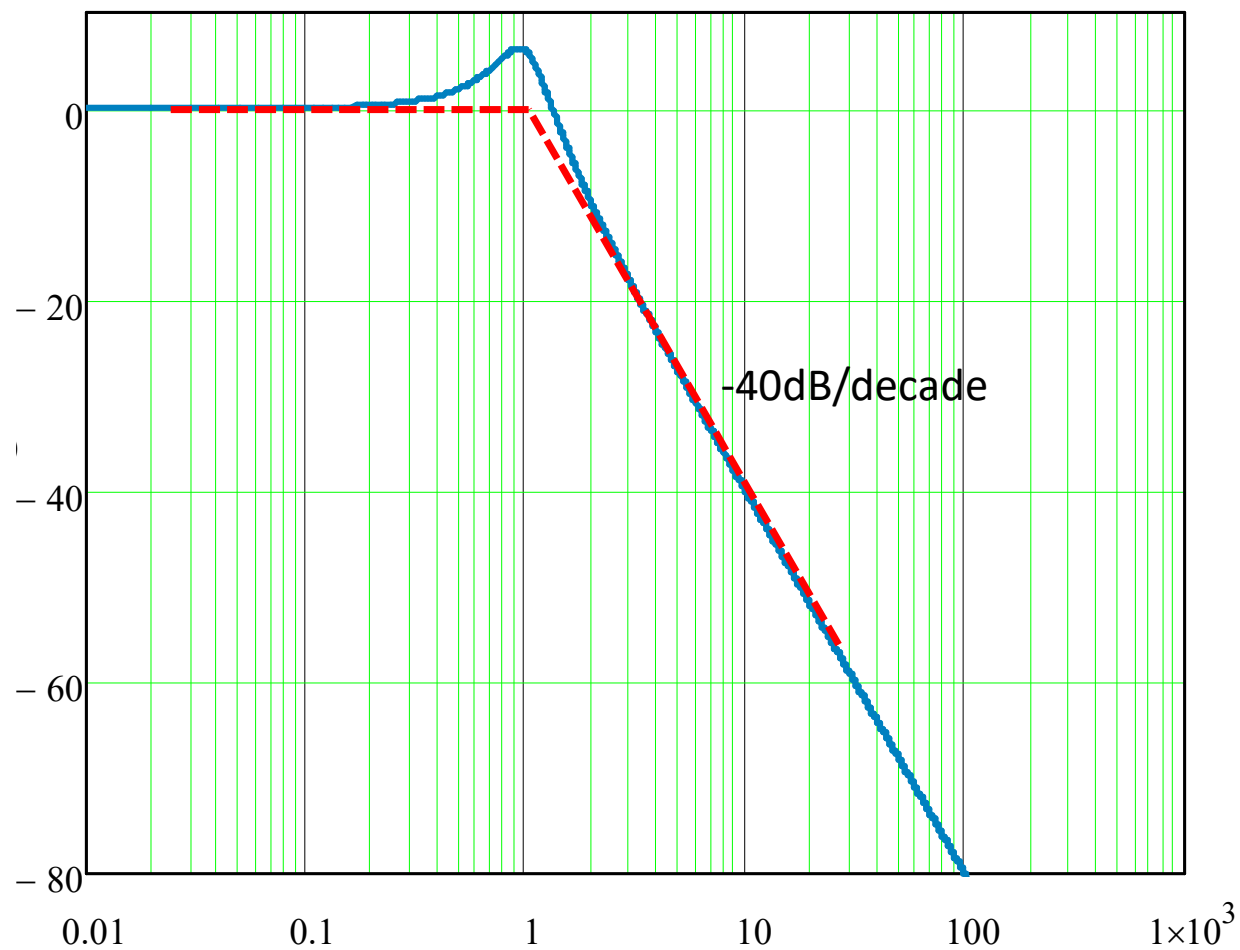

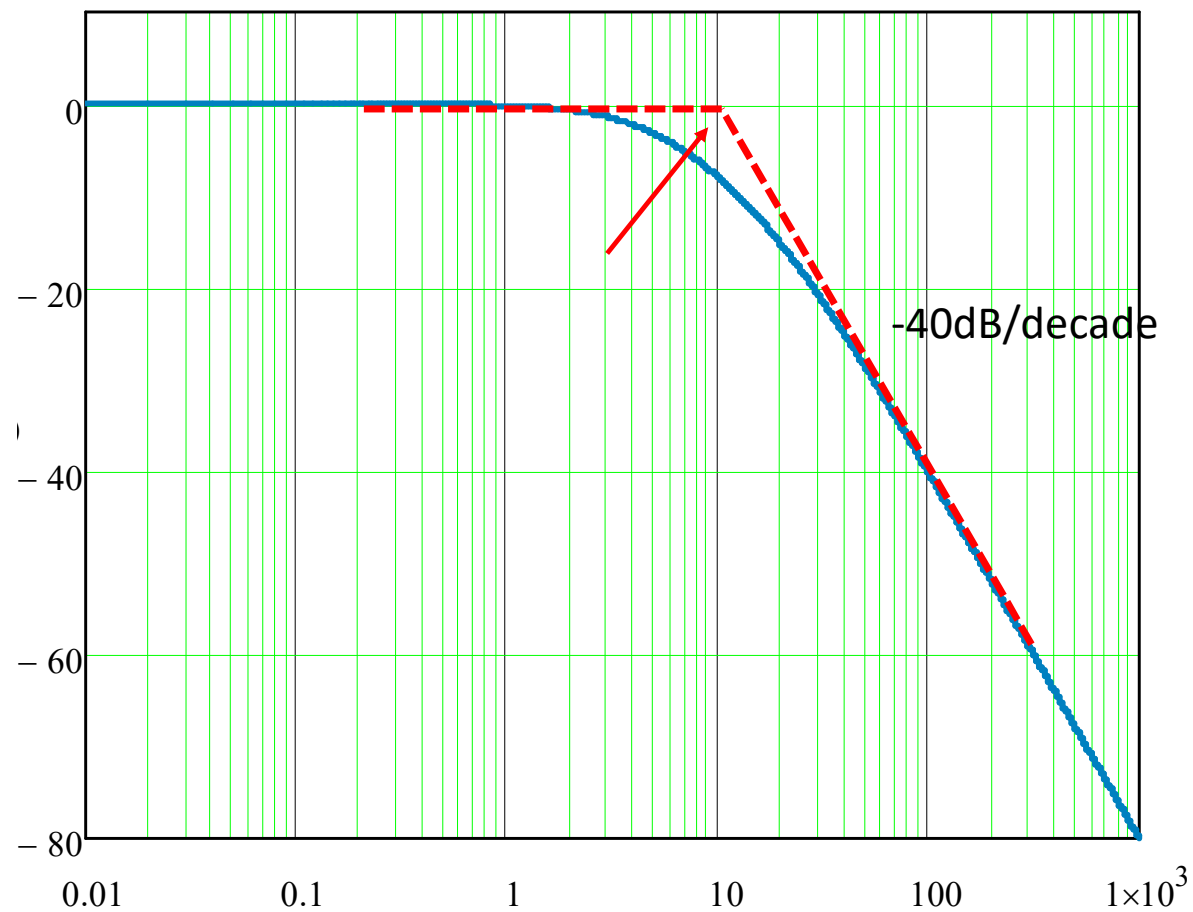
$$H(\omega) = \frac{1}{1 - \left(\frac{\omega}{10}\right)^2 + 2.5 \times j\left(\frac{\omega}{10}\right)}$$



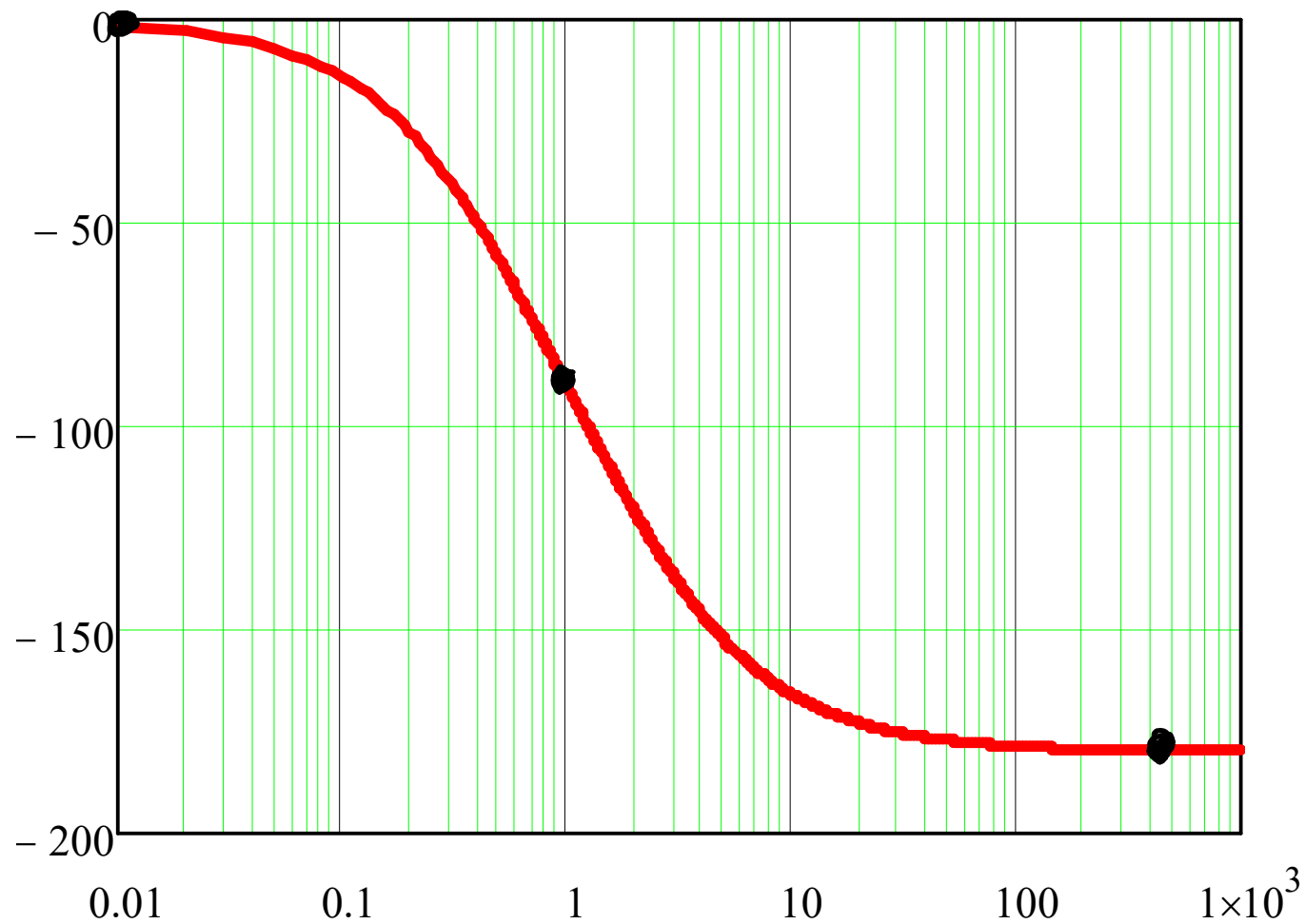
# Phase

$$H(\omega) = \frac{1}{1 - \left(\frac{\omega}{1}\right)^2 + 2.5 \times j\left(\frac{\omega}{1}\right)}$$




$$H(\omega) = \frac{2}{10} \times \frac{j \frac{\omega}{1}}{1 - \left(\frac{\omega}{1}\right)^2 + 2.5 \times j \left(\frac{\omega}{1}\right)} \quad 20\log(|H(\omega)|) = -14 + 20\log\left(\frac{\omega}{1}\right) - 10\log\left(\left(\left(\frac{\omega}{1}\right)^2 - 1\right)^2 + 2.5^2 \times \left(\frac{\omega}{1}\right)^2\right)$$

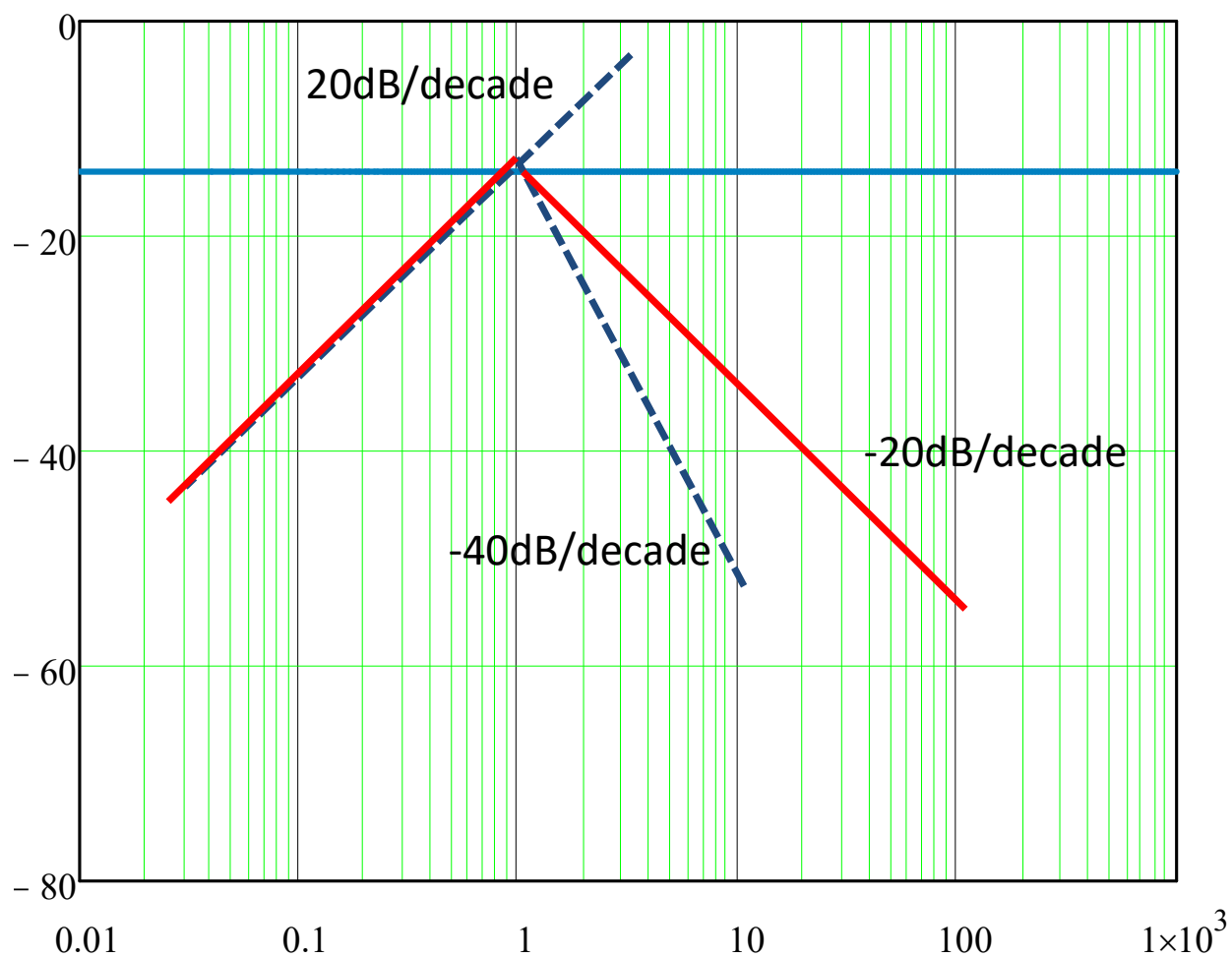





$$H(\omega) = \frac{2}{10} \times \frac{j \frac{\omega}{1}}{1 - \left(\frac{\omega}{1}\right)^2 + 2.5 \times j \left(\frac{\omega}{1}\right)} \quad 20\log(|H(\omega)|) = -14 + 20\log\left(\frac{\omega}{1}\right) - 10\log\left(\left(\left(\frac{\omega}{1}\right)^2 - 1\right)^2 + 2.5^2 \times \left(\frac{\omega}{1}\right)^2\right)$$

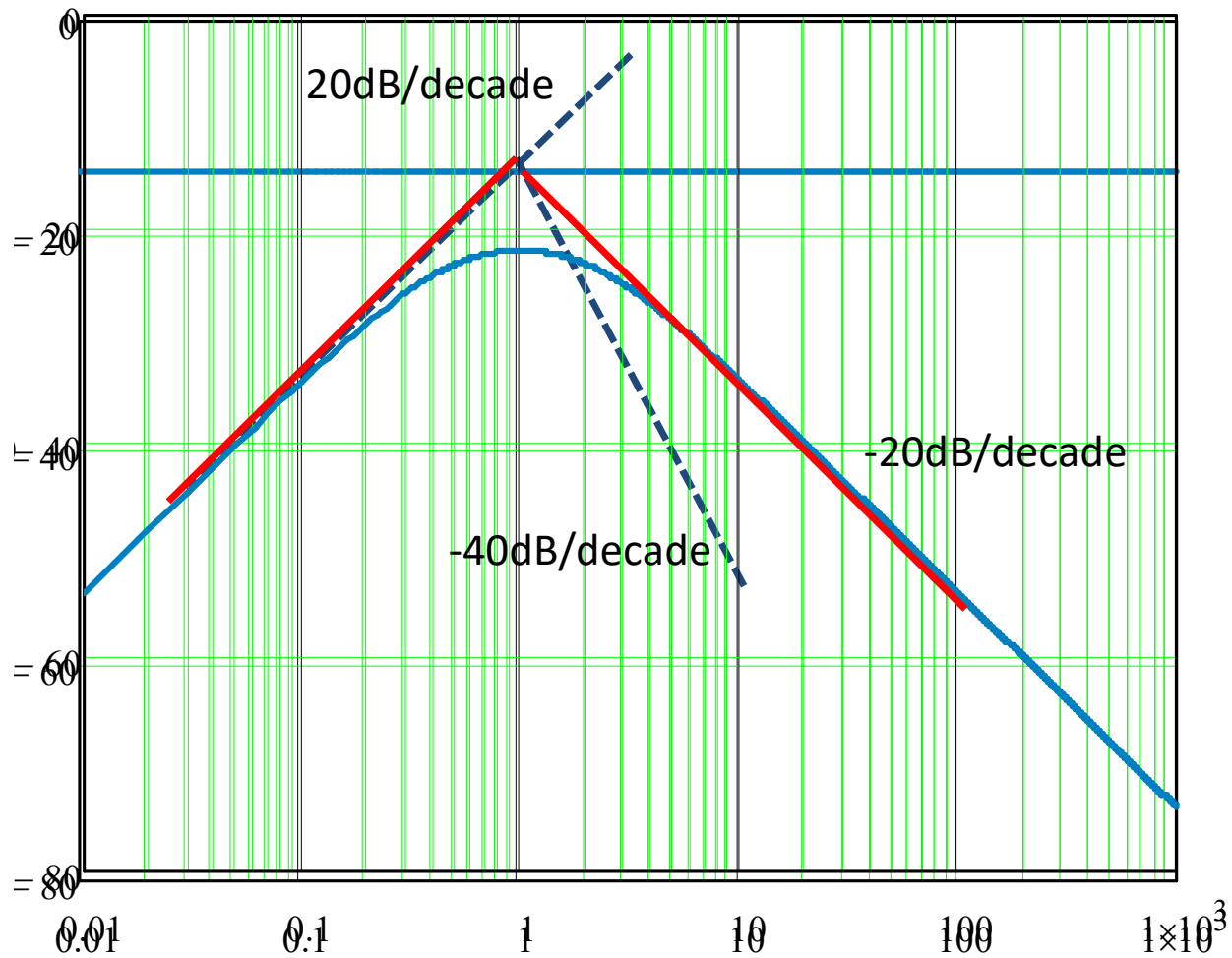
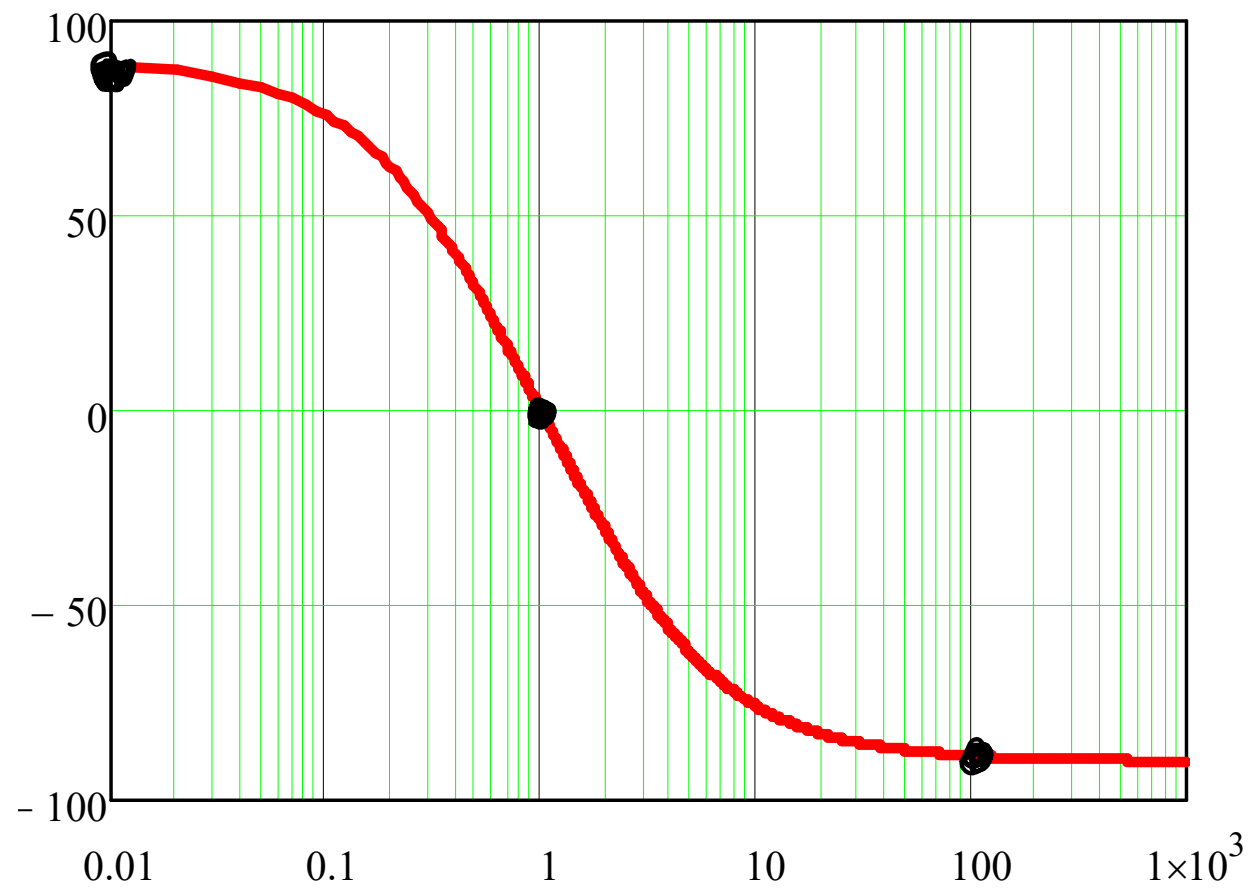
$$H(\omega) = \frac{2}{10} \times \frac{j \frac{\omega}{1}}{1 - \left(\frac{\omega}{1}\right)^2 + 2.5 \times j \left(\frac{\omega}{1}\right)}$$



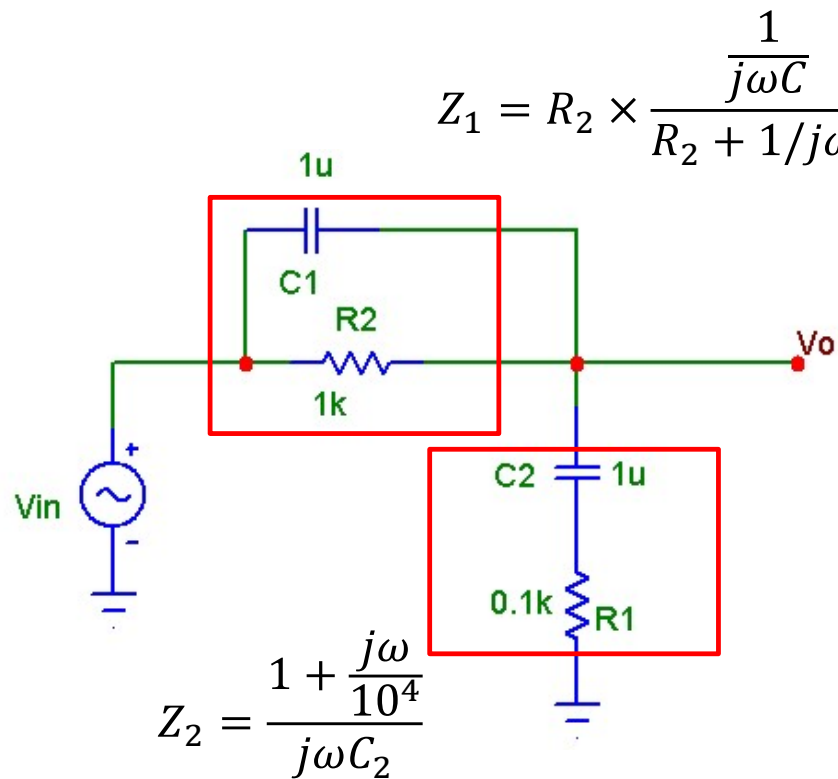Q.4 Derive the transfer function and sketch the Magnitude Bode plot of the circuit shown




$$Z_1 = R_2 \times \frac{1}{j\omega C} = \frac{10^3}{1 + \frac{j\omega}{10^3}}$$

$$H(\omega) = \frac{Z_2}{Z_1 + Z_2}$$


$$Z_2 = \frac{1 + \frac{j\omega}{10^4}}{j\omega C_2}$$

$$H(\omega) = \frac{\left(1 + \frac{j\omega}{10^4}\right) \times \left(1 + \frac{j\omega}{10^3}\right)}{1 + 6.64j \frac{\omega}{\omega_0} + \left(\frac{\omega}{\omega_0}\right)^2}; \omega_0 = 3.16 \times 10^3 \text{ rad/s}$$

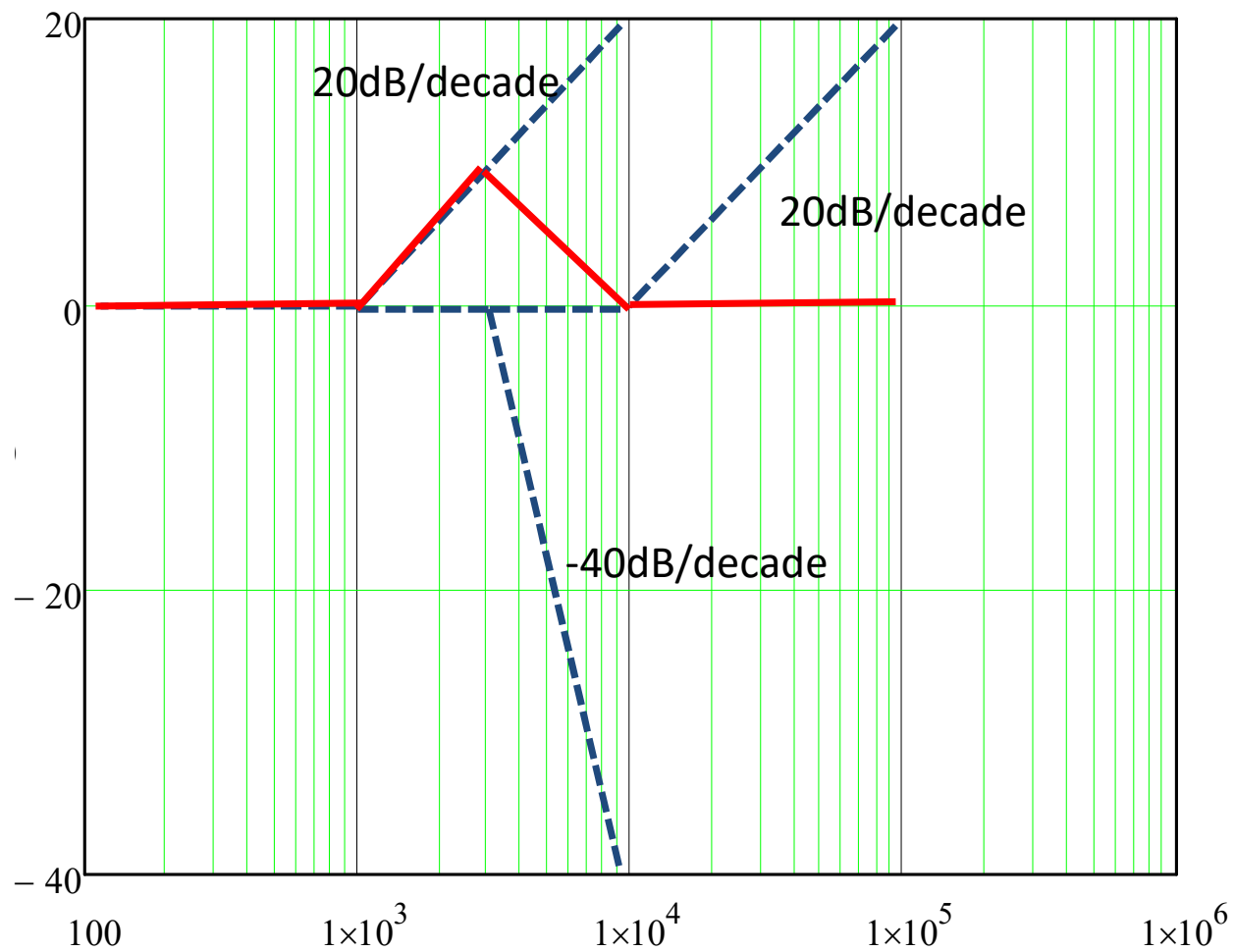
$$H(\omega) = \frac{\left(1 + \frac{j\omega}{10^4}\right) \times \left(1 + \frac{j\omega}{10^3}\right)}{1 + 6.64j \frac{\omega}{\omega_o} + \left(j \frac{\omega}{\omega_o}\right)^2}; \omega_o = 3.16 \times 10^3 \text{ rad/s}$$


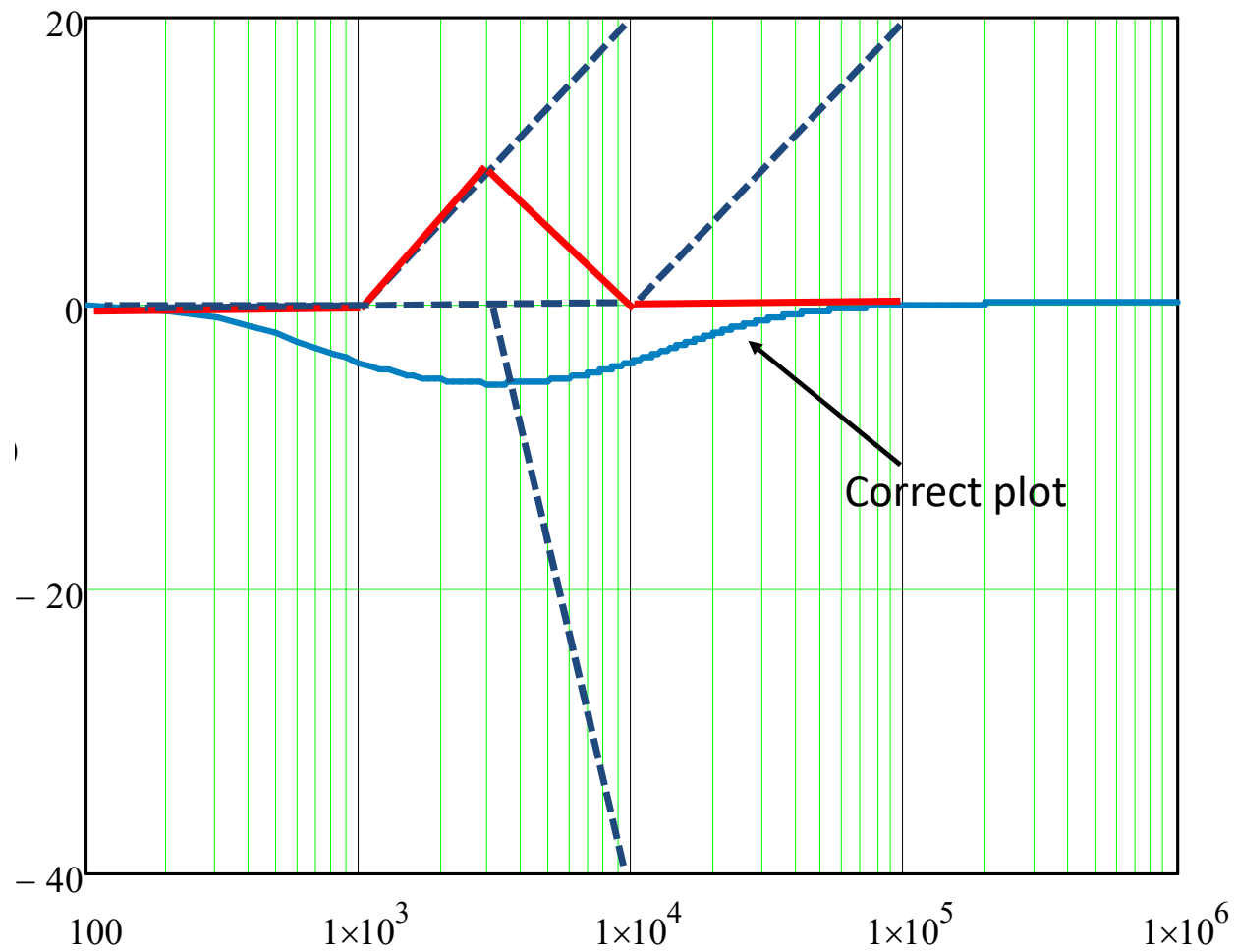
$$H(\omega) = \frac{\left(1 + \frac{j\omega}{10^4}\right) \times \left(1 + \frac{j\omega}{10^3}\right)}{1 + 6.64j \frac{\omega}{\omega_o} + \left(j \frac{\omega}{\omega_o}\right)^2}; \omega_o = 3.16 \times 10^3 \text{ rad/s}$$




$$H(\omega) = \frac{\left(1 + \frac{j\omega}{10^4}\right) \times \left(1 + \frac{j\omega}{10^3}\right)}{1 + 6.64j\frac{\omega}{\omega_o} + \left(j\frac{\omega}{\omega_o}\right)^2}; \omega_o = 3.16 \times 10^3 \text{ rad/s} \quad \Rightarrow \quad H(\omega) = \frac{\left(1 + \frac{j\omega}{10^5}\right) \times \left(1 + \frac{j\omega}{10^2}\right)}{1 + 6.64j\frac{\omega}{\omega_o} + \left(j\frac{\omega}{\omega_o}\right)^2}; \omega_o = 3.16 \times 10^3 \text{ rad/s}$$

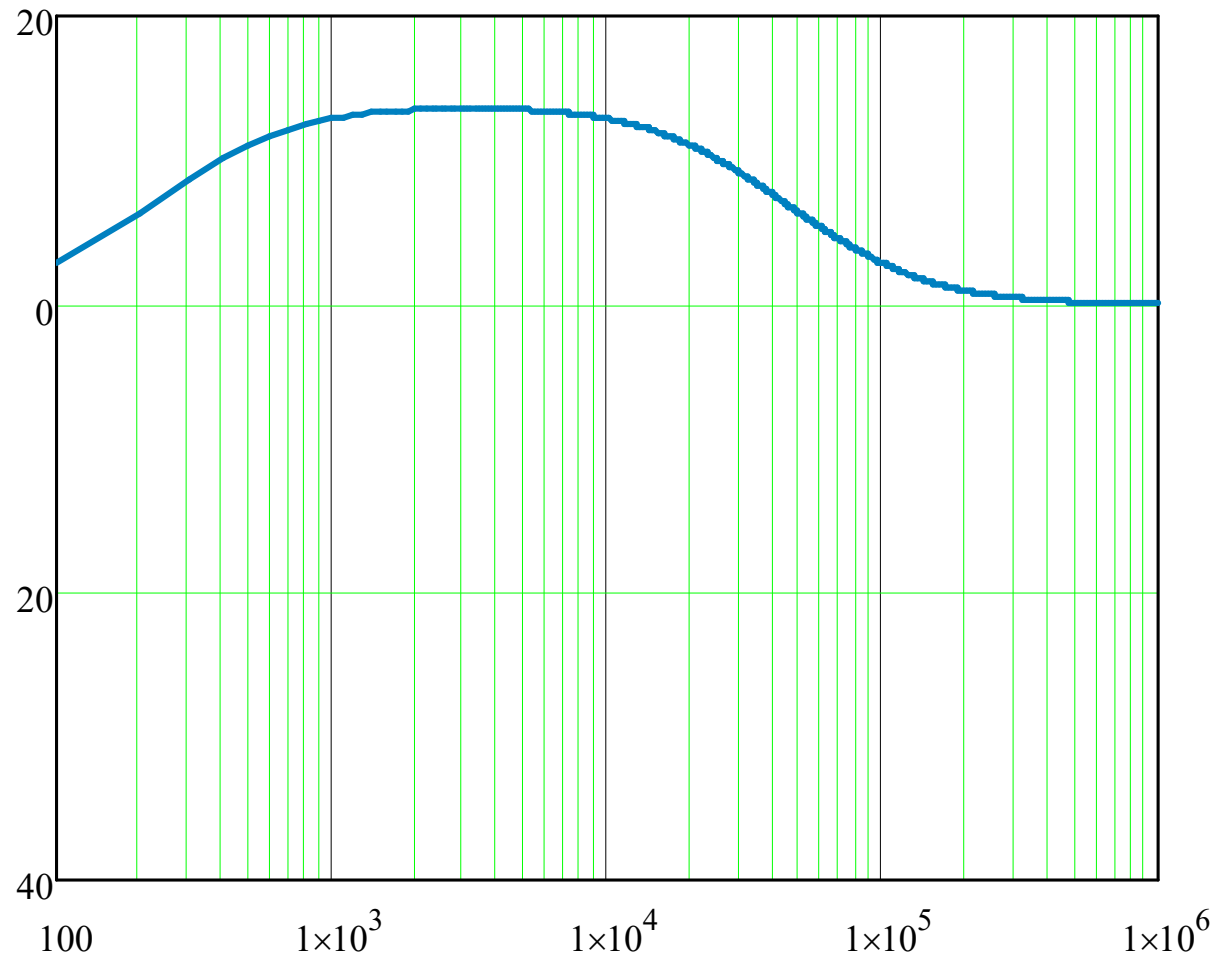


Corner frequencies are sufficiently far apart

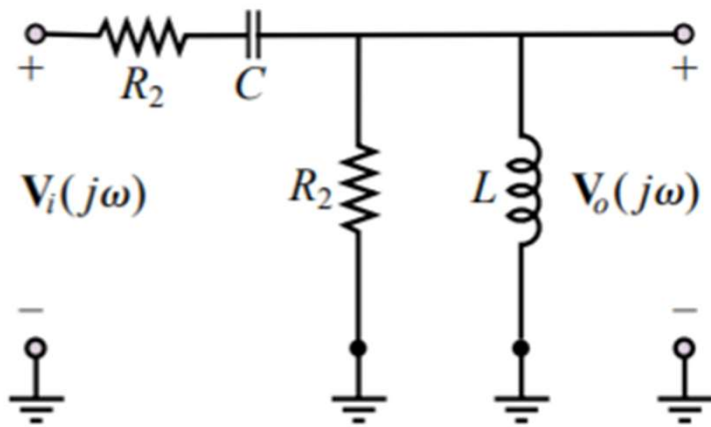Q.5 Determine the nature of filter for the circuit shown below




Low frequency

High frequency

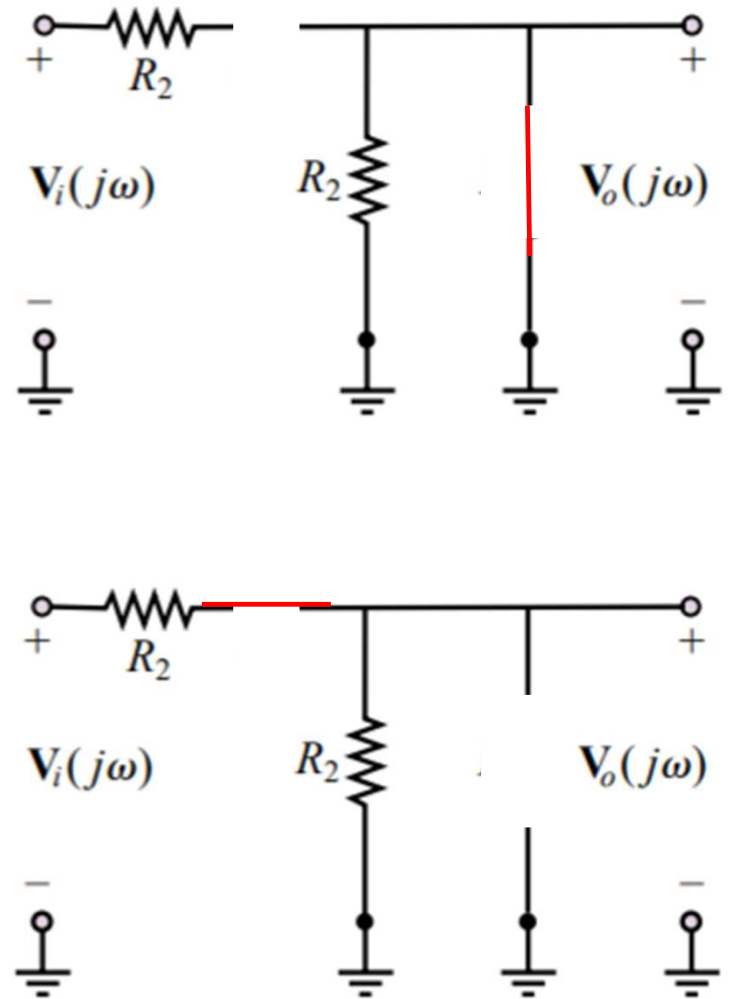

$\Rightarrow$  High Pass Filter

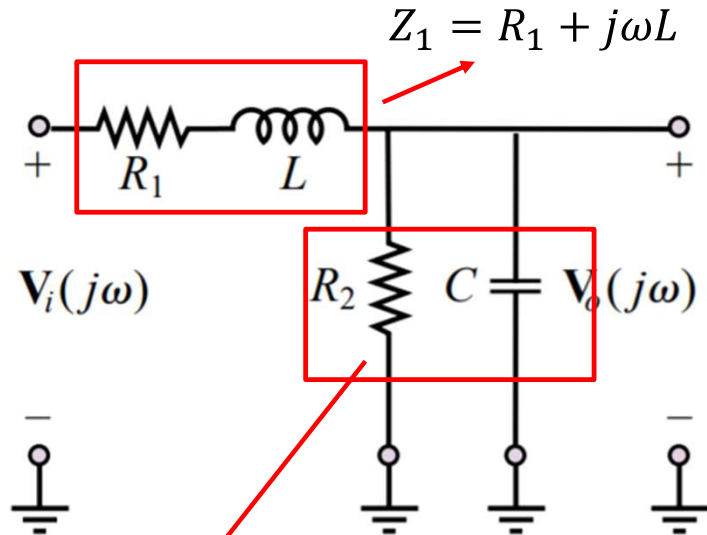Q.6 Determine the transfer function and sketch the Bode plot for the circuit shown below



$$L = 11 \text{ mH}$$

$$C = 0.47 \text{ nF}$$

$$R_1 = 2.2 \text{ k}\Omega$$

$$R_2 = 3.8 \text{ k}\Omega$$

$$H(\omega) = \frac{Z_2}{Z_2 + Z_1} = \frac{\frac{R_2}{1 + j\omega R_2 C}}{R_1 + j\omega L + \frac{R_2}{1 + j\omega R_2 C}}$$


$$Z_2 = R_2 \times \frac{1}{R_2 + 1/j\omega C} = \frac{R_2}{1 + j\omega R_2 C}$$

$$H(\omega) = \frac{R_2}{R_1 + R_2} \times \frac{1}{1 + \frac{j\omega L + j\omega R_1 R_2 C}{R_1 + R_2} + \frac{(j\omega)^2 (R_2 C L)}{R_1 + R_2}}$$

$$H(\omega) = \frac{0.63}{1 + 1.375 \frac{j\omega}{\omega_0} + \left(j \frac{\omega}{\omega_0}\right)^2}; \omega_0 = 5.5 \times 10^5 \text{ rad/s}$$


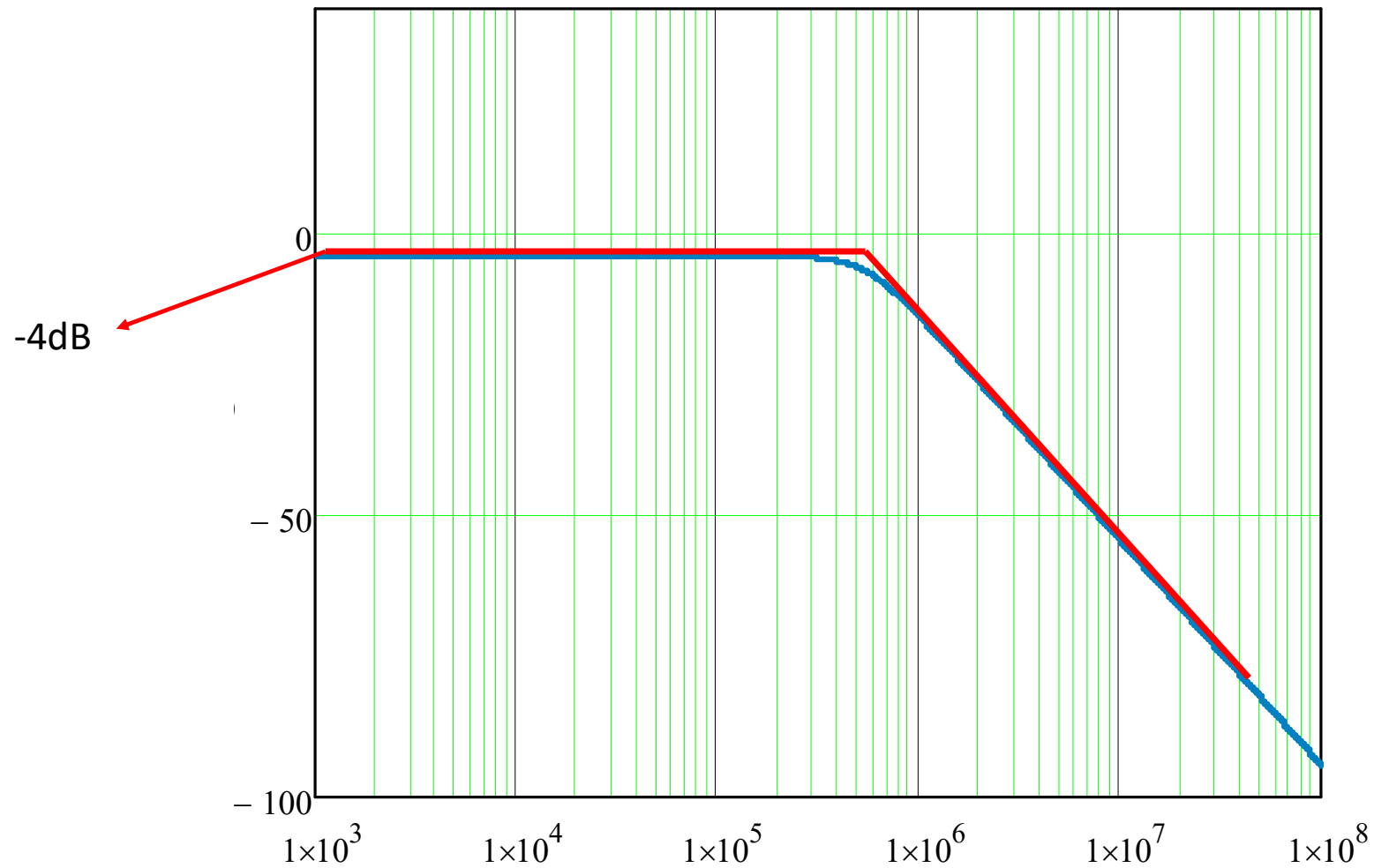
$$H(\omega) = \frac{0.63}{1 + 1.375 \frac{j\omega}{\omega_o} + \left(j \frac{\omega}{\omega_o}\right)^2}; \omega_o = 5.5 \times 10^5 \text{ rad/s}$$



$$H(\omega) = \frac{0.63}{1 + 1.375 \frac{j\omega}{\omega_o} + \left(j \frac{\omega}{\omega_o}\right)^2}; \omega_o = 5.5 \times 10^5 \text{ rad/s}$$

